

**B.E. INSTRUMENTATION AND ELECTRONICS ENGINEERING**  
**SECOND YEAR SECOND SEMESTER - 2019**  
**ELECTRONIC CIRCUITS 1**

Time : Three hours

Full Marks : 100

Answer any four questions

1. (i) Assuming the constant voltage model of a diode, plot the input output characteristics of the circuits shown in Fig. 1a, Fig 1b and Fig 1c respectively.

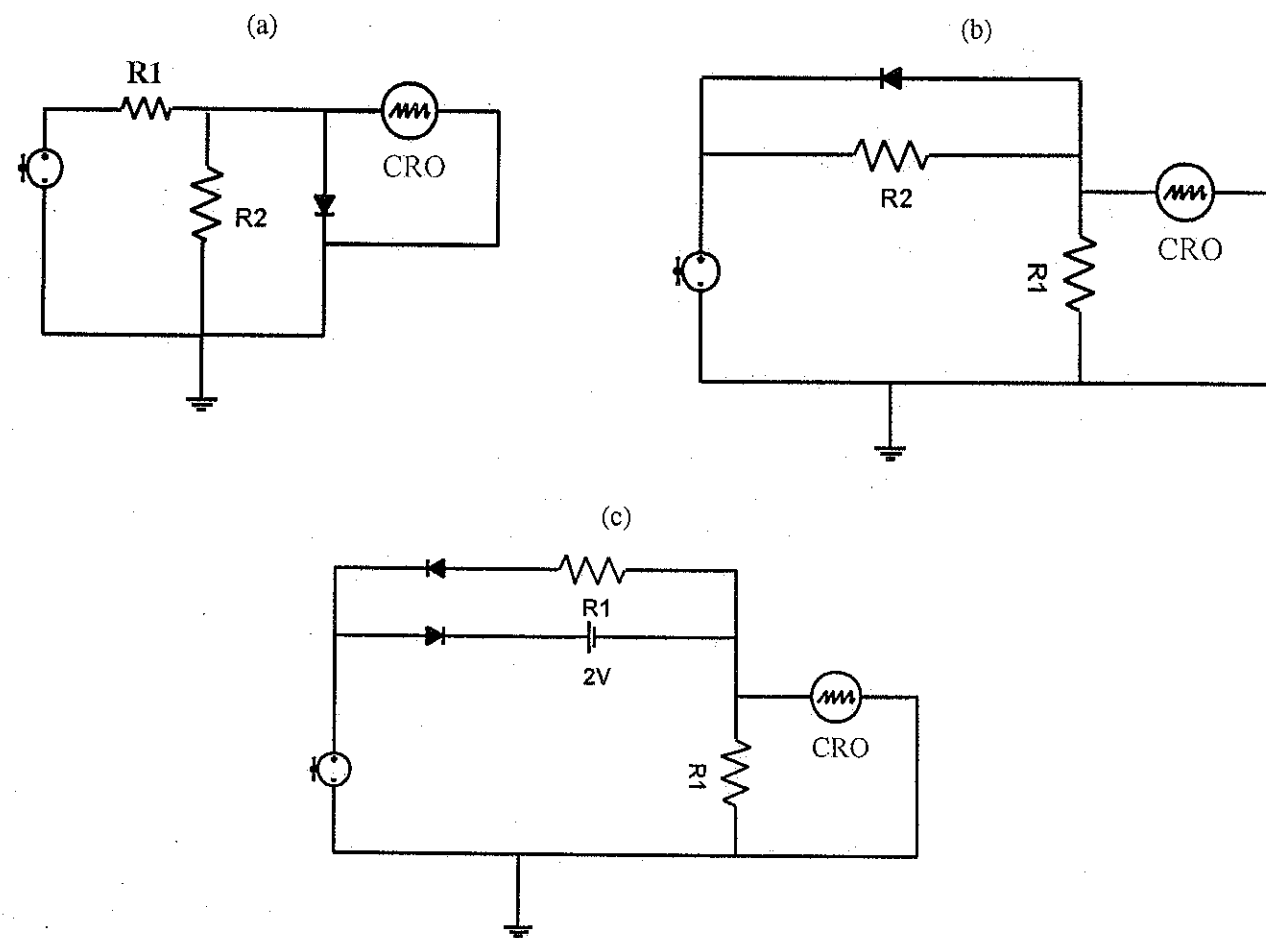


Figure 1

- (ii) A sinusoidal signal  $V(t) = V_0 + V_P \cos \omega t$  is applied across a diode. Considering  $V_P \ll V_T$ , determine the resulting diode current.
- (iii) Design a full-wave rectifier to deliver an average power of 2 W to a tablet with a voltage of 3.6 V and a ripple of 0.2 V.

(5 × 3)+3+7=25

2. (i) Find the transistor ( $\beta = 100$ ,  $I_{CBO} = 20 \text{ nA}$  and  $V_{BE} = 0.7 \text{ V}$ ) currents ( $I_E$ ,  $I_B$  and  $I_C$ ) in the circuit shown in Fig. 2a. Also find the region of operation of the transistor as per its output characteristics.

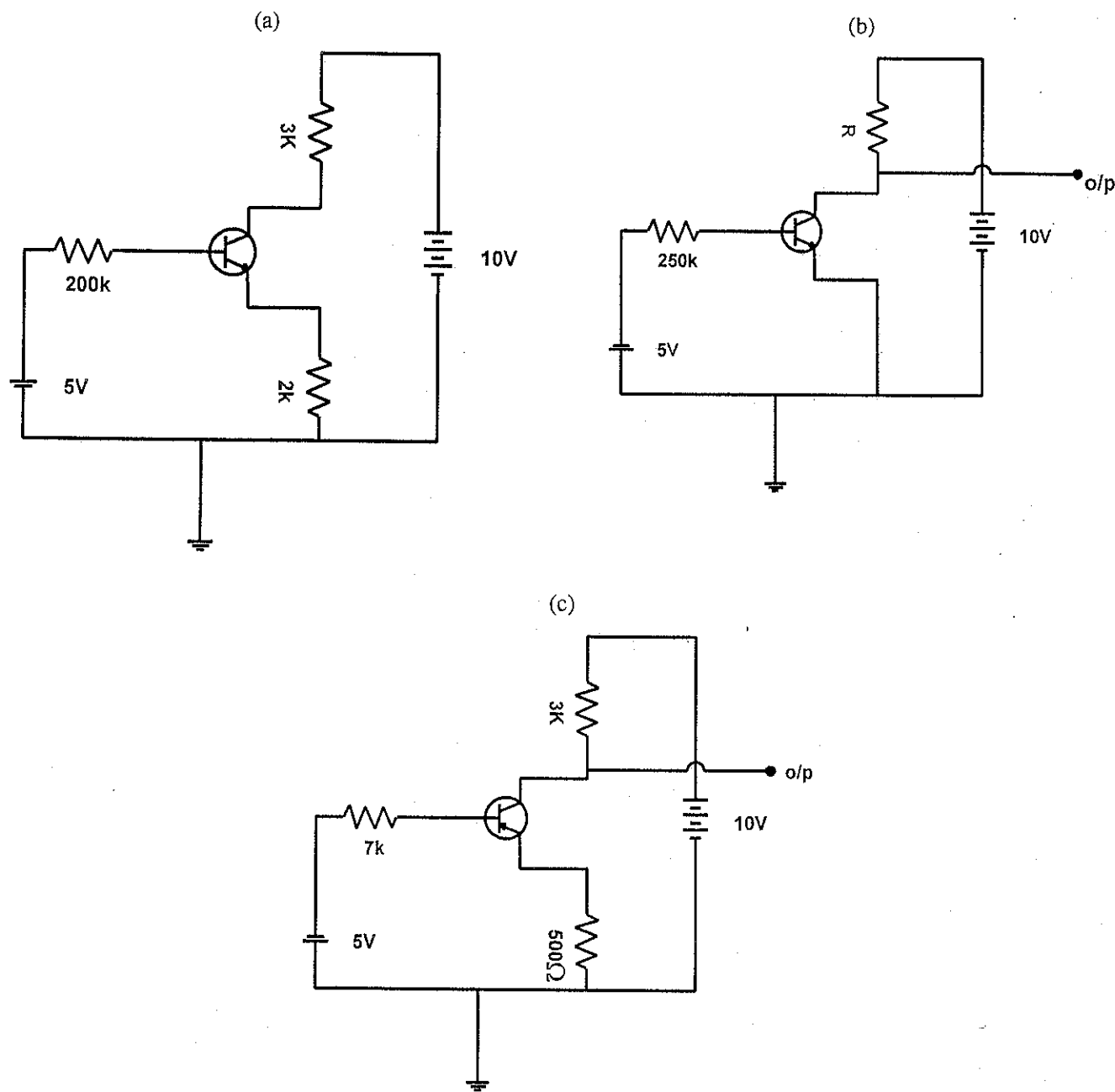


Figure 2

- (ii) What is the maximum value of the collector resistance in the circuit shown in Fig. 2b such that the transistor will be saturated? Consider  $\beta = 100$ ,  $V_{BE} = 0.8 \text{ V}$  and  $V_{CE} = 0.2 \text{ V}$ .
- (iii) Find the output voltage of the circuit shown in Fig. 2c considering the same value of  $\beta$ ,  $V_{BE}$  and  $V_{CE}$ .
- (iv) Design a circuit using only diodes (constant voltage) and  $10 \text{ k}\Omega$  resistors to provide an output signal limited to  $-2.17 \text{ V}$  and above.

- (v) Assuming the constant voltage model of a diode, design a two sided limiting circuit which can drive a  $1\text{ k}\Omega$  load with nominal limiting levels of  $\pm 3\text{ V}$  and having a voltage gain of  $0.95\text{ V}$  in the nonlimiting region.

$$(3+2)+5+5+4+6=25$$

3. (i) What is the value of the emitter current in the circuit shown in Fig. 3a ?  
 (ii) Find the output voltage and the emitter current of the circuit shown in Fig. 3b.  
 (iii) If the collector voltage is  $-4\text{V}$ , find the emitter voltage in the circuit shown in Fig. 3c.  
 (iv) Find the emitter current and  $V_1$  in the circuit shown in Fig. 3c.  
 (v) A pnp transistor has  $v_{EB} = 0.8\text{ V}$  at a collector current of  $1\text{A}$ . When  $i_C = 10\text{ mA}$ , what should  $v_{EB}$  be ?

$$5 \times 5=25$$

4. (i) A pnp transistor is biased to operate at  $I_C=2\text{ mA}$ .  
 (a) What is the associated value of  $g_m$  ?  
 (b) If  $\beta=50$ , what is the value of  $r_e$  seen looking into the emitter ?  
 (c) How does this resistance change when looked into the base ?  
 (d) If the collector is connected to a  $5\text{ k}\Omega$  load, with a signal of  $5\text{ mV(p-p)}$  applied between the base and emitter, what is the resultant output ?  
 (ii) A transistor ( $50 \geq \beta \leq 200$ ) operating with nominal  $g_m$  of  $60\text{ mA/V}$  has a  $\pm 20\%$  variation in  $I_C$ . Find the extreme values of the resistance while looking into the base.  
 (iii) The transistor in the circuit shown in Fig. 4a, has  $\beta=100$ .  
 (a) What is the dc collector current and the dc voltage at the collector ?  
 (b) Draw the small signal equivalent circuit of this amplifier.  
 (c) What is the voltage gain ?  
 (iv) For the amplifier shown in Fig. 4b,  
 (a) what should be the value of  $I$  so that the input resistance at E is equal to that of the source ?  
 (b) What is the resulting voltage gain from the source to the load ?  
 (v) A particular BJT operating at  $I_C=2\text{ mA}$  has  $C_\mu=1\text{pF}$ ,  $C_\pi=10\text{pF}$  and  $\beta=150$ . Find the value of  $f_T$  and  $f_B$  for this situation.

$$(2 \times 4) + 3 + (2+4+2) + (2+2) + 2 = 25$$

5. (i) An n-channel JFET operating in the active region carries a drain current of  $4\text{ mA}$  when  $V_{GS}=-2\text{V}$ , and a drain current of  $6\text{ mA}$ , when  $V_{GS}=-1\text{V}$ .  
 (a) Calculate the pinch-off voltage.  
 (b) Calculate the saturated drain current for  $V_{GS}=0\text{V}$ .  
 (c) If  $V_{DS}=10\text{V}$ , find the channel resistance for  $V_{GS}=-2\text{V}$ ,  $-1\text{V}$  and  $0\text{V}$ .

 


Figure 3

- (ii) The transconductance and the ac drain resistance of a FET are  $0.2 \text{ mA/V}$  and  $150 \text{ k}\Omega$  respectively. What is the small-signal voltage gain when this device is used in the CS configuration with a load resistance of  $150 \text{ k}\Omega$  ?
- (iii) A small-signal common-source FET amplifier has a variable load resistance  $R_L$ . For what value of  $R_L$  will the ac power dissipated in the load be maximum ?
- (iv) For a constant  $V_{GS}$ , the drain current of an FET changes by  $20 \mu\text{A}$  when  $V_{DS}$  is changed by  $2\text{V}$ . What is the ac drain resistance of the FET ?
- (v) Draw the equivalent circuit of the one shown in Fig. 5a and find the small signal voltage gain with  $g_m = 4 \times 10^{-3} \text{ mS}$  and  $r_d = 70 \text{ k}\Omega$ . Consider the capacitive reactances to be negligible at the operating frequency.

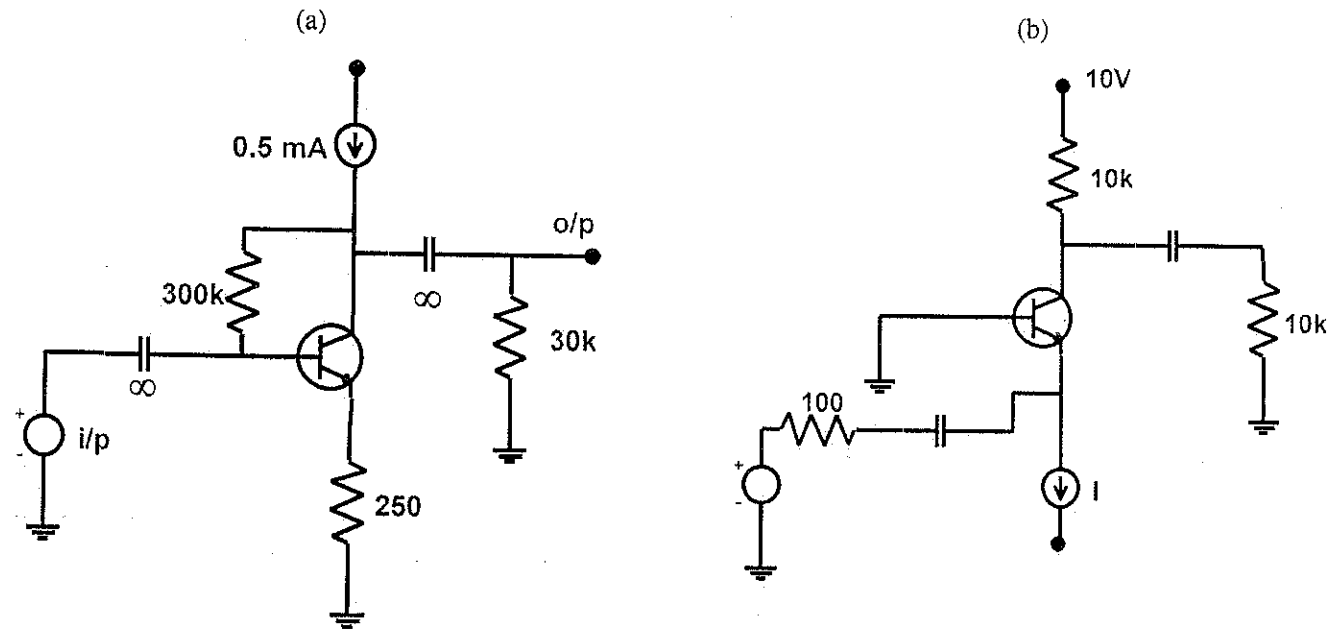


Figure 4

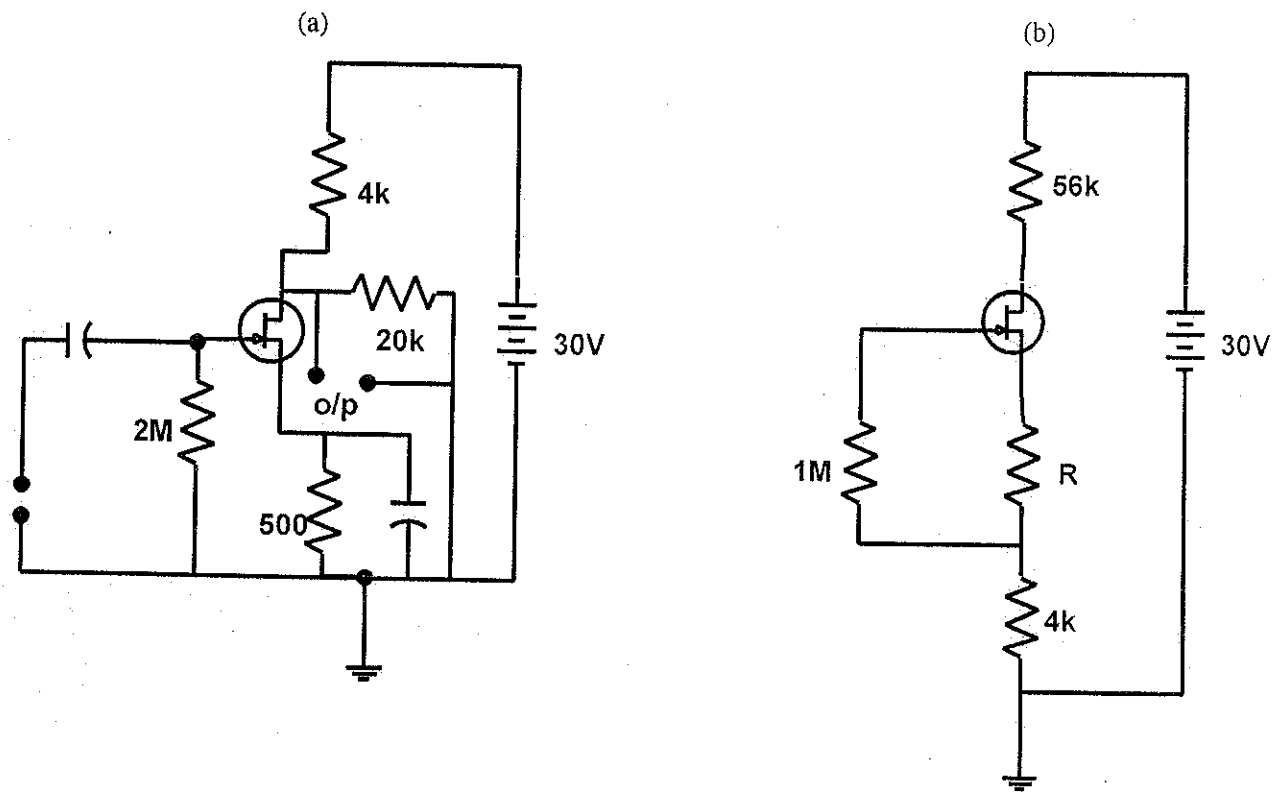


Figure 5

(vi) For the circuit shown in Fig. 5b, calculate the resistance R such that the quiescent value of  $V_{DG} = 16$  V. Find the transconductance at this point. Given  $I_{DSS} = 1$  mA and  $V_p = -1$  V.

$(2+2+3) + 3 + 3 + 2 + 5 + 5 = 25$