

Department of Instrumentation and Electronics Engineering

1st year, 2nd semester M.Tech Examination, 2025

Subject: Design of Digital CMOS Integrated Circuits


Time: 3 hours

Full marks:100

MODULE-1

Answer any **Four****4 × 10 = 40**

 1. a) What are the different generations of IC? What are the different steps a typical IC fabrication process consists of? 2+3
 b) Consider an NMOS transistor with $V_{th}=1V$ is operated in the triode region with small value of V_{ds} . With $V_{gs}=1.5V$ it is found to have a resistance $R_{ds} = R_{on} = 1Kohm$. What value of V_{gs} is required to obtain $R_{ds}=200\ ohm$? Find the corresponding resistance values obtained with a device having twice the value of W . 5
2. a) Write the use of SiO_2 as a passivating layer. For a controlled doping in a narrow gate region, which doping technique should be used and why? 2+4
 b) Determine the bias state for PMOS transistors in the following diagram where $V_{th}=-0.4V$ 4



3. a) What is the function of photoresist in the fabrication process? State differences between positive and negative photoresist. 2+2
 b) What are BiCMOS gates? Describe the basic steps in MOS fabrication process with suitable diagram. 6
4. a) In an n-channel MOSFET with a metal gate electrode, the original gate metal is replaced by a metal with a smaller work function. Explain qualitatively the effect on the threshold voltage. 3
 b) How do the gate-source capacitance of a MOSFET vary with gate to source voltage? Explain. 3
 c) What is channel pinch off? How does the drain current in a MOSFET vary beyond the pinch-off point? 4
5. a) What is interstitialcy? Give an example of a suitable dopant atom in Silicon lattice site. 4
 b) What is thermal diffusion? How it is carried out? 6

[Turn over


MODULE-2

Answer any **five**

5 × 10 = 50

5. a. It is not customary to shuffle the NMOS and PMOS in pull-down and pull-up network in a CMOS inverter “-Justify your answer 4
- b. Show that in a CMOS inverter for symmetric switching requires, $\left(\frac{W}{L}\right)_p \approx 2.5 \left(\frac{W}{L}\right)_n$ for all practical purposes, where, $\mu_p = 230 \text{ cm}^2/\text{V} \cdot \text{s}$ and $\mu_n = 580 \text{ cm}^2/\text{V} \cdot \text{s}$. 6
6. a) Consider a CMOS inverter circuit with the following parameters: $V_{DD}=3.3\text{V}$, $V_{TO,n}=0.6\text{V}$, $V_{TO,p}=-0.7\text{V}$, $k_n=200\mu\text{A}/\text{V}^2$, $k_p=80\mu\text{A}/\text{V}^2$. Calculate the noise margins of the circuit. 7
- b) How the switching threshold in a CMOS inverter shifts when $\frac{k_n}{k_p} > 1$. Show using suitable voltage-transfer characteristics curve. 3
7. For a simple CMOS inverter with a power supply voltage of $V_{DD}= 5\text{V}$, determine the fall time τ_{fall} , from $V_{out} = V_{90\%} = 4.5$ to $V_{out} = V_{10\%} = 0.5$. Use both the average-current method and the differential equation method for calculating τ_{fall} . The output load capacitance is 1pF. The NMOS parameters are given as; 10
- $$\mu_n C_{ox} = \frac{20\mu\text{A}}{\text{V}^2}$$
- $$\left(\frac{W}{L}\right)_n = 10$$
- $$V_{r,n} = 1.0\text{V}$$

 8. Consider the circuit of the given figure:



$$V_{DD} = 2.5\text{V}$$

$$(W/L)_2 = 1.5\mu\text{m}/0.25\mu\text{m}$$

$$(W/L)_1 = 0.5\mu\text{m}/0.25\mu\text{m}$$


$$(W/L)_{ni} = 0.5\mu\text{m}/0.25\mu\text{m}$$

$$k_n' = 115\mu\text{A}/\text{V}^2, k_p' = -30\mu\text{A}/\text{V}^2$$

Assume the inverter switches ideally at $V_{DD}/2$, neglect body effect, channel length modulation and all parasitic capacitance throughout this problem. Consider $V_{tn}=0.43\text{V}$ and $V_{tp}=0.4\text{V}$ for the network. 5+5

- a. What is the logic function performed by the circuit?
- b. Explain why this circuit exhibits non-zero static dissipation.

 9. a) Consider the following Boolean Expression: $Z = \overline{(A + B + C)} (DE)$ 5
 Calculate equivalent driver $\left(\frac{W}{L}\right)$ ratio of the pull-down network if for all NMOS transistors. $\left(\frac{W}{L}\right)_n = 10$. Draw a CMOS equivalent circuit for the expression.
- b) Suggest a design technique for large fan-in circuits to reduce propagation delay in a CMOS inverter with a suitable example. 5
10. Consider the circuit of the given figure: 10



The threshold voltage $|V_T|$ for each transistor = 2V. What should be the range of input voltage V_{in} , for the circuit to work as an inverter. Analyse the operation of the circuit to estimate the output voltage V_o .

MODULE-3

Answer any **one** $10 \times 1 = 10$

11. a) What are the various types of physical defects that can occur in a semiconductor chip? n what ways do these physical defects lead to electrical faults within the chip? How are these electrical faults further manifested as logical faults during chip operation? 5
- b) Explain the relationships between physical defects, electrical faults and logical faults using a simple NOR 2 logic 5
12. Describe the essential circuit modules for built-in self-test design 10