

M.E. Electronics and Tele-Communication Engineering
First Year First Semester Examination, 2025

Analog VLSI Circuits (NV)


Time: 3 Hours

Full Marks: 100

*All parts of the same question must be answered together. Ensure neatness and clarity.
 Any approximation used in solving problems need to be justified.*

Assume: $V_{DD} = 2\text{ V}$, $\mu_n C_{ox} = 200\text{ }\mu\text{A/V}^2$, $\mu_p C_{ox} = 50\text{ }\mu\text{A/V}^2$, $\lambda_n = 0.1\text{ V}^{-1} = 0.5\lambda_p$, $L = 0.5\text{ }\mu\text{m}$,
 and $|V_{TH}| = 0.5\text{ V}$ for all MOSFETs, if not specified otherwise.

 - Q1** Answer part (a) and any TWO from the rest: [PO1]
- a) Draw the circuit diagram of a cascoded common-source amplifier and discuss on its advantages. 5
- b) Derive the expression of the input-referred rms noise voltage of the following common-source amplifier, considering both thermal and flicker noise sources. 10




- c) Explain the advantages of differential signaling in an integrated circuit. Can two common-source amplifiers be fed with differential input signal in order to realize a fully-differential amplifier? 10
- d) In a PTAT cell, replace the diode-connected BJTs with diode-connected MOS transistors, and show that the MOSFETs maintain a constant- g_m . 10

 - Q2** Answer part (a) and any TWO from the rest: [PO2]
- a) Discuss on the realization of BJTs in CMOS technology. 5
- b) For a quiescent current consumption of $10\text{ }\mu\text{A}$ in the NMOS-based input-pair of a fully-differential *Folded-Cascode OTA*, calculate the width of the input transistors for obtaining unity-gain frequency of 10 MHz (at load capacitance of 5 pF). Draw the corresponding circuit schematic. 10
- c) Find the maximum permissible range of the output voltage for a *Telescopic Cascode OTA* being used to implement a unity-gain buffer (in figure below). 10

[Turn over


Derive the expression of the loop-gain (at low frequencies) of the negative-feedback loop involved in this circuit.



- d) Draw the circuit diagram and derive expressions for the dc-gain, ICMR, and output voltage swing of a 5T OTA with PMOS input-pair. 10

Q3 Answer part (a) and any TWO from the rest: [PO3]

 - a) Discuss how frequency compensation is done for ensuring stability of a two-stage OTA in negative feedback. 5
- b) Draw the CM half-circuit and hence derive the expression of the CM gain for low frequency operation of the following differential amplifier. Now assuming that $r_{o4} = (r_{o3} + \Delta r_o)$, derive the expression of its CM-to-DM gain. What might happen to the CMRR at higher frequencies due to the parasitic capacitance at the source node of M1/M2? 10



- c) For a fully-differential 5T OTA, draw the circuit schematic including the CMFB with resistive CM detection. What will be the expression of the open-loop DM gain of this OTA circuit? Describe how many poles are present in its CMFB path. 10
- d) Draw the circuit schematic of a Miller-compensated 2-stage OTA with single-ended output, where the first-stage is a folded-cascode stage with PMOS input pair and the second-stage is a common-source stage. Discuss about the poles 10

present in this circuit while deriving their approximate expressions.

- | | | |
|-----------|--|-------|
| Q4 | Answer <u>part (a)</u> and <u>any TWO</u> from the rest: | [PO4] |
| a) | Discuss how resistors are practically realized in CMOS integrated circuits with proper diagram(s). | 5 |
| b) | Explain how layout design must be done to enable proper transistor matching, together with a representative layout diagram (with clear labelling). | 10 |
| c) | Draw the schematic of a <i>Low Dropout Regulator</i> (LDO) and design its pass-transistor branch having quiescent power dissipation of $100\ \mu\text{W}$, output voltage of $1.5\ \text{V}$, and negative feedback loop-gain of $75\ \text{dB}$. Consider that the input reference voltage is $1.2\ \text{V}$ and open-loop gain of the constituent OTA is $40\ \text{dB}$. | 10 |
| d) | Design a <i>Beta Multiplier Current Reference</i> for generating $10\ \mu\text{A}$ output current (using any necessary assumption) and draw the final designed circuit. Discuss the necessity of a start-up circuit for this, using circuit diagram. Mention if there is any resultant limitation on the supply voltage range for the overall circuit. | 10 |
