

**B.E. ELECTRONICS AND TELE-COMMUNICATION ENGINEERING
SECOND YEAR SECOND SEMESTER EXAM, 2025**

ANALOG CIRCUITS- II

Time: 3 hours

Full Marks: 100

(All parts of the same question must be answered together)

use separate answer script for each part

PART-I (70)

Answer Any Three (3×20=60) CO1, CO2, CO3

1.
 - a) Why are multistage amplifiers used in electronic circuits? Discuss the different types of coupling methods used in multistage amplifiers. [3+3]
 - b) Explain that the gain bandwidth product of a capacitive coupled CE amplifier is constant. [4]
 - c) Determine mid frequency voltage gain, input resistance and output resistance with the help of small signal equivalent circuit of two stage amplifiers using MOSFETs. [10]

2.
 - a) Compare power amplifiers and voltage amplifiers, highlighting their key differences. Classify power amplifiers and define them. [3+3]
 - b) With the help of a circuit diagram and load lines determine the maximum conversion efficiency of class-B push-pull amplifier. [5]
 - c) Explain that the practical efficiency of class-B power amplifier is smaller than theoretical maximum. [4]
 - d) An LM380 audio power amplifier is used to deliver 2 W of power to an 8Ω speaker. The amplifier is powered with a 15 V DC supply, and the efficiency of the amplifier is 40%. The maximum junction temperature T_{Jmax} of the IC is 150°C , and the ambient temperature T_A is 35°C . The thermal resistances are: junction-to-case, $\theta_{JC} = 3^{\circ}\text{C/W}$ and case-to-sink, $\theta_{CS} = 1^{\circ}\text{C/W}$. Calculate the maximum allowable thermal resistance of the heat sink θ_{SA} to ensure safe operation. [5]

3.
 - a) What are the advantages of tuned amplifiers? Why cannot tuned circuits be used at audio frequency? [3+3]
 - b) Draw and explain the double tuned amplifier. [4]
 - c) Determine the condition to achieve maximum BW from the frequency response of double tuned amplifiers for different coupling coefficients. [10]

[Turn over

4. a) Draw the schematic of Schmitt Trigger circuit using BJTs and explain the operation. [10]
 b) Find the expression for the time period of square wave produced by astable multivibrator using BJTs. [10]
5. a) What are the various feedback topologies? Explain with block diagrams. [2+8]
 b) What is the topology used in the following circuit (Figure 1) where A is the open loop voltage gain. Find the expression for loop gain and closed loop voltage gain. Calculate input and output impedances of the closed circuit if R_{in} and R_o are input and output resistance of the open loop amplifier. [2+4+4]

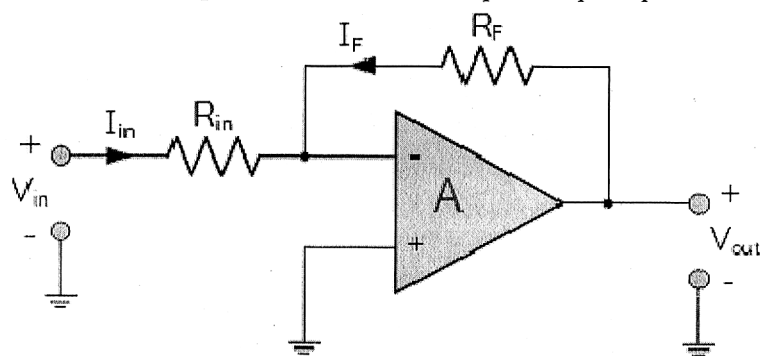


Figure 1

Answer Any One (1×10=10) CO4

6. Design a cascode amplifier for voltage gain =20. Given that $V_{DD}=10V$, $g_m=5mS$. If output capacitance and gate drain capacitance are given as 1pF and 0.1pF respectively, calculate the BW of the amplifier. Compare the calculated BW with a CS amplifier offering the same voltage gain and capacitances. Comment on the result. [10]
7. Design a class C tuned amplifier to amplify 1MHz signal. If the inductor is associated with a series resistance of 10Ω , find the BW of the amplifier. [10]

PART -II

(Answer any two)

Full Marks : 15x2 = 30

1. Using a 555 IC, **implement** an Astable Multivibrator and plot the following waveforms with explanations: $V_{\text{Threshold}}$, V_{Trigger} , $V_{\text{ff-Set}}$, $V_{\text{ff-Reset}}$, V_{Disch} and V_{Out} . Find the value of external **components** so that $T_H = 1\text{msec}$ and $T_L = 0.5\text{msec}$. (Assume the SR flip-flop used in the IC is a positive edge trigger FF, and use 5V supply voltage for your design)
[Marks: 2+9+4=15]

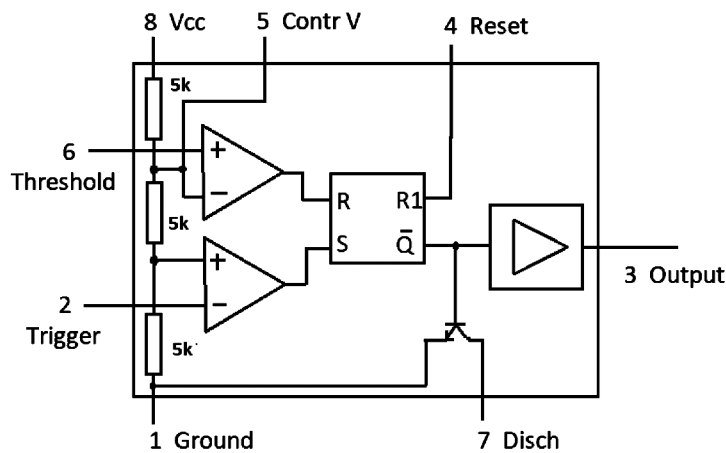


Figure 1

2. For the voltage-controlled oscillator shown in Figure 2, derive the expressions for T_L and T_H . If the input voltage to the circuit is 5V and the supply voltage of each Op-amp is $\pm 15\text{V}$, plot V_{Cap} (voltage across the capacitor), V_{out1} , and V_{out2} with respect to time.

[Marks: (3+3)+(3+3+3)=15]

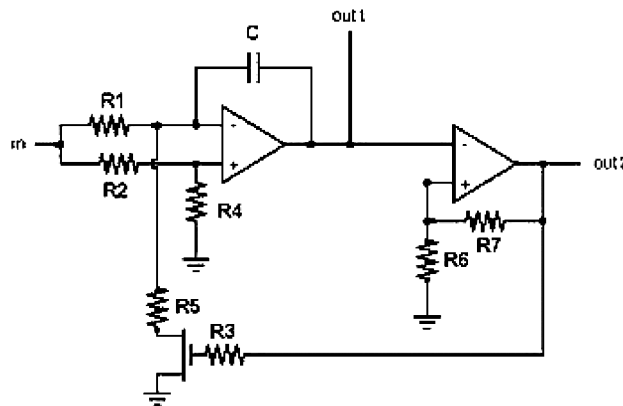


Figure 2

3. An astable multivibrator circuit is modified as shown in figure 3. Assume the diode shown in the figure is ideal. Plot waveforms V_{01} , V_{02} , V_{x1} , and V_{x2} with respect to time (use proper labels, shapes, and maintain approximate visualization of duty cycle and voltage values in your plot). Calculate the **time period** and **duty cycle** of the output waveform V_{02} .

[Marks: (3+3+3+3)+(2+1)=15]

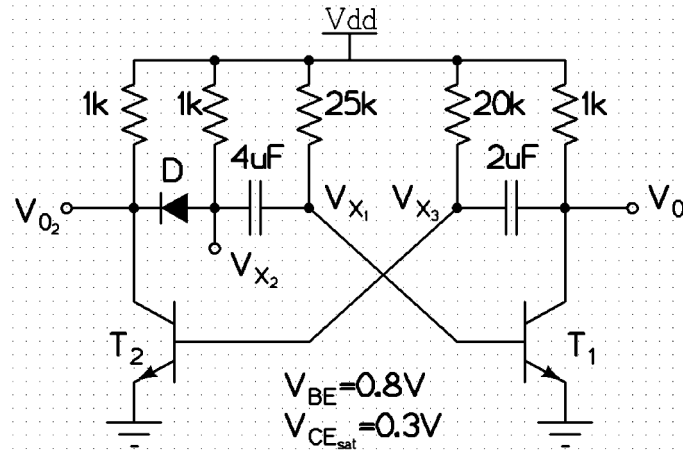


Figure 3

4. The circuit shown in Figure 4 is implemented using all ideal components with sufficient supply voltage to the Op-amps. If $R = 10K\Omega$ and $C = 1\mu F$ find the **Condition** for sustained oscillation and the **Frequency** of oscillation (in Hz).

[Marks: 10+5=15]

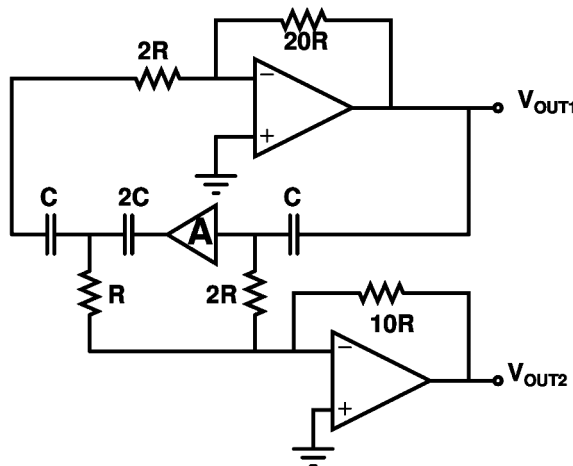


Figure 4