

**B.E. ELECTRONICS AND TELE-COMMUNICATION ENGINEERING SECOND YEAR
FIRST SEMESTER EXAM - 2025**

ANALOG CIRCUITS-I

Time: Three hours

Full Marks: 100

(All parts of the same question must be answered together)

Module I [Answer any one (1×10=10)] CO1

1. Explain the necessity of a filter in rectifier circuits. Illustrate a centre-tapped full wave rectifier with a capacitive filter. Draw the output waveforms for two different load conditions and justify. [2+4+4]

OR

Discuss the role of a capacitor in clamper circuits. Identify the circuit in fig. 1. Explain its operation and draw the output waveform for sinusoidal input. [2+1+(4+3)]

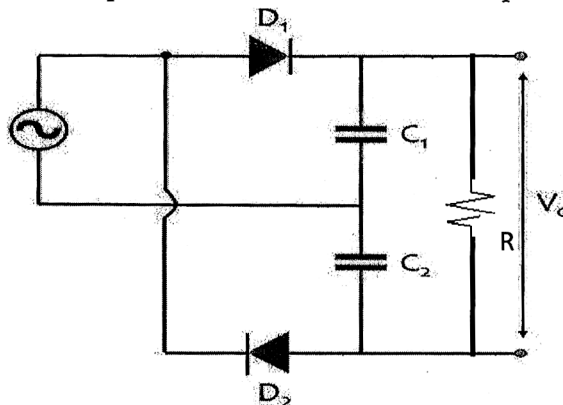


Figure 1

Module II [Answer any one (1×10=10)] CO2

2. Analyze the response of a low-pass RC circuit to a square wave input (10 V amplitude, 4 ms period). Sketch and annotate the capacitor voltage waveform ($V_C(t)$) over two cycles. [5+5]

OR

Explain RC circuit as differentiator and integrator with examples. For a differentiator circuit ($R=1\text{k}\Omega, C=0.1\mu\text{F}$), sketch the output waveform for a 1 kHz triangular wave input. [6+4]

[Turn over

**B.E. ELECTRONICS AND TELE-COMMUNICATION ENGINEERING SECOND YEAR
FIRST SEMESTER EXAM - 2025**

ANALOG CIRCUITS-I

Time: Three hours

Full Marks: 100

Module III [Answer any five from Q3A and any five from Q3B (5×6+5×2=40)] CO3

- 3.A**
- Explain how temperature variation affects the stability of operating point in a BJT biasing circuit. [6]
 - Explain a biasing circuit to mitigate the effects of temperature on Q-point. [6]
 - Find the operating point of the circuit in fig. 2. $V_{CC}=10V$, $R_C=2\text{ K}\Omega$, $R_E=1\text{ K}\Omega$ and $R_B=47\text{ K}\Omega$. Show the operating point on load line. [4+2]
 - With the help of small signal (g_m - r_π) equivalent circuit find the expressions for input impedance, output impedance and voltage gain of a CE amplifier. [6]
 - Draw the frequency response of RC-coupled amplifier and explain different regions of operation. [6]
 - Determine voltage gain, input impedance and output impedance of an MOSFET amplifier with $R_D=1\text{ k}\Omega$, $R_S=220\Omega$, $V_{DD}=5V$, $V_D=2.5V$, $V_{GS}=1V$ and $V_{th}=0.5V$. [6]
 - Compare CS, CD and CG amplifier configurations with respect to A_v , R_i & R_o . [6]

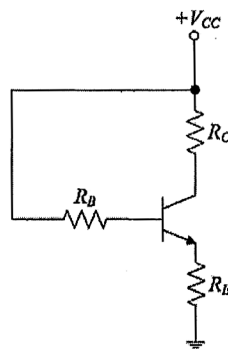


Figure 2

- 3.B**
- Explain the impact of source loading on the performance of a voltage amplifier. [2]
 - Discuss the origin of output resistance in a CE amplifier. [2]
 - Mention advantages of h-parameter model over pi model in small signal analysis. [2]
 - Compare biasing mechanisms of E-MOSFET and JFET. [2]
 - "A positive gate to source voltage cannot be applied for JFET biasing". Explain. [2]
 - What is the purpose of a bypass capacitor in an emitter bias circuit? [2]
 - Why is the bandwidth of a CD amplifier greater than CS amplifier? [2]

Ex/ET/PC/B/T/215/2025

**B.E. ELECTRONICS AND TELE-COMMUNICATION ENGINEERING SECOND YEAR
FIRST SEMESTER EXAM - 2025**

ANALOG CIRCUITS- I

Time: Three hours

Full Marks: 100

Module IV [Answer any questions totaling 25 marks] [CO4]

4. a) Draw and explain a balanced differential amplifier using BJT. [6]
 b) Explain the importance of very high differential gain and very high input impedance of OP-Amp. [4]
 c) Explain virtual short with example. [5]
 d) Draw and explain clamper circuit using OP-Amp. Mention its advantages over clamper without using OP-Amp. [4+1]
 e) Draw and explain the circuit diagram of an Instrumentation amplifier using op-amp. Derive the expression for the output voltage. [10]
 f) Define line and load regulation of a voltage regulator. Explain their importance. [5]
 g) Explain a short circuit protection circuit in a series voltage regulator. [5]
 h) Write characteristics of an ideal voltage buffer. Draw and explain a voltage buffer using OP-Amp. Mention applications. [5]

Module V [CO5]

5. Design a circuit to implement $(3x+5y-2x.y)/5z$ using OP-Amp. [15]

OR

Design a regulated power supply with 10V output. $V_Z=6V$, $P_Z=1W$. Input is 220V 50Hz signal. Assume diodes are ideal. [15]