

**B. E. Electronics and Telecommunication Engineering 2nd Year 1st Semester
Examination- 2025**

Digital Logic Circuits

Time: 3 Hours

Full Marks: 100

Answer all the parts of a question in the same place

Module-I [Answer question no. 1 (1×10) = 10] CO1

1. a) Convert $(11010111)_2$ to Gray code.
b) Perform the subtraction $+62 - (+29)$ using 8-bit 2's complement method.
c) Convert the hexadecimal number $(A2B.3C)_{16}$ to Octal
d) Write the importance of Gray code.
e) Convert the decimal number $(8476.35)_{10}$ to hexadecimal.

(2+2+2+2+2)

Module-II [Answer any three questions (3×10) = 30] CO2

2. a) What do you mean by synchronous counter? Draw a 4-stage synchronous serial counter using J-K flip-flops and logic gates. Sketch the counter output waveform considering 0 propagation delay and write the maximum clock frequency expression considering non-zero propagation delay.
(1+4+5)
3. a) Write the truth table and output expressions of a full subtractor. Implement the full subtractor using minimum number of two input NOR gates.
b) Draw a full subtractor circuit using two half subtractors and single OR gate.
(8+2)
4. a) What is an encoder? Write the truth table of a decimal-to-BCD encoder and draw corresponding gate level circuit.
b) Draw the block diagram of a BCD adder and label corresponding inputs and outputs.
(7+3)

[Turn over

5. a) Draw the circuit of a master-slave D flip-flop using NAND gates only and explain its operation briefly.
 b) What do you mean by excitation table?
 c) write the excitation table of a J-K flip-flop.


(6+2+2)

Module-III [Answer any four questions (4×10) = 40] CO3

6. a) Design a 4-input OR gate using one 4:1 multiplexer and one 2-input OR gate. Assume constants 0 and 1 are available.
 b) Implement the Boolean function $F(x, y, z) = x'y + yz + xz'$ using minimum number of 2:1 multiplexer and a single inverter only.
 c) Simplify the logic function $F(w, x, y, z) = \sum m(0, 1, 3, 7, 8, 9, 11, 15)$ using Karnaugh map method.

(3+3+4)

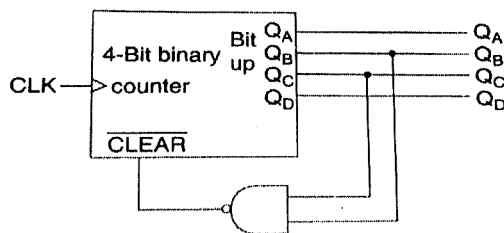7. a) Determine the MOD value of the synchronous counter shown in the following figure. Also write corresponding counter states.



- b) Design a decade counter using direct reset inputs. Also, sketch the corresponding counter circuit using minimum number of J-K flip-flops and logic gates.
 c) What is lockout of a counter? How it can be removed?

(3+5+2)


8. a) Implement the following Boolean functions using a decoder and minimum number of 2-input OR gates.

$$F_1(A, B, C, D) = \sum (1, 3, 5, 6, 14, 15);$$

$$F_2(A, B, C, D) = \sum (4, 6, 7, 12, 14);$$

$$F_3(A, B, C, D) = \sum (1, 4, 5, 6, 15);$$

 - b) Given logic module P that compares the magnitudes of two 3-bit number $X_3 = x_1x_2x_3$ and $Y_3 = y_1y_2y_3$, where x_3 and y_3 are the least significant bits. Module P has two outputs G3 and S3, such that $G3 = 1$ if $X_3 > Y_3$; $S3 = 1$ if $X_3 < Y_3$; and $G3 = S3 = 0$ if $X_3 = Y_3$. Design the logic unit Q such that together with module P it will serve as a comparator for two 4-bit numbers $X_4 = x_1x_2x_3x_4$ and $Y_4 = y_1y_2y_3y_4$ as shown in the following figure. Find the expressions for G4 and S4 in terms of the inputs to unit Q and show a realization of these expressions using NAND gates only.



(4+6)

9. a) Define propagation delay and noise margin for a logic family.
 b) Draw a 2-input CMOS XNOR gate using minimum number of transistors.
 c) Why is the static power dissipation low in CMOS circuits?


(4+4+2)

10. a) Design a sequence generator to produce the output sequence 1110010.
 b) Draw the state diagram of a sequential circuit that detects three or more consecutive 1's in a string of bits coming through an input line.

(7+3)

Module-IV [Answer any two questions (2×10) = 20] CO4

 11. a) With a neat sketch, briefly explain the operation of a 4-bit R-2R ladder Digital to Analog Converter (DAC).
 b) The output of a three stage Johnson (switch-tail ring) counter is fed to a DAC. Assume that the counter initially at reset state. Draw the waveform at the DAC output.
 (7+3)
12. a) With a neat sketch, briefly explain the operation of a 3-bit parallel (flash) type ADC.
 b) Draw a simplified logic diagram of a 12-hour digital clock, label each block of your design and mention their specifications.
 (7+3)
13. a) What do you mean by resolution and settling time of a DAC? Write their importance for hardware based system design.
 b) An ADC has a total conversion time of 200 μ s. What is the maximum frequency that its analog input should be allowed to contain?
 c) Determine the frequency of the pulses at points w, x, y and z in the following figure. Give logic in each case.



(4+2+4)