

Department of Instrumentation and Electronics Engineering

3rd year, 1st semester Examination, 2025

Subject: VLSI Design

Full Marks-100

Time-3hrs

MODULE-1

(Answer any three)

6 × 3 = 18

1. What are the advantages and disadvantages of IC? What are the different steps a typical IC fabrication process consists of? 3+3
2. Write the use of SiO₂ as a passivating layer. For a controlled doping in a narrow gate region, which doping technique should be used and why? 2+4
3. What is the function of photoresist in the fabrication process? State differences between positive and negative photoresist. 3+3
4. Describe the basic steps in MOS fabrication process with suitable diagram. 6

MODULE-2


(Answer any six)

12 × 6 = 72

5. Consider a CMOS inverter circuit with the following parameters: $V_{DD}=3.3V$, $V_{TO,n}=0.6V$, $V_{TO,p}=-0.7V$, $k_n=200\mu A/V^2$, $k_p=80\mu A/V^2$. Calculate the noise margins of the circuit. 12
6. a) “ It is not customary to shuffle the NMOS and PMOS in pull-down and pull-up network in a CMOS inverter “-Justify your answer. 6
 b) State advantages of CMOS inverter over depletion load NMOS inverter configuration. Draw a neat diagram for both inverter configurations. 6
7. a) Show that in a CMOS inverter for symmetric switching requires, $\left(\frac{W}{L}\right)_p \approx 2.5 \left(\frac{W}{L}\right)_n$ for all practical purposes, where, $\mu_p = 230 \text{ cm}^2/V.s$ and $\mu_n = 580 \text{ cm}^2/V.s$. 6
 b) How the switching threshold in a CMOS inverter shifts when $\frac{k_n}{k_p} > 1$. Show using suitable voltage-transfer characteristics curve. 6

[Turn over

 8. Calculate the critical voltages $V_{OL}, V_{OH}, V_{IL}, V_{IH}$ and find the noise margins of the following depletion-load inverter circuit: 12




$$\begin{aligned} V_{DD} &= 5V \\ V_{T0,driver} &= 1.0V \\ V_{T0,load} &= -3.0V \\ (W/L)_{driver} &= 2, (W/L)_{load} = 1/3 \\ k_{n,driver}' &= k_{n,load}' = 25\mu A/V^2 \\ \gamma &= 0.4V^{1/2} \\ \phi_F &= -0.3V \end{aligned}$$

9. Consider the following Boolean Expression:

$$Z = A(B + C) + DE$$

- a) Calculate equivalent driver $\left(\frac{W}{L}\right)$ ratio of the pull-down network if $\left(\frac{W}{L}\right)_n = 10$ for all NMOS transistors. 5
- b) Suggest a design technique for large fan-in circuits to reduce propagation delay in a CMOS inverter with a suitable example. 7

 10. Consider the circuit of the given figure:




$$\begin{aligned} V_{DD} &= 2.5V \\ (W/L)_2 &= 1.5\mu m/0.25\mu m \\ (W/L)_1 &= 0.5\mu m/0.25\mu m \\ (W/L)_{ni} &= 0.5\mu m/0.25\mu m \\ k_n' &= 115\mu A/V^2, k_p' = -30\mu A/V^2 \end{aligned}$$

Assume the inverter switches ideally at $V_{DD}/2$, neglect body effect, channel length modulation and all parasitic capacitance throughout this problem. Consider $V_{tn}=0.43V$ and $V_{tp}=0.4V$ for the network.

- a. What is the logic function performed by the circuit? 6+6
- b. Explain why this circuit exhibits non-zero static dissipation.

 11. Consider the circuit of the given figure:



The threshold voltage $|V_T|$ for each transistor = 2V. What should be the range of input voltage V_{in} , for the circuit to work as an inverter. Analyse the operation of the circuit to estimate the output voltage V_o .

MODULE-3

(Answer any one)

10 × 1 = 10

12. a) Discuss different physical defects in a chip. How are they translated into electrical and logical faults? 5
- b) Explain the relationships between physical defects, electrical faults and logical faults using a simple NOR 2 logic. 5
13. Describe the essential circuit modules for built-in self-test design. 10