

Ref. No.: Ex/PE/PC/B/T/215/2025

**B. POWER ENGINEERING EXAMINATION -2025**  
 (2<sup>nd</sup> Year – 1<sup>st</sup> Semester)  
 SUBJECT – Circuit Theory

Time: Three hours

Full Marks: 100

Answer any **five** questions as directed under each group


Assume suitable value for missing data, if any

All the values of resistors are in  $\Omega$ .

**All parts of a question to be answered at one place.**

| No. of Question |                                                                                                                                    | Marks |
|-----------------|------------------------------------------------------------------------------------------------------------------------------------|-------|
|                 | Group A (CO1)<br>Answer <b>any one</b> questions                                                                                   |       |
| 1.(a)           | What is a supernode? Explain the techniques for the solution of networks having supernodes with suitable example.                  | 6     |
| (b)             | For the network as shown below, Find the node voltages and hence find current through the $4\Omega$ resistor using nodal analysis. | 14    |
|                 | <p style="text-align: center;">Fig. 1</p>                                                                                          |       |
| 2. (a)          | State and explain Reciprocity Theorem with suitable example.                                                                       | 8     |
| (b)             | Find the voltage $V$ and verify the reciprocity theorem for the circuit shown below.                                               | 12    |

[ Turn over

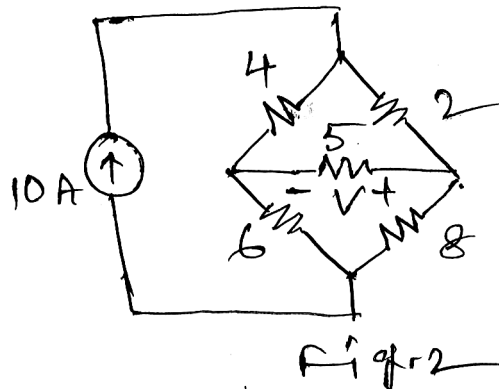

Group B (CO2)  
Answer *any one* question

3. (a) Define and explain the following with suitable examples:

4+3+3

- (i) Distinguish between Cut set and fundamental cut set matrix
- (ii) Tie set matrix
- (iii) Isomorphic graph


(b) The incidence matrix of a directed graph is shown below. Draw the directed graph. Select a particular tree of your choice and write down the fundamental cut set matrix for the same.



10

$$[A] = \begin{bmatrix} 0 & -1 & 0 & 1 & -1 & 0 & 1 & 0 \\ -1 & 0 & -1 & 0 & 0 & +1 & 0 & -1 \\ 0 & -1 & 1 & 0 & 1 & -1 & -1 & 0 \\ 1 & 0 & 0 & -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

4. For the network as shown below, draw the directed graph and write down the fundamental tie set matrix for a particular tree of your choice. Use it to determine loop currents. Source conversion is not permitted.

20

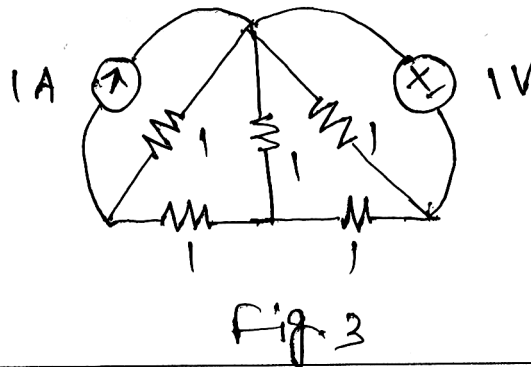
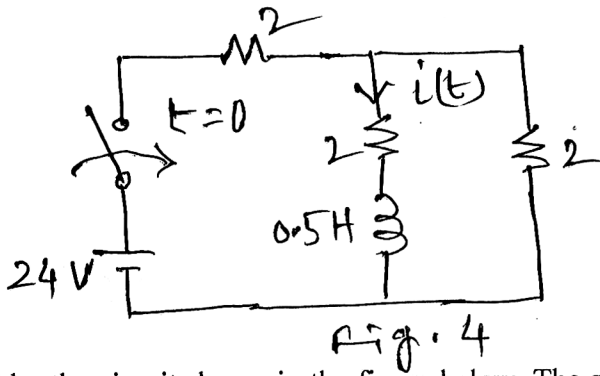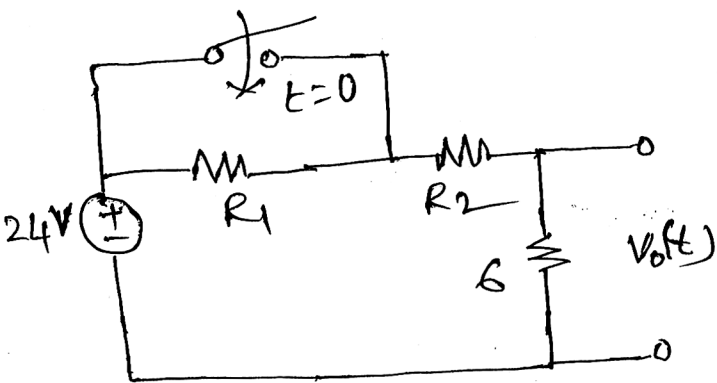
|  |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                      |                                |
|--|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--------------------------------|
|  | <p style="text-align: center;"><b>Group C (CO3)</b><br/>Answer <b>any one</b> question</p> <p>5. (a) State and prove Final Value Theorem and Initial Value Theorem.</p> <p>(b) Using final value theorem, find the steady state value of current <math>i(t)</math> for the network shown below. The switch is closed at <math>t=0</math>. The initial current through the inductor current is assumed to be zero.</p>  <p style="text-align: center;">Fig. 4</p> <p>6. Consider the circuit shown in the figure below. The switch is closed at time <math>t = 0</math>. The input to the circuit is the voltage of the voltage source, 24 V. The output of this circuit, the voltage across the 6 <math>\Omega</math> resistor is given by</p> $v_o(t) = 12 - 6e^{-0.35t} \text{ V} \quad \text{for } t > 0$ <p>Determine the value of inductance <math>L</math> and of the resistances <math>R_1</math> and <math>R_2</math>.</p>  <p style="text-align: center;">Fig. 5</p> | <p>5+5</p> <p>10</p> <p>20</p> |
|--|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--------------------------------|

|                                                                                                                    |                                                                                                                                                                                                                                                                                                                                                                                                                                                       |      |
|--------------------------------------------------------------------------------------------------------------------|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|------|
| <p style="text-align: center;">Group D (C04)</p> <p style="text-align: center;">Answer <i>any one</i> question</p> |                                                                                                                                                                                                                                                                                                                                                                                                                                                       |      |
| 7.                                                                                                                 | Discuss the half wave symmetry of a periodic function with suitable example. Determine the Fourier Series coefficients for such functions                                                                                                                                                                                                                                                                                                             | 5+15 |
| 8.                                                                                                                 | A $6.36 \mu F$ capacitor is connected in parallel with a resistance of $500 \Omega$ and the combination is connected in series with a $500 \Omega$ resistor. The whole circuit is connected across an ac voltage given by $v = 300 \sin \omega t + 100 \sin(3\omega t + \pi/6)$ . If $\omega = 314 \text{ rad/sec}$ , determine (i) power (ii) expression for voltage across the series resistance (iii) % harmonic content in the resultant current. | 20   |
| <p style="text-align: center;">Group E (C05)</p> <p style="text-align: center;">Answer <i>any one</i> question</p> |                                                                                                                                                                                                                                                                                                                                                                                                                                                       |      |
| (9)                                                                                                                | What is reciprocity and symmetry of two port network? Derive the conditions for reciprocity and symmetry in terms of transmission ( $A, B, C, D$ ) parameter and $h$ -parameter representation of a two port network.                                                                                                                                                                                                                                 | 4+16 |
| 10. (a)                                                                                                            | Find $z$ -parameters in terms of in transmission ( $A, B, C, D$ ) parameters and $h$ -parameters                                                                                                                                                                                                                                                                                                                                                      | 10   |
| (b)                                                                                                                | Two two port networks $A$ and $B$ are connected in parallel. Find the $y$ -parameters of the resultant network in terms of $y$ -parameters of the networks $A$ and $B$ .                                                                                                                                                                                                                                                                              | 10   |