## B.E. ELECTRICAL ENGINEERING (PART TIME) SECOND YEAR SECOND SEMESTER 2019

(1st-/2nd Semester/Repeat/Supplementary/Annual/Bi-Annual)

## SUBJECT: - SEQUENTIAL SYSTEMS AND MICROPROCESSOR

Time: Three hours

Full Marks 100 (50 marks for each part)

Use a senarate Answer-Script for each part

No. of Questions	Use a separate Answer-Script for each part PART I	Marks
	Answer any three Questions  Two marks are for neat and systematic answers	
Q1.	<ul> <li>a) Describe the terms NO, NC and Rung in the context of ladder diagram.</li> <li>b) A system is described by,Y=A(B+AB)+B.(A+AB) <ol> <li>i) Simplify the system using Boolean Algebra</li> <li>ii) Implement the simplified expression through ladder diagram.</li> <li>iii) Implement the original expression through ladder diagram.</li> </ol> </li></ul>	6 10
Q2.	<ul><li>a) Explain the advantages of programmable logic over a relay logic based system. With the help of neat sketch show the essential parts of a relay.</li><li>b) Draw and explain the block diagram of a 4-bit shift left register using D-FF.</li></ul>	8
Q3.	<ul><li>a) Enumerate the difference between the excitation table and truth table. With help of truth tables develop the excitation table of J-K and T FF.</li><li>b) What is state diagram? Explain different symbols that are used to draw state diagram of a sequential system.</li></ul>	4+6
Q4.	a) Define Propagation delay time, Set-up time and Hold time in the context of flipflop operation.	8
	b) What is tri-stating logic? Define Read Cycle time, Write Cycle time and Access time with respect to the specification of a memory chip.	8

### B.E. ELECTRICAL ENGINEERING (PART TIME) SECOND YEAR SECOND SEMESTER 2019

(1st / 2nd Semester/Repeat/Supplementary/Annual/Bi-Annual)

### SUBJECT: - SEQUENTIAL SYSTEMS AND MICROPROCESSOR

Time: Three hours

Full Marks 100 (50 marks for each part)

Use a separate Answer-Script for each part

No. of Questions	Use a separate Answer-Script for each part PART I	Marks
Q5.	<ul> <li>a) Draw the PLC Ladder diagram and the power circuit diagram for a DOL starter for three phase induction motor with following description:</li> </ul>	12
	The motor will be ON when START button is pressed. The system is having a STOP switch and an overload protection for safety purpose.	
	b) What are field switches? Name four field switches that are commonly used in PLC based system.	4

#### PART - II

# Answer any three questions.

Two marks are for neatness and well organised answer.

6.	a) Draw the block diagram of Intel 8085 Microprocessor.	8
	b) Explain the requirement of Accumulator, Program Counter, Flags in Intel 8085	8
	Microprocessor.	
7.	a) Discuss the function of ALE, IO/M, READY, HOLD signals in Intel 8085 microprocessor.	8
	b) Draw and explain the timing diagram for memory read operation.	8
8.	a) Classify 8085 instructions in various groups. Give instructions for each group.	8
	b) Explain the operation is performed when the following instructions are executed:	8
	DAD rp, DAA, CMP r, CMP M, CMA, RAL, RAR, and SHLD addr	
9.	a) Discuss different types of Addressing Modes of Intel 8085 with suitable example.	8
	b) What is Stack? What is the function of Stack Pointer? Discuss PUSH and POP operation.	8
10.	a) Write an assembly language program to add two 8-bit numbers, the sum may be 16-bits.	6
; ;	b) Write an assembly language program to find the largest number in a data array.	10