

Ref. No.: Ex/Prod/ET/T/125/2019(Old)
B.E. PRODUCTION ENGINEERING
FIRST YEAR SECOND SEMESTER (Old) EXAM 2019

Subject: Basic Electronics Engineering

Time : Three hours

Full Marks: 100

All parts of the same question must be answered at one place only

I. Answer any two(2) from Q. 1 (a), (b) and (c) in this block:

- 1. (a)** i. Cut-in voltage of silicon and germanium PN junction diode is ____ and ____.
ii. In P type semiconductors, the majority carriers are ____ and, in N type semiconductors, the majority carriers are ____.
iv. Differentiate semiconductor, conductor and insulator.
v. Define hole and electron in a semiconductor.

[4+3+3]

- (b)** i. An ideal diode offers ____ resistance when forward biased, and ____ resistance when it is reverse biased.
ii. Draw and explain the VI characteristics of a PN junction diode.
iii. What is an intrinsic semiconductor?
iv. What are the majority carrier and minority carrier of p type and n type semiconductor.

[2+4+2+2]

- (c)** i. What is doping? Why it is needed?
ii. Name the elements which are used as N-type impurities and P-type impurities.
iii. Explain the operation of a PN junction diode under no bias condition.
iv. What is meant by the term “Barrier potential”? What is its value for Germanium diode? [3+2+3+2]

II. Answer any three(3) from 2 (a), (b), (c) and (d) in this block:

- 2. (a)** i. Draw the circuit diagram of centre tap half-wave rectifier and explain its operation.
ii. Discuss the working of full-wave rectifier circuit and give the output voltage waveform.
iii. Define breakdown voltage. [4+4+2]

- (b)** i. State whether the statement is true or false:
i.i A transistor has two PN junction.
i.ii The emitter of a transistor is heavily doped.
i.iii Base has the biggest size in a transistor.
i.iv The value of α of a transistor is less than 1.
ii. Draw and explain a fixed bias circuit. [4+6]

- (c)** i. Explain the CE configuration of BJT with circuit diagram, input and output characteristics.
ii. Derive the relation between α , β . [6+4]

- (d)** i. State whether the statement is true or false:
i.i In P-type semiconductor, the majority carriers are hole.
i.ii A full-wave rectifier utilizes only positive half cycle.
i.iii For a half-wave rectifier : $PIV = 2V_m$.

[Turn over

- ii. Distinguish between zener breakdown and avalanche breakdown.
 iii. What is Q point? [4+4+2]

III. Answer 3 (a) OR (b) in this block.:

3. (a) i. Compare class A, class B and class C amplifier.
 ii. Define cross over distortion and how it can be overcome?
 iii. What do you mean by efficiency in power amplifier? [4+3+3]
- (b) i. Explain the working of schmit trigger with proper circuit diagram
 ii. Describe the working of astable multivibrator with a neat circuit diagram [3+3+4]

IV. Answer any three (03) from 4 (a), (b), (c) and (d) in this block:

4. (a) i. Convert base of the following numbers:
 i.i. $(64.5)_{10} \equiv (?)_2$
 i.ii. $(7CA3)_{16} \equiv (?)_8$
 i.iii. $(742.46)_8 \equiv (?)_2$
 ii. Obtain 2's complement of $(1010100)_2$ and $(1101001)_2$.
 iii. Subtract (i) $(1110)_2$ from $(10101)_2$ and (ii) $(10011)_2$ from $(11101)_2$ (without converting base). [6+2+2]
- (b) i. State De-Morgan's theorem. Show its logic implementation.
 ii. Simplify the following Boolean expression:
 $f = (A + \overline{BC}) + (\overline{A + BC})$ and $f = AB + ABC + \overline{AB} + \overline{ABC}$ [4+6]
- (c) i. Realize the following two Boolean expressions using basic gates $f = (C(A + B) + D)$ and
 $f = (\overline{AB} + \overline{C})$
 ii. Add (a) $(38)_{10}$ and $(17)_{10}$ and (b) $(84)_{10}$ and $(53)_{10}$ using BCD numbers. [6+4]
- (d) i. Draw the symbols of universal gates. Write their truth table (for 2-input gate).
 ii. Realize AND, OR and NOT using only NAND gates. [4+6]

V. Answer 5.(a) OR (b) from this block:

5. (a) i. Distinguish between combinational circuit and sequential circuits.
 ii. What is a flip-flop?
 iii. Describe the working of SR flip-flop with circuit diagram and truth table. [3+3+4]
- (b) i. What is the difference between latch and flip-flop?
 ii. What is a clock? What is the purpose of the clock signal?
 iii. Draw the circuit diagram of JK flip-flop.
 iv. What is race around in JK flip-flop? [2+2+3+3]