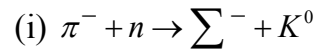


(4)

- (b) Why does a free neutron does not decay into an electron and a positron ?  
(c) Check if the following reaction are allowed or forbidden in strong interaction.



10. (a) Which are the properties, of the solids, that change from normal to superconducting state ?  
(b) 'Zero resistance and perfect diamagnetism are two independent criteria for superconductivity'—Explain the statement. 2+3
11. (a) What is cooper pair ?  
(b) Calculate the current flowing through a Josephson's junction when dc source is applied to it. 1+4
12. (a) Below 10K, what are the important cryogenic temperatures ? What is  $\lambda$  point ?  
(b) What are the special properties of superfluid Helium ? 3+2

Ex:B.SC/PHY/32/H14/GR-A/79/2019

**FINAL B.Sc. EXAMINATION, 2019**

(3rd Year, 2nd Semester)

**PHYSICS (HONOURS)**

**Paper : HO-14**

Time : Two hours

Full Marks : 50

Use separate answer-script for each group.

**GROUP - A**

(Electronics Devices and Circuit II)

Answer *q.no. 5* and any *three* from the rest. 7x3+4


1. (a) Draw the circuit diagram of a two stage RC coupled transistor amplifier and obtain expression for the voltage gain of this amplifier in low frequency range.  
(b) The mid-frequency gain of an amplifier is 120. Find its lower half power frequency if at frequency 100 Hz, the gain falls to 60. 5+2
2. (a) Draw a circuit diagram of Class A direct coupled power amplifier and show its maximum efficiency is 25%.  
(b) Mid frequency gain and bandwidth of an amplifier are 100 and 20 KHz respectively. What would be the new bandwidth if negative feedback of feedback ratio  $\beta = 0.02$  is introduced ? 5+2

— X —

(Turn Over)

(2)

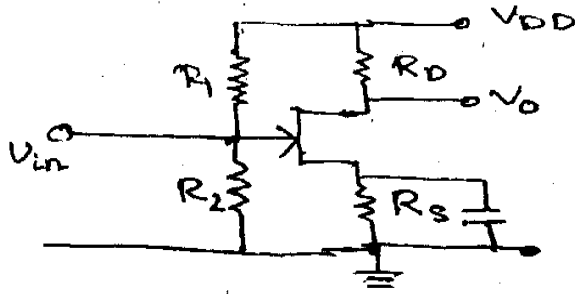3. (a) A n-channel JFET has  $I_{DSS} = 12 \text{ mA}$ . If the transconductance  $g_m$  at  $V_{GS} = 0$  is 4 millimho, find the pinch-off voltage.
- (b) The amplifier circuit uses a n-channel FET with  $V_p = -2\text{V}$  and  $I_{DSS} = 10 \text{ mA}$ . Given  $V_{DD} = 20\text{V}$ ,  $R_1 = 12 \text{ M}\Omega$ ,  $R_2 = 8 \text{ M}\Omega$ ,  $R_D = 1 \text{ K}\Omega$  and  $R_S = 2\text{k}$ . Calculate the drain current ( $I_D$ ).



2+5

4. (a) State and explain Barkhausen criterion for sustained oscillation.
- (b) Draw a circuit diagram of a Hartley oscillator and calculate its frequency of oscillation. 2+5
5. Write short note (any *two*): 2x2=4
- (a) Emitter follower
- (b) Advantages of negative feedback
- (c) Crystal Oscillator

(3)

**GROUP - B (25 marks)**  
 Answer any *five* questions.

6. The most successful predictions between theory and observations of cosmic abundances that we probably do know, correspond a great deal about the state of the Universe during the era spanning 1 to 1000 sec. With the help of Wagonar diagram, briefly describe how the abundances of light elements produce during cosmic nucleosynthesis in this era. 5
7. (a) Write down the names of the elementary particles such as Quarks, Leptons, and Mediators in Standard Model. Listed them in terms of Bosons and Fermions?
- (b) Explain the CPT violation (if any) with an example. 3+2
8. (a) Which particles correspond to quarks compositions uud and udd? Write down the quarks compositions of the ( $\Sigma^+$ ,  $\Sigma^0$ ,  $\Sigma^-$ ) particles.
- (b) The decay  $\Sigma^0 \rightarrow \Lambda^0 + \gamma$  is observed in nature whereas apparently similar decay  $\Sigma^+ \rightarrow p^+ + \gamma$  is never observed. Why? 1+2+2
9. (a) A hadron is symbolized by  $\Omega^-$ . What are its spin, parity, isospin, strangeness, and hypercharge? Is it a boson or a fermion?