

Master of Laser Science and Technology Examination, 2019

(2<sup>nd</sup> Semester)

SUBJECT: Laser Electronics

Time : Three hours

Full Marks 100

Answer any Five questions

- |       |  |    |
|-------|--|----|
| 1. a) | Draw the basic structure of a JFET.  | 4  |
| b)    | Explain the principle of n-channel JFET operation.   | 6  |
| c)    | Discuss the static characterization of the n - channel JFET.   | 5  |
| d)    | How pinch-off occurs in JFET. Explain with diagram.  | 5  |
| 2. a) | Draw the structure of Schottky diode and discuss its operation.  | 10 |
| b)    | Draw V-I characterization of Schottky diode. What is the difference with p-n junction diode.   | 5  |
| c)    | The reverse saturation current at 300 K of a p-n junction Ge-diode is $5 \mu\text{A}$ . Find the voltage to be applied across the junction to obtain a forward current of 50 mA. | 5  |
| 3. a) | Explain full-wave rectifier with a suitable diagram.   | 10 |
| b)    | How the DC output voltage of a full wave rectifier is improved when a capacitor filter is used. Draw waveform of the load voltage and the diode current.                         | 10 |
| 4. a) | What is Diac? Discuss Diac operation by drawing the structure of Diac.   | 8  |
| b)    | Draw a symbol and V- I characteristic of a diac.   | 5  |
| c)    | Write some of its applications. Explain how diac can be used to trigger Triac-Draw circuit.  | 7  |
| 5. a) | What is a unijunction transistor (UJT)?  | 2  |
| b)    | Give its circuit. Draw and explain its current-voltage characterisation.   | 8  |
| c)    | Show how the device can be used on a relaxation oscillator.  | 10 |

6. a) What are the different types of MOSFETS? Explain with a neat sketch the structure and the working of an n-channel depletion MOSFET. How channel depletion results from a negative gate voltage. 10
- b) In the voltage divider circuit fig (a) the JFET has  $I_D=4$  mA, and  $V_{DS}=8$  V. Given: 10  
 $V_{DD} = 24$  V,  $R_1=2$  m $\Omega$ ,  $R_2 = 1$  m $\Omega$ ,  $I_{DSS} = 10$  mA, and  $V_p = -5$  V. Calculate  $R_S$ .  
 What is the channel resistor.

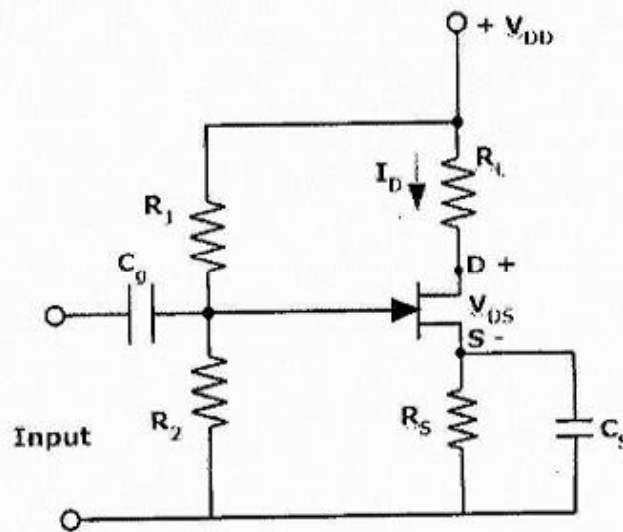


Fig. (a)

7. Write short notes (Answer any four) (4×5=20)
- i. CMOS
  - ii. Chopper circuit
  - iii. Class C commutation
  - iv. Operation of SCR using two transistor model
  - v. McMurray inverter circuit