# Transformation Matrix Models of Machines

Day 10

## ILOs - Day10

- Draw and explain the linear transformation matrix model for
  - DC machine
- Explain operating characteristics there from

- DC machines have salient poles in stator
- Armature winding in rotor is distributed in slots and connected to the commutator segments making it pseudo-stationary
- *d*-axis of the primitive machine is along field poles
- q-axis is along brush axis (inter-polar axis)
- Thus, for DC machines, the 2-pole equivalent structure, and Kron's primitive machine structure are nearly identical

Hence, no transformation is necessary



- However, some more assumptions are necessary for using the generalized mathematical model to a real DC machine
  - The effect of armature MMF along q-axis on total *d*-axis flux is neglected, i.e. the cross-magnetizing and de-magnetizing effects of armature reaction are neglected
    - The commutation process is such that the stationary armature MMF wave is always along *q*-axis
  - Effects of saturation is neglected, i.e. magnetic circuit is assumed to stay linear



- Steady state and transient analysis of DC generators
  - With electrical load connected to the generator armature terminals, the output quantities are voltage, current, and power
  - Voltage equations of Kron's generalized model:





Basic 2-pole DC machine equivalent





Load connected to armature

Generalized Kron's machine

• Steady state and transient analysis of DC generators

Basic 2-pole DC machine equivalent	Generalized Kron's machine
Stator has only DS coil, but QS coil is not present	Stator has both DS and QS coils
Rotor has only QR coil, but DR coil is not present	Rotor has both DR and QR coils



- Steady state and transient analysis of DC generators
  - Comparing with the DC machine model, the matrices can be suitably modified so that rows and columns relating to *qs* and *dr* can be omitted











Load connected to armature

Generalized Kron's machine

- Steady state and transient analysis of DC generators
  - Comparing with the DC machine model, the matrices can be suitably modified so that rows and columns relating to *qs* and *dr* can be omitted:

$$\begin{array}{ccc}
ds & qr \\
\hline v_{ds} \\
v_{qr} \\
\end{array} = \begin{array}{ccc}
ds & r_{ds} + L_{ds} p & 0 \\
qr & M_{d} \omega_{r} & r_{qr} + L_{qr} p \\
\hline i_{qr} \\
\end{array}$$



- Steady state and transient analysis of DC generators
  - Voltage equations

$$\frac{ds}{v_f} = \frac{ds}{qr} \frac{r_f + L_f p}{M_d \omega_r} \frac{0}{r_a + L_a p} \frac{i_f}{-i_a}$$

1

$$v_f = (r_f + L_f p)i_f$$
$$v_t = M_d \omega_r i_f - (r_a + L_a p)i_a$$

• These equations are valid for both steady state as well as transient conditions



## Steady state analysis of DC machine

#### Steady state analysis of DC generators

- Voltage equations  $v_f = (r_f + L_f p) i_f$  $v_t = M_d \omega_r i_f - (r_a + L_a p) i_a$
- At steady state operation, the transient term (derivative, p) is omitted



- At no-load, the armature current is zero, i.e.  $I_a = 0$
- Thus, no-load terminal voltage (induced EMF) is:  $V_t = M_d \omega_{r0} I_f = E_{a0}$
- $E_{ao}$  is the armature terminal voltage at no-load (induced EMF) and at a constant speed  $\omega_{ro}$

• Steady state analysis of DC generators: No-load characteristics

• The plot of  $E_{ao}$  vs.  $I_f$  gives the OCC, or saturation curve, or magnetization curve



- Initially, the open circuit armature voltage  $E_{ao}$  increases linearly with field current
- But, at higher value of  $I_f$ , when the magnetic path saturates, the *rotational mutual inductance* or *motional inductance*  $M_d$  begins to decrease
- The OCC plot starts to bend horizontal indicating saturation

#### Steady state analysis of DC generators: Load characteristics

- Armature EMF at no-load:  $E_{a0} = M_d \omega_{r0} I_f$
- Hence, armature generated EMF at any other speed:

$$V_f = r_f I_f$$
$$V_t = M_d \omega_r I_f - r_a I_a$$



• Thus, armature terminal voltage at any load current  $I_a$  is:

$$V_{t} = E_{a} - r_{a} I_{a}$$
$$= M_{d} \omega_{r} I_{f} - r_{a} I_{a}$$
$$V_{t} = K_{g} I_{f} - r_{a} I_{a}$$

#### • Steady state analysis of DC generators: Load characteristics

$$V_t = K_g I_f - r_a I_a \qquad y = C - mx$$

• The plot of  $V_t$  vs.  $I_a$  gives the load, or external characteristics of a separately excited DC generator



## Transient analysis of DC machine

Transient analysis of DC generators

• Voltage equations 
$$v_f = (r_f + L_f p)i_f$$
  
 $v_t = M_d \omega_r I_f - (r_a + L_a p)i_a$ 

- The generator is running at no-load ( $i_a = 0$ ) with a constant no-load speed  $\omega_{r0}$
- There is sudden application of step field excitation  $V_f U(t)$
- The field circuit transient equation in Laplace domain is:

$$\frac{V_f}{s} = \left(r_f + L_f s\right) I_f(s) \implies I_f(s) = \frac{V_f}{s(r_f + L_f s)}$$

• The armature circuit equation under no-load condition in Laplace domain is:

$$V_t(s) = M_d \omega_{r0} I_f(s) = E_{a0}(s)$$

$$\Rightarrow E_{a0}(s) = M_d \omega_{r0} I_f(s) = M_d \omega_{r0} \frac{V_f}{s(r_f + L_f s)}$$

Transient analysis of DC generators

$$E_{a0}(s) = M_d \omega_{r0} I_f(s) = M_d \omega_{r0} \frac{V_f}{s(r_f + L_f s)}$$

$$\Rightarrow E_{a0}(s) = M_d \omega_{r0} \frac{V_f}{sr_f \left(1 + \frac{L_f}{r_f} s\right)} = M_d \omega_{r0} \frac{V_f}{sr_f \left(1 + \tau_f s\right)} = \frac{M_d \omega_{r0} I_f}{s(1 + \tau_f s)}$$

$$\tau_f = \frac{L_f}{r_f} = \text{field time constant}$$

 $M_d \omega_{r0} I_f = E_{a0}$  = no-load armature terminal voltage (induced EMF) at  $\omega_{r0}$  $\Rightarrow E_{a0}(s) = \frac{E_{a0}}{s(1 + \tau_f s)}$ 

• Expression for generator terminal voltage at no-load under transient condition can be obtained by taking Laplace inverse of the above eqn.

Transient analysis of DC generators

$$E_{a0}(s) = \frac{E_{a0}}{s(1+\tau_f s)}$$

• Expression for generator terminal voltage at no-load under transient condition can be obtained by taking Laplace inverse of the above eqn.

$$e_{a0}(i) = E_{a0}\left(1 - e^{-\frac{t}{\tau_f}}\right)$$

• The transient characteristics looks like:



Transient analysis of DC generators with load

• Voltage equations 
$$v_f = (r_f + L_f p)i_f$$
  
 $v_t = M_d \omega_r I_f - (r_a + L_a p)i_a$ 

- The generator is running at load  $(i_a \neq 0)$  with a speed  $\omega_r$ , load is  $R_L + jX_L$
- There is sudden application of step field excitation  $V_f U(t)$
- The field circuit transient equation in Laplace domain is:

$$\frac{V_f}{s} = \left(r_f + L_f s\right) I_f(s) \implies I_f(s) = \frac{V_f}{s(r_f + L_f s)}$$

• The armature circuit equation in Laplace domain is:

$$V_t(s) = M_d \omega_r \frac{V_f}{s(r_f + L_f s)} - (r_a + L_a s) I_a(s)$$
$$V_t(s) = M_d \omega_r \frac{V_f}{sr_f(1 + \tau_f s)} - (r_a + L_a s) I_a(s)$$

• Transient analysis of DC generators with load

$$V_t(s) = M_d \omega_r \frac{V_f}{sr_f(1+\tau_f s)} - (r_a + L_a s) I_a(s)$$

• The load current expression in Laplace domain:

$$I_L(s) = I_a(s) = \frac{V_t(s)}{(R_L + L_L s)}$$



$$I_a(s)(R_L + L_L s) = V_t(s) = M_d \omega_r \frac{V_f}{sr_f(1 + \tau_f s)} - (r_a + L_a s) I_a(s)$$

$$I_a(s)(R_L + L_L s) = \frac{M_d \omega_r I_f}{s(1 + \tau_f s)} - (r_a + L_a s) I_a(s)$$

 $M_d \omega_r I_f = E_a$  = Induced EMF at  $\omega_r$ 

$$I_a(s)(R_L + L_L s) = \frac{E_a}{s(1 + \tau_f s)} - (r_a + L_a s) I_a(s)$$

$$I_a(s)(R_L + L_L s + r_a + L_a s) = \frac{E_a}{s(1 + \tau_f s)}$$

• Transient analysis of DC generators with load

$$I_{a}(s)(R_{L} + L_{L}s + r_{a} + L_{a}s) = \frac{E_{a}}{s(1 + \tau_{f}s)}$$

$$\Rightarrow I_{a}(s)[(R_{L} + r_{a}) + s(L_{L} + L_{a})] = \frac{E_{a}}{s(1 + \tau_{f}s)}$$

$$\Rightarrow I_{a}(s)(R_{L} + r_{a})\left[1 + s\frac{(L_{L} + L_{a})}{(R_{L} + r_{a})}\right] = \frac{E_{a}}{s(1 + \tau_{f}s)}$$

$$\Rightarrow I_{a}(s)(R_{L} + r_{a})[1 + s\tau] = \frac{E_{a}}{s(1 + \tau_{f}s)}$$

$$\tau = \frac{(L_{L} + L_{a})}{(R_{L} + r_{a})} = \text{Effective armature circuit time constant}$$

$$\Rightarrow I_{a}(s) = \frac{E_{a}}{s(R_{L} + r_{a})(1 + s\tau_{f})(1 + s\tau)}$$
Terminal voltage:  $V_{t}(s) = (R_{L} + L_{L}s)I_{a}(s) = \frac{E_{a}(R_{L} + L_{L}s)}{s(R_{L} + r_{a})(1 + s\tau_{f})(1 + s\tau_{f})(1 + s\tau)}$ 

• Transient analysis of DC generators with load

Terminal voltage: 
$$V_t(s) = (R_L + L_L s)I_a(s) = \frac{E_a(R_L + L_L s)}{s(R_L + r_a)(1 + s\tau_f)(1 + s\tau_f)}$$

To get  $V_t$  in time domain, we need to take Laplace inverse of the above equation (partial fractions)

Armature current: 
$$I_a(s) = \frac{E_a}{s(R_L + r_a)(1 + s\tau_f)(1 + s\tau_f)}$$

To get  $I_a$  in time domain, we need to take Laplace inverse of the above equation (partial fractions)