Read/Write memories consist of an array of registers, in which each register has unique address. The size of the memory is N x M where N is the number of registers and M is the word length, in number of bits.



8085 can access 64Kbytes memory since address bus is 16-bit.

When both, EPROM and RAM are used, the total address space 64Kbytes is shared by them. Generally EPROMs are used for storing Programs and RAMs are used for storing data

program memory (EPROM) should be located from address 0000H since reset address of 8085 microprocessor is 0000H. It is not necessary to place RAMS and EPROMs in consecutive Address blocks

Memory Interface follows the following steps.

- •Select the chip
- •Identify the register
- •Enable the appropriate buffer.

An Example of Memory Interfacing :Full Address Decoding

Consider a system in which 32kb memory space is implemented using four numbers of 8kb memory. Interface the EPROM and RAM with 8085 processor using 2 Nos. 8KB EPROMs



Address lines A0- A12 of the processor are connected to 13 address pins of all the memory.

address lines and A13 - A14 can be decoded using a 2-to-4 decoder to generate four chip select signals

address line A15 can be used to enable the decoder

Device	Binary address														
	Decoder enable/input			Input to address pins of memory IC											Hexa address
	A,15	A	A,3	A12	A,,	A 10	A, A	Α,	A.,	A ₅ A ₄	A.3	A ₂	Α,	A ₀	
, 8kb	0	000	000	0000	. 0 0 0	0000	0 0 0 0 0 0	000	000	0 0 0 0 0 0	000	0 0 0	001	0 1 0	0000 0001 0002
EPROM - I			:	:	:						2			:	:
	ò	ò	ō	i	i	i	iji	i	i	i i	i	i	i	i	1 FFF
8kb EPROM - II	000	000	1	000	0 0 0	000	0 0 0 0 0. 0	0000	000	0 0 0 0 0 0	000	000	001	0 1 0	2000 2001 2002
	:		1	:	:			1:	10 13	11					•
			1	·		•	• • •			• •	÷		·		
	0	Ò	i	i	i	i	i i	i	ì	i i	i	ì	ì	i	3FPF
8kb RAM - I	0000	1	0.00	0000	0000	0000	0 0 0 0 0 0 0	000	000	0 0 0 0 0 0 0 0 0	000	0.0	001	0 1 0	4000 4001 4002
	ò	i	ò	i	i	i	i i	i	i	i i	i	i	ì	1	5FFF
8kb RAM -11	0000	1	1]]	0000	0 0 0	0000	0 0 0 0 0 0	000	000	0 0 0 0 0 0 0	000	000	001	0 1 0	6000 6001 6002
	Ō	i	i	i	i	i	i i	i	i	i i	i	i	i	i	7FFF
					1		12 23	1			1				

An Example of Memory Interfacing: Partial Address Decoding



Decoder Logic is Eliminated Works for small Systems Leads to shadow addresses





At the end of the state T2 in a machine cycle, 8085 processor senses the Ready input pin. If it is logic 0, 8085 processors enter the T wait state, else it enters to the T3 state. The Ready input is permanently fixed to logic 1.

Wait State Generation : Contd..





In T1, the ALE signal is activated, which makes output Q_0 of the first D flip-flop HI.

In the next rising edge of the CLKOUT signal of the 8085, the output of the second D flip-flop goes LO and resets the first D flip-flop making its Q_0 output LO,. At next low to high transition of CLKOUT, f the second D flip-flop goes high making READY pin high and inactivating reset input of the first flip-flop.