


Displacement Transducers

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

Motion Transducers

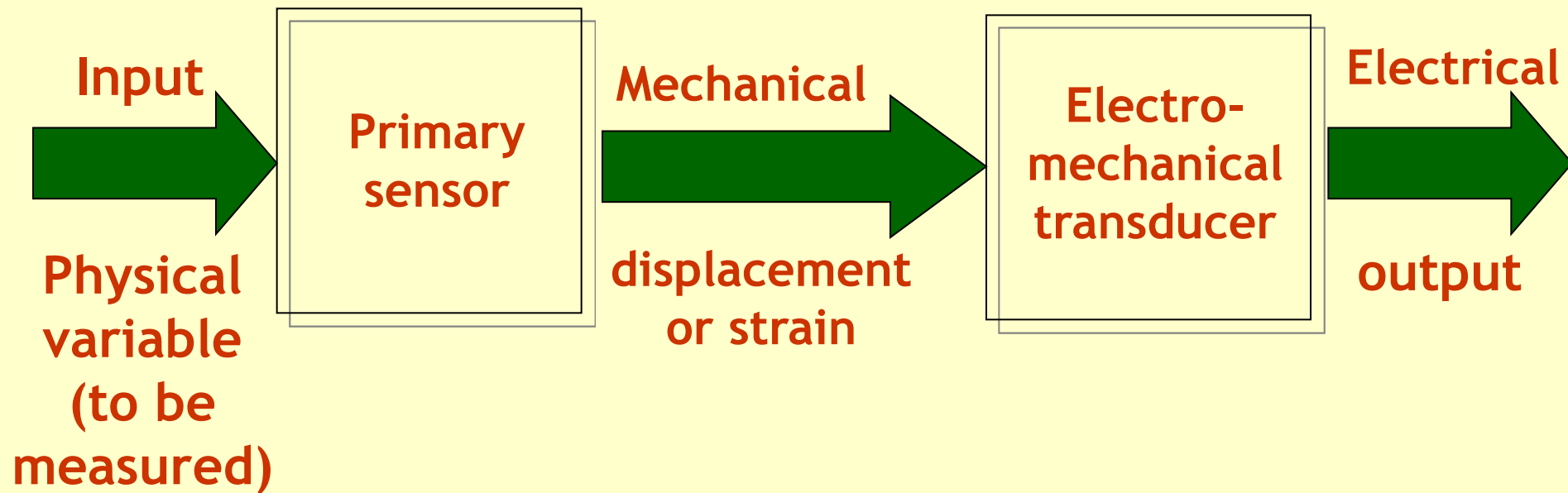- ✓ Electromechanical transducers produce an electrical output in response to an input of mechanical displacement or strain produced by physical variables like pressure, flow etc.




Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

Primary Sensors

Example 1

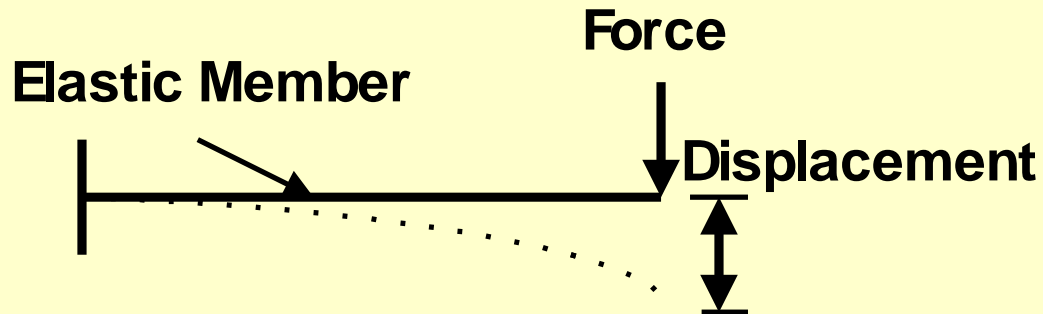


Primary Sensor for Force Input

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

Primary Sensors

Example 2

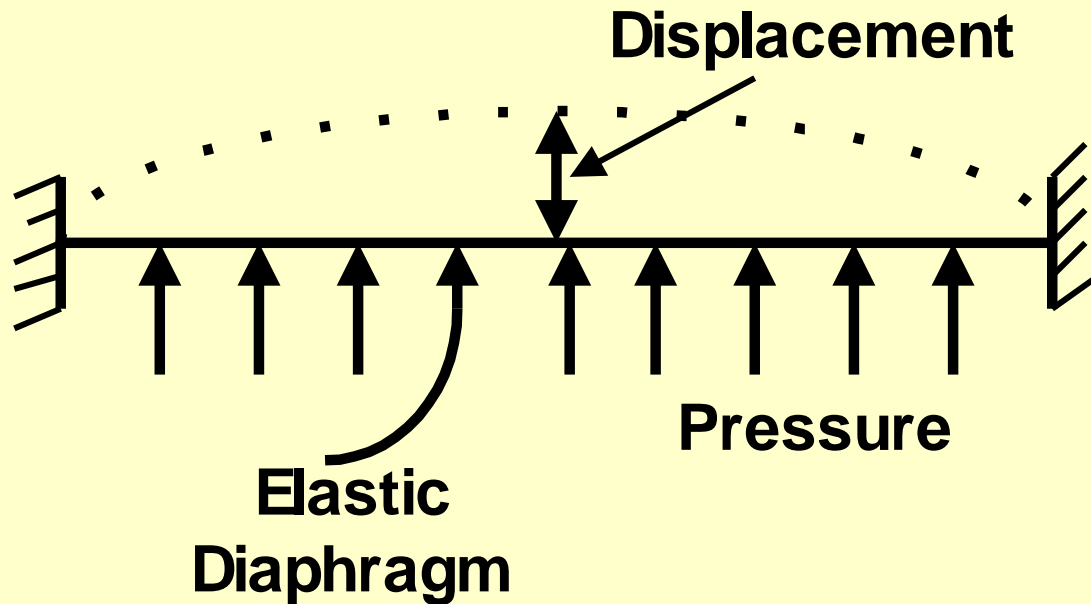


Primary Sensor for Pressure Input

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

Primary Sensors

Example 3

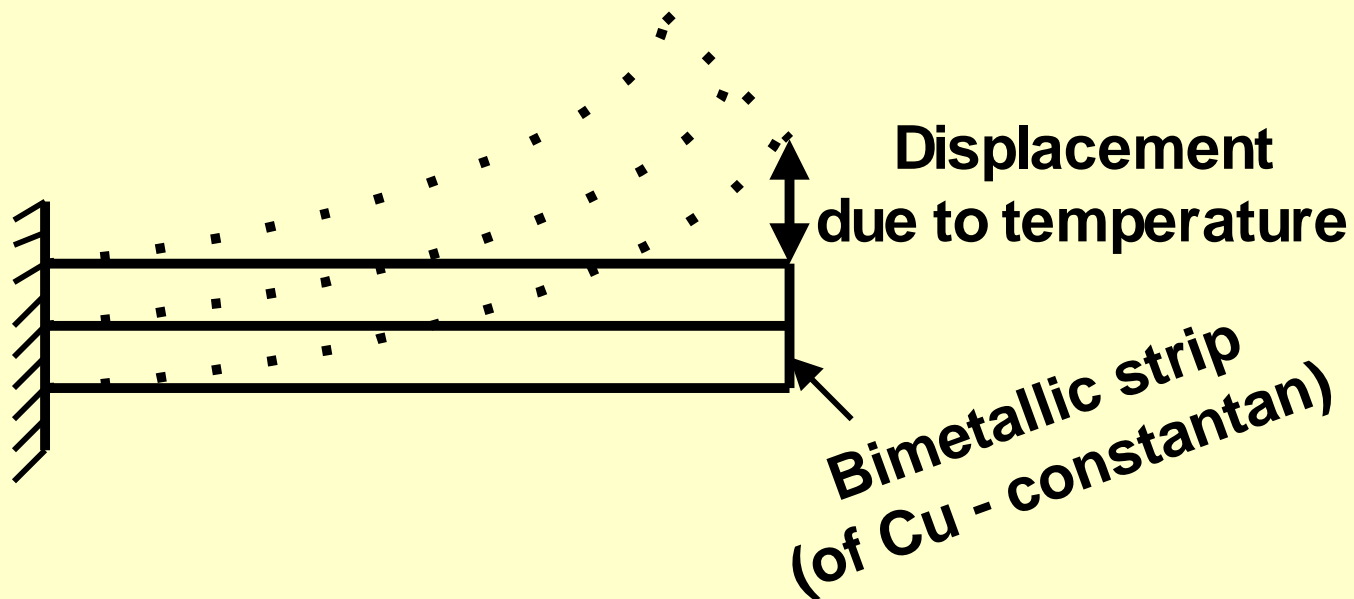


Primary Sensor for Temperature Input

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

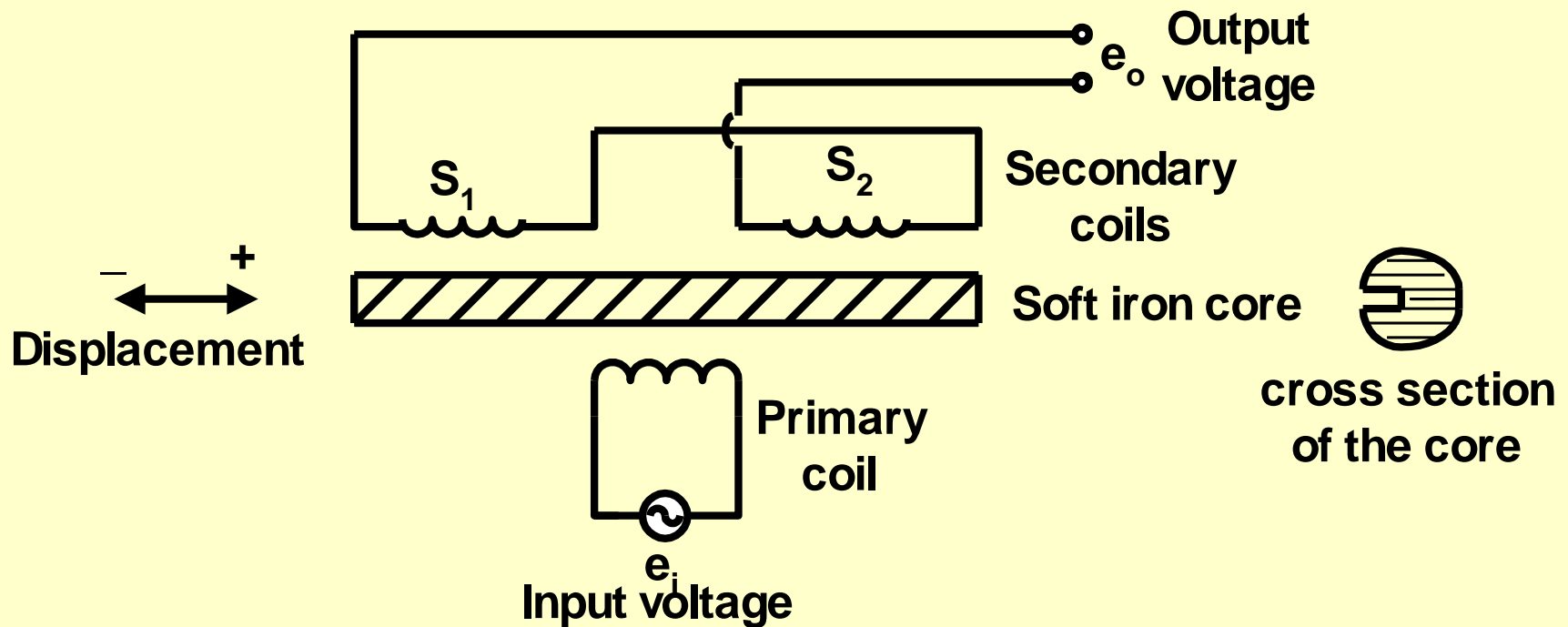Linear Variable Differential Transformer (LVDT)




Schematic diagram of LVDT

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

LVDT (contd....)

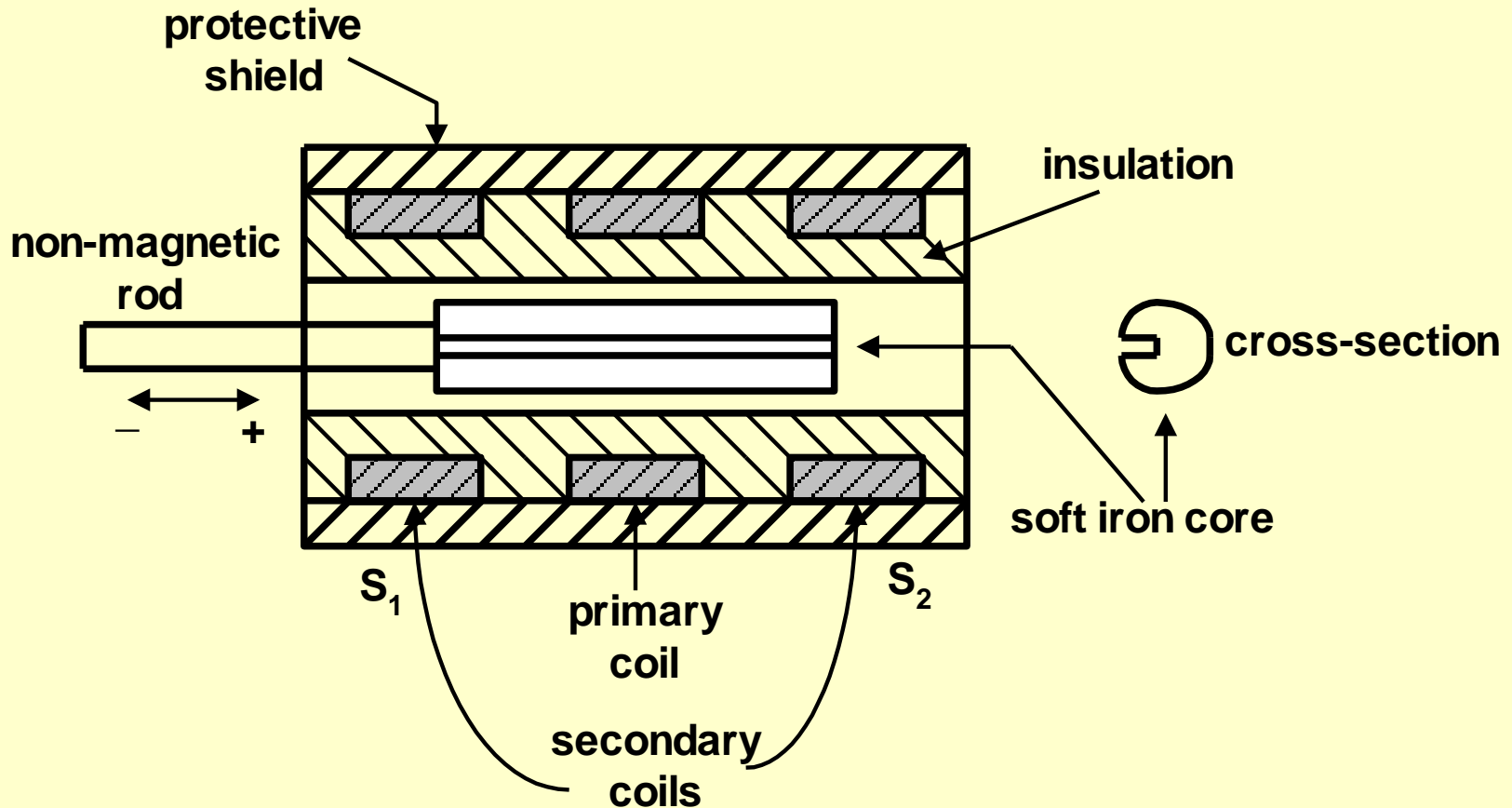


Construction of a commercial LVDT

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

LVDT (contd....)

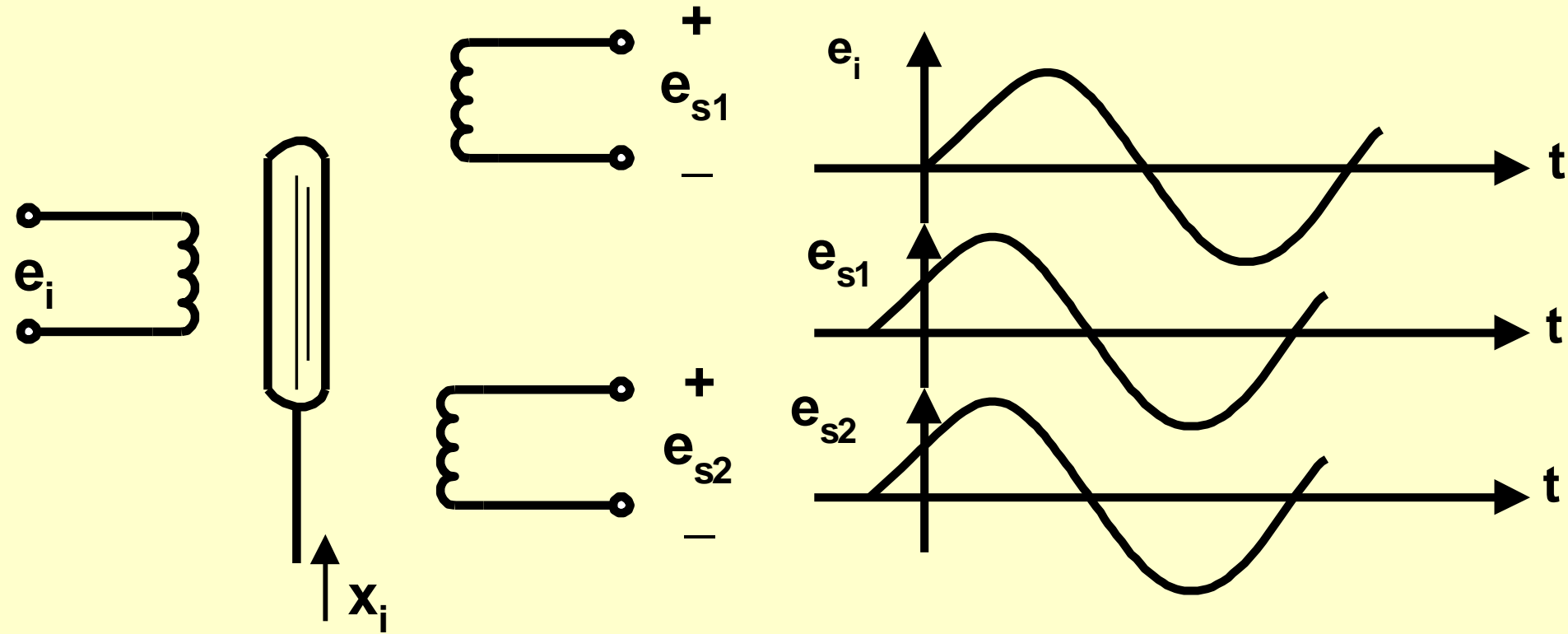


Core in null position


Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

LVDT (contd...)

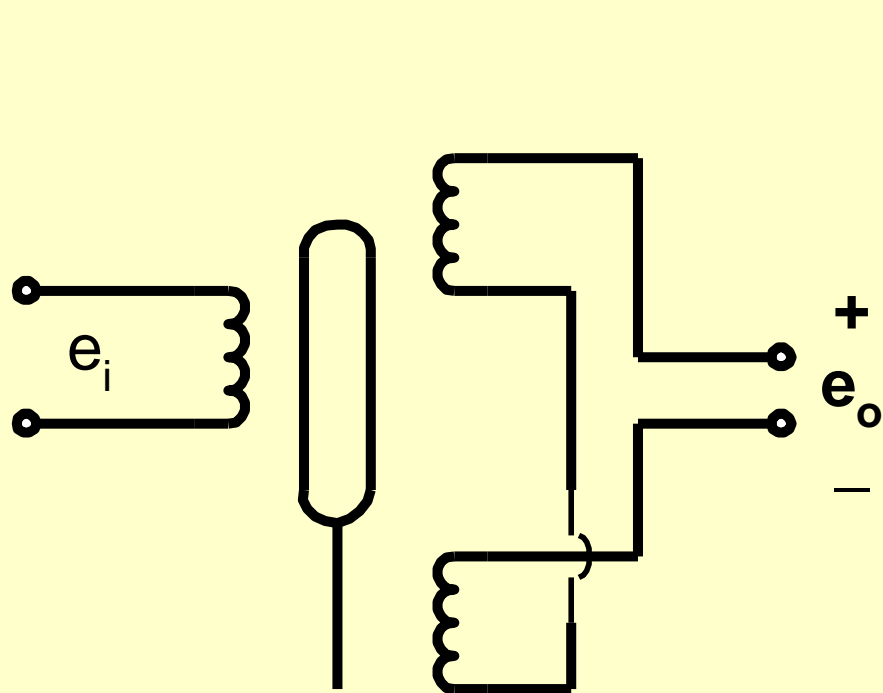


Series opposing secondaries

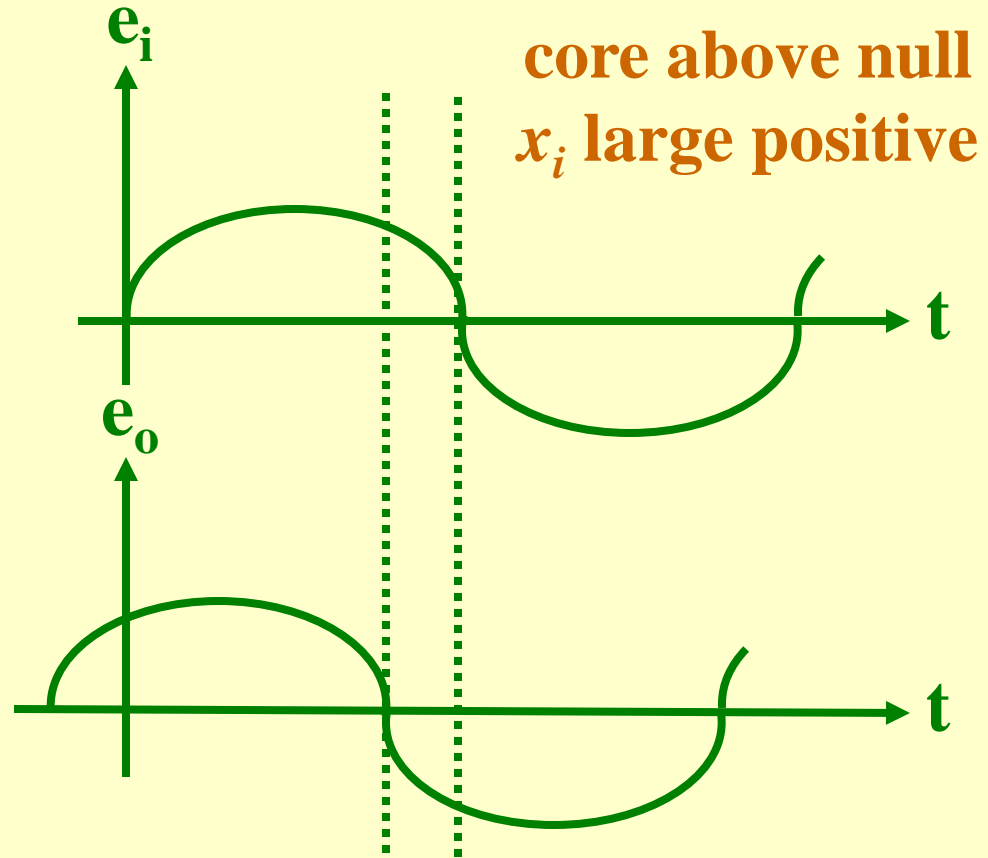


Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

LVDT (contd...)

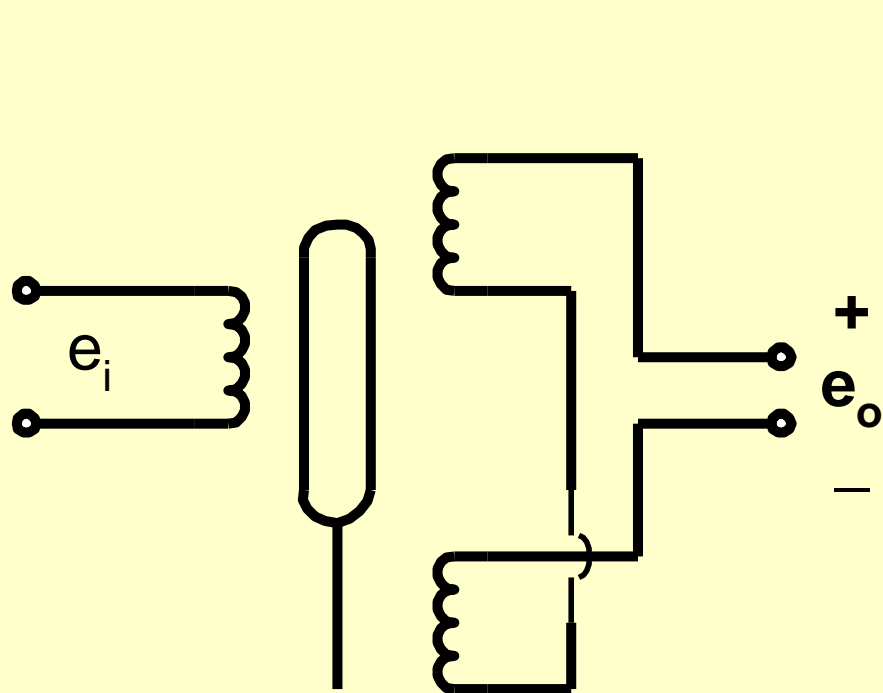


Series opposing secondaries

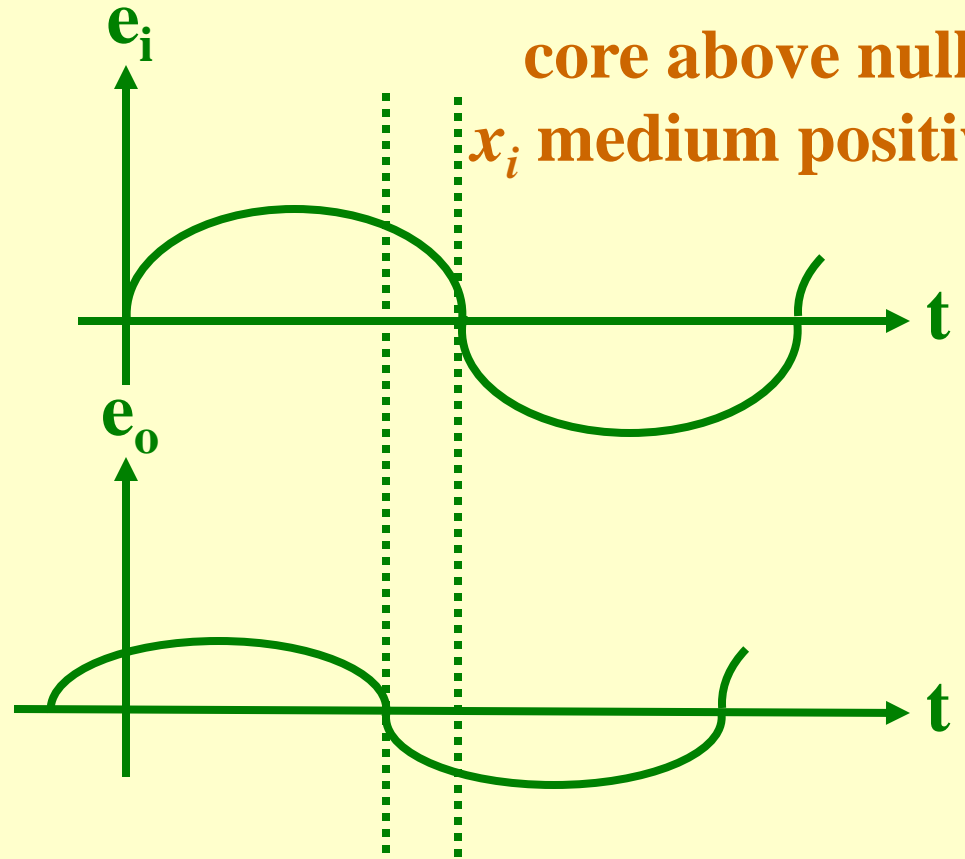


core above null
 x_i medium positive

Amitava Chatterjee

LVDT (contd...)

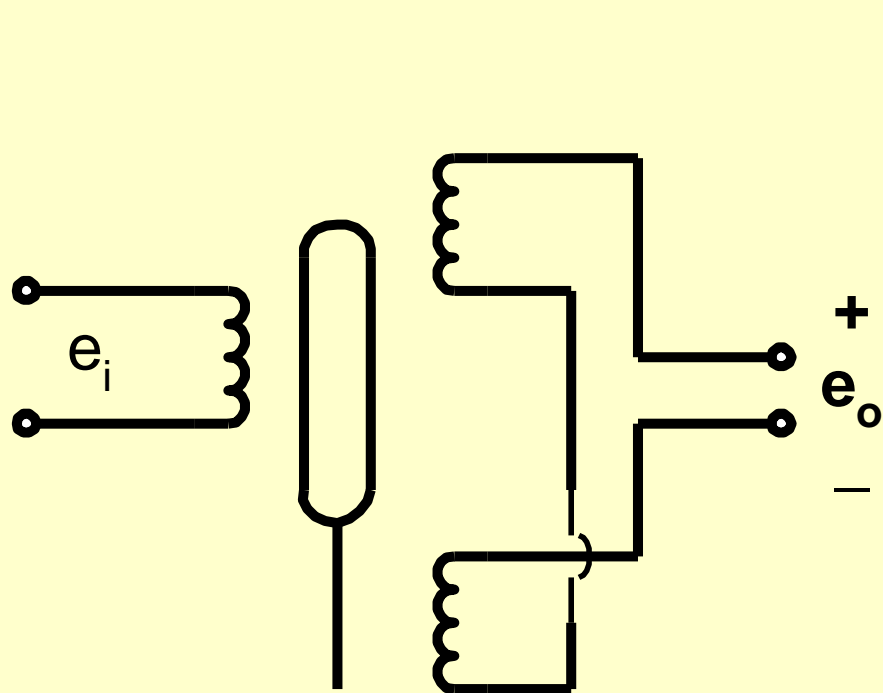


Series opposing secondaries

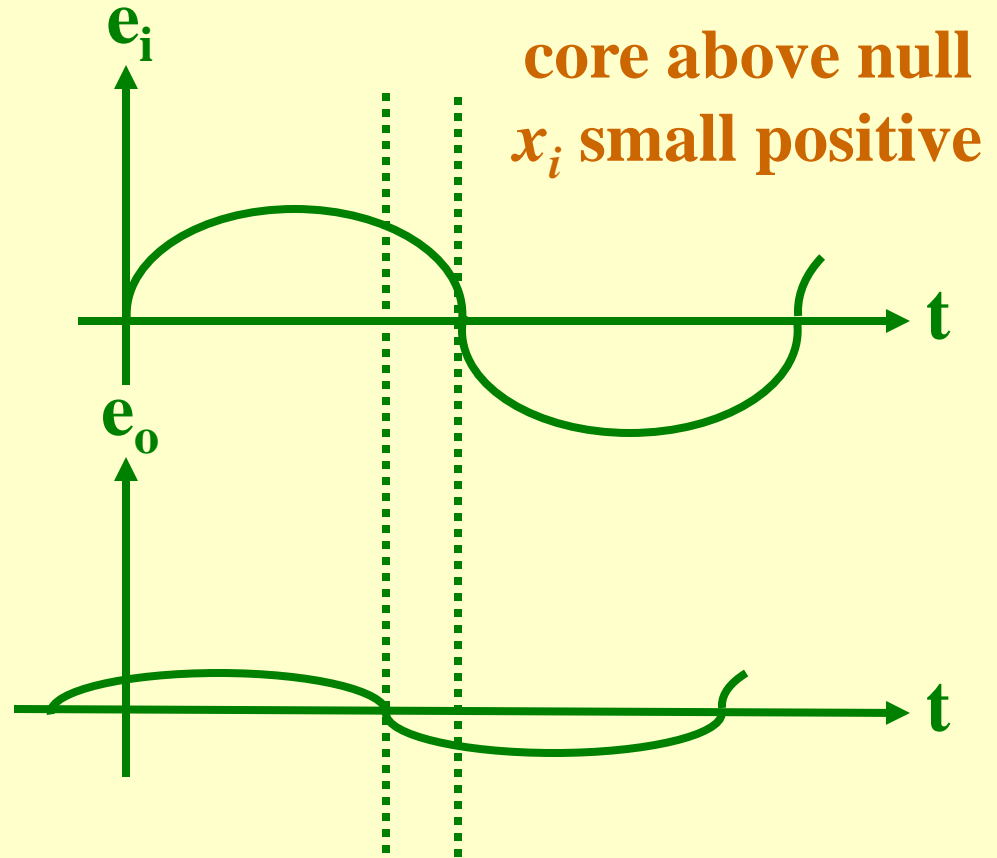


Amitava Chatterjee

LVDT (contd...)

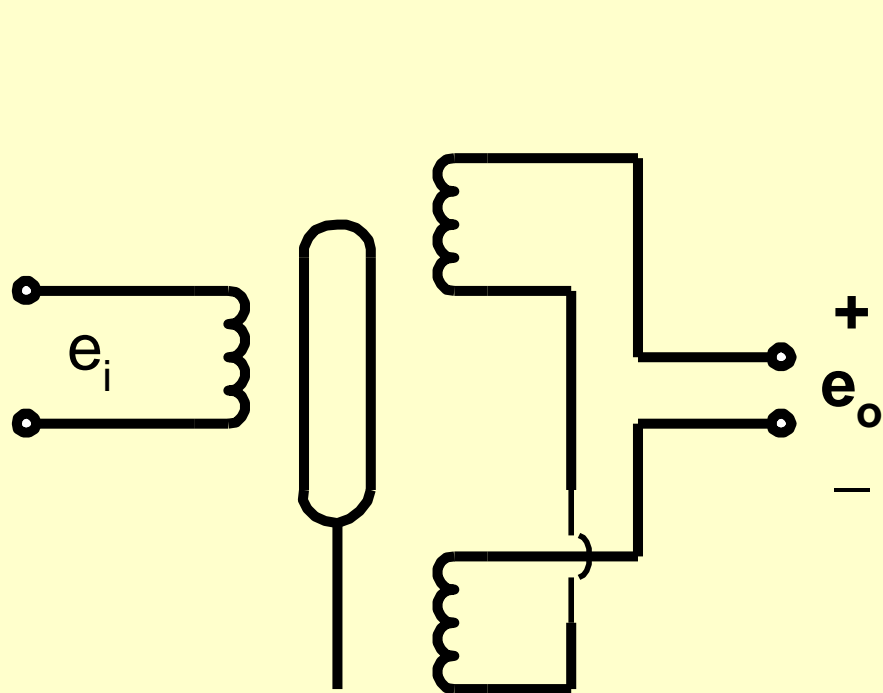


Series opposing secondaries

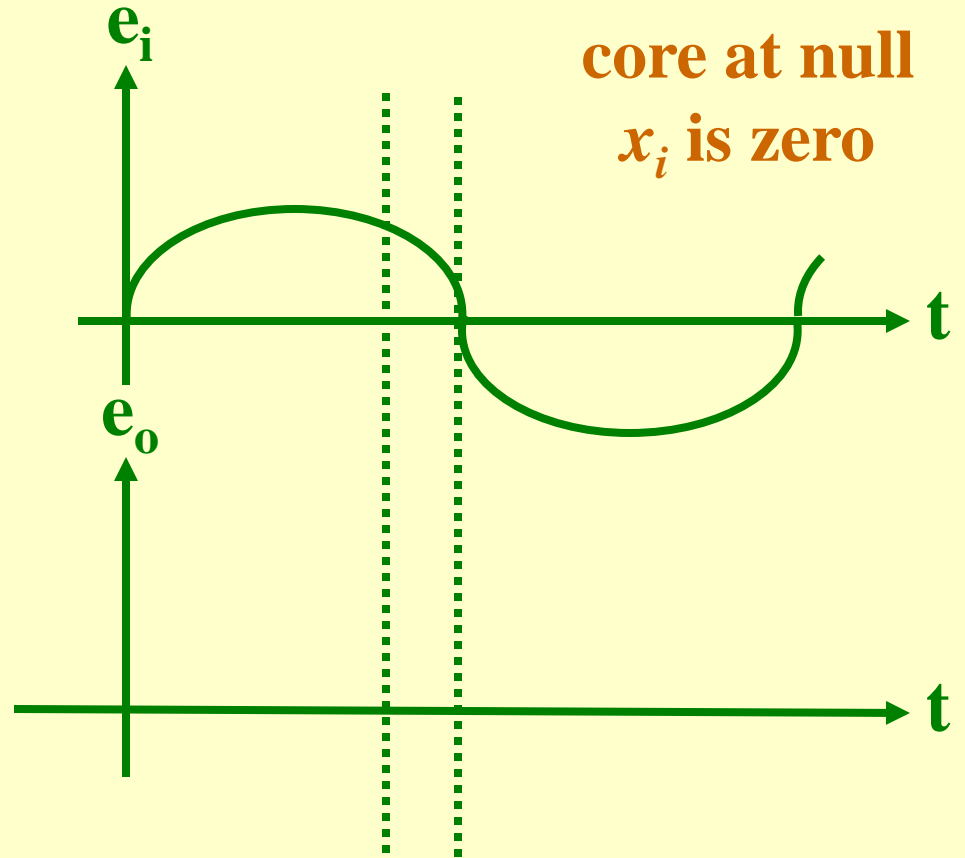


**core at null
 x_i is zero**

LVDT (contd...)

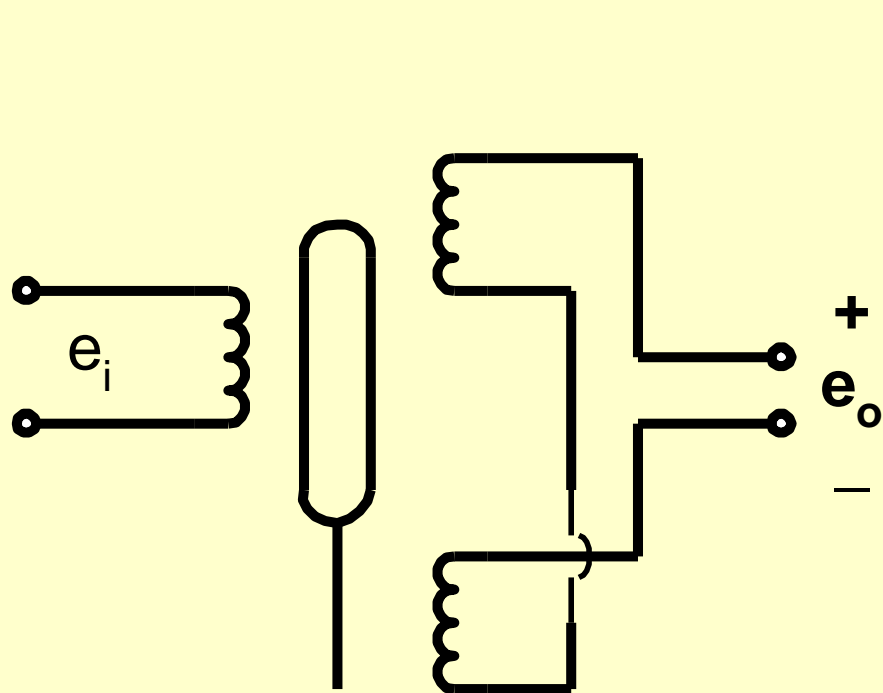


Series opposing secondaries

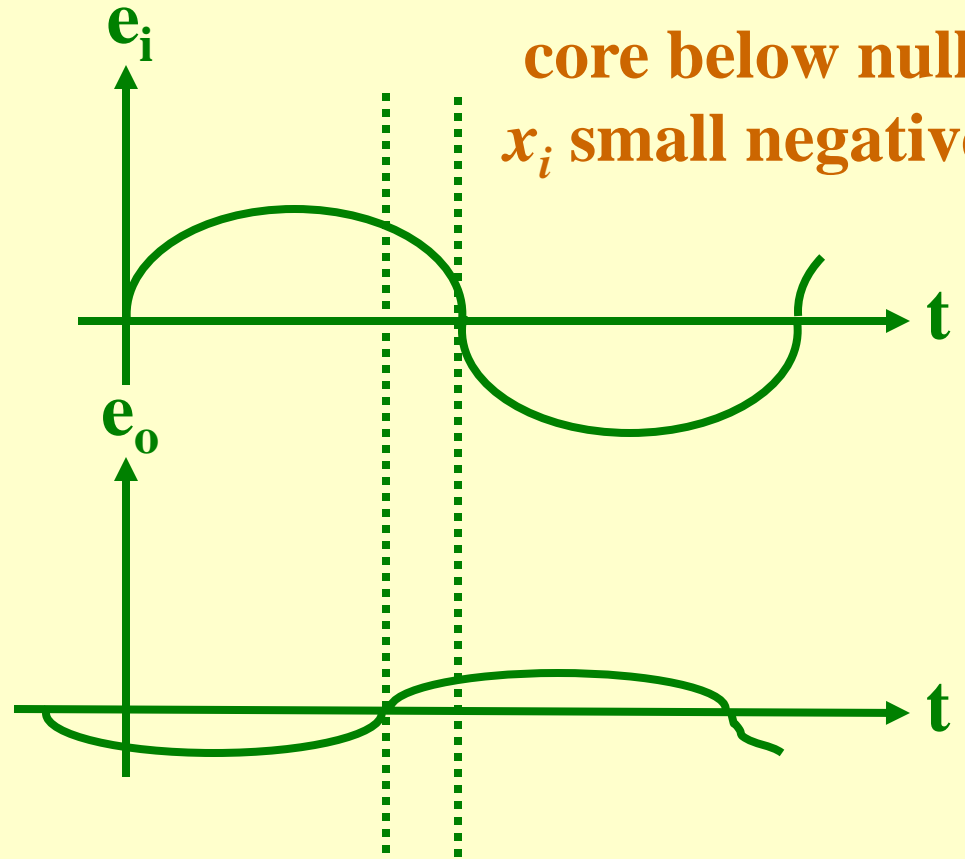


**core below null
 x_i small negative**

LVDT (contd...)

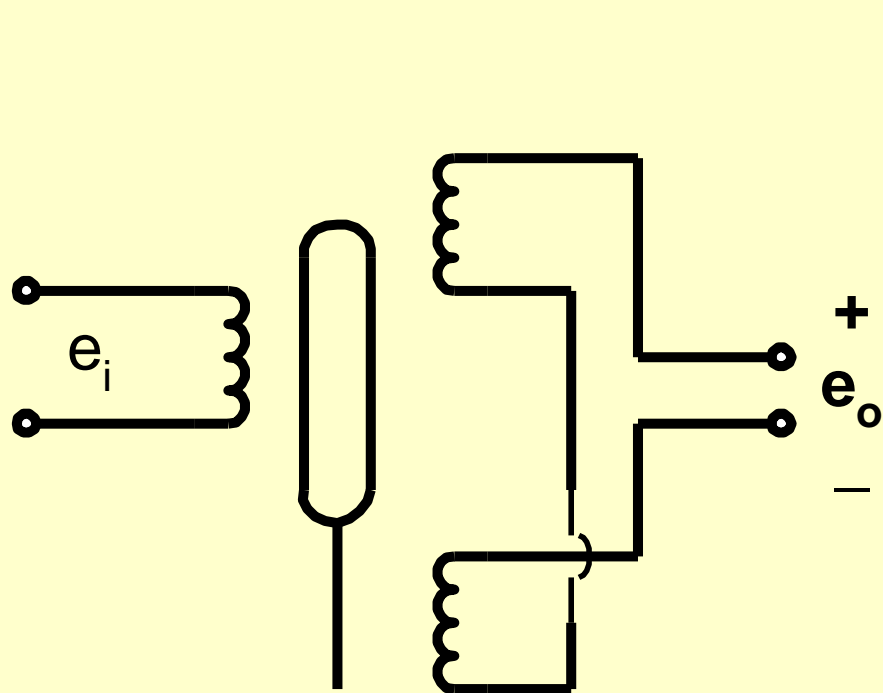


Series opposing secondaries

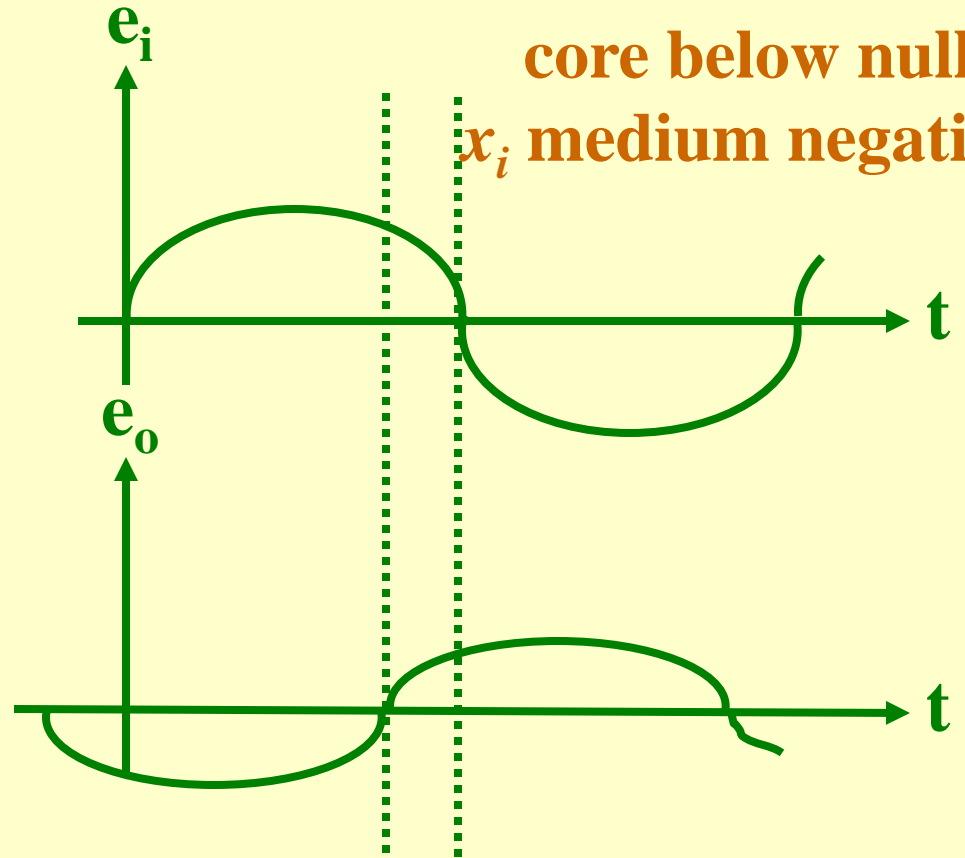


Amitava Chatterjee

LVDT (contd...)

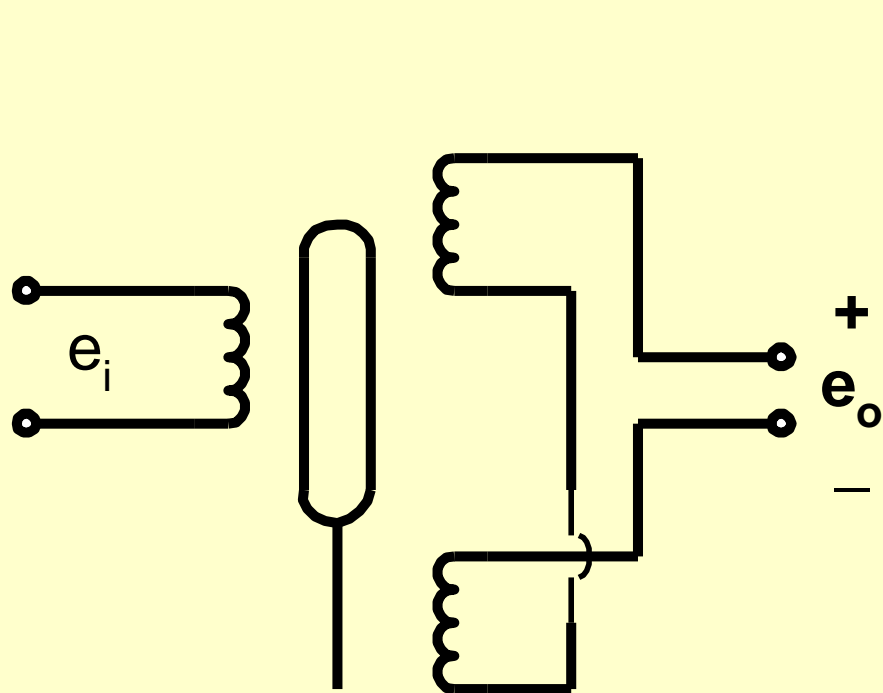

Series opposing secondaries

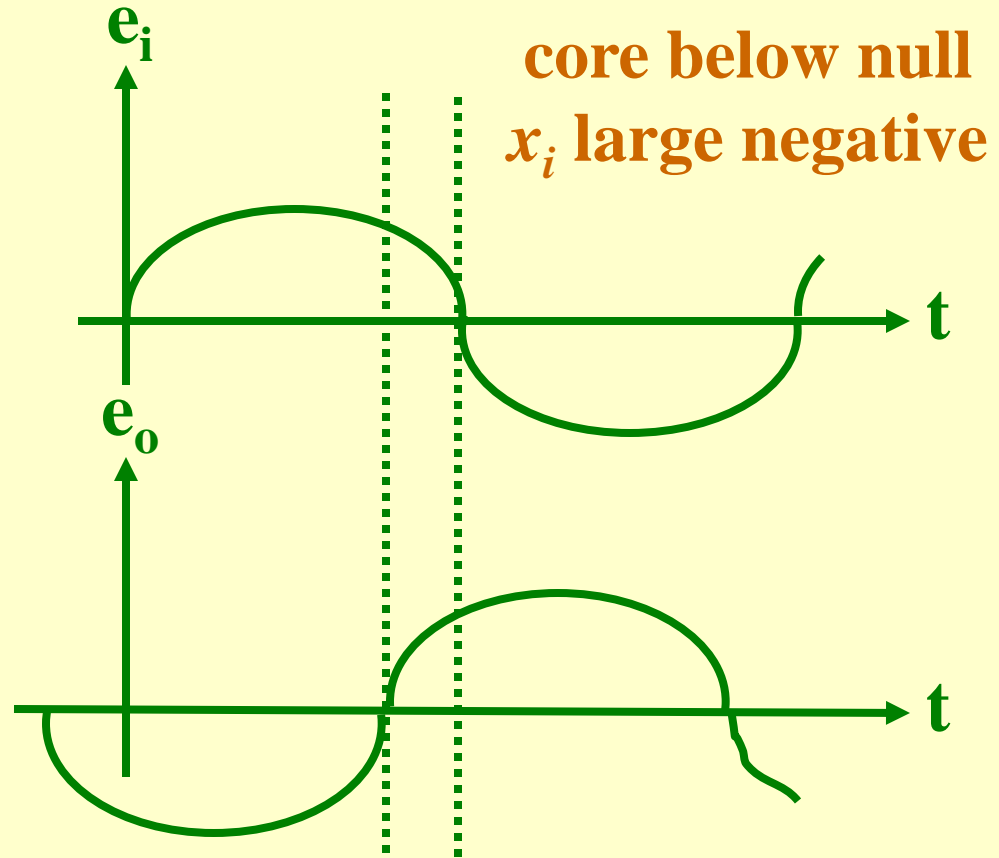


Amitava Chatterjee

15

Department of Electrical Engg., Jadavpur University, Kolkata, India

LVDT (contd....)

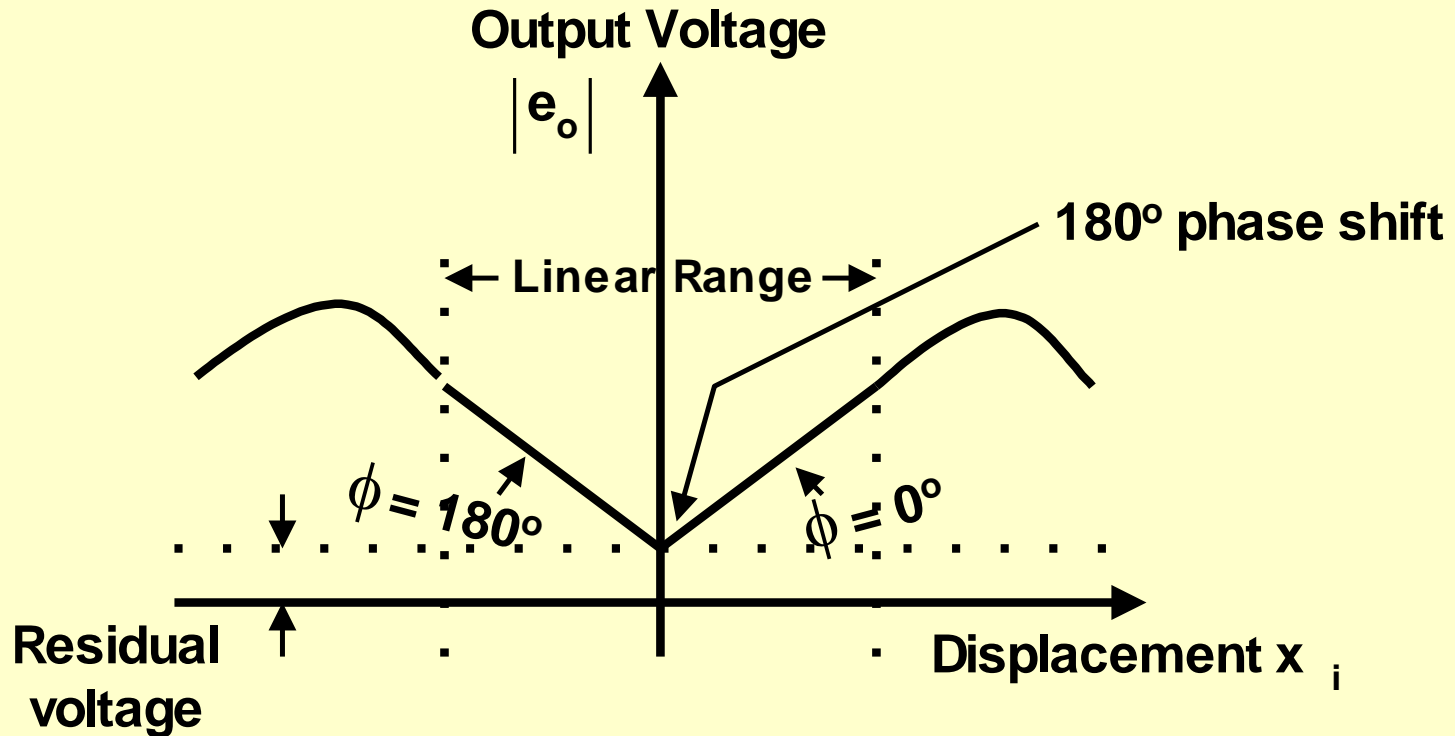

Output characteristic of an LVDT

Amitava Chatterjee

16

Department of Electrical Engg., Jadavpur University, Kolkata, India


Residual voltage exists in null position

Why ?

- ✓ May be on account of harmonics present in the input supply voltage
- ✓ Due to stray capacitance coupling between primary and secondary
- ✓ Due to harmonics produced in the output supply voltage
- ✓ Due to stray magnetic fields
- ✓ Due to temperature effect ...

Methods for Null Reduction

Method – 1:

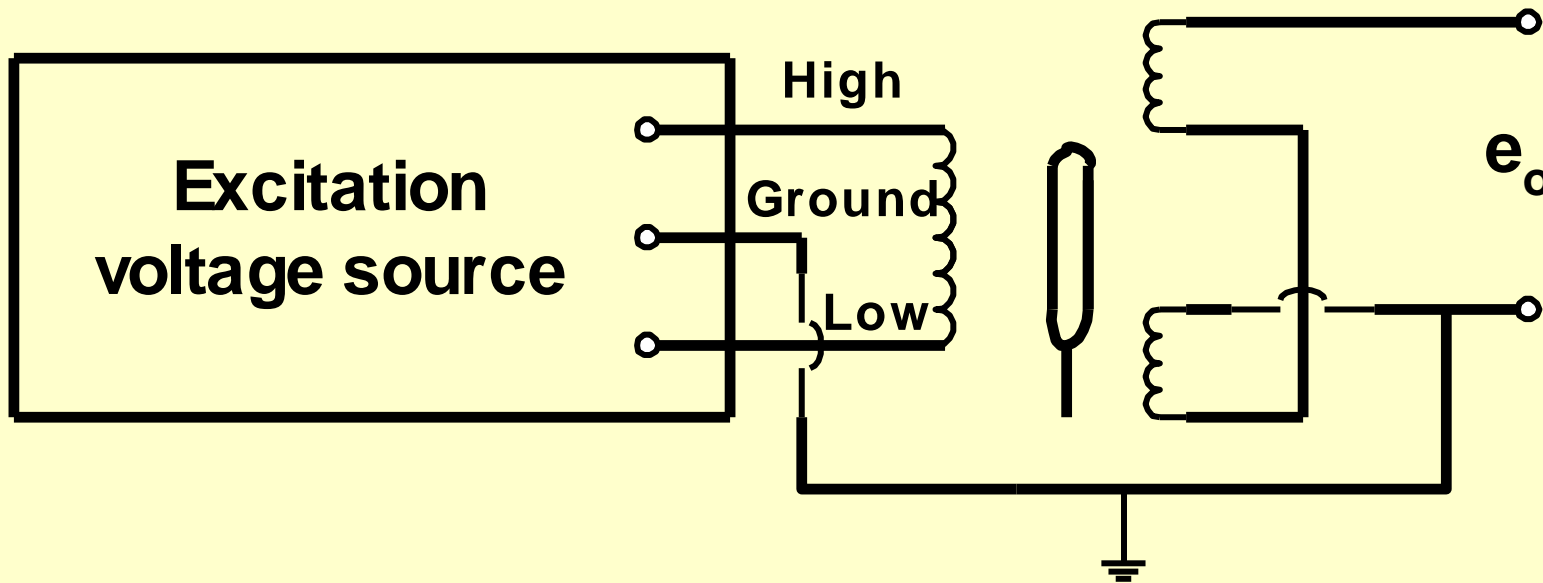

- ✓ The method can be used if a centre-tapped excitation voltage source is available.


Amitava Chatterjee

18

Department of Electrical Engg., Jadavpur University, Kolkata, India

Methods for Null Reduction (contd...)

Method – 2:

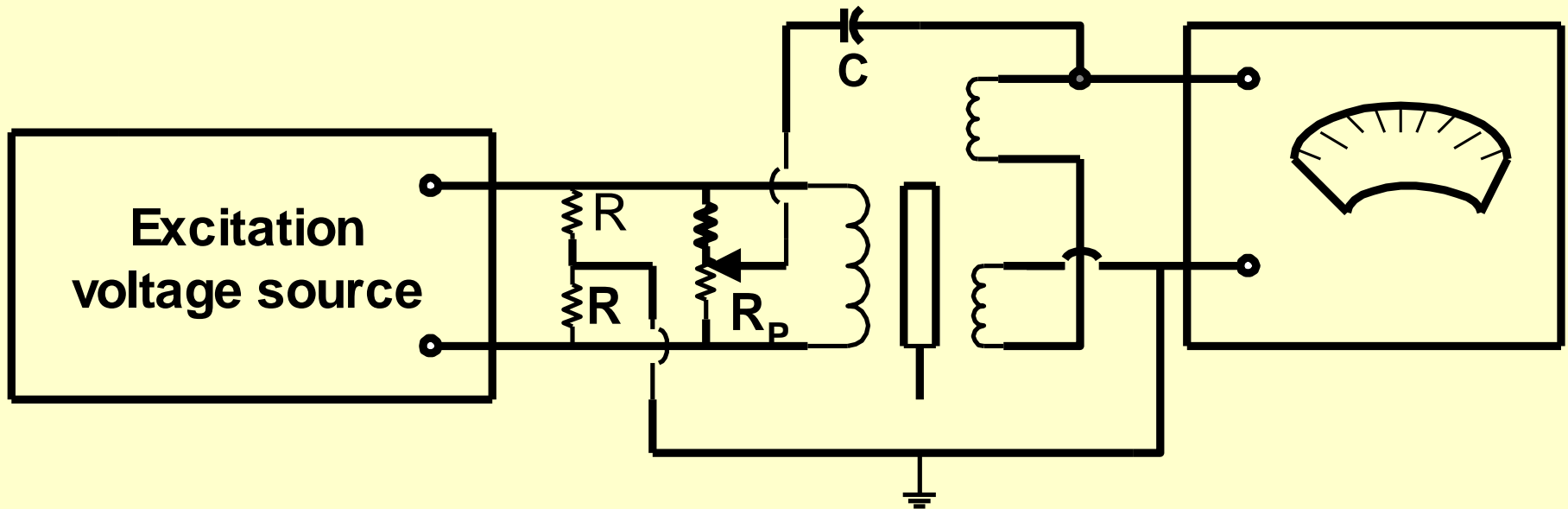


- ✓ This method is used when a centre-tapped excitation voltage source is not available.

Amitava Chatterjee

19

Department of Electrical Engg., Jadavpur University, Kolkata, India

Analysis of the Equivalent Circuit

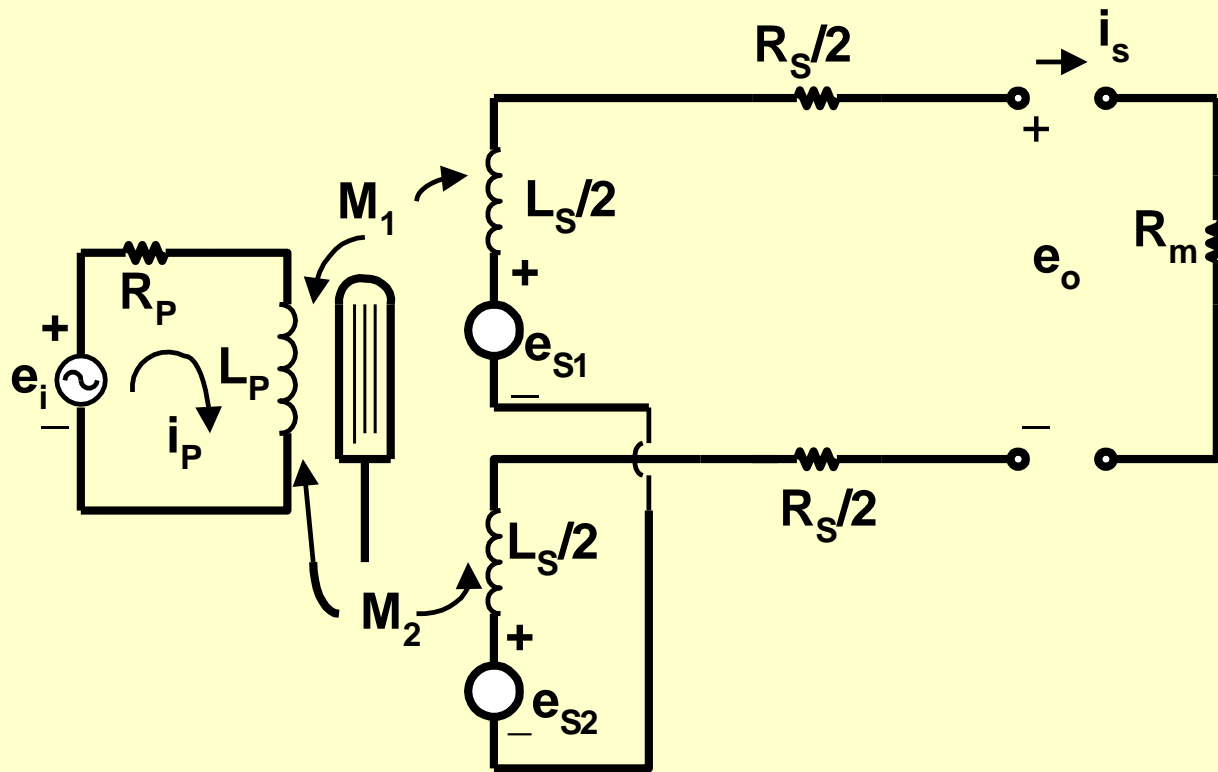

Amitava Chatterjee

20

Department of Electrical Engg., Jadavpur University, Kolkata, India

Analysis of the Equivalent Circuit (contd...)

Case I: A voltage measuring device with infinite R_m


Governing equations:

$$i_p R_p + L_p \frac{di_p}{dt} - e_i = 0$$

$$e_{s1} = -M_1 \frac{di_p}{dt}$$

$$e_{s2} = -M_2 \frac{di_p}{dt}$$
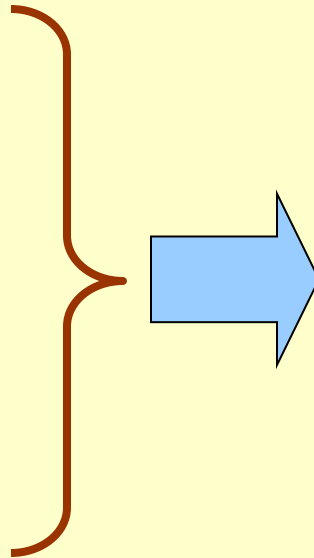
$$e_o = e_{s1} - e_{s2} = (M_2 - M_1) \frac{di_p}{dt}$$



Input-output relation:

For a given core position

$$\frac{E_o(s)}{E_i(s)} = \frac{\left[\frac{(M_2 - M_1)}{R_p} \right] s}{\tau_p s + 1} \quad \text{where } \tau_p = \frac{L_p}{R_p}$$

Frequency response

$$\frac{E_o(j\omega)}{E_i} = \frac{\omega (M_2 - M_1) / R_p}{\sqrt{(\omega \tau_p)^2 + 1}} \angle \phi \quad \text{where,}$$
$$\phi = 90^\circ - \tan^{-1}(\omega \tau_p)$$


✓ This demonstrates the phase shift between e_o and e_i .

Analysis of the Equivalent Circuit (contd...)

Case II: A voltage measuring device with finite R_m

Governing equations:
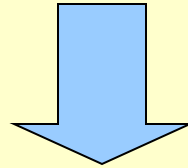
$$e_i - \left[-(M_1 - M_2) \frac{di_s}{dt} \right] = i_p R_p + L_p \frac{di_p}{dt}; \quad -(M_1 - M_2) \frac{di_p}{dt} = i_s (R_s + R_m) + L_s \frac{di_s}{dt}$$



Input-output relation:

For a given core position

$$\frac{E_o(s)}{E_i(s)} = \frac{sR_m(M_2 - M_1)}{s^2 \left[(M_1 - M_2)^2 + L_p L_s \right] + s \left[L_p (R_s + R_m) + L_s R_p \right] + R_p (R_s + R_m)}$$

Analysis of the Equivalent Circuit (contd..)

Case II: A voltage measuring device with finite R_m (contd.)

Frequency response


$$\frac{E_o}{E_i}(j\omega) = \frac{\omega R_m (M_2 - M_1)}{\sqrt{\left\{R_p (R_s + R_m) - \omega^2 [(M_1 - M_2)^2 + L_p L_s]\right\}^2 + \omega^2 [L_p (R_s + R_m) + L_s R_p]^2}} \angle \phi$$

where phase response:


$$\phi = 90^\circ - \tan^{-1} \left(\frac{\omega \left[L_p + \frac{L_s R_p}{R_s + R_m} \right]}{R_p - \frac{\omega^2}{R_s + R_m} [(M_1 - M_2)^2 + L_p L_s]} \right)$$

Methods for retarding a leading phase angle

Method – 1

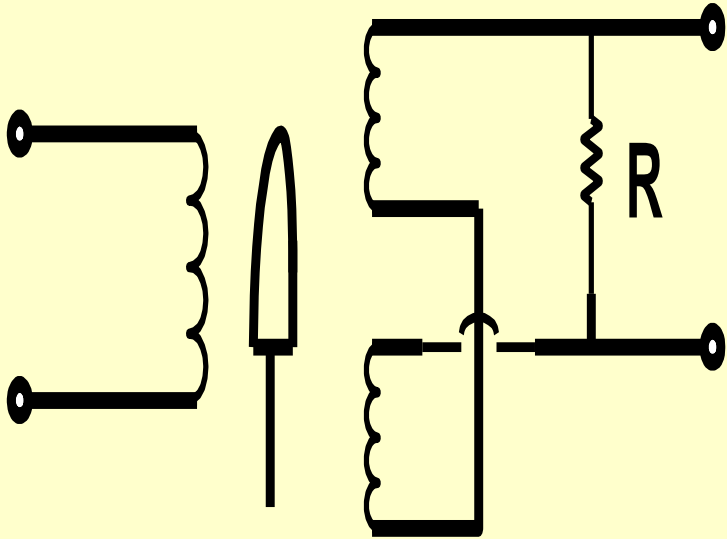

Method – 2

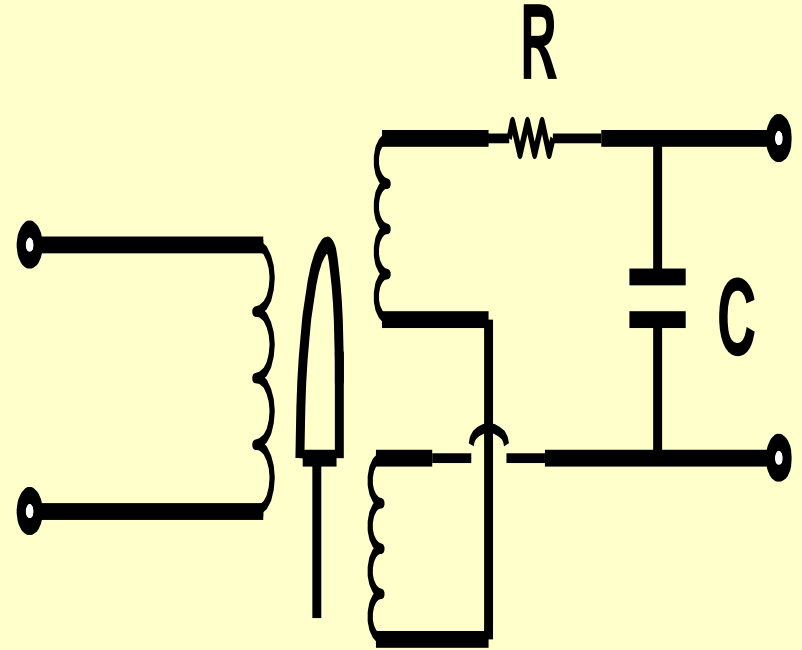

Amitava Chatterjee

24

Department of Electrical Engg., Jadavpur University, Kolkata, India

Method Analysis


Method – 1

$$\frac{E_o(s)}{E_i(s)} = \frac{R(M_2 - M_1)s}{\left\{ (M_1 - M_2)^2 + L_p L_s \right\} s^2 + \left[L_p (R_s + R) + L_s R_p \right] s + (R_s + R)R_p}$$

Frequency response

$$\frac{E_o(j\omega)}{E_i} = \frac{\omega R(M_2 - M_1)}{\sqrt{\left\{ (R_s + R)R_p - \omega^2 \left[(M_1 - M_2)^2 + L_p L_s \right] \right\}^2 + \left\{ \omega \left[L_p (R_s + R) + L_s R_p \right] \right\}^2}} \angle \phi$$

$$\phi = 90^\circ - \tan^{-1} \left(\frac{\omega \left[L_p (R_s + R) + L_s R_p \right]}{(R_s + R)R_p - \omega^2 \left[(M_1 - M_2)^2 + L_p L_s \right]} \right)$$

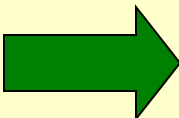when phase angle is zero  $R = \frac{\omega^2 \left[(M_1 - M_2)^2 + L_p L_s \right]}{R_p} - R_s$

Amitava Chatterjee

25

Department of Electrical Engg., Jadavpur University, Kolkata, India

Method Analysis (contd...)

Method – 2

$$\frac{E_o(s)}{E_i(s)} = \frac{\left[\frac{(M_2 - M_1)}{R_p} \right] s}{\tau_p s + 1} \cdot \frac{1}{1 + sRC} = \frac{(M_2 - M_1)s}{(R_p + sL_p)(1 + sRC)}$$

Frequency response

$$\frac{E_o(j\omega)}{E_i} = \frac{\omega(M_2 - M_1)}{\sqrt{(R_p - \omega^2 L_p RC)^2 + \{\omega(L_p + R_p RC)\}^2}} \angle \phi$$

$$\phi = 90^\circ - \tan^{-1} \left(\frac{\omega(L_p + R_p RC)}{(R_p - \omega^2 L_p RC)} \right)$$

when phase angle is zero  $RC = \frac{R_p}{\omega^2 L_p}$


Amitava Chatterjee

26


Department of Electrical Engg., Jadavpur University, Kolkata, India

Methods for advancing a lagging phase angle

Method – 3

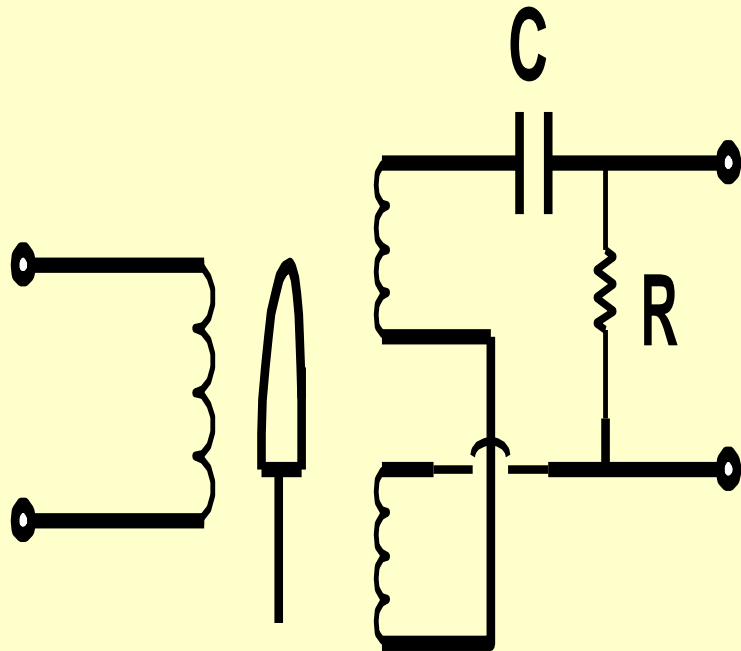

Method – 4

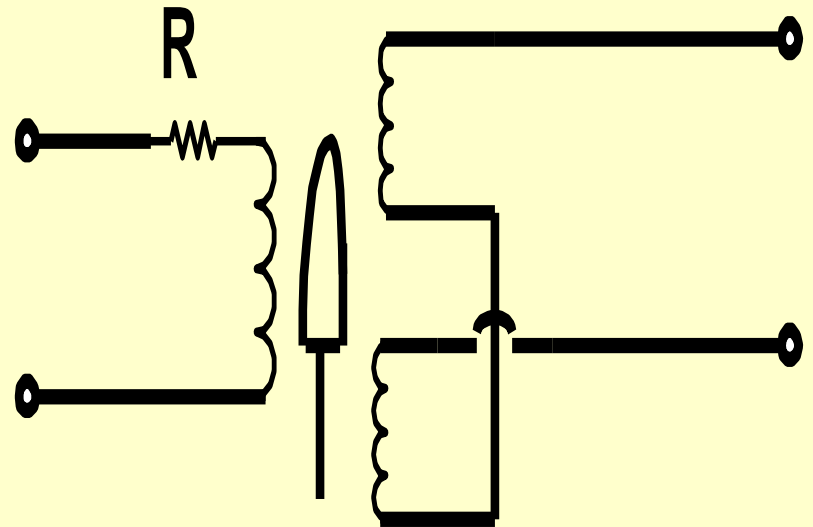


Amitava Chatterjee

27

Department of Electrical Engg., Jadavpur University, Kolkata, India

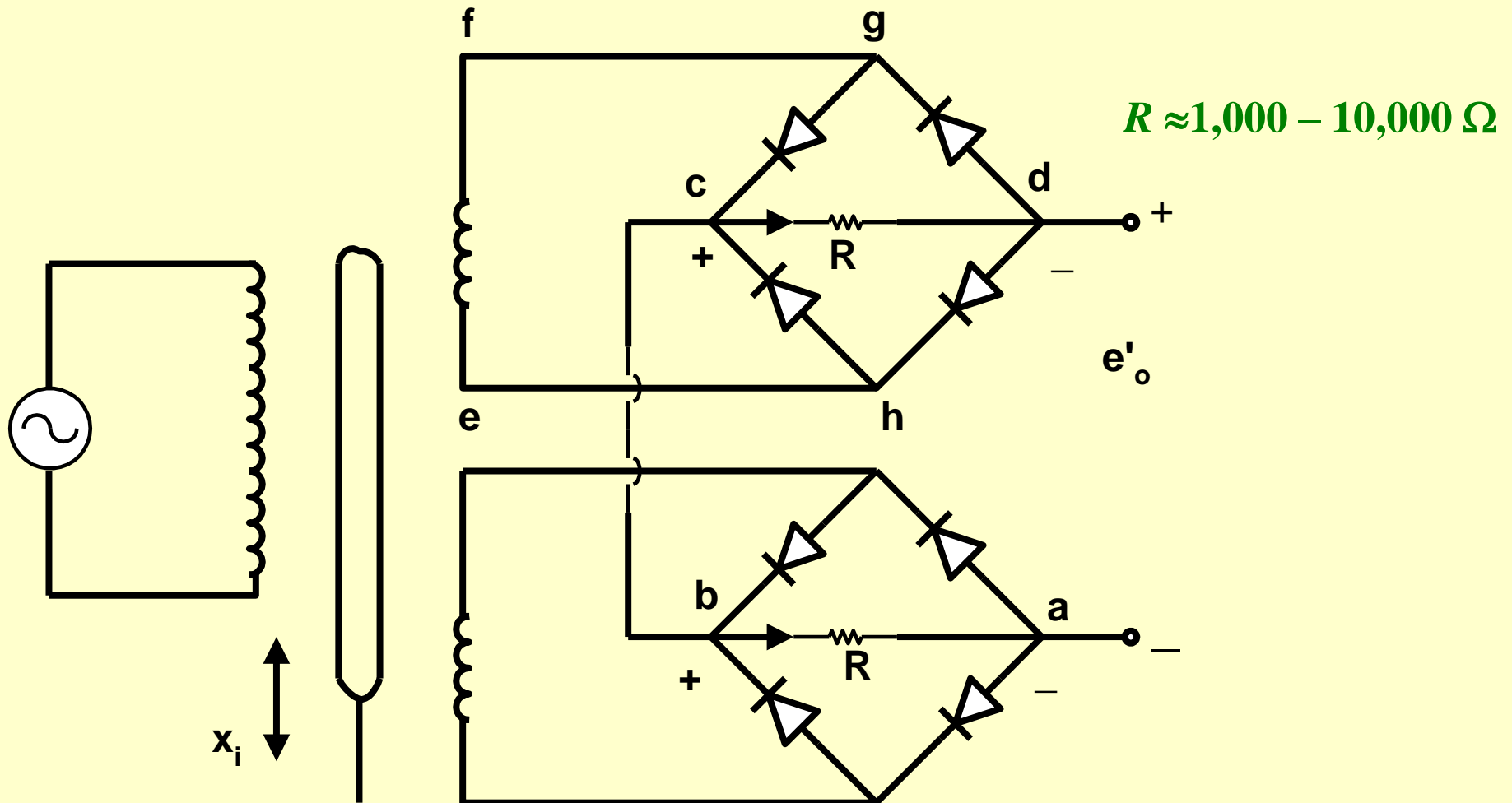Phase Sensitive Demodulation and Filtering Circuit Arrangement




Amitava Chatterjee

28

Department of Electrical Engg., Jadavpur University, Kolkata, India

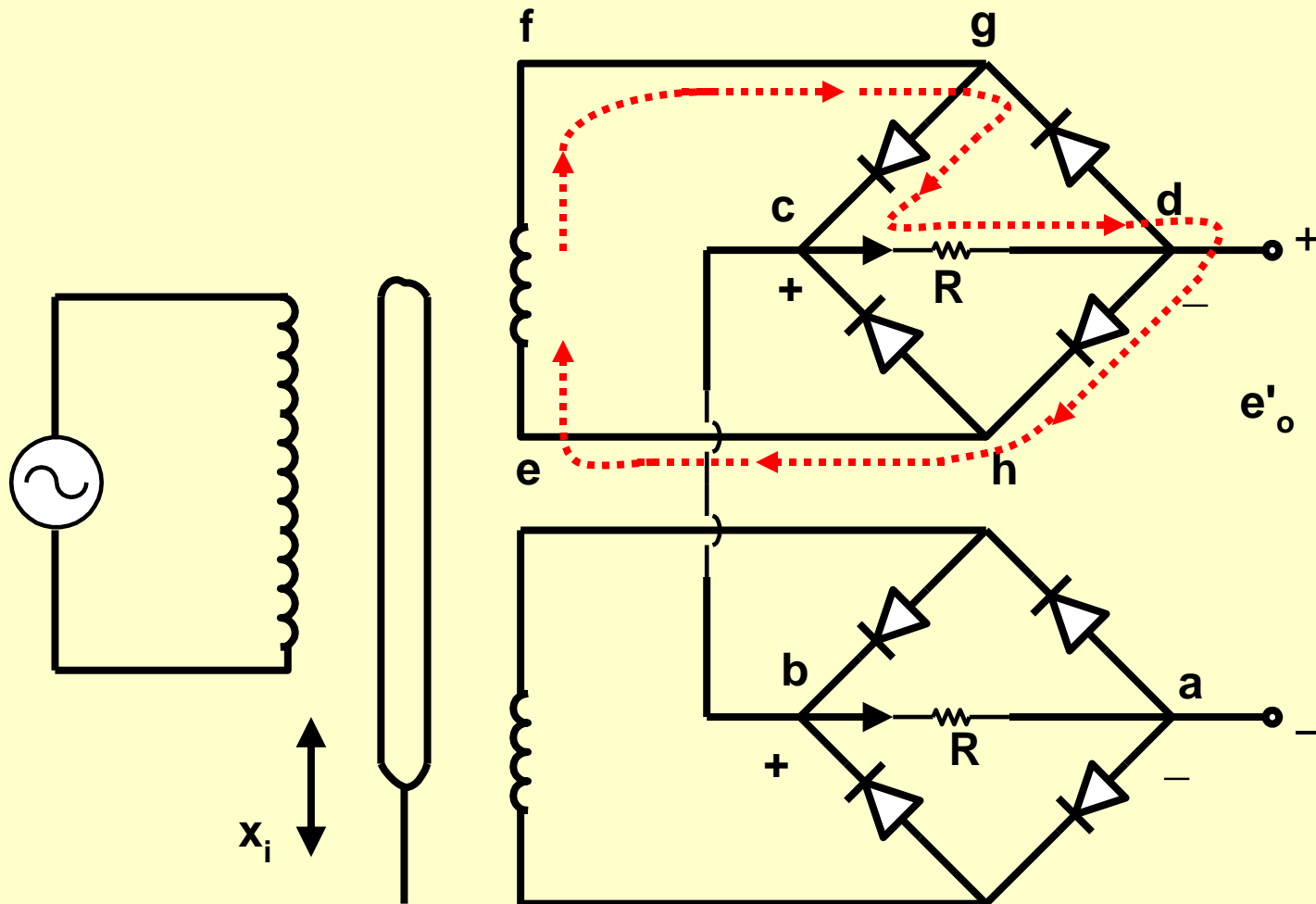Phase Sensitive Demodulation and Filtering Circuit Arrangement




when f +ve
and e -ve

Amitava Chatterjee

29

Department of Electrical Engg., Jadavpur University, Kolkata, India

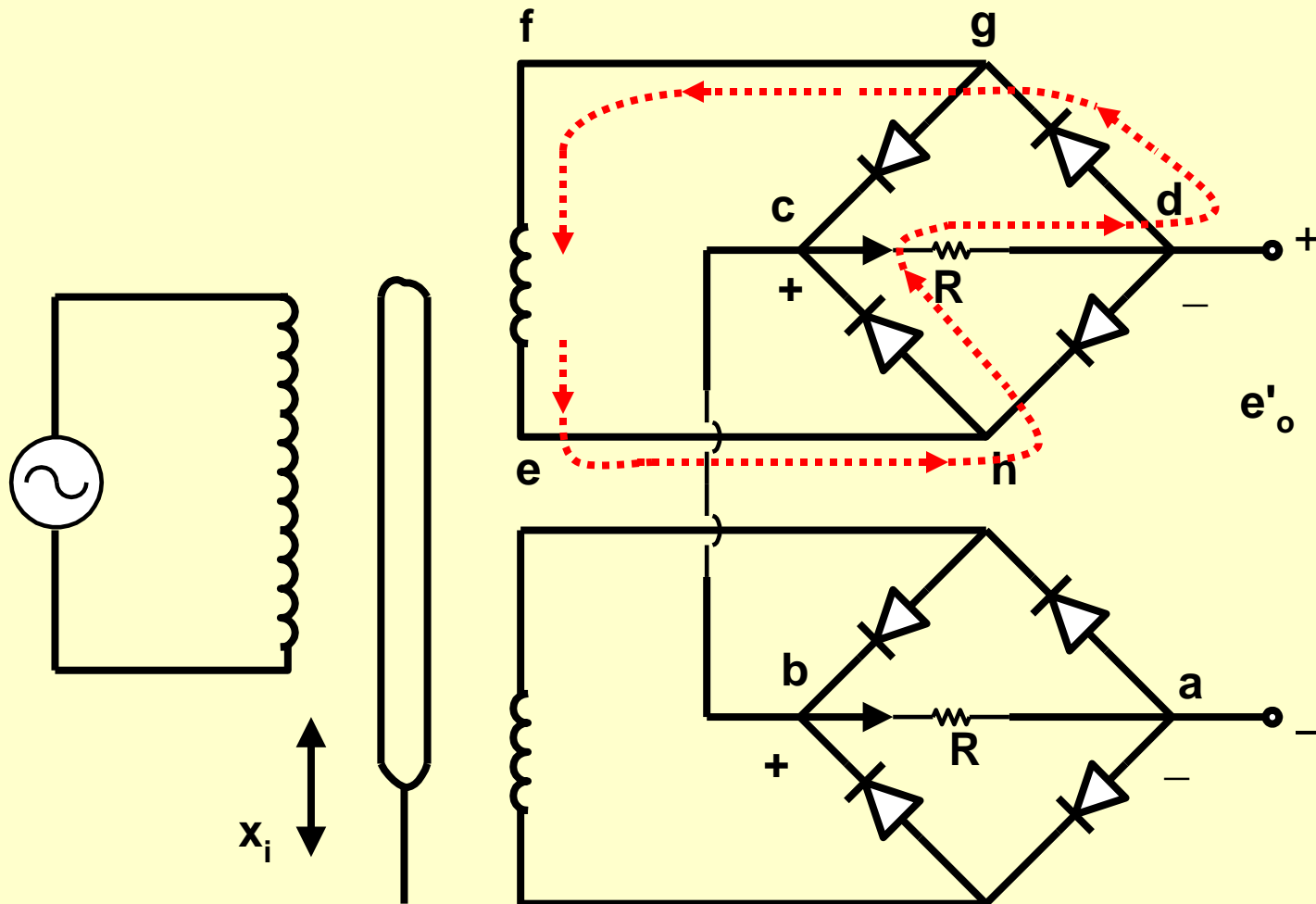Phase Sensitive Demodulation and Filtering Circuit Arrangement




when f -ve
and e +ve

Amitava Chatterjee


30

Department of Electrical Engg., Jadavpur University, Kolkata, India

PSD and Filtering (contd...)

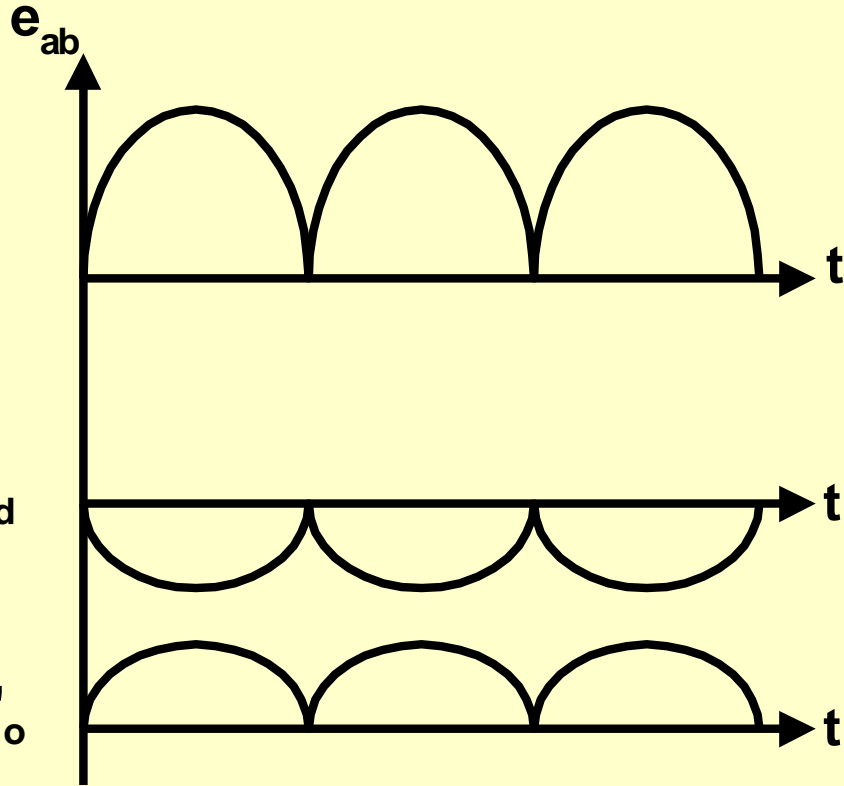


Core below null

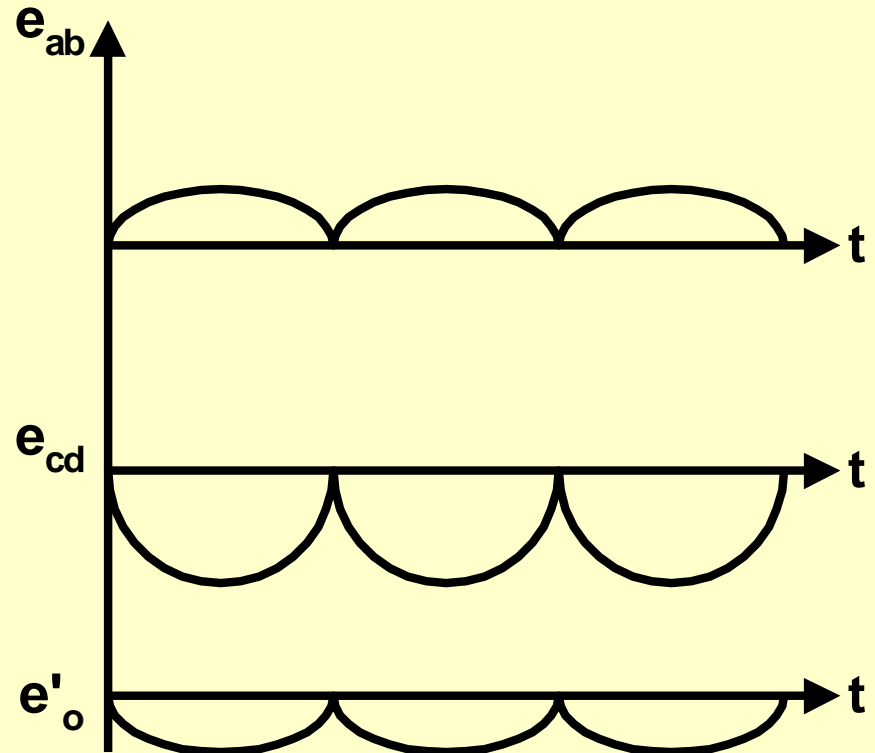


Core above null

PSD and Filtering (contd...)

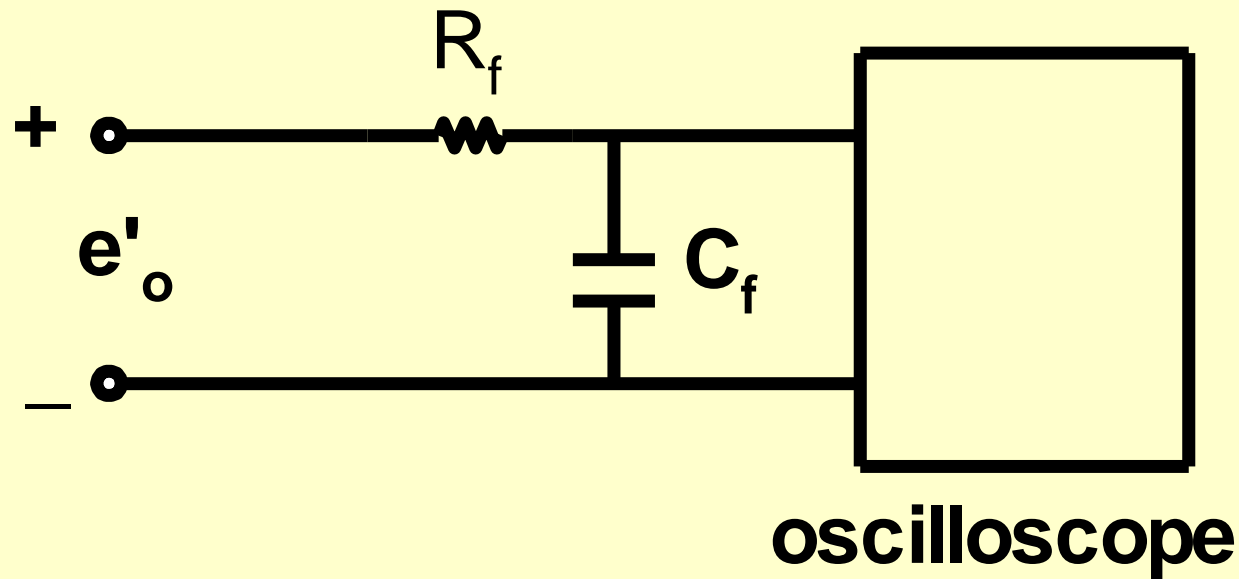


- ✓ For rapid core motions, a low-pass (RC) filter is connected between e'_o and the oscilloscope.

LVDT without PSD and Filtering

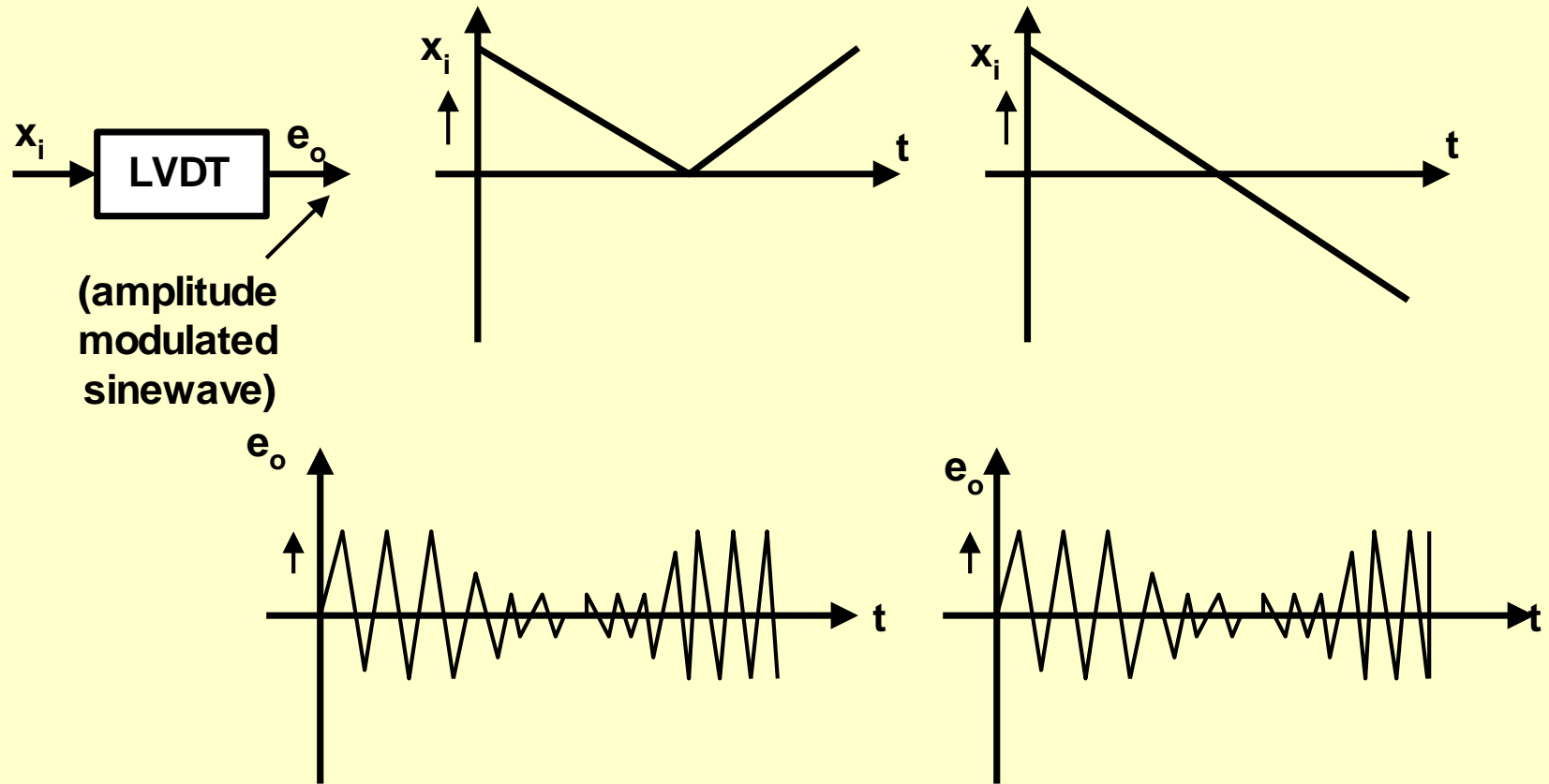

- ✓ e_o visually looks the same for two very different variations of x_i , if seen in an oscilloscope.

LVDT with PSD and Filtering

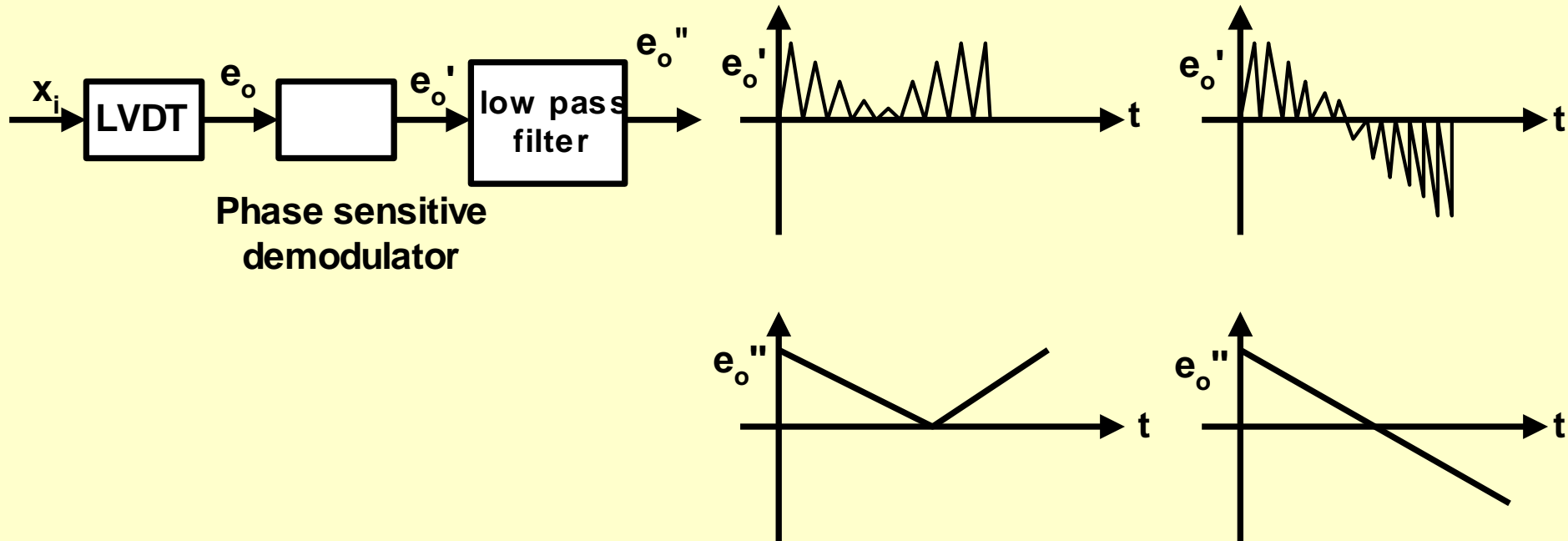

✓ now e_o'' can visually capture the two very different variations of x_i , if seen in an oscilloscope.

Amitava Chatterjee

34

Department of Electrical Engg., Jadavpur University, Kolkata, India

PSD and Filtering


Where applicable ?

- ✓ The PSD circuit with semiconductor diodes can only be applied for those LVDTs where all four terminals are accessible at the output.

Alternate solution ?

- ✓ For those LVDTs where only two terminals are accessible at the output, *synchronous demodulation technique* is employed.

Synchronous Demodulation Technique

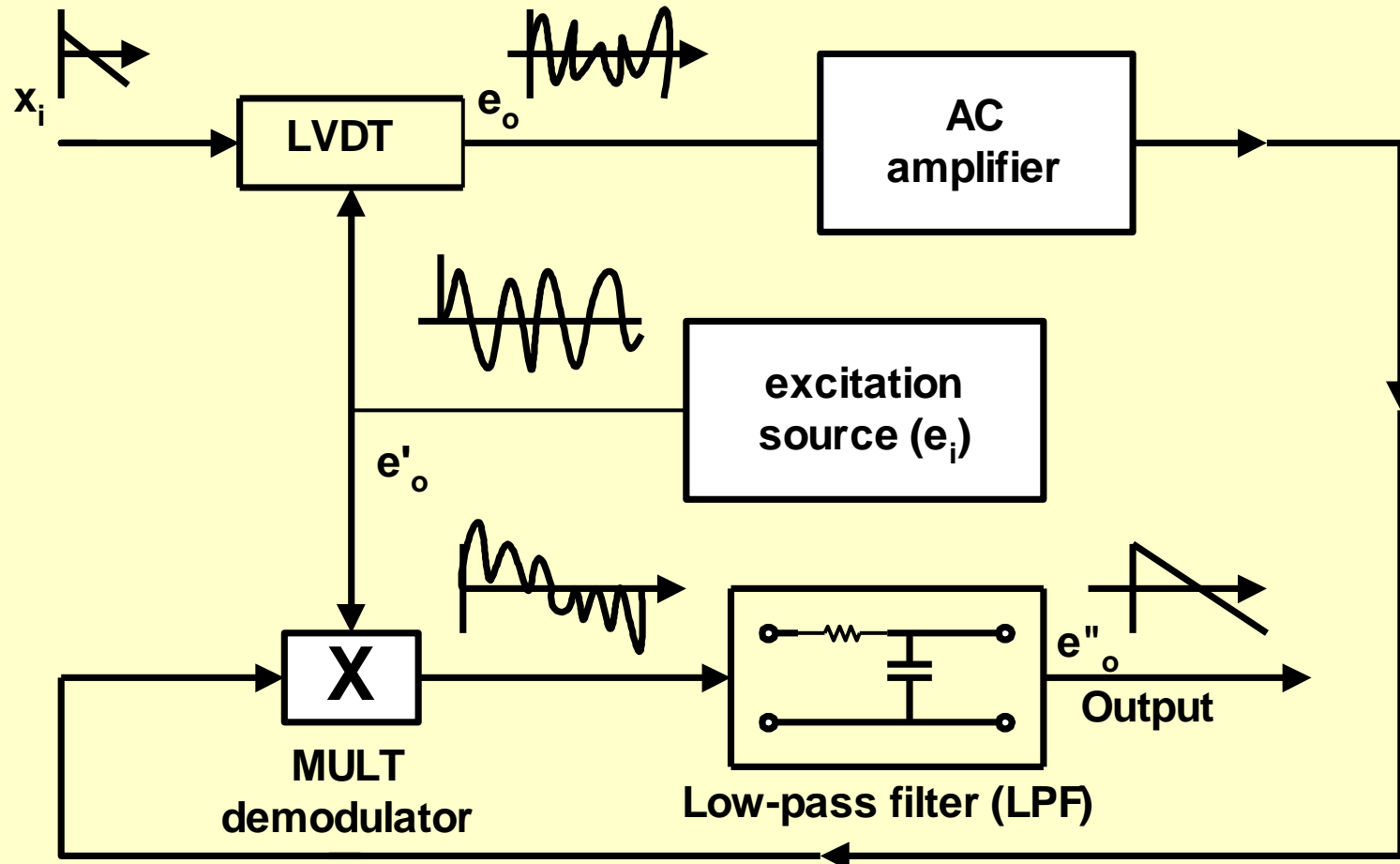

✓ *Constraint:*

This scheme requires that e_i and e_o should be in phase.

Amitava Chatterjee

36

Department of Electrical Engg., Jadavpur University, Kolkata, India

Advantages and Disadvantages of LVDT

Advantages:

- ✓ The output voltage of this transducer is practically *linear* for displacements upto 5 mm. A linearity of 0.5% is available in commercial LVDTs.
- ✓ *Infinitesimal resolution*: the change in output voltage is stepless, since the variation in coupling due to core motion is continuous in nature. It is possible to build a transducer with a resolution as fine as 1×10^{-3} mm.
- ✓ *High output*: therefore many a times there is no need for amplification. The full range stroke of commercially available LVDTs ranges from ± 0.005 to about ± 3 inch.

Advantages and Disadvantages of LVDT

Advantages (contd...):


- ✓ **Sensitivity:** 0.6 to 30 mV per 0.001 inch for normal excitation voltage 3 to 6 V, depending on frequency of excitation and stroke. A higher frequency gives more sensitivity and smaller strokes usually have higher sensitivity.
- ✓ **Low hysteresis:** hence repeatability is excellent.
- ✓ **Low Power consumption:** usually less than 1 W.

Advantages and Disadvantages of LVDT

Disadvantages:

- ✓ Affected by temperature variations and stray magnetic fields.
- ✓ The receiving instrument must be a.c. or a demodulation network must be used, if a d.c. output is required.
- ✓ The dynamic response of LVDTs is limited mainly by the excitation frequency, since it must be much higher than the core motion frequencies, so as to be able to distinguish between them in the amplitude modulated output signal.

LVDT for Rotary Motion

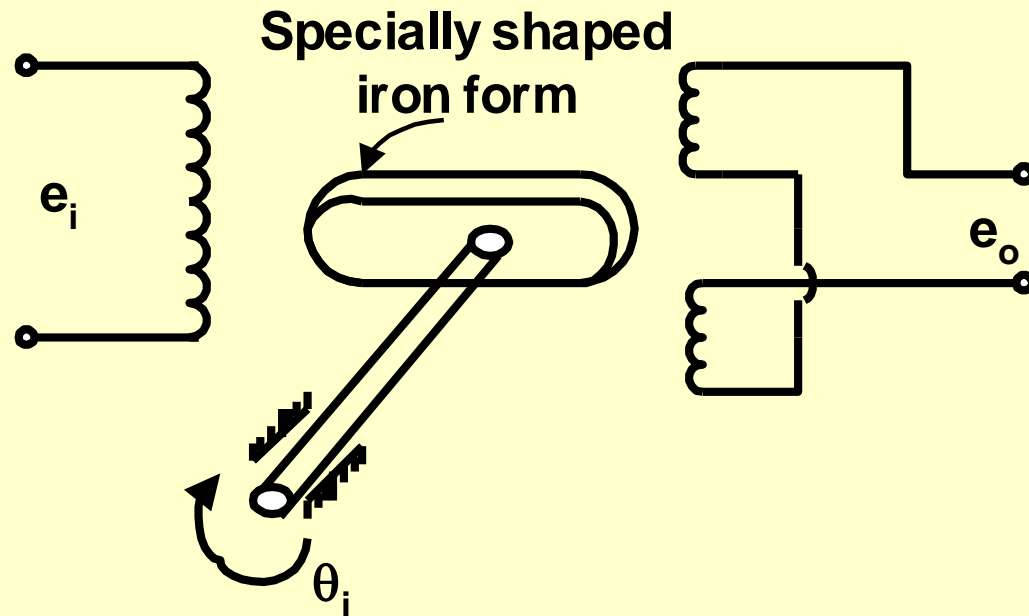

Rotational differential transformer

- ✓ Linear for limited rotation, $-40^\circ < \theta_i < +40^\circ$
- ✓ Sensitivity 10 to 20 mV/degree.
- ✓ Linearity $\pm 1\%$ of full scale for travel of $\pm 40^\circ$ and $\pm 3\%$ for travel of $\pm 60^\circ$.

Amitava Chatterjee

40

Department of Electrical Engg., Jadavpur University, Kolkata, India

Thank You