

Linearization of Sensors

Amitava Chatterjee
Department of Electrical Engg., Jadavpur University, Kolkata, India

Topics to be covered

- ❑ **Linearization Techniques for RTDs**
- ❑ **Linearization Techniques for Thermistors**

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

Resistance Temperature Detectors (RTDs)

- ✓ Resistance Temperature Detectors (**RTDs**) are temperature transducers which produce an output resistance (**R**) in response to an input temperature (**t**).

$$R = R_0 \left(1 + \alpha_1 t + \alpha_2 t^2 + \dots + \alpha_n t^n \right)$$


- ✓ Most commonly used materials for construction of RTDs: **Platinum, Nickel and Copper.**
- ✓ Usually **2** or **3** of the α constants are good enough for highly accurate representation.

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

Linearization of RTDs

Scheme 1

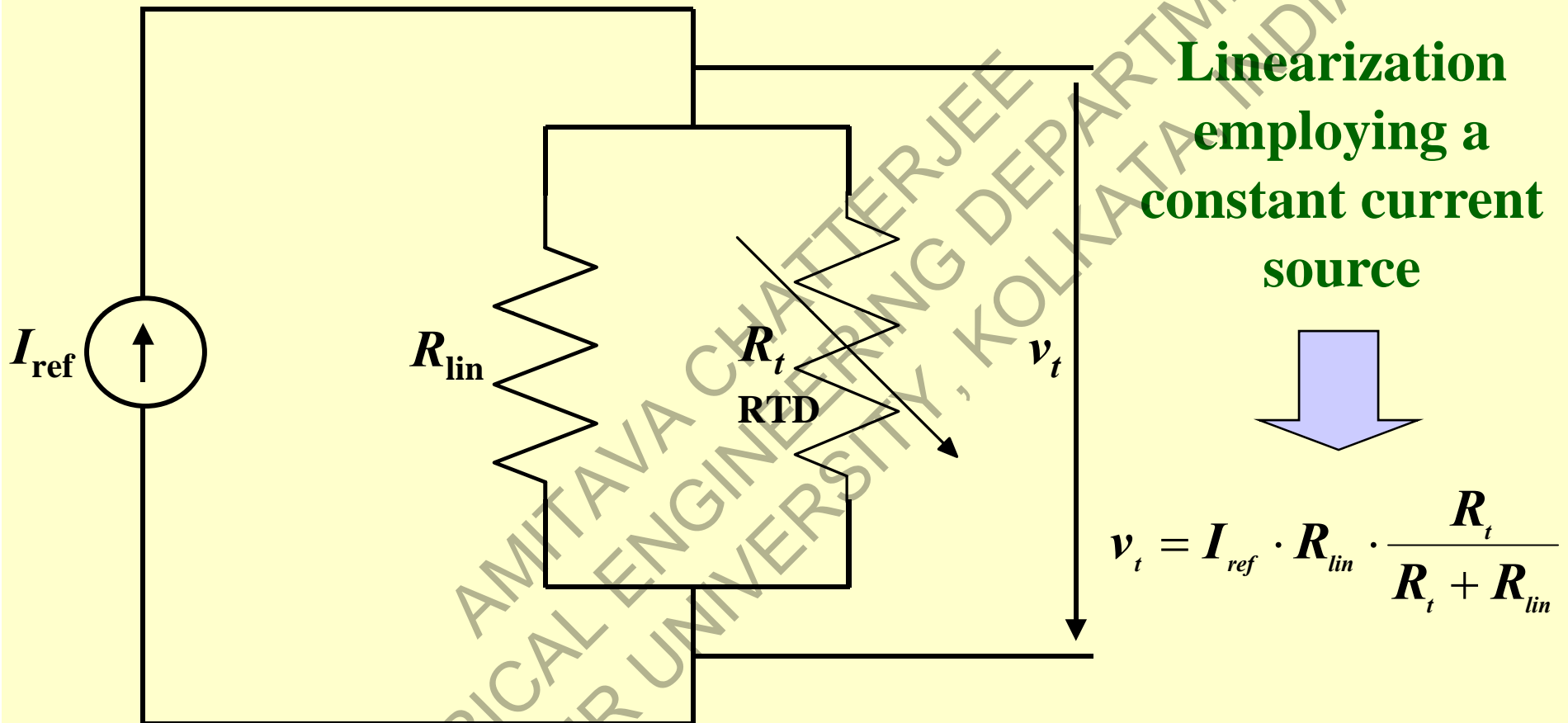


- ✓ A suitable fixed resistor R_{lin} is connected in parallel with the RTD and the arrangement is fed from a constant current source.

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

Linearization of RTDs (contd...)

Scheme 2

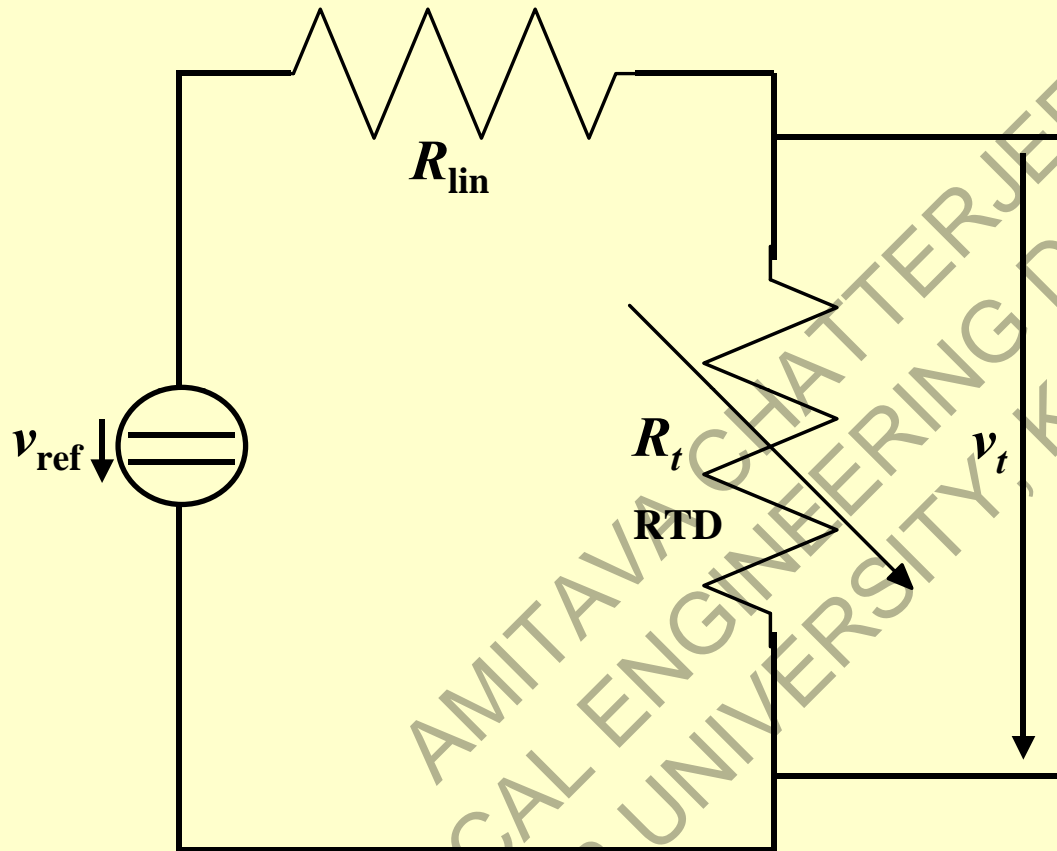

Linearization
employing a
voltage source


$$v_t = v_{ref} \cdot \frac{R_t}{R_t + R_{lin}}$$

- ✓ A suitable fixed resistor R_{lin} is connected in series with the RTD and the arrangement is fed from a constant voltage source.

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

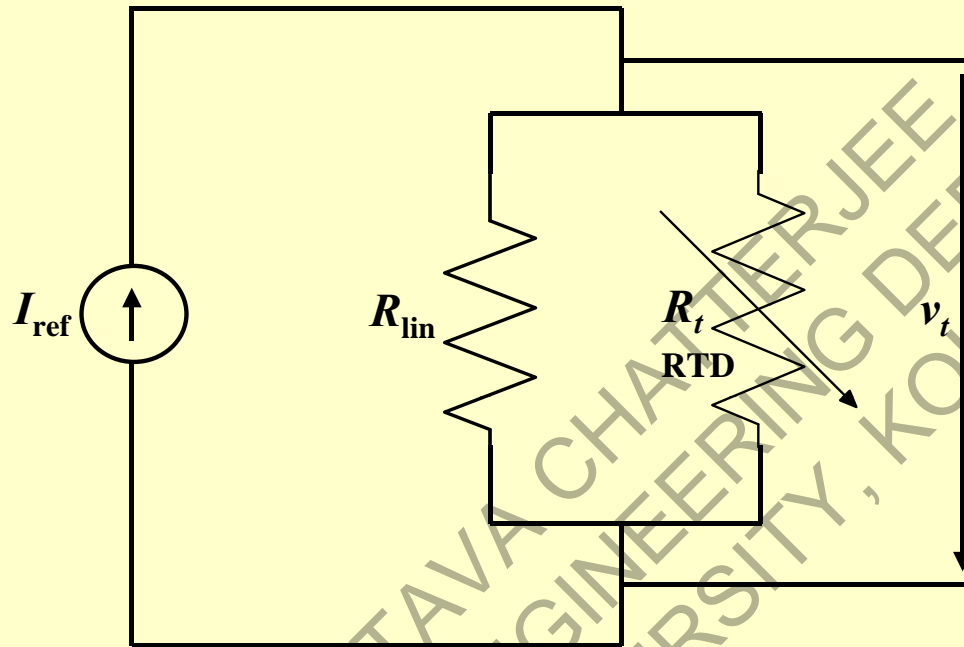Analysis of the Circuit employing Constant Current Source




- ✓ If $R_{eq} = (R_t \parallel R_{lin}) = \frac{R_t R_{lin}}{R_t + R_{lin}}$ vary linearly with t , v_t will also vary linearly with t .
- ✓ The design is based on the resistance values of the sensor at three temperatures: R_{t_L} (lower), R_{t_U} (upper), and R_{t_M} (mid-point).

Amitava Chatterjee


Department of Electrical Engg., Jadavpur University, Kolkata, India

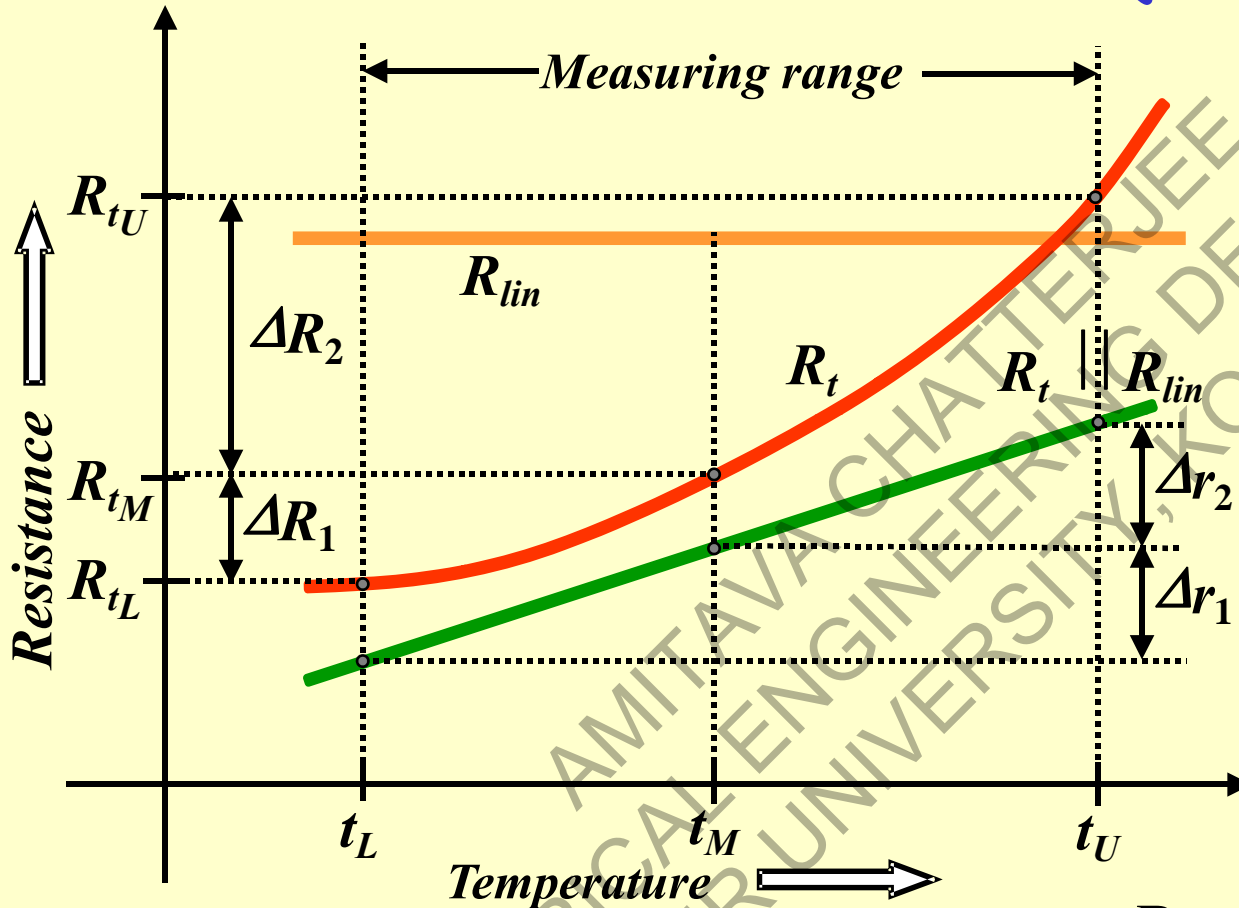Analysis of the Circuit employing Constant Current Source (contd...)



linearization condition
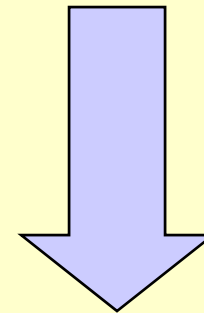
$$R_{eq}(t_M) - R_{eq}(t_L) = R_{eq}(t_U) - R_{eq}(t_M)$$




$$R_{lin} = \frac{R_{t_M}(R_{t_L} + R_{t_U}) - 2R_{t_L}R_{t_U}}{R_{t_L} + R_{t_U} - 2R_{t_M}}$$

Linearization of RTD
employing a parallel resistor

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

Linearization of Pt-100 Sensor

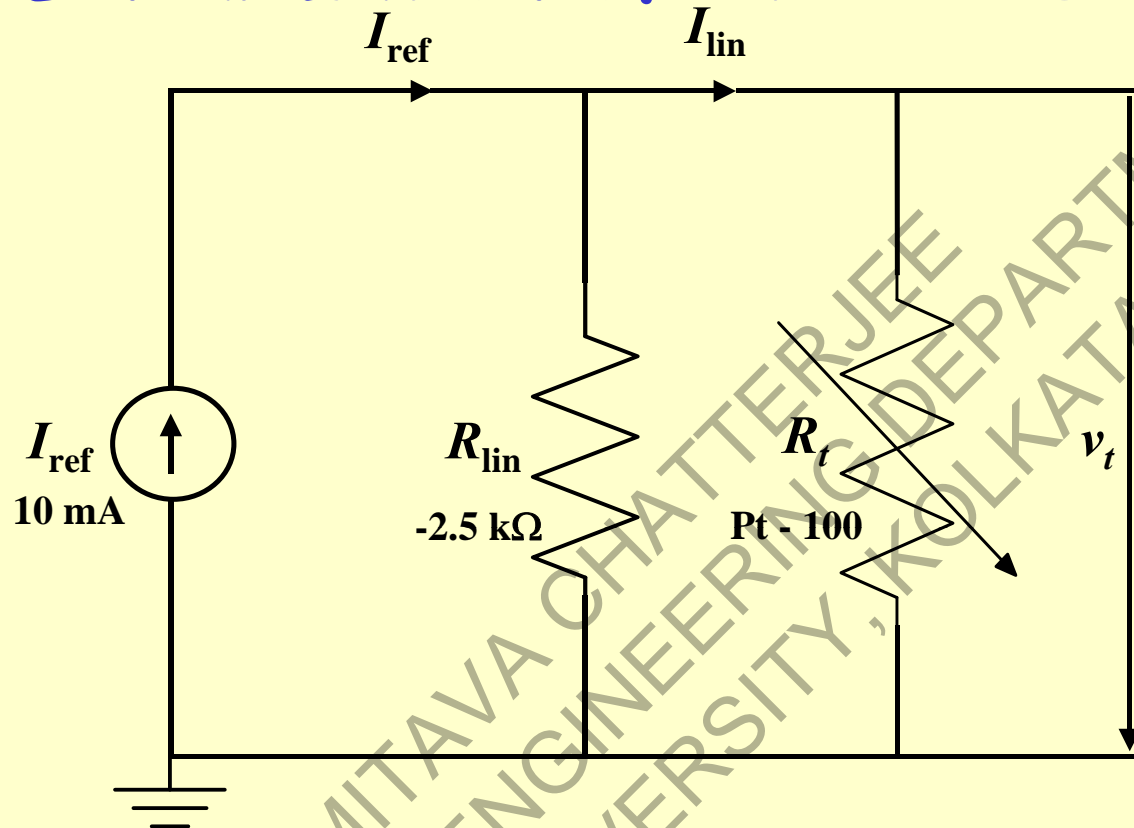


- ✓ For a **Pt-100** sensor, operated in the temperature range between **0°C** and **400°C**, a linearizing resistor $R_{lin} = -2.5 \text{ K}\Omega$ is required.
- ✓ A current source of negative internal resistance must be used in this case.

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

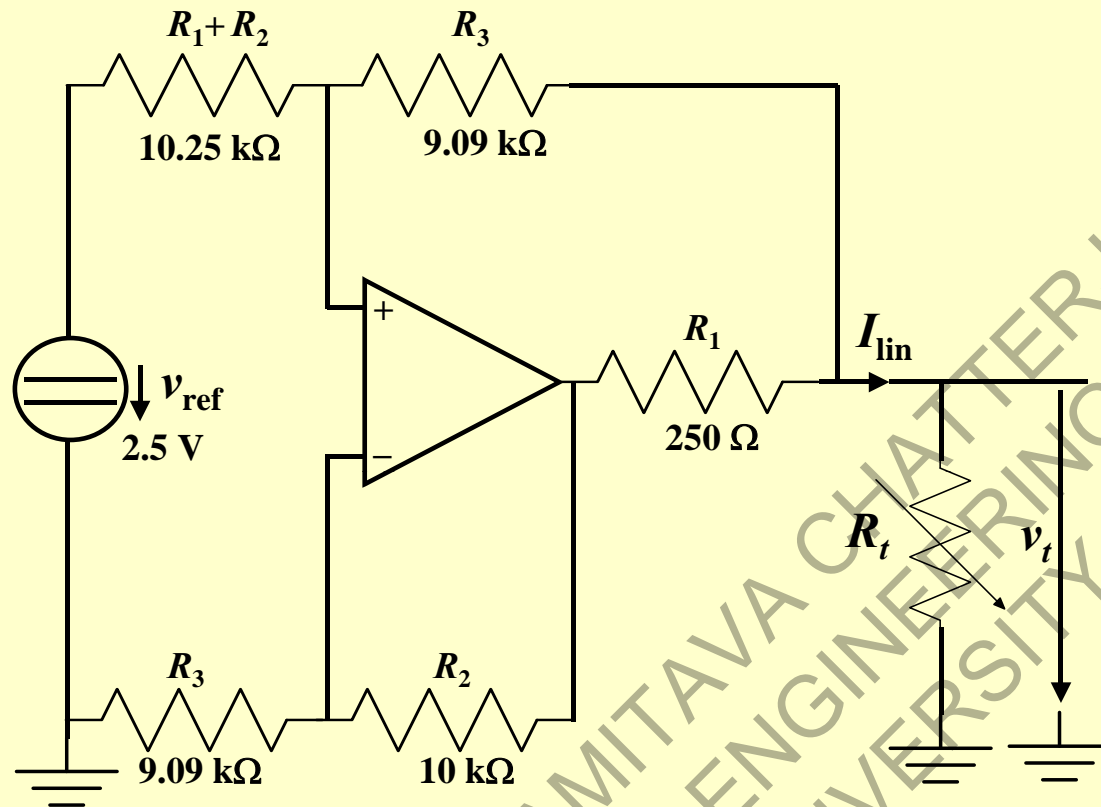Linearization of Pt-100 Sensor (contd...)



$$\begin{aligned}
 r_o &= -\frac{\Delta v_t}{\Delta I} \\
 &= \frac{R_1 R_3 (R_2 + R_3)}{R_3^2 - R_2^2} \\
 &= R_{lin}
 \end{aligned}$$

**Implementation of current source
having a negative output resistance**

- ✓ If we make $R_1 = 250 \Omega$, $R_2 = 10 \text{ K}\Omega$ and $R_{lin} = -2.5 \text{ K}\Omega$, we obtain $R_3 = 9.09 \text{ K}\Omega$.

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

Thermistors

- ✓ Thermistors are semiconductor type temperature transducers with a negative temperature co-efficient of resistance.

$$R_T = R_0 \cdot \exp \left[\beta \left(\frac{1}{T} - \frac{1}{T_0} \right) \right]$$

R_0 : resistance at the reference temperature T_0 ,

β : an experimentally determined constant, varies between 3500K and 4600K ,

T and T_0 : measured in Kelvin.


- ✓ Thermistors have large temperature co-efficients (-3 to -5% per °C .
- ✓ More accurate temperature-resistance relation:

$$\frac{1}{T} = \frac{1}{T_0} + \frac{1}{\beta} \ln \frac{R_T}{R_0} + \frac{1}{C} \left(\ln \frac{R_T}{R_0} \right)^3$$

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

Linearization of Thermistors

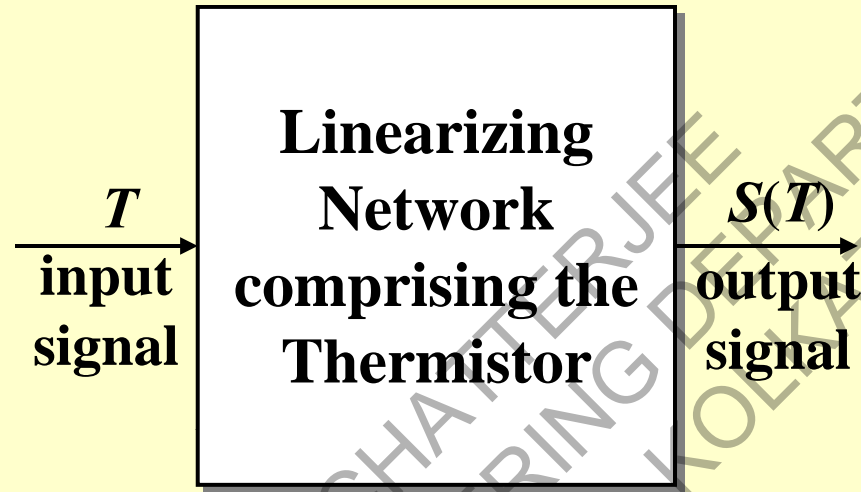

Schematic representation of linearizing networks for the thermistors

$$S(T) = S(T_r) + h \cdot S'(T_r) + \frac{h^2}{2!} \cdot S''(T_r) + \frac{h^3}{3!} \cdot S'''(T_r) + \dots$$

- ✓ $h = T - T_r$ is the increment or decrement in temperature about T_r . $S'(T_r)$, $S''(T_r)$, ... are derivatives of $S(T)$ with respect to T , at $T = T_r$.

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

Linearization of Thermistors (contd...)


Considerations

- ✓ The major contribution to non-linearity comes from the h^2 term containing $S''(T_r)$. This term can be made zero by proper choice of circuit components.
- ✓ Under this condition, the $S(T)$ vs. T characteristic can be assumed to be linear over a wide span of temperature, as long as the h^3 term remains negligibly small.
- ✓ The condition $S''(T_r) = 0$ implies that the $S(T)$ vs. T curve should have a point of inflection at $T = T_r$.
- ✓ In practice, by proper selection of components, the point of inflection is located at the midpoint T_M of the range of temperature over which linearization is to be carried out.

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

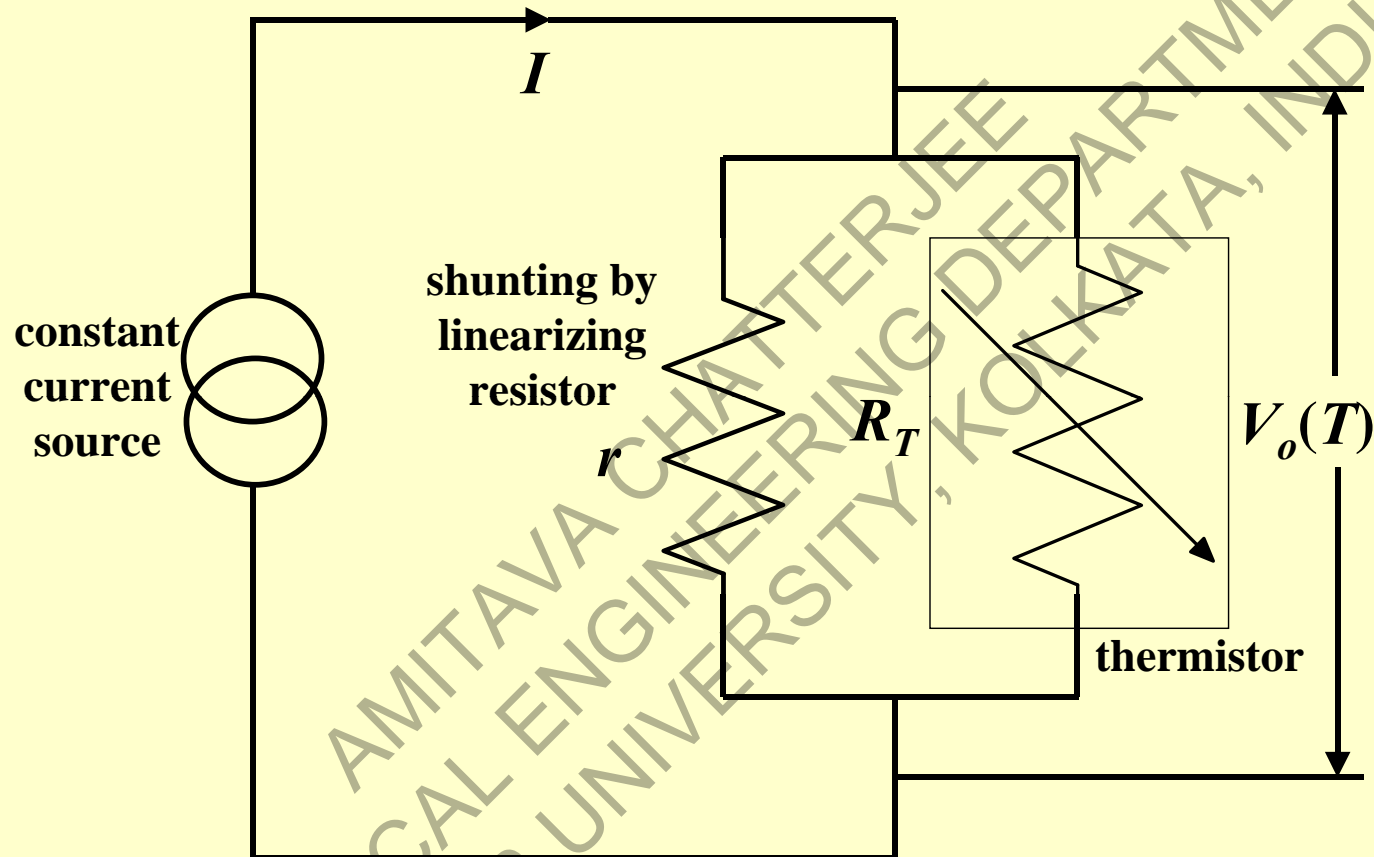Linearization of Thermistors by a Shunt Resistor




A simple linearization circuit for thermistors

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

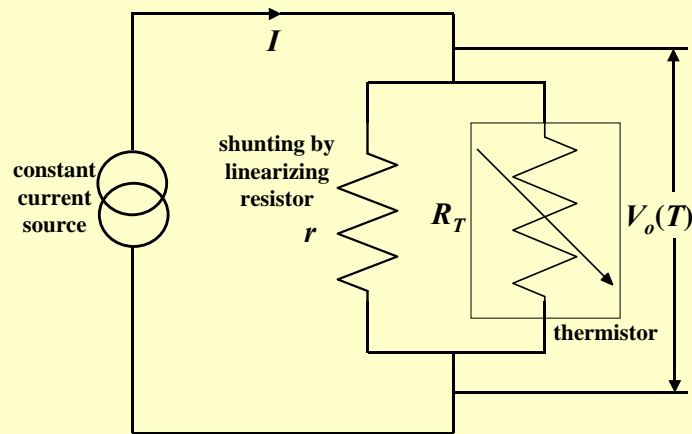Linearization of Thermistors by a Shunt Resistor (contd...)



output signal = voltage across the thermistor

$$S(T) = V_o(T) = I \cdot R_{eq}(T) = I \cdot \frac{rR_T}{r + R_T}$$

as I is const., equivalent $S(T) = R_{eq}(T) = \frac{rR_T}{r + R_T}$

$$S'(T) \approx R'_{eq}(T) = \frac{r \cdot R'_T(r + R_T) - r \cdot R_T \cdot R'_T}{(r + R_T)^2} = \frac{r^2 \cdot R'_T}{(r + R_T)^2}$$

similarly $S''(T) \approx R''_{eq}(T) = \frac{r^2 \cdot R''_T(r + R_T)^2 - 2r^2 \cdot (R'_T)^2(r + R_T)}{(r + R_T)^4}$


Design Procedure: make $S''(T_M) = 0 \Rightarrow R''_{eq}(T_M) = 0 \Rightarrow r = \frac{2(R'_{T_M})^2}{R''_{T_M}} - R_{T_M}$

Now, $R'_{T_M} = R_{T_M} \cdot \left(-\frac{\beta}{T_M^2}\right) = R \cdot e^{\frac{\beta}{T_M}} \cdot \left(-\frac{\beta}{T_M^2}\right) \Rightarrow R''_{T_M} = R_{T_M} \cdot \left(\frac{\beta}{T_M^3}\right) \left(2 + \frac{\beta}{T_M}\right)$

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

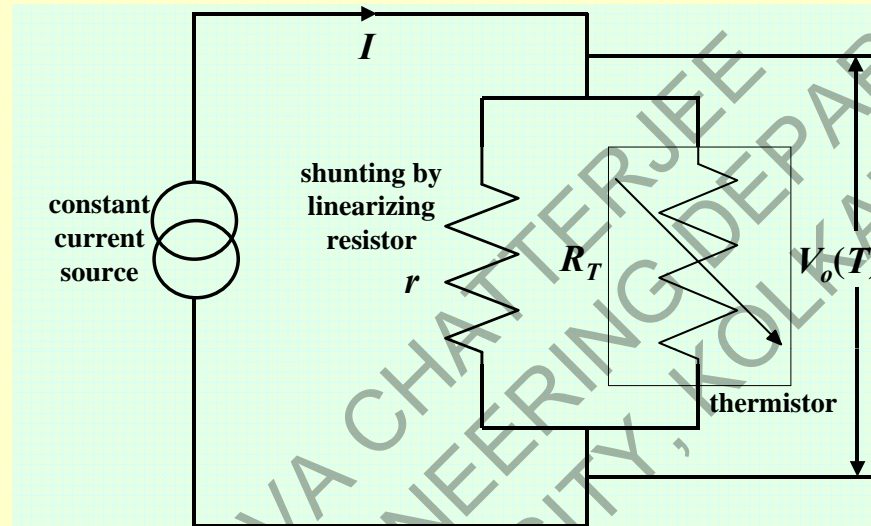Linearization of Thermistors by a Shunt Resistor (contd...)




Final expression for the linearizing shunt resistance r :

$$r = R_{T_M} \left[\frac{\beta - 2T_M}{\beta + 2T_M} \right]$$

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

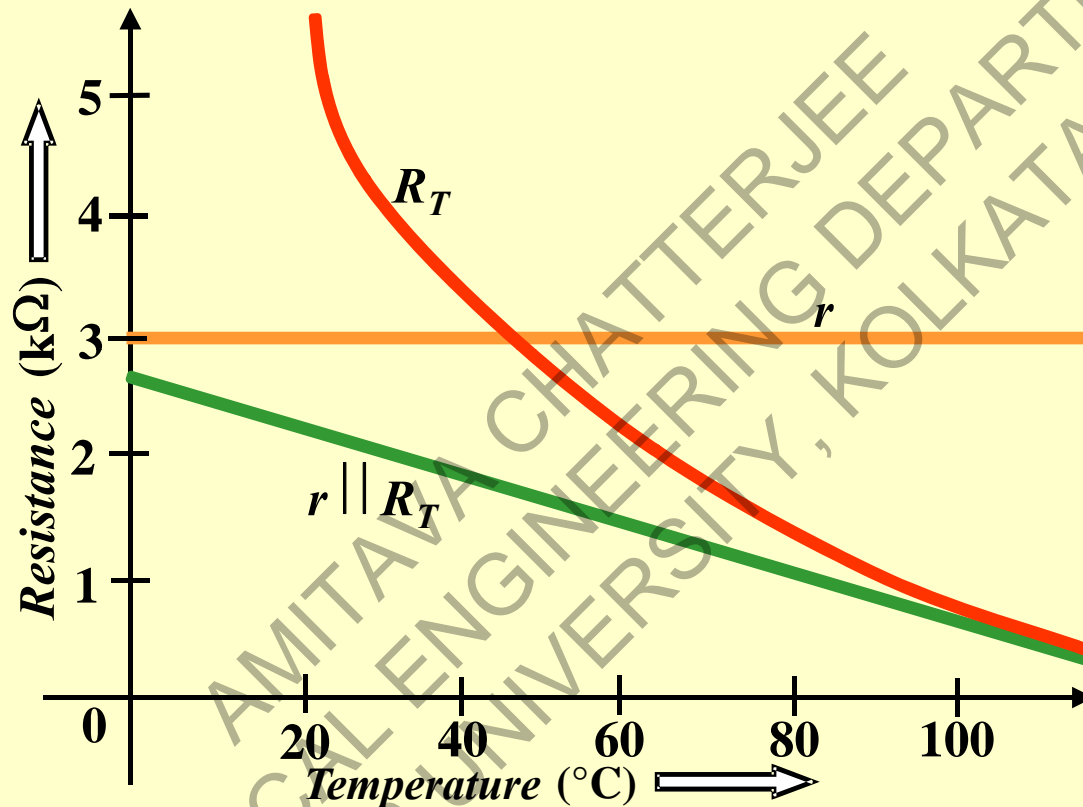Linearization of Thermistors by a Shunt Resistor (contd...)




**Linearization of NTC thermistor
employing a parallel resistor**

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

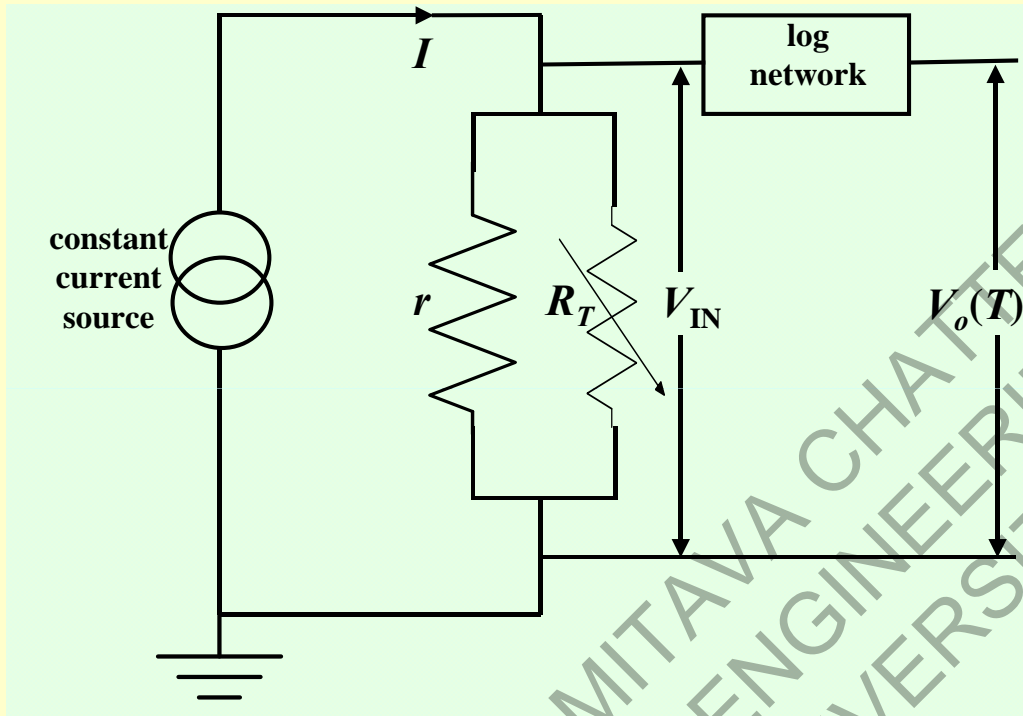Linearization of Thermistors by a Logarithmic Network



Thermistor linearization using logarithmic network

$$V_{IN} = I \cdot R_{eq} \quad \text{and}$$

$$V_o(T) = -K \log_{10} \frac{V_{IN}}{V_{ref}}$$

K = scale factor of the logarithmic network,

V_{ref} = effective internally generated voltage in the log-network,

R_T = thermistor resistance at T K


$$R_{eq} = \frac{rR_T}{r + R_T}$$

- ✓ This scheme can display a linear voltage-temperature relation over a much wider range of temperature (-25°C to $+100^{\circ}\text{C}$) with reasonably good response linearity.

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

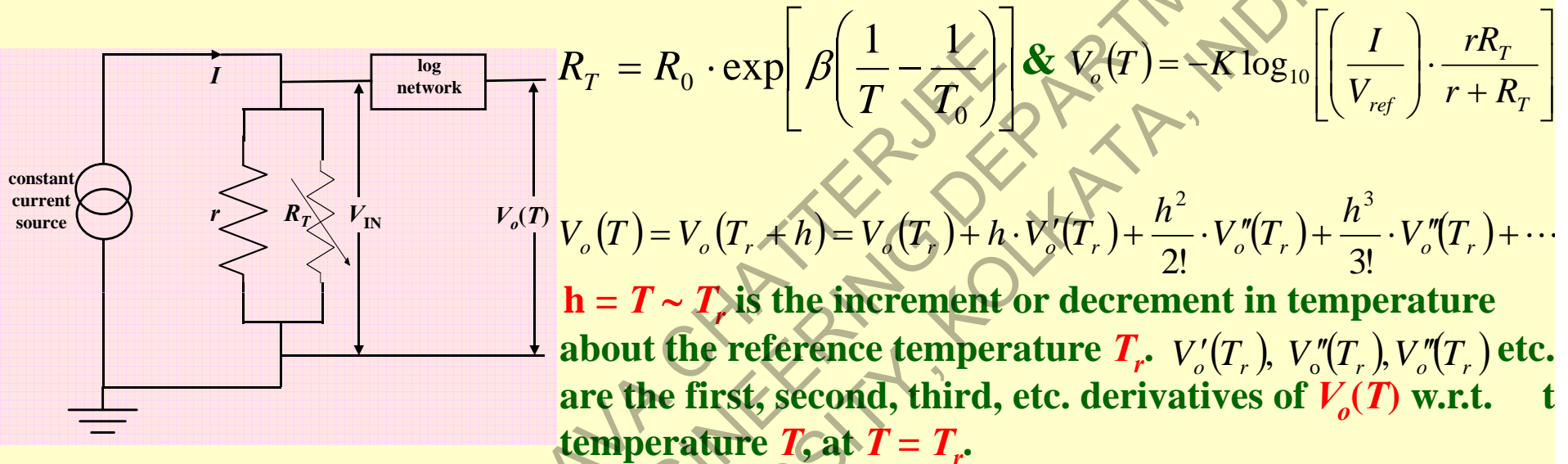
Linearization of Thermistors by a Logarithmic Network (contd...)



Design Procedure: make the h^2 term zero $\Rightarrow V_o''(T_r) = 0$

T_r is considered at the midpoint T_M of the range of temperature over which linearization is to be carried out

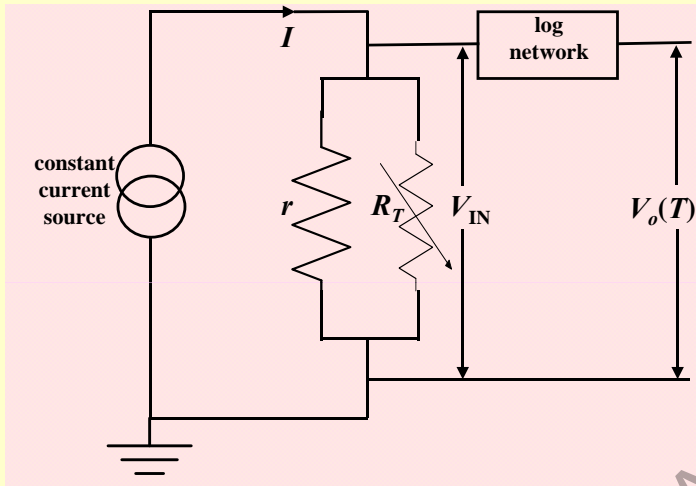Linearization of Thermistors by a Logarithmic Network (contd...)



$$V_o(T) = -K \log_{10} \left[\left(\frac{I}{V_{ref}} \right) \cdot \frac{rR_T}{r + R_T} \right] = -K \log_{10} \left[Y \cdot \frac{rR_T}{r + R_T} \right] \quad \left(Y = \frac{I}{V_{ref}} \right)$$

$$V_o'(T) = \frac{-K}{Y} \cdot \frac{r^2 R_T'}{rR_T(r + R_T)} = -K_1 \cdot \frac{R_T'}{R_T(r + R_T)} \quad \left(K_1 = \frac{Kr}{Y} \right)$$


$$V_o''(T) = -K_1 \cdot \frac{[rR_T R_T'' + R_T^2 R_T'' - R_T'^2 (r + 2R_T)]}{R_T^2 (r + R_T)^2}$$

Design condition: $V_o''(T_M) = 0$ \rightarrow $r = \frac{-R_{T_M} [2R_{T_M}'^2 - R_{T_M} R_{T_M}'']}{[R_{T_M}'^2 - R_{T_M} R_{T_M}'']}$

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

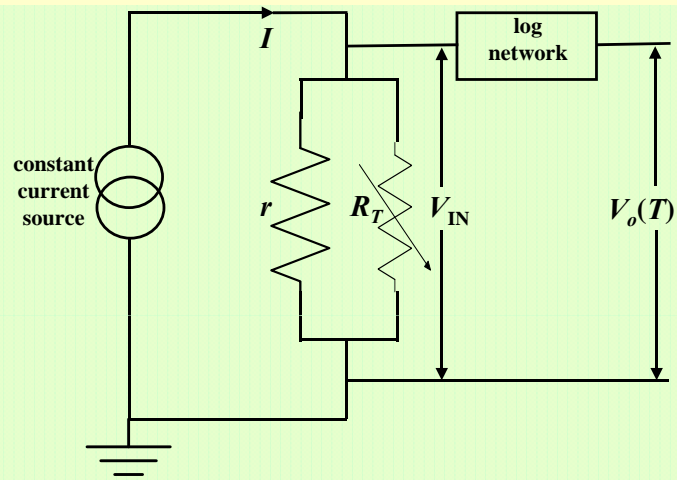Linearization of Thermistors by a Logarithmic Network (contd...)



$$R'_T = R \cdot e^{\frac{\beta}{T}} \cdot \left(-\frac{\beta}{T^2} \right) = R_T \cdot \left(-\frac{\beta}{T^2} \right)$$

$$R''_T = R \cdot e^{\frac{\beta}{T}} \cdot \left(\frac{\beta^2}{T^4} \right) + R \cdot e^{\frac{\beta}{T}} \cdot \left(\frac{2\beta}{T^3} \right) = R \cdot e^{\frac{\beta}{T}} \cdot \left(\frac{\beta}{T^3} \right) \left(2 + \frac{\beta}{T} \right)$$

$$r = \frac{-R_{T_M} \left[2 \left(R \cdot e^{\frac{\beta}{T_M}} \right)^2 \left(\frac{\beta^2}{T_M^4} \right) - \left(R \cdot e^{\frac{\beta}{T_M}} \right)^2 \left(\frac{\beta}{T_M^3} \right) \left(2 + \frac{\beta}{T_M} \right) \right]}{\left[\left(R \cdot e^{\frac{\beta}{T_M}} \right)^2 \left(\frac{\beta^2}{T_M^4} \right) - \left(R \cdot e^{\frac{\beta}{T_M}} \right)^2 \left(\frac{\beta}{T_M^3} \right) \left(2 + \frac{\beta}{T_M} \right) \right]}$$

$$r = \frac{R_{T_M} [\beta - 2T_M]}{2T_M}$$

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

Logarithmic Conversion with an Inherently Logarithmic Device

Shockley's first order theory for a single p-n junction:

$$I = I_0 \left(\exp \frac{qV}{kT} - 1 \right)$$

I = current through the junction (A)

I_0 = the theoretical reverse saturation current (A)

V = the voltage across the junction

q = magnitude of the electronic charge (1.6×10^{-19} C)

k = Boltzmann's constant (1.38×10^{-23} J/K) and

T = the temperature in K


$\frac{kT}{q} \approx 26 \text{ mV}$ at 27°C . Hence, for $V > 100 \text{ mV}$, $I \approx I_0 \exp \frac{qV}{kT} \Rightarrow V = 2.3 \frac{kT}{q} \log_{10} \frac{I}{I_0}$

$\log_{10} I$ varies linearly with V , with a slope of $2.3 \frac{kT}{q}$ Volts/decade of current change.


Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

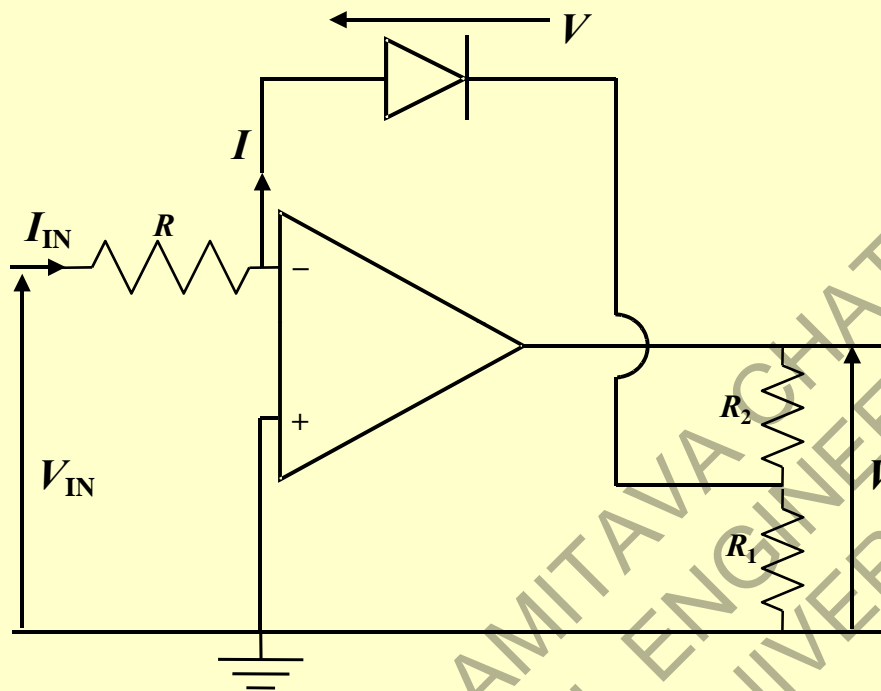Logarithmic Conversion with an Inherently Logarithmic Device (contd...)


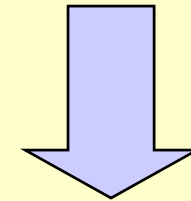
$$V = -\frac{R_1}{R_1 + R_2} V_o = 2.3 \frac{kT}{q} \log_{10} \frac{I_{IN}}{I_o}$$




$$\begin{aligned} V_o &= -\left(\frac{R_1 + R_2}{R_1}\right) 2.3 \frac{kT}{q} \log_{10} \frac{I_{IN}}{I_o} \\ &= -\left(\frac{R_1 + R_2}{R_1}\right) 2.3 \frac{kT}{q} \log_{10} \left(\frac{V_{IN}}{R \cdot I_o}\right) \end{aligned}$$

An op-amp based log amplifier with a diode as a log element

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

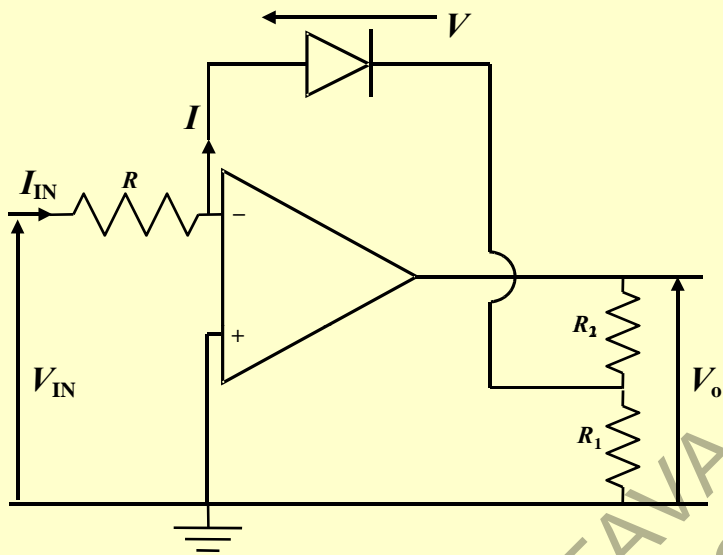
Logarithmic Conversion with an Inherently Logarithmic Device (contd...)




Limitations

- ✓ The problem of temperature dependence of scaling factor, E_o .
- ✓ Marked nonlinear temperature dependence exhibited by I_o .
- ✓ Diodes, used as ideal log elements, do not actually obey Shockley's relation accurately.

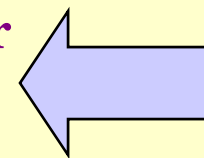Conclusion: Transistors appear to be better candidates than diodes as logarithmic elements.



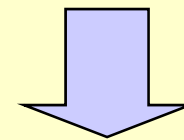
$$I_j = I_{0j} \left(\exp \frac{qV}{m_j kT} - i \right)$$



Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

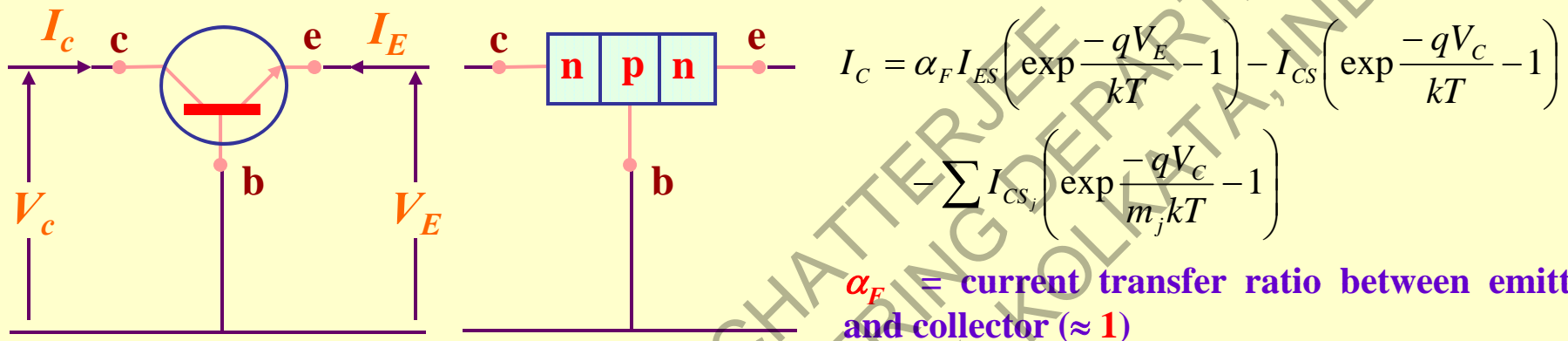Logarithmic Conversion with an Inherently Logarithmic Device (contd...)



A simple n-p-n transistor model, along with its sign conventions

α_F = current transfer ratio between emitter and collector (≈ 1)

I_{CS} = collector reverse saturation current with the emitter shorted to the base

I_{ES} = emitter reverse saturation current with the collector shorted to the base

m_j = a constant, between 1 and 4


If $V_C = 0$ \longrightarrow $I_C = \alpha_F I_{ES} \left(\exp \frac{-qV_E}{kT} - 1 \right)$

When $I_C \gg I_{ES}$ \longrightarrow $-V_E = 2.3 \frac{kT}{q} \log_{10} \left(\frac{I_C}{I_o} \right)$ where $I_o = \alpha_F I_{ES}$

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

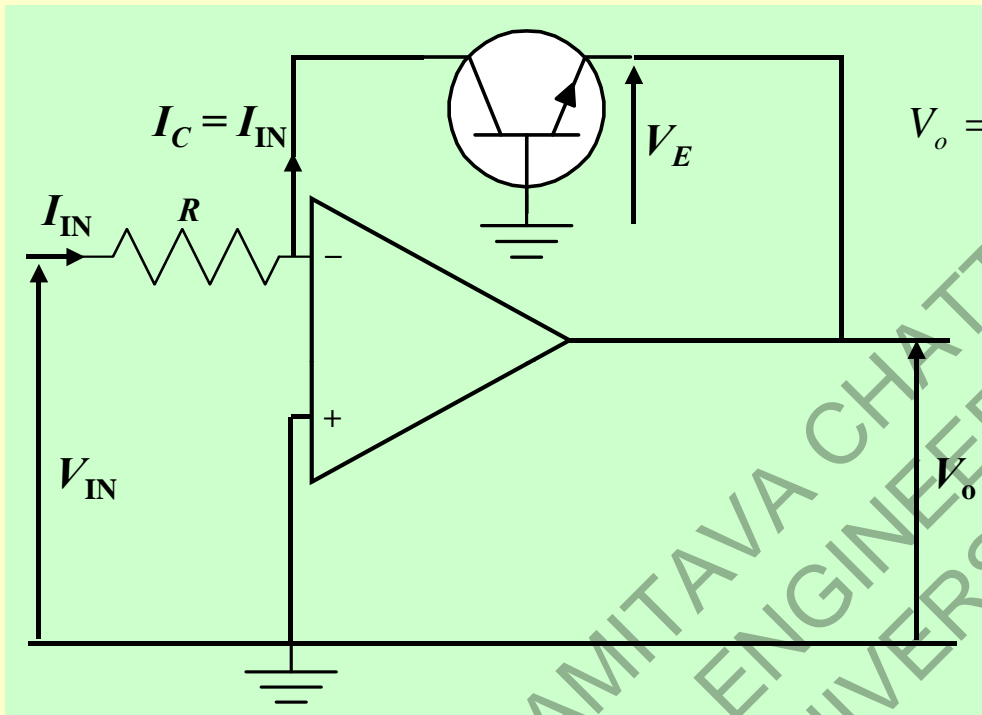Logarithmic Conversion with an Inherently Logarithmic Device (contd...)




$$V_o = -2.3 \frac{kT}{q} \log_{10} \left(\frac{I_{IN}}{\alpha_F I_{ES}} \right) = -2.3 \frac{kT}{q} \log_{10} \left(\frac{V_{IN}}{R \cdot \alpha_F I_{ES}} \right)$$

Practical considerations

- ✓ Temperature dependent errors.

Sources:
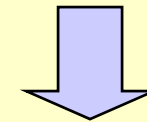
$$I_0 = \alpha_F I_{ES} \quad \text{and} \quad E_o = 2.3 \frac{kT}{q}$$



Solution??


- ✓ Use matched transistors to enable cancellation of the I_0 terms.

The transdiode configuration of a logarithmic amplifier

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

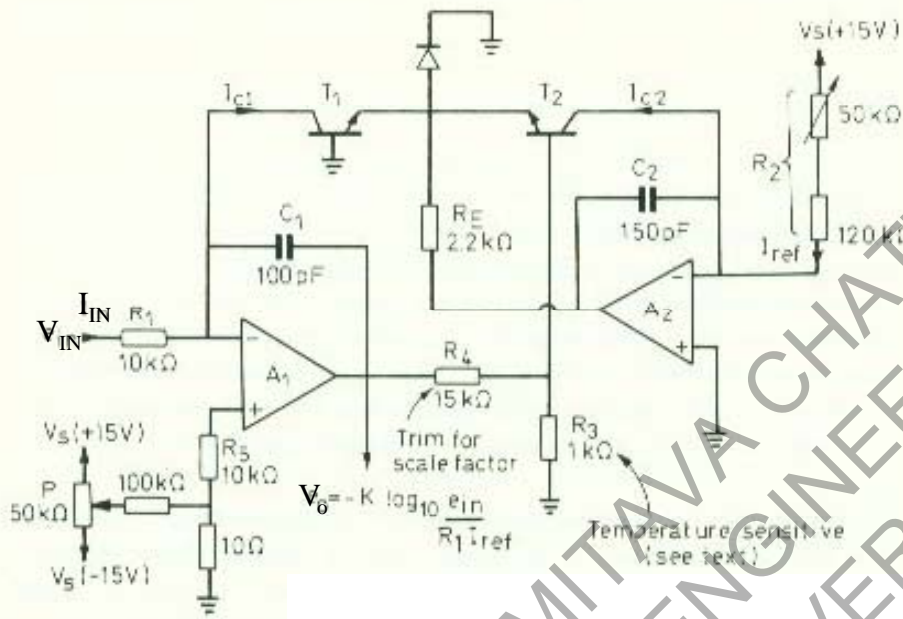Logarithmic Conversion with an Inherently Logarithmic Device (contd...)




$$V_{E_1} - V_{E_2} = V_o \frac{R_3}{R_3 + R_4}$$

We can write:

$$V_{E_1} = -E_o \log_{10} \left(\frac{I_{C_1}}{I_{O_1}} \right)$$

$$V_{E_2} = -E_o \log_{10} \left(\frac{I_{C_2}}{I_{O_2}} \right)$$

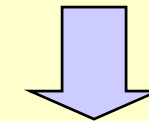Hence: $V_{E_2} - V_{E_1} = E_o \log_{10} \frac{I_{C_1}}{I_{C_2}} \cdot \frac{I_{O_2}}{I_{O_1}}$



$$\begin{aligned} V_o &= -\frac{R_3 + R_4}{R_3} 2.3 \frac{kT}{q} \log_{10} \frac{I_{IN}}{I_{ref}} \\ &= -\frac{R_3 + R_4}{R_3} 2.3 \frac{kT}{q} \log_{10} \frac{V_{IN} \cdot R_2}{V_s \cdot R_1} \end{aligned}$$

A temperature compensated log converter
(with 2 op-amps and 2 logging transistors)

Amitava Chatterjee

Department of Electrical Engg., Jadavpur University, Kolkata, India

Thank You

AMITAJAYA CHATTERJEE
ELECTRICAL ENGINEERING DEPARTMENT
JADAVPUR UNIVERSITY, KOLKATA, INDIA