

# Design and Synthesis of Active Filter

## References:

H. Lam, "ANALOG AND DIGITAL FILTERS: Design and Realization"


W. K. Chen, "Passive and Active Filters: Theory and Implementations"

V. K. Aatre, "Network Theory And Filter Design"


## What is a Filter?

- An **electric filter** is a **frequency selective circuit** that passes a specified band of frequencies and blocks or attenuates signals of frequencies outside this band.
- Filter modifies signals in frequency domain – **both in amplitude and phase.**

## What is a Filter?


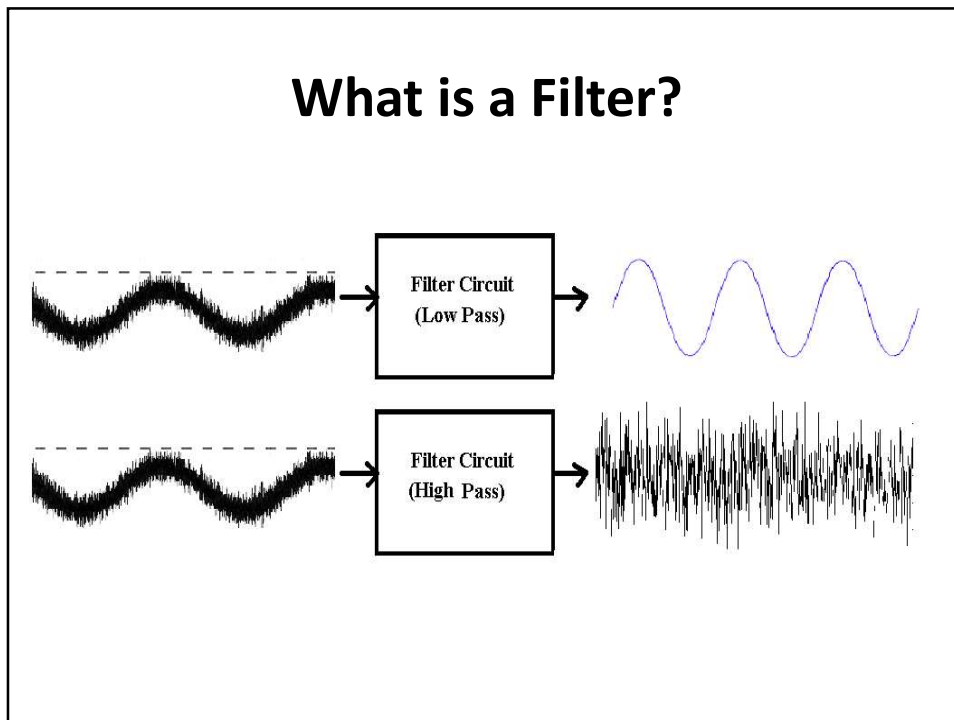


## Filter Types

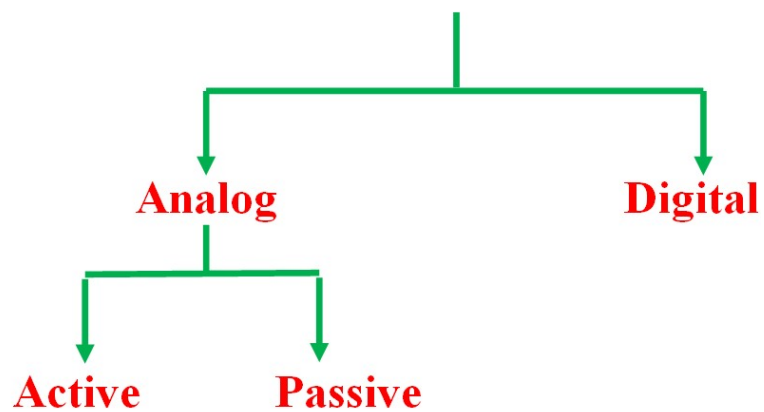


• Analog filters are designed to process analog signals.

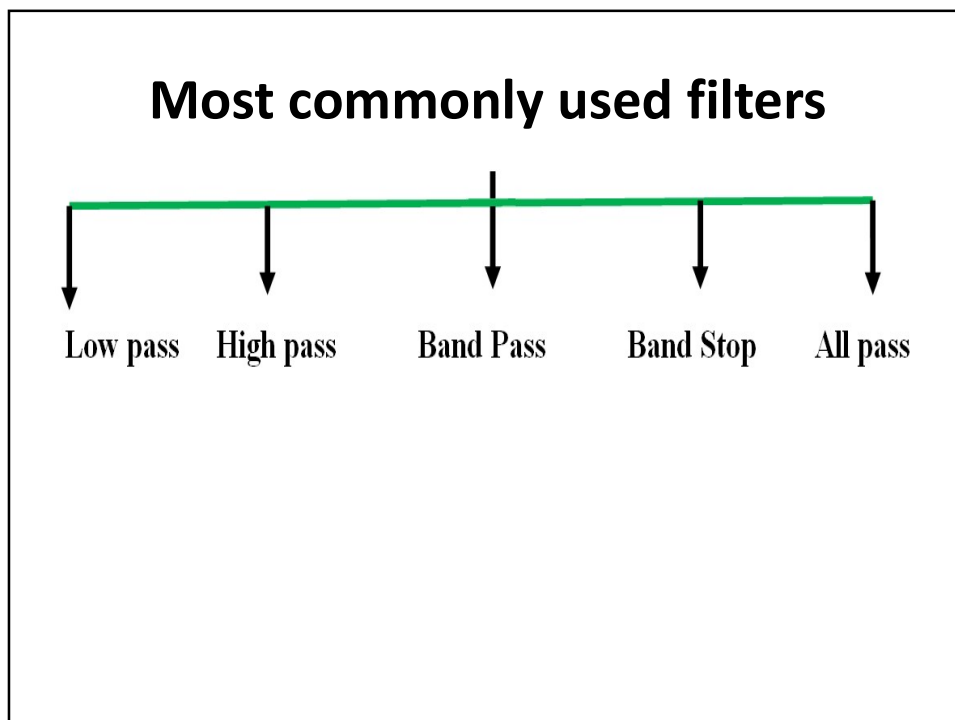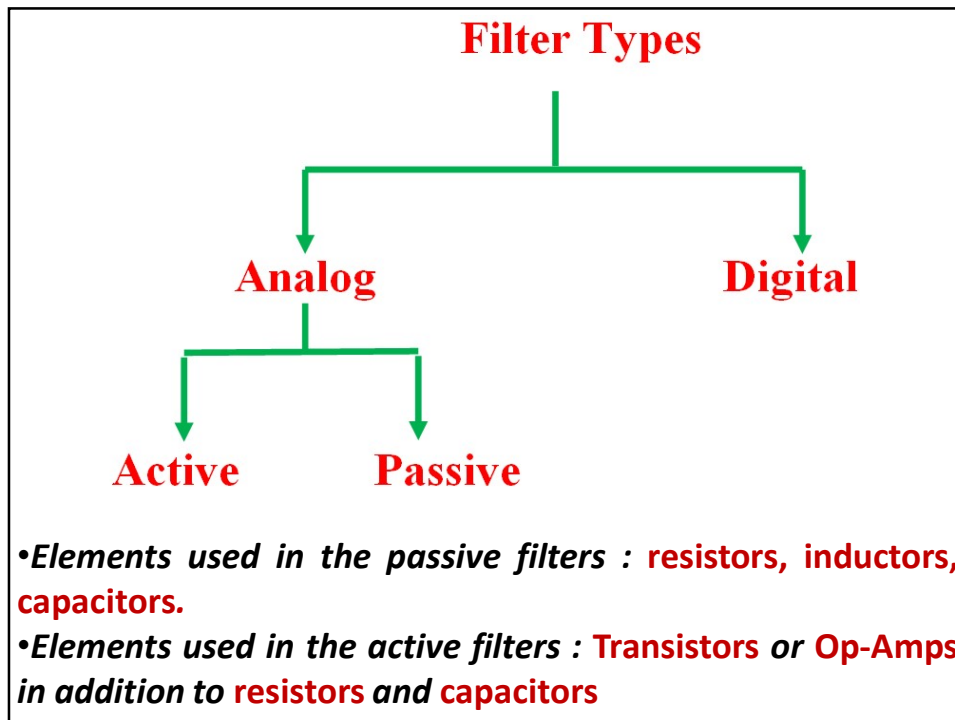• Digital filters process analog signals using digital techniques.




## Most commonly used filters

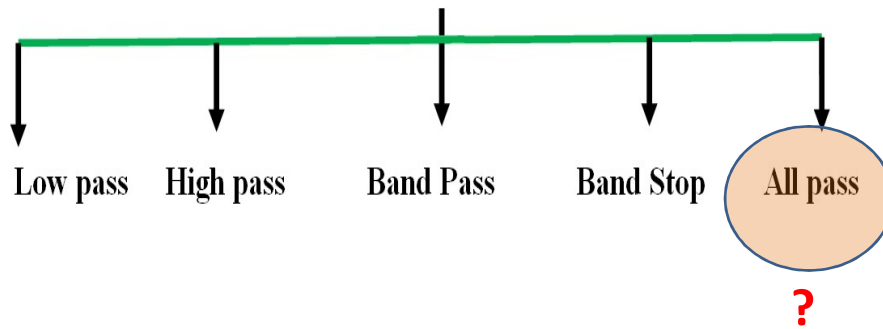
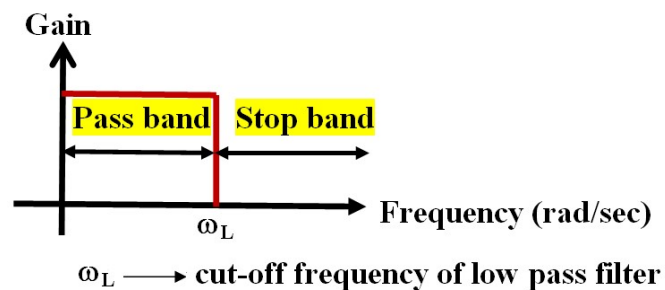
## Low pass Filter


- **Passes low frequency** components and attenuates high frequency components



**Ideal Characteristics of Low pass filter**
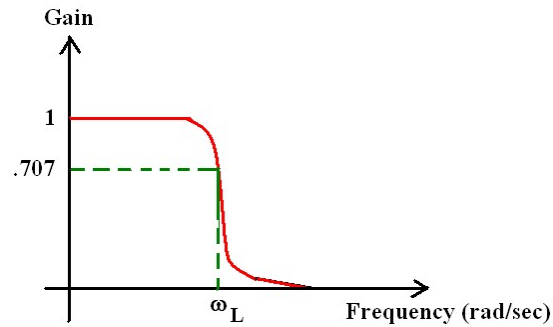
## Low pass Filter


- **Passes low frequency** components and attenuates high frequency components



**Actual Characteristics of Low pass filter**
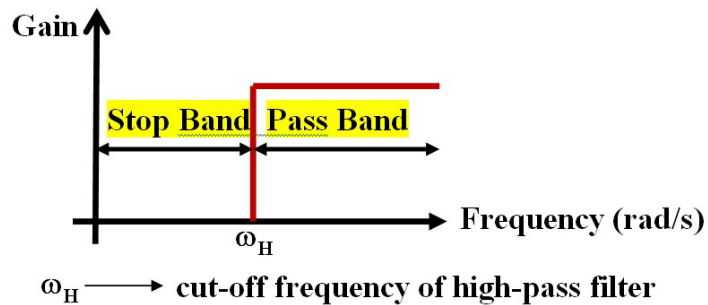
## High pass Filter


- **Passes high frequency** components and attenuates low frequency components



**Ideal Characteristics of High pass filter**
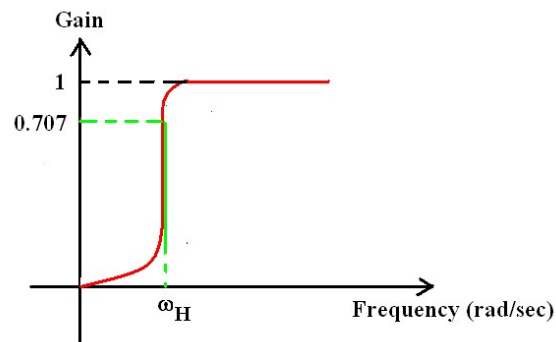
## High pass Filter

- Passes high frequency components and attenuates low frequency components




Actual Characteristics of High pass filter

## Band pass Filter


- Passes certain band of frequencies and attenuates frequencies outside this band.
- Has pass-band between two stop-bands
- **Bandwidth=**  $(\omega_H - \omega_L)$

## Band pass Filter

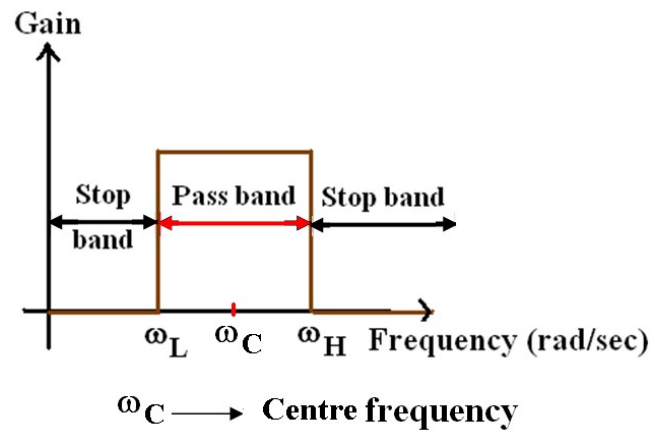


**Ideal Characteristics of Band pass filter**

## Band pass Filter

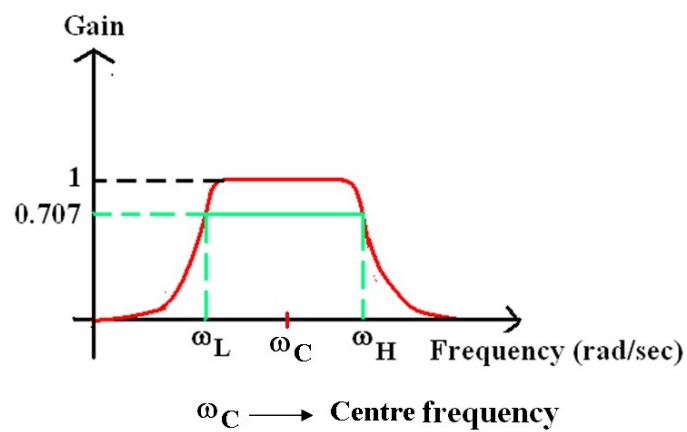


**Actual Characteristics of Band pass filter**

## Band stop Filter

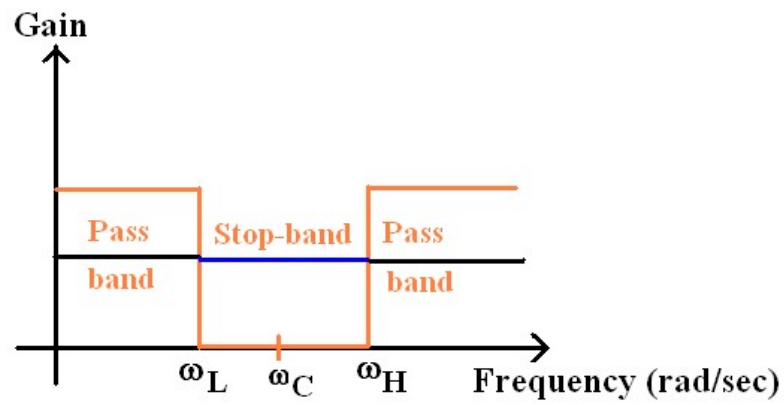

Ideal Characteristics of Band stop filter


## Band stop Filter

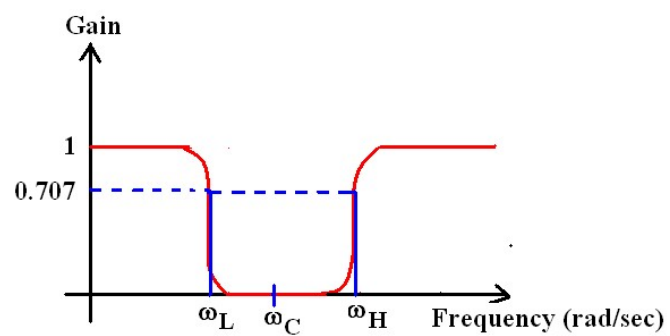

Actual Characteristics of Band stop filter



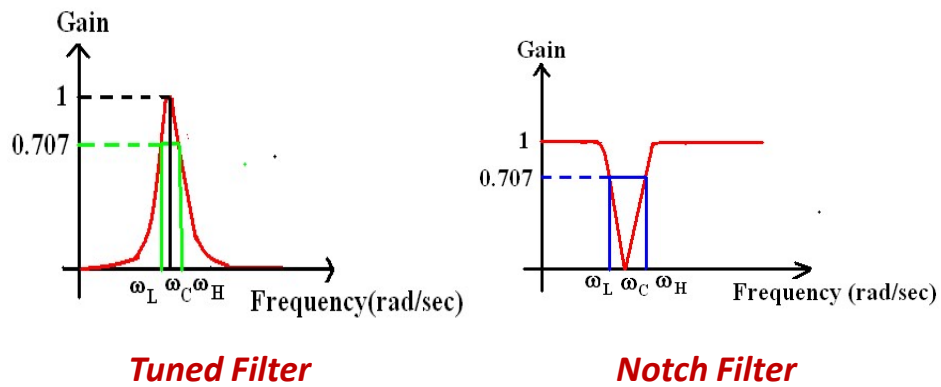**Narrow Band-pass filter: known as *Tuned Filter***  
**Narrow Band-stop filter: known as *Notch Filter***



## Filter Transfer Function

$$H(s) = \frac{a_m s^m + a_{m-1} s^{m-1} \dots \dots \dots a_1 s + a_0}{s^n + b_{n-1} s^{n-1} \dots \dots \dots b_1 s + b_0}$$

$$= \frac{\sum_{i=0}^m a_i s^i}{s^n + \sum_{i=0}^{n-1} b_i s^i}$$

$m$  = number of **zeros** and  $n$  = number of **poles**

## First Order Filter

$$H(s) = \frac{a_1 s + a_0}{s + b_0}$$

For Low-pass Filter:


$$H_{LP}(s) = \frac{a_0}{s + b_0}$$

Pass-band gain =  $(a_0 / b_0)$

Cut-off frequency =  $b_0$  rad/sec

## First Order Filter

For Low-pass Filter:

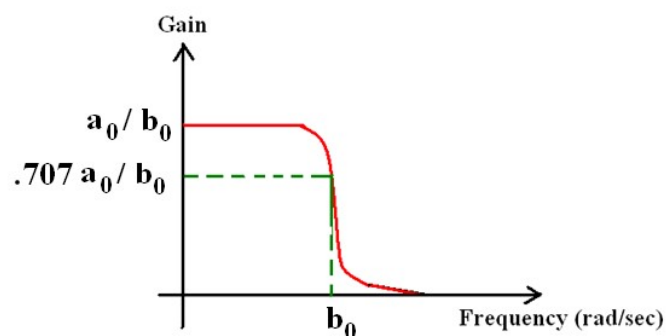


Pass-band gain =  $(a_0 / b_0)$

Cut-off frequency =  $b_0$  rad/sec
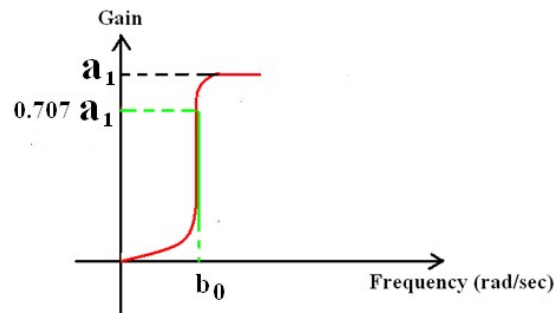
## First Order Filter

For **High-pass Filter**:  $H_{HP}(s) = \frac{a_1 s}{s + b_0}$



Pass-band gain =  $a_1$

Cut-off frequency =  $b_0$  rad/sec

## Second Order Filter

$$H(s) = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + b_1 s + b_0}$$

For **Low-pass Filter**:

$$H_{2LP}(s) = \frac{a_0}{s^2 + b_1 s + b_0}$$

Pass-band gain =  $a_0 / b_0$

Cut-off frequency of the filter =  $\sqrt{b_0}$  rad/s

## Second Order Filter

$$H(s) = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + b_1 s + b_0}$$

For **High-pass Filter:**

$$H_{2HP}(s) = \frac{a_2 s^2}{s^2 + b_1 s + b_0}$$

Pass-band gain =  $a_2$

Cut-off frequency of the filter =  $\sqrt{b_0}$  rad/s

## Second Order Filter

$$H(s) = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + b_1 s + b_0}$$

For **Band-pass Filter:**

$$H_{2BP}(s) = \frac{a_1 s}{s^2 + b_1 s + b_0}$$

Pass-band gain =  $a_1 / b_1$

Centre frequency of the filter =  $\sqrt{b_0}$  rad/s

## Second Order Filter

$$H(s) = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + b_1 s + b_0}$$


For **Band-stop Filter**:

$$H_{2BS}(s) = \frac{a_2(s^2 + b_0)}{s^2 + b_1 s + b_0} \quad [a_2 = a_0 / b_0]$$


Pass-band gain =  $a_2$

Centre frequency of the filter =  $\sqrt{b_0}$  rad/s

### Schematic of **Band-stop Filter**:

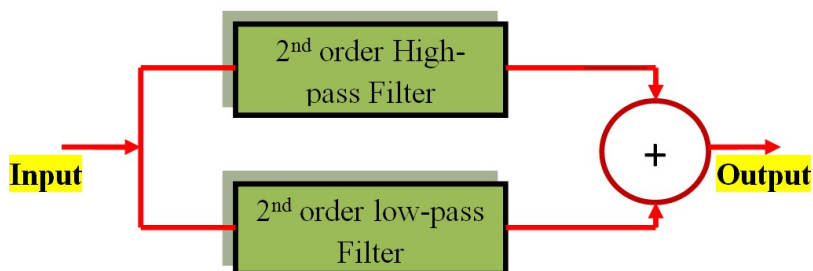

### Schematic of Band-stop Filter:

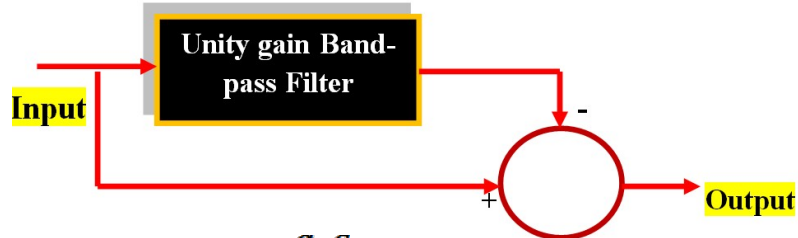

$$H_{BS}(s) = 1 - \frac{a_1 s}{s^2 + b_1 s + b_0} \quad a_1/b_1 = 1$$

$$H_{BS}(s) = \frac{s^2 + b_0}{s^2 + b_1 s + b_0}$$

Pass-band gain = 1

Centre frequency of the filter =  $\sqrt{b_0}$  rad/s

## Filter Circuit Components


*Basic Building Blocks:*

**Resistors, Capacitors & Op-Amps**

## Filter Circuit Components

*Secondary Building Block:*

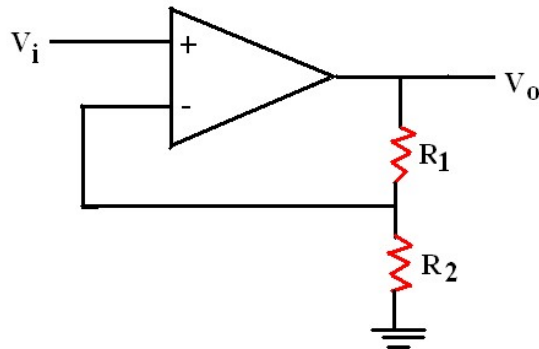
**Voltage Controlled Voltage Source (VCVS)**



$$V_o = KV_i, \quad K = \frac{R_1 + R_2}{R_2} = \text{VCVS gain}$$

## First Order Low-pass Filter

$$H_{1LP}(s) = \frac{a_0}{s + b_0}$$

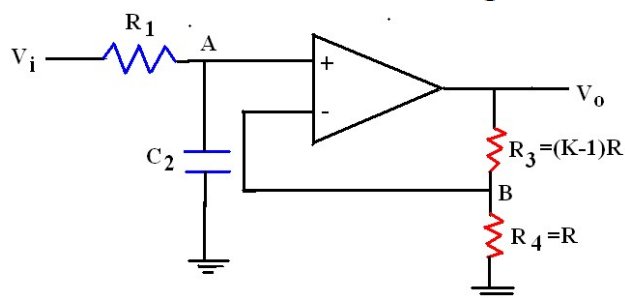


$$H_{1LP}(s) = \frac{K/R_1C_2}{s + \frac{1}{R_1C_2}}$$

Pass-band gain =  $a_0/b_0 = K$   
Cut-off frequency  $b_0 = 1/R_1C_2$

## First Order High-pass Filter


$$H_{1HP}(s) = \frac{a_1 s}{s + b_0}$$

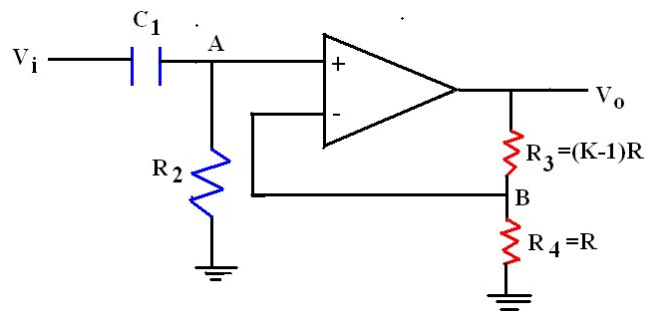

$$H_{1HP}(s) = \frac{Ks}{s + 1/C_1 R_2}$$

Pass-band gain =  $a_1 = K$   
Cut-off frequency  $b_0 = 1 / R_2 C_1$

## Second Order Filter Circuit

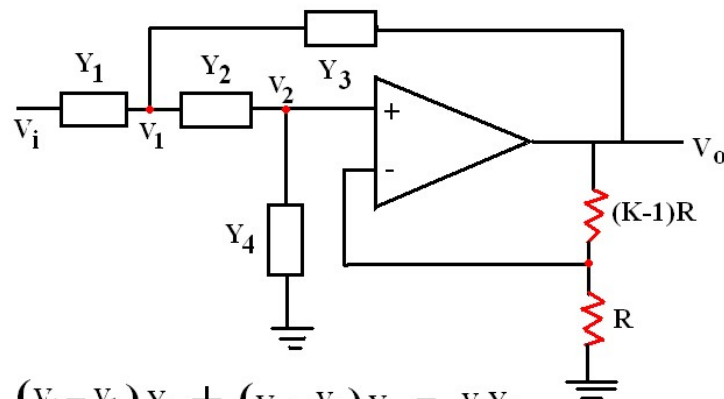


$$(V_i - V_1) Y_1 + (V_o - V_1) Y_3 = V_2 Y_4$$

$$V_2 = \frac{Y_2}{Y_2 + Y_4} V_1$$

$$V_2 = \frac{V_o}{K}$$



## Second Order Filter Circuit

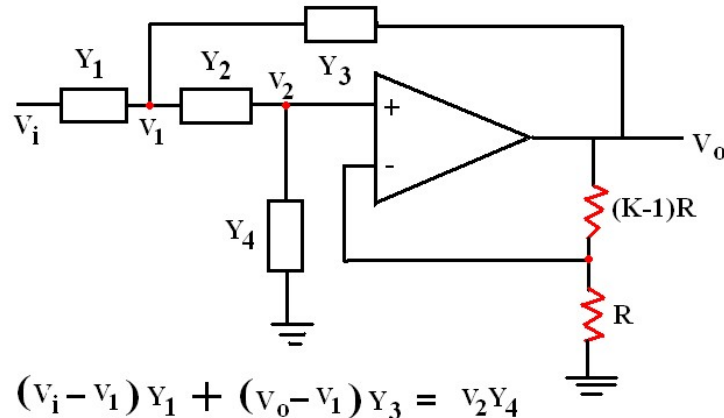


$$(V_i - V_1)Y_1 + (V_0 - V_1)Y_3 = V_2Y_4$$

$$V_2 = V_0/K \quad \& \quad (V_1 - V_2)Y_2 = V_2Y_4$$

$$\frac{V_0}{V_i} = \frac{KY_1Y_2}{Y_3Y_4 + Y_2Y_3(1-K) + Y_4(Y_1 + Y_2) + Y_1Y_2}$$

## Second Order Low-pass Filter

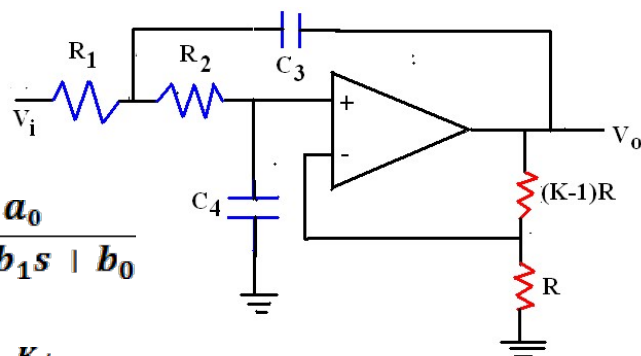


$$H_{2LP}(s) = \frac{a_0}{s^2 + b_1s + b_0}$$

$$H_{2LP}(s) = \frac{K/R_1R_2C_3C_4}{s^2 + s \left[ \frac{1-K}{R_2C_4} + \frac{R_1+R_2}{R_1R_2C_3} \right] + \frac{1}{R_1R_2C_3C_4}}$$

Pass-band gain =  $a_0/b_0 = K = \text{VCVS gain}$

Cut-off frequency =  $\sqrt{b_0} = \frac{1}{\sqrt{R_1R_2C_3C_4}}$

## Second Order High-pass Filter

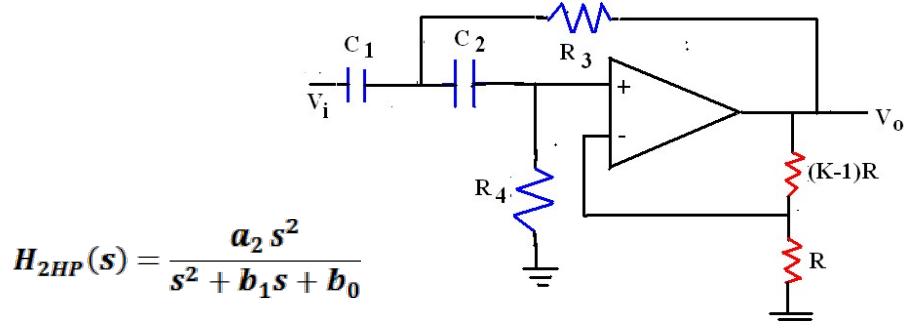


$$H_{2HP}(s) = \frac{a_2 s^2}{s^2 + b_1 s + b_0}$$

$$H_{2HP}(s) = \frac{Ks^2}{s^2 + s \left[ \frac{1-K}{R_3 C_1} + \frac{C_1 + C_2}{C_1 C_2 R_4} \right] + \frac{1}{C_1 C_2 R_3 R_4}}$$

Pass-band gain =  $a_2 = K = \text{VCVS gain}$

Cut-off frequency =  $\sqrt{b_0} = 1/\sqrt{C_1 C_2 R_3 R_4}$

## Band-pass Filter Circuit

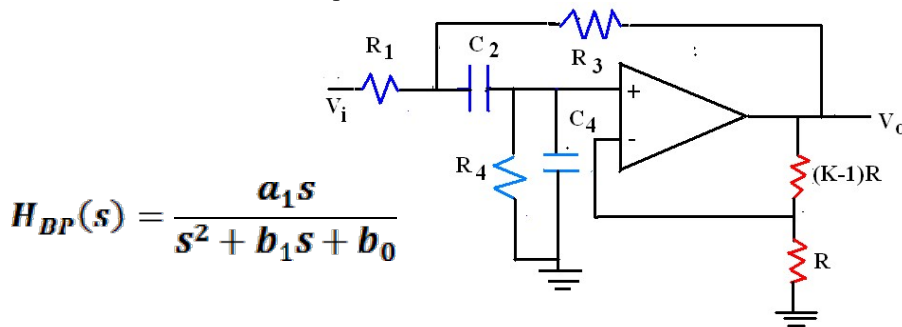


$$H_{BP}(s) = \frac{a_1 s}{s^2 + b_1 s + b_0}$$

$$H_{BP}(s) = \frac{Ks/R_1 C_4}{s^2 + s \left[ \frac{1}{R_3 C_2} + \frac{1}{R_4 C_4} + \frac{1}{R_1 C_2} + \frac{1}{R_1 C_4} + \frac{1-K}{R_3 C_4} \right] + \frac{1}{R_4 \left[ \frac{1}{R_1} + \frac{1}{R_3} \right] C_2 C_4}}$$

Pass-band gain =  $a_1/b_1 = \frac{K/R_1 C_4}{\frac{1}{R_3 C_2} + \frac{1}{R_4 C_4} + \frac{1}{R_1 C_2} + \frac{1}{R_1 C_4} + \frac{1-K}{R_3 C_4}}$

## Band-pass Filter Circuit

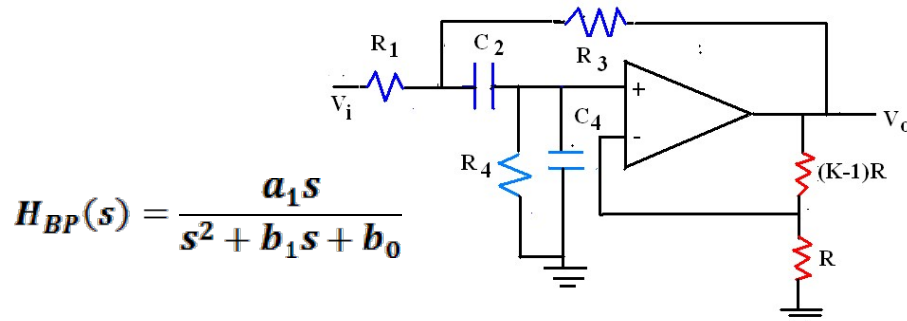

$$H_{BP}(s) = \frac{a_1 s}{s^2 + b_1 s + b_0}$$

$$H_{BP}(s) = \frac{Ks/R_1C_4}{s^2 + s \left[ \frac{1}{R_3C_2} + \frac{1}{R_4C_4} + \frac{1}{R_1C_2} + \frac{1}{R_1C_4} + \frac{1-K}{R_3C_4} \right] + \frac{1}{R_4} \left[ \frac{1}{R_1} + \frac{1}{R_3} \right] \frac{1}{C_2C_4}}$$

$$\text{Center/ cut-off frequency} = \sqrt{b_0} = \sqrt{\frac{1}{R_4} \left[ \frac{1}{R_1} + \frac{1}{R_3} \right] \frac{1}{C_2C_4}}$$

## Filter Approximation Techniques


Why?

**Ideal characteristic is impossible to achieve**

Why?

**Commonly used filter approximation techniques:**

**1) Butterworth Filter**

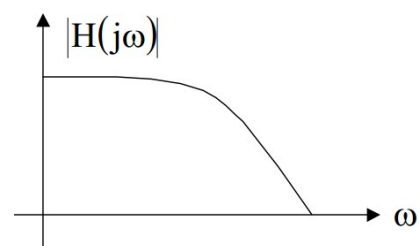


Why?

Commonly used filter approximation techniques:

1) Butterworth Filter

2) Chebyshev Filter

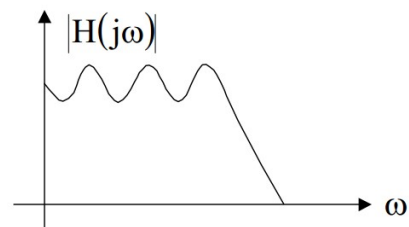


Why?

Commonly used filter approximation techniques:

1) Butterworth Filter

2) Chebyshev Filter


3) Inverse-Chebyshev Filter

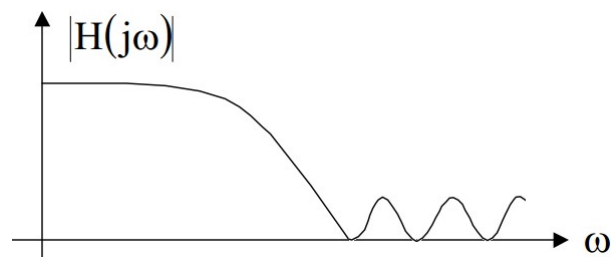

Why?

Commonly used filter approximation techniques:

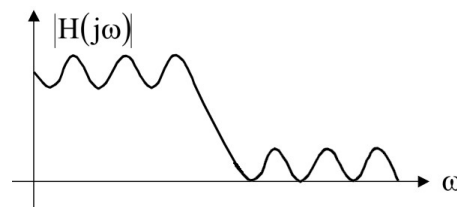
- 1) Butterworth Filter
- 2) Chebyshev Filter
- 3) Inverse-Chebyshev Filter
- 4) Elliptic (Cauer) Filter**



Why?

Commonly used filter approximation techniques:

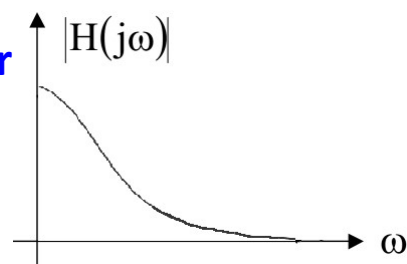- 1) Butterworth Filter
  - 2) Chebyshev Filter
  - 3) Inverse-Chebyshev Filter
  - 4) Elliptic (Cauer) Filter
  - 5) Bessel-Thomson Filter**
- And many more...**



Why?

Commonly used filter approximation techniques:

- 1) Butterworth Filter
- 2) Chebyshev Filter
- 3) Inverse-Chebyshev Filter
- 4) Elliptic (Cauer) Filter
- 5) Bessel-Thomson Filter

And many more...

Why?

Commonly used filter approximation techniques:

- 1) Butterworth Filter
- 2) Chebyshev Filter

These techniques are based on *normalized ideal low-pass filter.*


*The normalized ideal low-pass filter has gain of one in the band of frequencies 0 to 1 rad/s and gain of zero for all frequencies above 1 rad/s*

## Normalized ideal low-pass filter

$$H(j\omega) = e^{-j\omega} \text{ for } 0 \leq \omega \leq 1$$

$$= 0 \text{ for } |\omega| > 1$$


Magnitude

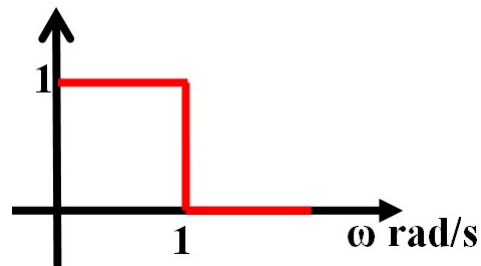

## Butterworth filter Approximation

- Characterized by a monotonically decreasing magnitude function of  $\omega$  for  $\omega \geq 0$ .

Magnitude Function

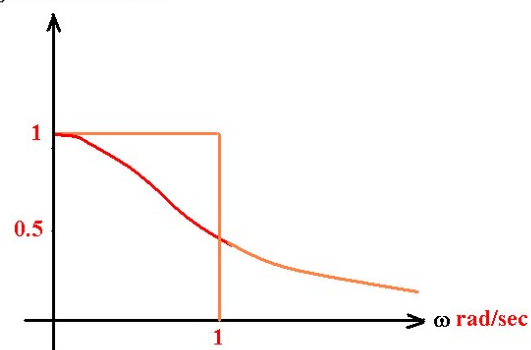



## Butterworth filter Approximation

The  $n$ th order normalized low-pass Butterworth filter has a **magnitude function** given by

$$|H(j\omega)|^2 = \frac{1}{1 + B_n^2(\omega)} = \frac{1}{1 + \omega^{2n}}$$

$B_n(\omega)$  is an  **$n$ th order Butterworth polynomial**

## Butterworth Polynomial

•  **$n$ th order Butterworth polynomial  $B_n(\omega)$**  satisfies the conditions:

- $B_n(\omega)$  is an  $n$ th order polynomial.
- $B_n(0) = 0$
- $B_n(\omega)$  is maximally flat at  $\omega = 0$
- $B_n(1) = 1$

## Butterworth Polynomial

- $B_n(\omega)$  is an  $n^{\text{th}}$  order polynomial.
- $B_n(0) = 0$
- $B_n(\omega)$  is maximally flat at  $\omega = 0$
- $B_n(1) = 1$

From 1<sup>st</sup> condition

$$B_n(\omega) = c_0 + c_1\omega + c_2\omega^2 + \dots + C_n\omega^n$$

## Butterworth Polynomial

- $B_n(\omega)$  is an  $n^{\text{th}}$  order polynomial.
- $B_n(0) = 0$
- $B_n(\omega)$  is maximally flat at  $\omega = 0$
- $B_n(1) = 1$

From 2<sup>nd</sup> condition,  $c_0 = 0$

$$B_n(\omega) = c_1\omega + c_2\omega^2 + \dots + C_n\omega^n$$

## Butterworth Polynomial

- $B_n(\omega)$  is an  $n^{\text{th}}$  order polynomial.
- $B_n(0) = 0$
- $B_n(\omega)$  is maximally flat at  $\omega = 0$
- $B_n(1) = 1$

From 3<sup>rd</sup> condition, as many derivatives as possible of  $B_n(\omega)$  are zero at  $\omega = 0$

$$\frac{dB_n}{d\omega} = c_1 + 2c_2\omega + \dots + nc_n\omega^{n-1} = 0$$

$$\text{Hence, } c_1 = 0$$

## Butterworth Polynomial

- $B_n(\omega)$  is an  $n^{\text{th}}$  order polynomial.
- $B_n(0) = 0$
- $B_n(\omega)$  is maximally flat at  $\omega = 0$
- $B_n(1) = 1$

$$\text{Similarly, } \frac{d^2 B_n}{d^2 \omega} = 0 \quad \text{So } c_2 = 0$$

$$\frac{d^{n-1} B_n}{d^{n-1} \omega} = 0 \quad \text{So } c_{n-1} = 0$$

$$\text{Therefore, } B_n(\omega) = c_n \omega^n$$

## Butterworth Polynomial

- $B_n(\omega)$  is an  $n^{\text{th}}$  order polynomial
- $B_n(0) = 0$
- $B_n(\omega)$  is maximally flat at  $\omega = 0$
- $B_n(1) = 1$

From 4<sup>th</sup> condition,  $c_n = 1$

Therefore,  $B_n(\omega) = \omega^n$

## Properties of Butterworth filter magnitude function

For all  $n$ ,  $|H(j0)|^2 = 1, |H(j1)|^2 = 0.5, |H(j\infty)|^2 = 0$

This implies that the **dc gain is 1**  
and  
**3dB cut-off frequency is at 1 rad/s**

## Butterworth Pole location

$$|H(j\omega)|^2|_{\omega=s/j} = H(j\omega)H(-j\omega)|_{\omega=s/j} = \frac{1}{1 + \omega^{2n}}|_{\omega=s/j}$$

$$= \frac{1}{1 + (-1)^n s^{2n}}$$

The poles of

$H(s)H(-s)$  are the solution of the equation

$$1 + (-1)^n s^{2n} = 0$$

$$-s^{2n} = (-1)^n = e^{\frac{j(2k-1)\pi}{n}}$$


## Butterworth Pole location

$$-s^{2n} = (-1)^n = e^{\frac{j(2k-1)\pi}{n}}$$

$$s_k = e^{\frac{j(2k+n-1)\pi}{2n}}$$

The pole in the **right half-plane** corresponds to an **unstable system**, so pole on the **left-half of the s-plane** have to be considered

## Butterworth Pole location

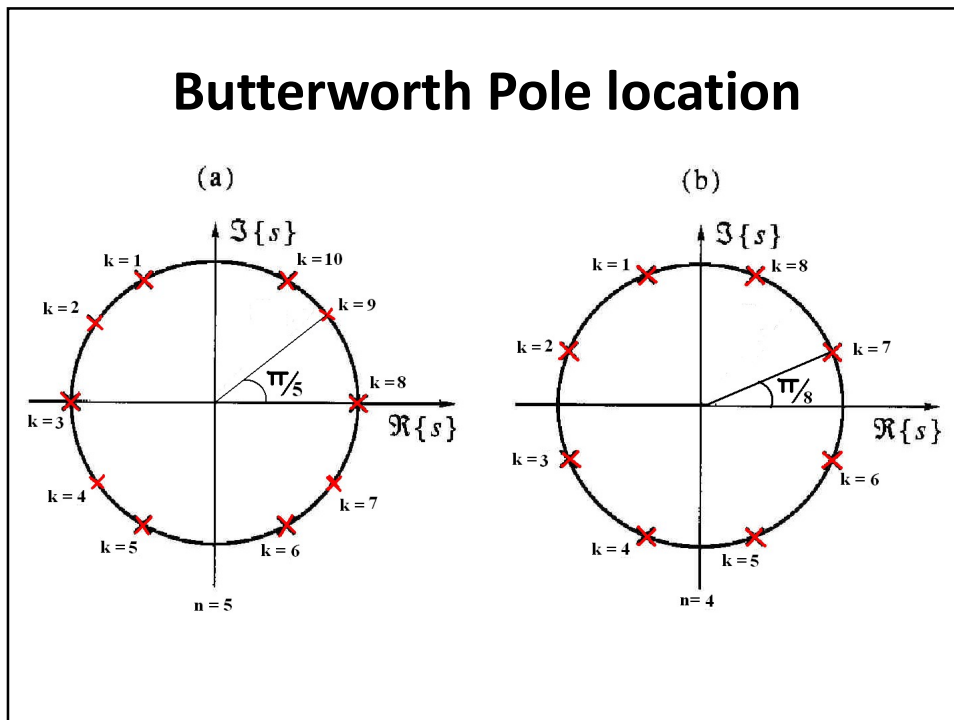

## Butterworth Pole location

Considering poles on the left-hand side of s-plane

$$S_k = \cos\left(\frac{2k+n-1}{2n}\pi\right) + j \sin\left(\frac{2k+n-1}{2n}\pi\right)$$

$$= \cos\left(\frac{2k-1}{2n}\pi + \frac{\pi}{2}\right) + j \sin\left(\frac{2k-1}{2n}\pi + \frac{\pi}{2}\right)$$

$$= -\sin\left(\frac{2k-1}{2n}\pi\right) + j \cos\left(\frac{2k-1}{2n}\pi\right)$$

for  $k = 1, 2, \dots, n$

$$= -\sin \theta_k + j \cos \theta_k$$

where  $\theta_k = \frac{2k-1}{2n}\pi$

The transfer function of the ***nth* order Butterworth filter**

$$H(s) = \prod_{k=1}^n \frac{1}{s - s_k} = \prod_{k=1}^n \frac{1}{(s - \sigma_k - j\omega_k)}$$

Where

$$s_k = \sigma_k + j\omega_k$$

$$\sigma_k = -\sin \theta_k$$

$$\omega_k = \cos \theta_k$$

$$\theta_k = \frac{2k-1}{2n} \pi$$

Therefore, the **poles of the Butterworth filter** are **on unit circle** as,

$$|s_k|^2 = \sigma_k^2 + \omega_k^2 = \sin^2 \theta_k + \cos^2 \theta_k = 1$$

For 1<sup>st</sup> order (i.e. n=1)  
normalized low-pass filter


$$H_{1LP}(s) = \frac{1}{s + 1}$$

For 2<sup>nd</sup> order (i.e. n=2)  
normalized low-pass filter

$$H_{2LP}(s) = \frac{1}{s^2 + 1.414s + 1}$$
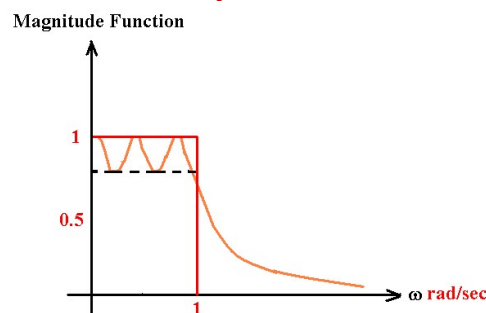
### Chebyshev Filter Approximation Technique

- *equiripple magnitude function* across the *pass-band*
- and*
- *monotonically decreasing magnitude function* in the *stop-band*.





## Chebyshev Filter Approximation Technique

- The  $n$ th order Chebyshev polynomial is:

$$T_n(\omega) = \cos(n \cos^{-1} \omega) \quad \text{for } 0 \leq \omega \leq 1$$

$$= \cosh(n \cosh^{-1} \omega) \quad \text{for } \omega > 1$$

$$\text{If, } x = \cos^{-1} \omega, \quad \text{then } T_n(\omega) = \cos nx$$

Remember,  $\cosh(ju) = \cos u$  &  $\sinh(ju) = j \sin u$

## Chebyshev Filter Approximation

Remember,  $\cosh(ju) = \cos u$  &  $\sinh(ju) = j \sin u$

$$T_n(\omega) = \cos(n \cos^{-1} \omega) \quad \text{for } 0 \leq \omega \leq 1$$

$$= \cosh(n \cosh^{-1} \omega) \quad \text{for } \omega > 1$$

$$\text{If, } x = \cos^{-1} \omega, \quad \text{then } T_n(\omega) = \cos nx$$

$$T_0(\omega) = \cos 0 = 1$$

$$T_1(\omega) = \cos x = \cos(\cos^{-1} \omega) = \omega$$

$$T_2(\omega) = \cos 2x = 2\omega^2 - 1$$

$$T_3(\omega) = \cos 3x = -3\omega + 4\omega^3$$

$$T_4(\omega) = \cos 4x = 1 - 8\omega^2 + 8\omega^4$$

## Properties of Chebyshev polynomial

$$\Rightarrow |T_n(0)| = 0 \quad \text{when } n \text{ is odd}$$

$$\Rightarrow |T_n(0)| = 1 \quad \text{when } n \text{ is even}$$

$$\Rightarrow |T_n(1)| = +1$$

## Recursive formula for Chebyshev Polynomials

$$T_{n+1}(\omega) = 2\omega T_n(\omega) - T_{n-1}(\omega)$$

$$T_0(\omega) = 1 \quad \& \quad T_1(\omega) = \omega$$

## Chebyshev Magnitude Response

The *n*th order normalized low-pass Chebyshev filter is given by:


$$|H(j\omega)|^2 = \frac{1}{1 + \epsilon^2 T_n^2(\omega)}$$

$\epsilon$  is a free parameter that sets the amplitude of the ripple called ripple factor

## Chebyshev Magnitude Response

1.  $|H(j0)|^2=1$  when  $n$  is odd and  $|H(j0)|^2 = \frac{1}{1+\epsilon^2}$  when  $n$  is even.
2. At  $\omega = 1$ ,  $|T_n(1)| = +1$  so  $|H(j0)|^2 = \frac{1}{1+\epsilon^2}$
3. For  $|\omega| \leq 1$ ,  $|H(j\omega)|^2$  oscillates between 1 and  $\frac{1}{1+\epsilon^2}$  and attains a maximum value 1 or minimum value  $\frac{1}{1+\epsilon^2}$ .
4. If  $\frac{1}{1+\epsilon^2} > 0.5$  the 3dB cut-off frequency of the Chebyshev filter is larger than 1 radian/sec.

## Chebyshev Magnitude Response

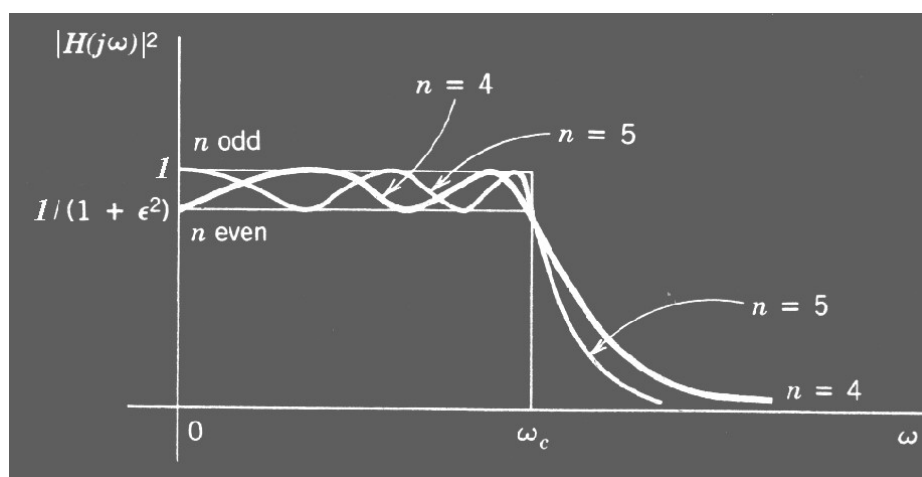

## Chebyshev Pole Locations

The magnitude function of ***n*th order normalized low-pass Chebyshev filter** is

$$|H(j\omega)|^2 = \frac{1}{1 + \epsilon^2 T_n^2(\omega)} = H(j\omega)H(-j\omega)$$

Put  $\omega = s/j$ , then

$$H(s)H(-s) = \frac{1}{1 + \epsilon^2 T_n^2(s/j)}$$

## Chebyshev Pole Locations

$$H(s)H(-s) = \frac{1}{1 + \epsilon^2 T_n^2(s/j)}$$

The pole locations are determined by solving the equation:

$$1 + \epsilon^2 T_n^2(s/j) = 0 \text{ or } T_n^2(s/j) = -\frac{1}{\epsilon^2} = \frac{j^2}{\epsilon^2}$$

$$T_n\left(\frac{s}{j}\right) = \pm \frac{j}{\epsilon} = 0 \pm \frac{j}{\epsilon}$$

## Chebyshev Pole Locations

If  $s_k = \sigma_k + j\omega_k$  we have

$$\sigma_k = \pm \sin \frac{\pi}{2n} (2k - 1) \sinh a$$

$$\omega_k = \cos \frac{\pi}{2n} (2k - 1) \cosh a$$

where  $k=1, 2, \dots, 2n$  and  $a = \frac{1}{n} \sinh^{-1} \frac{1}{\varepsilon}$

## Chebyshev Pole Locations

Considering **left-hand-side s plane** poles,

$$\bar{s}_k = -\sin \frac{\pi}{2n} (2k - 1) \sinh a + j \cos \frac{\pi}{2n} (2k - 1) \cosh a$$

$$= \bar{\sigma}_k + j\bar{\omega}_k \text{ where } k=1, 2, \dots, n$$

$$\bar{\sigma}_k = -\sinh a \sin \frac{\pi}{2n} (2k - 1)$$

$$\bar{\omega}_k = \cosh a \cos \frac{\pi}{2n} (2k - 1)$$

## Chebyshev Pole Locations

$$\frac{\bar{\sigma}_k}{\sinh a} = -\sin \frac{\pi}{2n} (2k - 1)$$


$$\frac{\bar{\omega}_k}{\cosh a} = \cos \frac{\pi}{2n} (2k - 1)$$

$$\frac{\bar{\sigma}_k^2}{\sinh^2 a} + \frac{\bar{\omega}_k^2}{\cosh^2 a} = \sin^2 \frac{\pi}{2n} (2k - 1) + \cos^2 \frac{\pi}{2n} (2k - 1) = 1$$

Hence, poles of Chebyshev filter are on  
*s-plane ellipse*
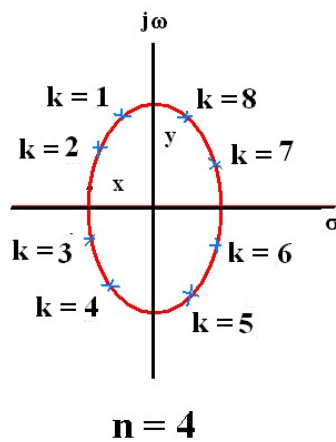
## Chebyshev Pole Locations

$$\frac{\bar{\sigma}_k^2}{\sinh^2 a} + \frac{\bar{\omega}_k^2}{\cosh^2 a} = \sin^2 \frac{\pi}{2n} (2k - 1) + \cos^2 \frac{\pi}{2n} (2k - 1) = 1$$



## Chebyshev Filter Transfer Function

$$H(s) = \frac{H_0}{\prod_{k=1}^n (s - \bar{s}_k)}$$

$$\bar{\sigma}_k = -\sinh a \sin \frac{\pi}{2n} (2k - 1)$$

$$\bar{\omega}_k = \cosh a \cos \frac{\pi}{2n} (2k - 1)$$

where  $k=1,2,\dots,n$  and  $a = \frac{1}{n} \sinh^{-1} \frac{1}{\varepsilon}$

## Chebyshev Filter Transfer Function

$$H(s) = \frac{H_0}{\prod_{k=1}^n (s - \bar{s}_k)}$$

$$H_0 = \frac{1}{\sqrt{1 + \varepsilon^2}} \prod_{k=1}^n (-\bar{s}_k) \text{ for } n \text{ even}$$

$$= \prod_{k=1}^n (-\bar{s}_k) \text{ for } n \text{ odd}$$

## Important Observations

Max value in pass band for  $|H(j\omega)|^2 = H_0$

Min value in pass band for  $|H(j\omega)|^2 = \frac{H_0}{1 + \varepsilon^2}$

Note: at  $\omega = \omega_c$   $|H(j\omega)|^2 = \frac{H_0}{1 + \varepsilon^2}$

## Comparison of

### Butterworth & Chebyshev Responses

• **Butterworth filter** is **maximally flat** filter while **Chebyshev filter** has **ripple in the passband** and **monotonically decreasing stopband**.

• For **Butterworth response**,  $\omega=1$  rad/s identifies the **half-power frequency**, but for **Chebyshev response**  $\omega=1$  rad/s identifies the **end of the ripple band**.

• The **normalized cut-off frequency** of the **Butterworth filter** is always at **1 rad/s** & **Chebyshev filter** has **normalized cut-off frequency more than 1 rad/s**.

• For Butterworth pole locations (**on unit circle**):

$$\sigma_k = -\sin \theta_k$$

$$\omega_k = \cos \theta_k$$

• For Chebyshev pole locations (**on s-plane ellipse**):

$$\sigma_k = -\sinh a \sin \frac{\pi}{2n} (2k-1)$$

$$\omega_k = \cosh a \cos \frac{\pi}{2n} (2k-1)$$