

Sinusoidal Steady State Analysis :



Sinusoidally varying voltage $v(t) = V_m \sin \omega t$.

Amplitude V_m

Argument ωt

Angular freq. ω

~~Period 2π~~

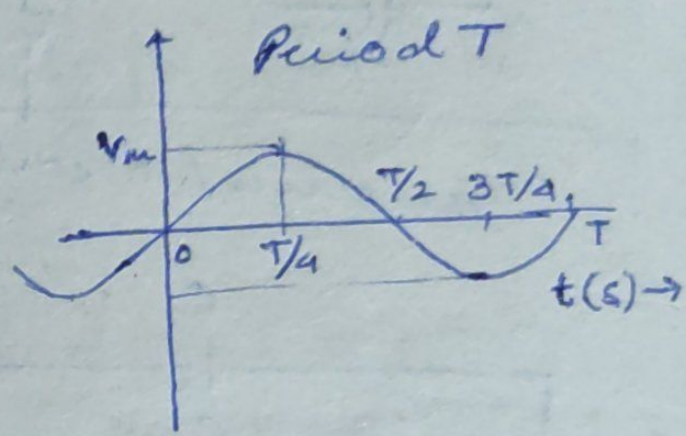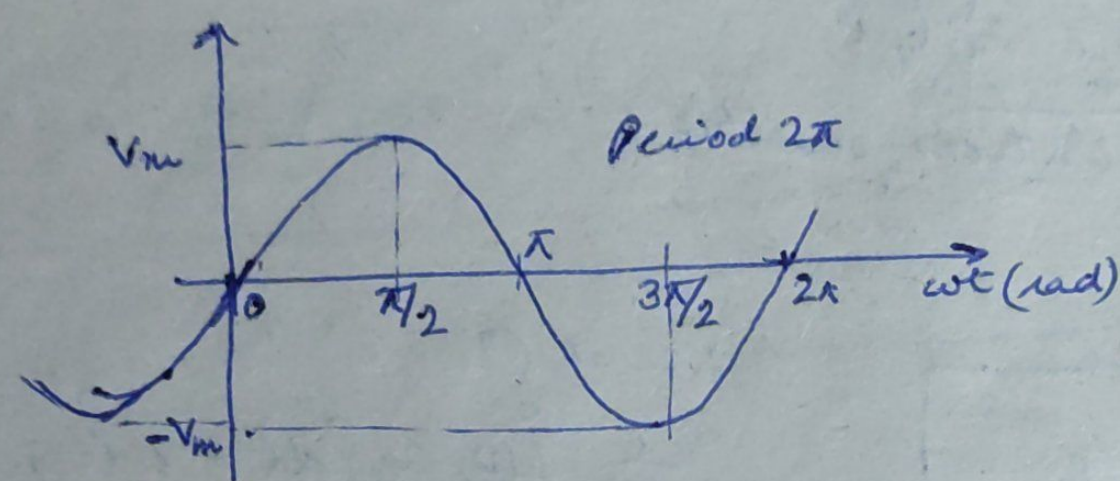

frequency $f = 1/T$


$$\omega = \frac{2\pi}{T} = 2\pi f$$

General form: $v_1(t) = V_m \sin(\omega t + \theta)$.

Phase angle θ .

leads $v_2 = V_m \sin \omega t$ by θ rad.

~~the~~ v_2 lags $v_1(t)$ by θ rad.

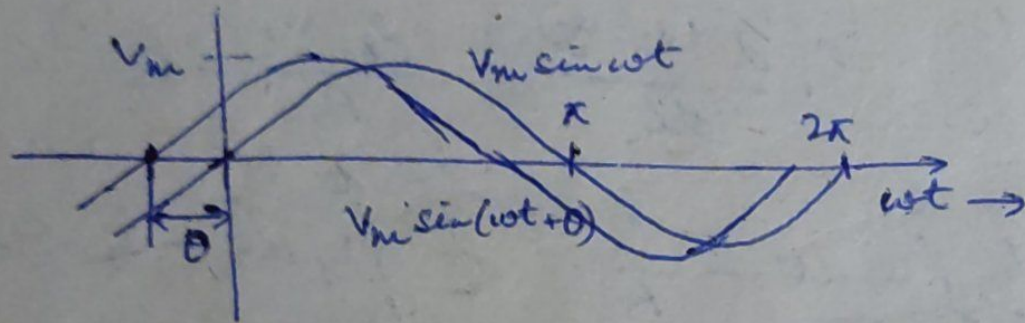

- Both to be written as sine/cos waves. PREFERRED \cos [note:
 $\cos \theta = \sin(90^\circ + \theta)$
 $\sin \theta = \cos(90^\circ - \theta)$
 $= \cos(\theta - 90^\circ)$
 $\therefore \cos \theta = \cos(-\theta)$]
- V_{m1}, V_{m2} assumed +ve
- diff. in phase expressed as $\angle \leq 180^\circ$ in magnitude.

$$v_1 = V_{m1} \sin(5t - 30^\circ)$$

$$v_2 = V_{m2} \cos(5t + 10^\circ) = V_{m2} \sin(5t + 90^\circ + 10^\circ) = V_{m2} \sin(5t + 100^\circ)$$

$\therefore v_2$ leads v_1 by 130° .

Transformation to a phasor: expressed as COSINE wave with PHASE.

Suppose a current $i(t) = I_m \cos(\omega t + \phi)$
 $= \text{Re} (I_m e^{j(\omega t + \phi)})$



\therefore Euler's identity: $e^{j\theta} = \cos\theta + j \sin\theta$

Drop (Re) [adding imag. part], then suppress $e^{j\omega t}$ [common to all sinusoids] $\therefore \mathbf{I} = I_m e^{j\phi} \triangleq I_m \angle \phi$ PHASOR

$i(t) \rightarrow$ TIME DOMAIN REPRESENTATION
 $\mathbf{I} \rightarrow$ FREQ. DOMAIN REPRESENTATION.

So $v(t) = 100 \cos(400t - 30^\circ) \Leftrightarrow \mathbf{V} = 100 \angle -30^\circ$
 $i(t) = 5 \sin(377t + 150^\circ) = 5 \cos(377t - 90^\circ + 150^\circ) = 5 \cos(377t + 60^\circ)$
 $\Leftrightarrow \mathbf{I} = 5 \angle 60^\circ$

Phasor relationships for R, L and C:

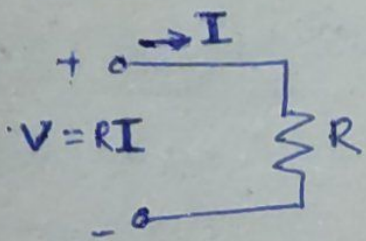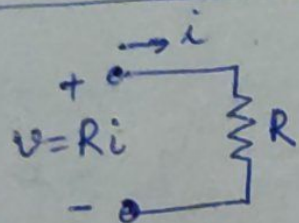

$$v(t) = R i(t)$$

Apply $V_m e^{j(\omega t + \theta)}$ and assume response $I_m e^{j(\omega t + \phi)}$

$$\therefore V_m e^{j(\omega t + \theta)} = R I_m e^{j(\omega t + \phi)}$$


Divide all through by $e^{j\omega t}$ $\therefore V_m e^{j\theta} = R I_m e^{j\phi}$



$$\Rightarrow V = R I$$

Now equality of θ and ϕ apparent as directly related.

$$i(t) = \frac{v(t)}{R} = \frac{8 \cos(100t - 50^\circ)}{4} = 2 \cos(100t - 50^\circ) \text{ A}$$
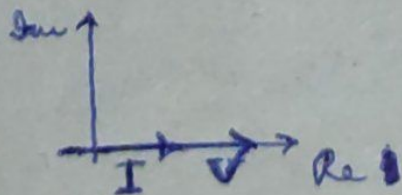
$$\therefore V = 8 \angle -50^\circ \quad I = \frac{8 \angle -50^\circ}{4} = 2 \angle -50^\circ \text{ A}$$



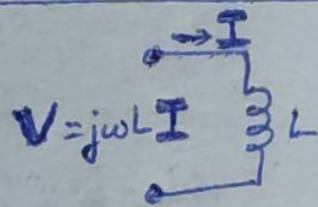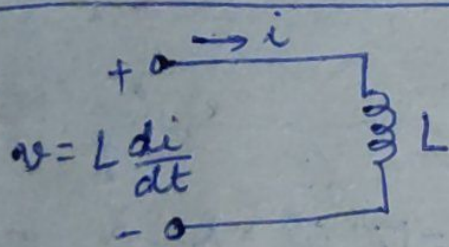

$$v(t) = L \frac{di(t)}{dt}$$

$$\begin{aligned} \therefore V_m e^{j(\omega t + \theta)} &= L \frac{d}{dt} I_m e^{j(\omega t + \phi)} \\ &= j\omega L I_m e^{j(\omega t + \phi)} \end{aligned}$$

Suppress $e^{j\omega t}$

$$V_m e^{j\theta} = j\omega L I_m e^{j\phi}$$

$$\therefore \mathbf{V} = j\omega L \mathbf{I}$$

Note \angle of factor $j\omega L = +90^\circ$

$$e^{j\phi} = \cos\phi + j\sin\phi$$


$$\text{phase } \angle = \phi = \tan^{-1} \left(\frac{\text{Im}}{\text{Re}} \right)$$

$$\text{if } \cos\phi = 0 \quad \sin\phi = 1$$

$$\Rightarrow \tan^{-1} \phi = \infty \therefore \phi = 90^\circ$$

~~V leads I by 90°~~

V lags I by 90°


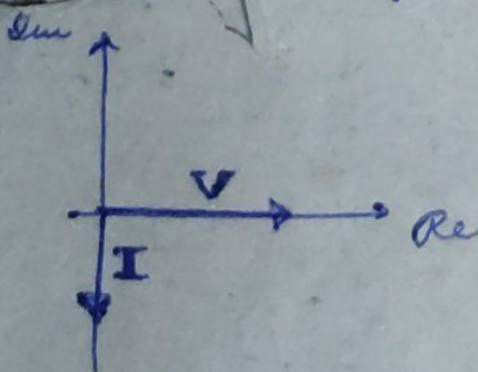


For $\omega = 100 \text{ rad/s}$,

$$\mathbf{I} = \frac{\mathbf{V}}{j\omega L} = \frac{8 \angle -50^\circ}{j 100 (4)} = -j 0.02 \angle -50^\circ$$


$$= 0.02 \angle -50^\circ - 90^\circ = 0.02 \angle -140^\circ$$
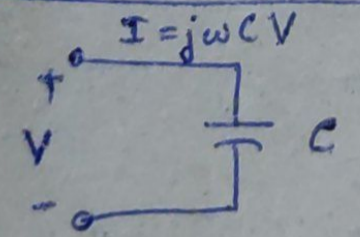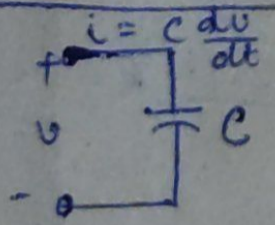
$$i(t) = 0.02 \cos(100t - 140^\circ) \text{ A}$$



$$i(t) = C \frac{dv(t)}{dt}$$

$$I = j\omega C V$$

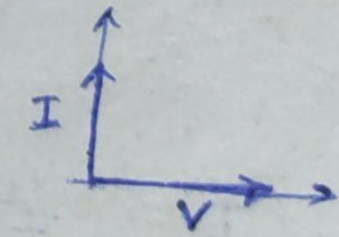

$V = 8 \angle 50^\circ \text{ V}$ then

$$I = j 100 (4) (8 \angle 50^\circ) = 3200 \angle 40^\circ \text{ A.}$$


Not practical (4-F capacitor!)

$$\text{KVL} : v_1(t) + v_2(t) + \dots + v_N(t) = 0$$

Replace by $v_i e^{j\omega t}$, suppress $e^{j\omega t}$

$$V_1 + V_2 + \dots + V_N = 0$$

why KCL holds.

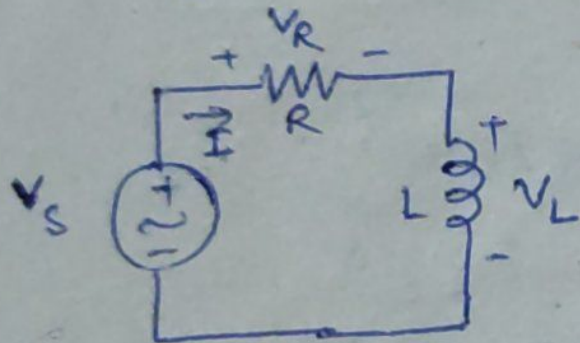

$$v_R + v_L = v_s$$

$$\therefore RI + j\omega LI = v_s$$

$$\Rightarrow I = \frac{v_s}{R + j\omega L}$$

Say source = $V_m \angle 0^\circ$

$$= \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \angle -\tan^{-1} \frac{\omega L}{R}$$

~~Impedance~~

Time domain	Freq. domain
$v = Ri$	$V = RI$
$v = L \frac{di}{dt}$	$V = j\omega L I$
$v = \frac{1}{C} \int i dt$	$V = \frac{1}{j\omega C} I$

Impedance.

$$\boxed{\frac{V}{I} = \text{Impedance } Z} \text{ (complex quantity dimension resist } \Omega \text{). } = |Z| \angle \theta = R + jX.$$


Cannot be transformed to time domain.

Inductor ; time domain : inductance L	Capacitor	C
freq. domain : impedance $j\omega L$		$\frac{1}{j\omega C}$

Series combination $Z_L + Z_C = Z_{eq} = j\omega L + \frac{1}{j\omega C} = j(\omega L - \frac{1}{\omega C})$

Parallel $Z_{eq} = Z_L \parallel Z_C = \frac{Z_L \cdot Z_C}{Z_L + Z_C}$

RLC ckt.
40 $\sin 3000t$ V

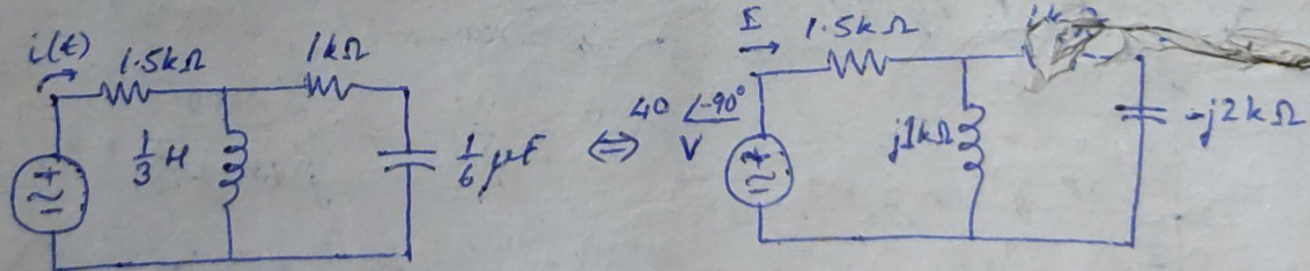

$$Z_{eq} = 1.5 + \frac{j1(1-j2)}{j1+1-j2} = 1.5 + \frac{2+j1}{1-j1}$$

$$= 1.5 + \frac{1+j3}{2} = 2 + j1.5 = 2.5 \angle 36.9^\circ \text{ k}\Omega.$$

$$I = \frac{V_s}{Z_{eq}} = \frac{40 \angle -90^\circ}{2.5 \angle 36.9^\circ} = 16 \angle -126.9^\circ \text{ mA.}$$


$$i(t) = 16 \cos(3000t - 126.9^\circ) \text{ mA.}$$

Use current division in freq. domain to obtain i_2 .

Note: Always use freq. domain or time domain ALTOGETHER.

$$\boxed{Y = \text{admittance} = \frac{1}{Z} = G + jS} \text{ (conductance) } \rightarrow \text{susceptance.}$$

Sinusoidal Steady State Response:

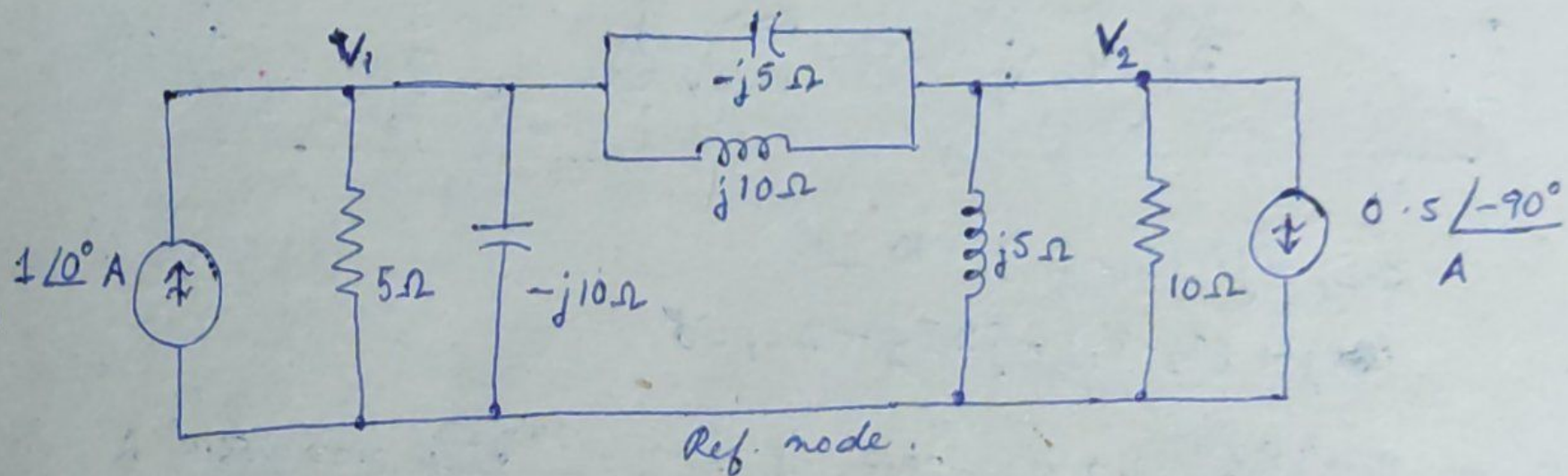

Nodal analysis

KCL at left node:
$$\frac{V_1}{5} + \frac{V_1}{-j10} + \frac{V_1 - V_2}{-j5} + \frac{V_1 - V_2}{j10} = 1 + j0$$

right node:
$$\frac{V_2 - V_1}{-j5} + \frac{V_2 - V_1}{j10} + \frac{V_2}{j5} + \frac{V_2}{10} = -(-j0.5)$$


→
$$V_1 = 1 - j2 \text{ V} \quad , \quad V_2 = -2 + j4 \text{ V}$$

$$= 2.24 \angle -63.4^\circ \text{ V} \quad = 4.47 \angle 116.6^\circ \text{ V}$$

Both sources assumed to be operating at same frequency ω [if known, then L, C can be found] → $v_1(t) = 2.24 \cos(\omega t - 63.4^\circ) \text{ V}$; $v_2(t) = 4.47 \cos(\omega t + 116.6^\circ) \text{ V}$

All assumed linear elements \therefore linearity, superposition hold.

\therefore Redraw as

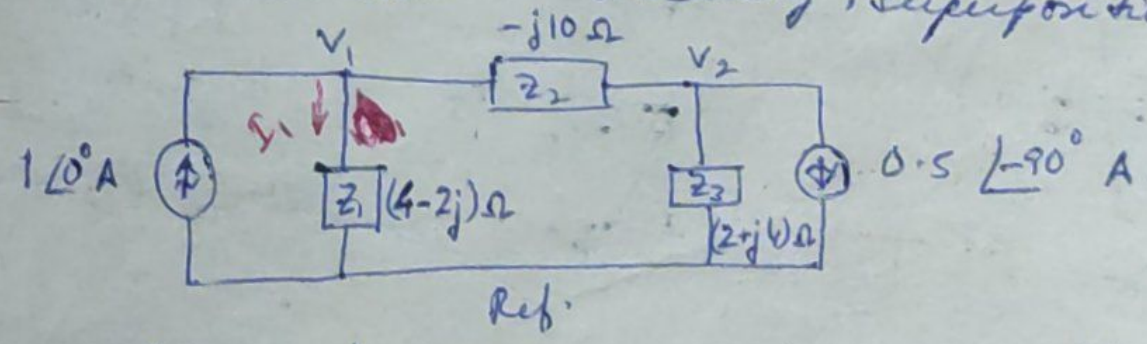

Superposition

$$V_{1L} \text{ (due to left source)} = 1\angle 0^\circ \cdot (4-j2) \cdot \frac{2-j10+j4}{4-2j-j10+2+j4} V = 2-j2 V$$

$$V_{1R} = (-0.5\angle -90^\circ) \cdot (4-j2) \cdot \frac{2+j4}{4-2j-j10+2+j4} = -1$$

$$V_1 = V_{1L} + V_{1R} = 1-j2V$$

Say Th. equivalent for $-j10\Omega$ impedance.

$$V_{oc} \text{ (left +ve)} = [1\angle 0^\circ (4-2j) - (-0.5\angle -90^\circ)(2+j4)] V = 6-j3 V$$




$$Z_{th} = Z_1 + Z_3 = (6+j2)\Omega$$

$$I_{12} = \frac{6-j3}{Z_{th} + Z_c} = (0.6+j0.3) A \quad (\text{from 1 to 2})$$

$$\therefore I_1 = I_{SL} - I_{12} = 0.4-j0.3 \Rightarrow V_1 = I_1 Z_1 = 1-j2 V$$

we can use Norton's or even source transformations.

$$10 \cos 10^3 t \text{ V}$$

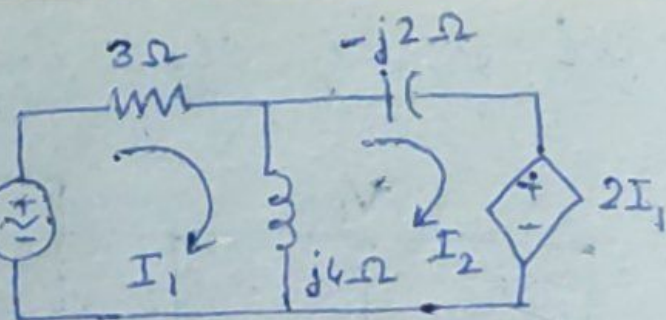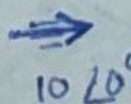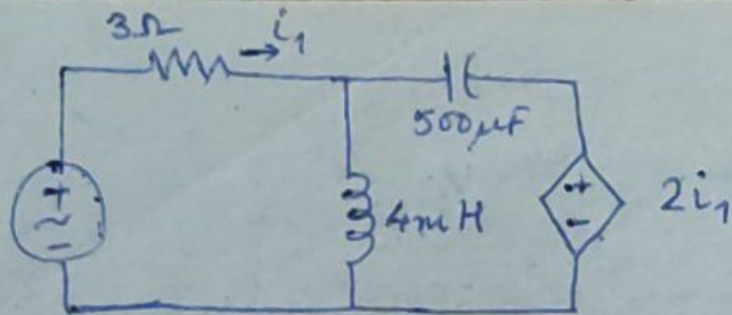

Mesh Analysis

$$3I_1 + j4(I_1 - I_2) \stackrel{!}{=} 10 \angle 0^\circ$$





$$j4(I_2 - I_1) - j2I_2 + 2I_1 = 0$$

$$I_1 = \frac{14 + j8}{13} \text{ A} = 1.24 \angle 29.7^\circ \text{ A} ; I_2 = \frac{20 + j30}{13} \text{ A} = 2.77 \angle 56.3^\circ \text{ A}$$

$$\therefore i_1(t) = 1.24 \cos(10^3 t + 29.7^\circ) \text{ A} ; i_2(t) = 2.77 \cos(10^3 t + 56.3^\circ) \text{ A}$$

Note: Same techniques applicable for any complex frequency in general.

Phasor diagrams:

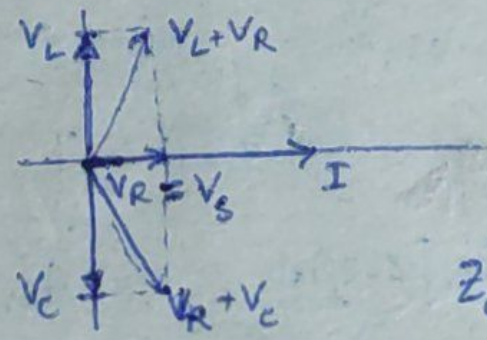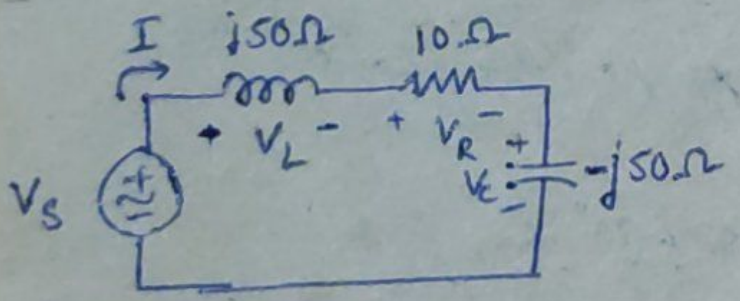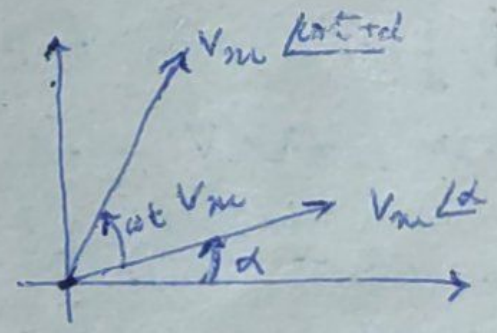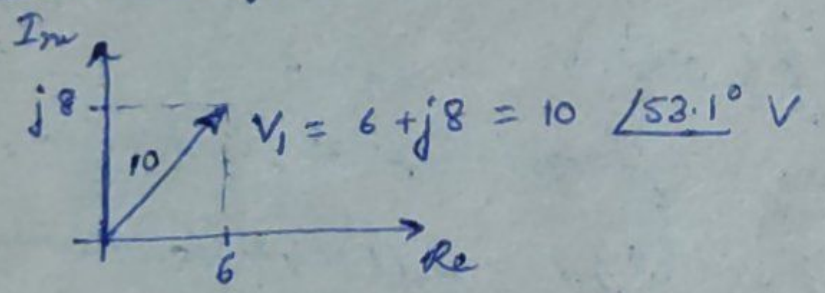



I & V on same plot magnitudes diff.

$Z_C = -Z_L$ Resonant cond.

Add & Subtraction: vector rules.

Mul. & div: add & sub. \angle , change amplitudes.

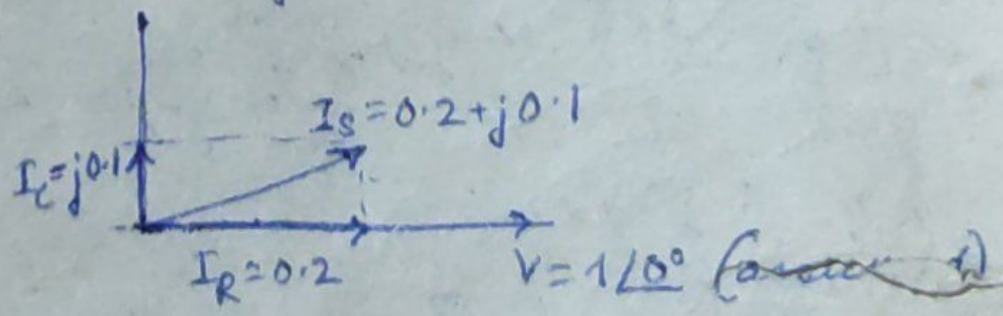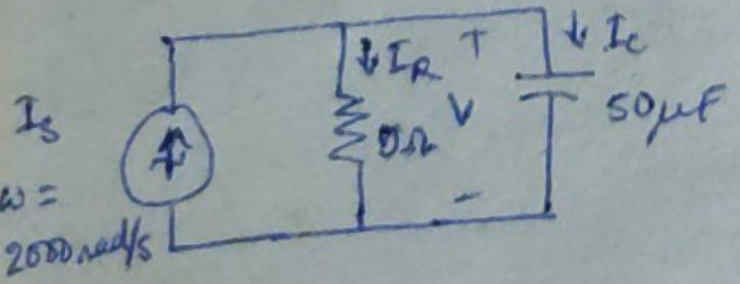$j\omega C = j \cdot 0.1 \text{ V}, \frac{1}{R} = 0.2 \text{ V}$



Even if I_s known, yet same technique, then scale suitably.



Response as fn. of ω :

1. Consider series RL ckt.

$$\therefore I = \frac{V_s}{R + j\omega L} \quad \therefore Y = \frac{1}{R + j\omega L}$$

$$\therefore |Y| = \frac{1}{\sqrt{R^2 + \omega^2 L^2}}$$
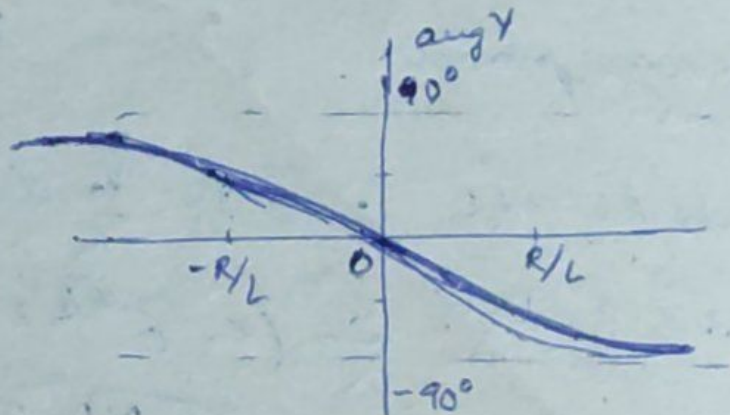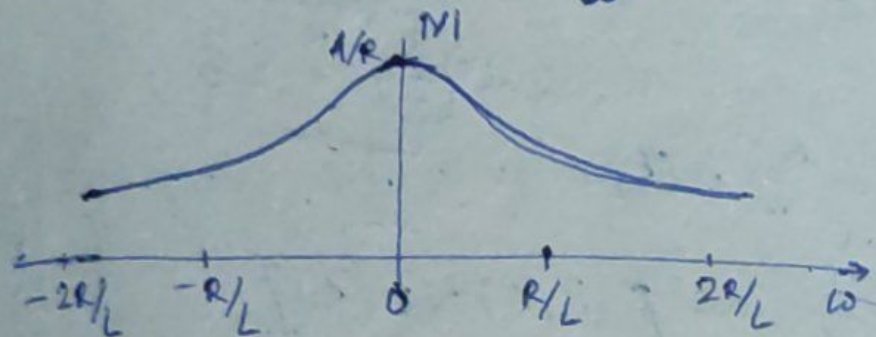
$$\text{ang. } Y = -\tan^{-1} \frac{\omega L}{R}$$



$$\omega = +100 \text{ rad/s} \Rightarrow v(t) = 50 \cos(\omega t + 30^\circ)$$

$$v(t) = 50 \cos(-100t + 30^\circ)$$

$$\text{at } \omega = \pm R/L = \pm 1/\tau \rightarrow |Y| = 0.707 |Y|_{\text{max}}, \text{ ang } Y = 45^\circ$$

↓
∴ Half power frequency.

avg power = 0.5 max. power.

$$\rightarrow \therefore \text{For same } V, I = \frac{1}{\sqrt{2}} I_{\text{max}}$$

avg. power =
 $(0.707)^2 P_{\text{max}}$
 $= 0.5 P_{\text{max}}$

only due to R