

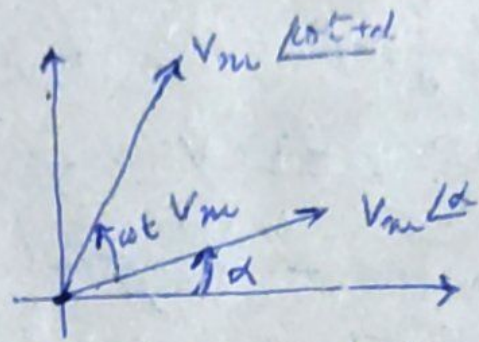
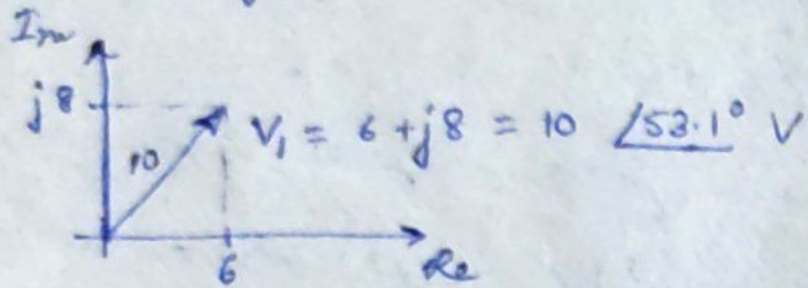


Phasor diagrams:

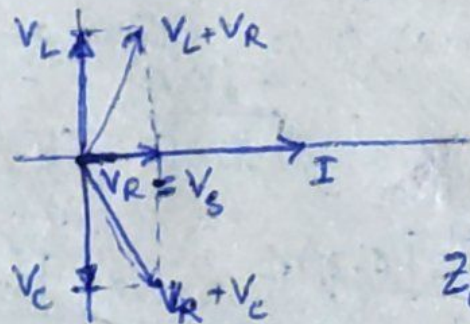

For diff. ωt , rotate anticlockwise.

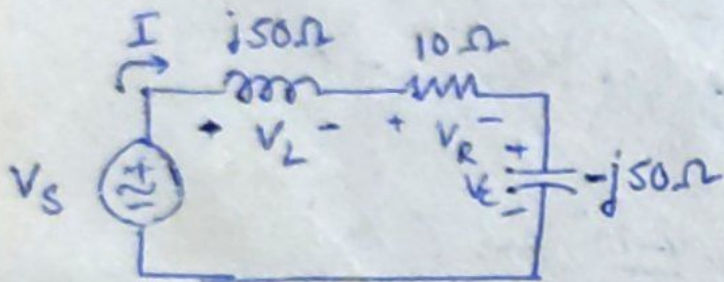



I & V on same plot
magnitudes diff.

$Z_C = -Z_L$ Resonant condn.

Addn & Subtraction: vector rules

Mul. & div: add & sub. L, change amplitudes.
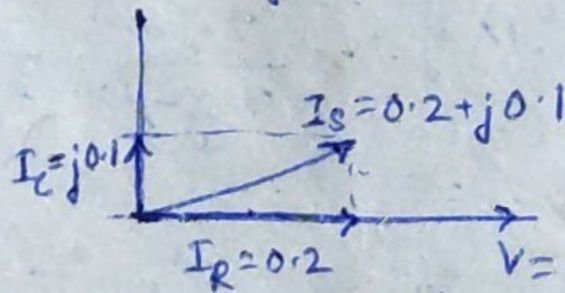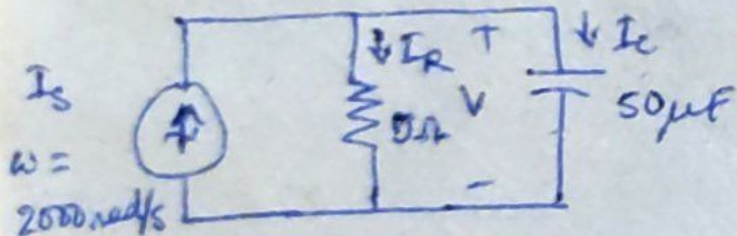
$$j\omega C = j \cdot 0.1 \text{ V}; \quad \frac{1}{R} = 0.2 \text{ V}$$



$V = 1 \angle 0^\circ$ (assumed)

Even if I_s known, yet same technique, then scale suitably.



Response as fn. of ω :

3. Consider series RL ckt.

$$\therefore I = \frac{V_s}{R + j\omega L} \quad \therefore Y = \frac{1}{R + j\omega L}$$

$$\therefore |Y| = \frac{1}{\sqrt{R^2 + \omega^2 L^2}}$$
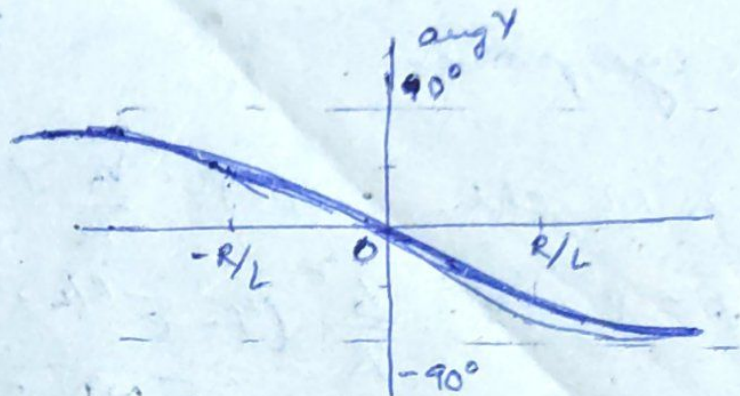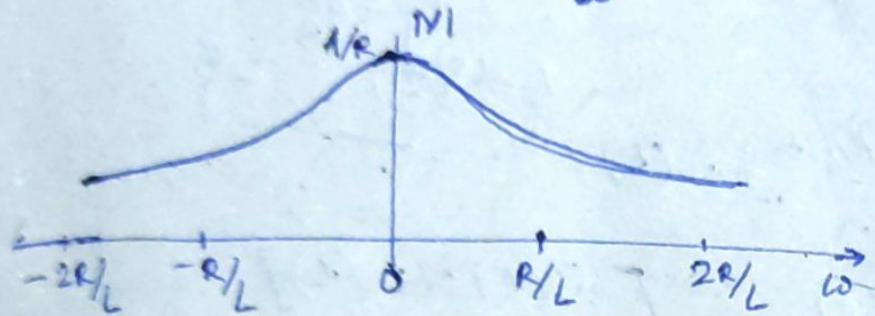
$$\text{ang. } Y = -\tan^{-1} \frac{\omega L}{R}$$



$$\omega = 100 \text{ rad/s} \Rightarrow v(t) = 50 \cos(\omega t + 30^\circ)$$

$$v(t) = 50 \cos(-100t + 30^\circ)$$



$$\text{at } \omega = \pm R/L = \pm 1/\tau \rightarrow |Y| = 0.707 |Y|_{\text{max}}, \quad \text{ang } Y = 45^\circ$$

↓
 ∴ Half power frequency. → ∴ For same V , $I = \frac{1}{\sqrt{2}} I_{\text{max}}$
 avg power = 0.5 max. power.


avg. power =
 $(0.707)^2 P_{\text{max}} = 0.5 P_{\text{max}}$

only due to R

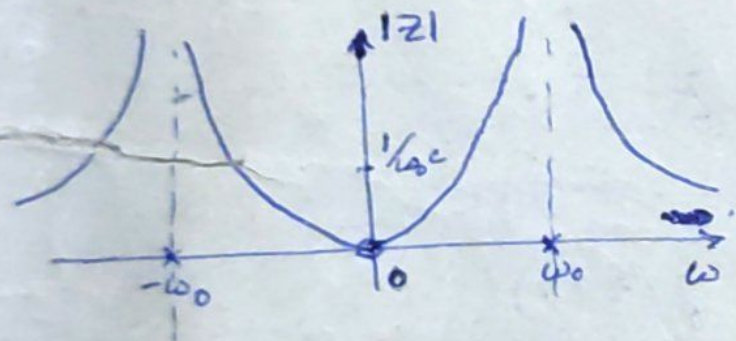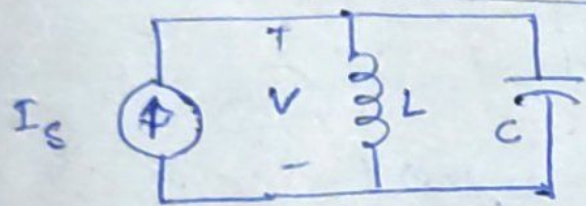2. Parallel LC ckt, driven by sinusoidal source:


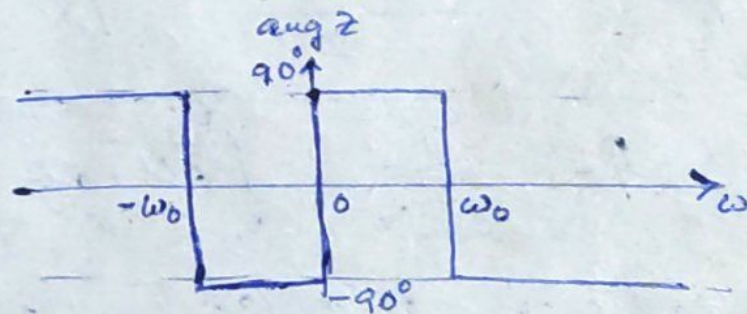
$$V = I_s \cdot \frac{(j\omega L) \cdot (1/j\omega c)}{j\omega L - j(1/\omega c)}$$



$$Z = \frac{L/c}{j(\omega L - 1/\omega c)} = -j/c \cdot \frac{\omega}{\omega^2 - 1/Lc}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{Critical frequencies}$$

at which responses
 0 or ∞
 \downarrow zero (o) \rightarrow poles (x)

$$\therefore |Z| = \frac{1}{c} \frac{|\omega|}{|(\omega - \omega_0)(\omega + \omega_0)|}$$


note: $\omega = \pm \omega_0$ is a zero

Power:

Instantaneous power (req. to be limited else distortion in speakers \rightarrow audio systems)

used to calculate
average power.

$$p = v i$$

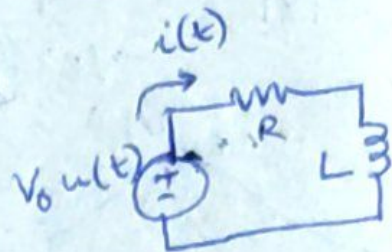

Say series RL ckt. $\therefore i(t) = \frac{V_0}{R} (1 - e^{-R/L t}) u(t)$.

supplied $p = v i = \frac{V_0^2}{R} (1 - e^{-R/L t}) u(t)$. $[u^2(t) = u(t)]$

$$p = p_R + p_L$$



$$i^2 R = p_R$$

$$L \frac{di}{dt} = p_L$$

$$+ \frac{V_0}{R} e^{-R/L t} u(t), i_L = p_L$$

$$\therefore p_L = \frac{V_0^2}{R} e^{-R/L t} (1 - e^{-R/L t})$$

Let $v(t) = V_m \cos \omega t$

$\therefore i(t) = I_m \cos(\omega t + \phi)$

$$I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}}$$

$$\phi = -\tan^{-1} \frac{\omega L}{R}$$

$\therefore p = v i = V_m I_m \cos(\omega t + \phi) \cdot \cos \omega t$

$$= \frac{V_m I_m}{2} [\cos \phi + \cos(2\omega t + \phi)]$$

supplied by source

\therefore Avg. power = $\frac{V_m I_m \cos \phi}{2}$ $[2^{\text{nd}}$ term has avg. 0]


Avg. power :
$$P = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} p(t) dt.$$

For a periodic fn. of period T i.e. $f(t) = f(t+T)$

$$P = \frac{1}{T} \int_{t_2}^{t_2+T} p dt = \frac{1}{nT} \int_{t_2}^{t_2+nT} p dt \quad n=1,2,3,\dots$$

$$\stackrel{n \rightarrow \infty}{=} \lim_{n \rightarrow \infty} \frac{1}{nT} \int_{-nT/2}^{nT/2} p dt = \lim_{\ell \rightarrow \infty} \frac{1}{\ell} \int_{-\ell/2}^{\ell/2} p dt$$

Ex. Sawtooth waveform:

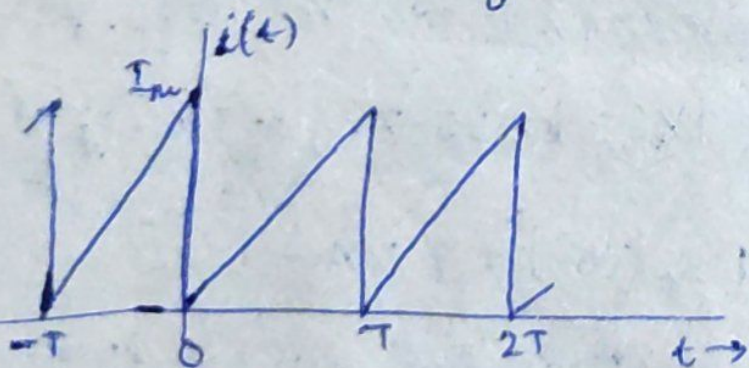

$$i(t) = \begin{cases} \frac{I_m}{T} t & 0 < t \leq T \\ \frac{I_m}{T} (t-T) & T < t \leq 2T \\ \vdots & \vdots \end{cases}$$

So, avg. power delivered to $R \Omega$ resistor

$$p(t) = i^2 R = \begin{cases} \frac{1}{T^2} I_m^2 R t^2 & 0 < t \leq T \\ \frac{1}{T^2} I_m^2 (t-T)^2 R & T < t \leq 2T \\ \vdots & \vdots \end{cases}$$

$$\therefore P = \frac{1}{T} \int_0^T \frac{I_m^2 R}{T^2} t^2 dt = \frac{1}{3} I_m^2 R$$

General expression:

$$v(t) = V_m \cos(\omega t + \theta) \quad i(t) = I_m \cos(\omega t + \phi)$$

$$p(t) = V_m I_m \cos(\omega t + \theta) \cos(\omega t + \phi) \\ = \frac{1}{2} V_m I_m [\cos(\theta - \phi) + \cos(2\omega t + \theta + \phi)]$$

Note: period of v & $i = T$, period of $p = \frac{1}{2}T$

$$\text{Avg. power } p = \frac{1}{2} V_m I_m \cos(\theta - \phi)$$

— Sense of diff. immaterial
 $\therefore \cos(\theta) = \cos(-\theta)$

$$v(t) = 4 \cos \frac{\pi t}{6} \text{ V} \quad \therefore \underline{V} = 4 \angle 0^\circ \text{ V across } \underline{Z} = 2 \angle 60^\circ \Omega$$

$$\therefore \underline{I} = 2 \angle -60^\circ \text{ A}, \quad P = \frac{1}{2} 4 \cdot 2 \cos 60^\circ = 2 \text{ W}$$

$$i(t) = 2 \cos\left(\frac{\pi t}{6} - 60^\circ\right) \quad p(t) = 8 \cos \frac{\pi t}{6} \cdot \cos\left(\frac{\pi t}{6} - 60^\circ\right) \quad \left[\begin{array}{l} \cos A \cos B \\ = \frac{\cos(A+B) + \cos(A-B)}{2} \end{array} \right] \\ = 2 + 4 \cos\left(\frac{\pi t}{3} - 60^\circ\right)$$

Note: P_R (pure resistor) = $\frac{1}{2} V_m I_m = \frac{1}{2} I_m^2 R, \frac{V_m^2}{2R}$

V_m : voltage across resistor, I_m : current through R


Avg. power of a purely reactive device = 0 $[\cos(\theta - \phi) = \cos 90^\circ = 0]$

Ex. 1. $Z_L = (8 - j11) \Omega$ $I = 5 \angle 20^\circ \text{ A}$ $\therefore P = \frac{1}{2} (5^2) 8 = 100 \text{ W}$.

\therefore no power can be absorbed by $-j11 \Omega$.

say $I = (2 + j5) \text{ A}$ then $|I|^2 = 2^2 + 5^2 = 29$.

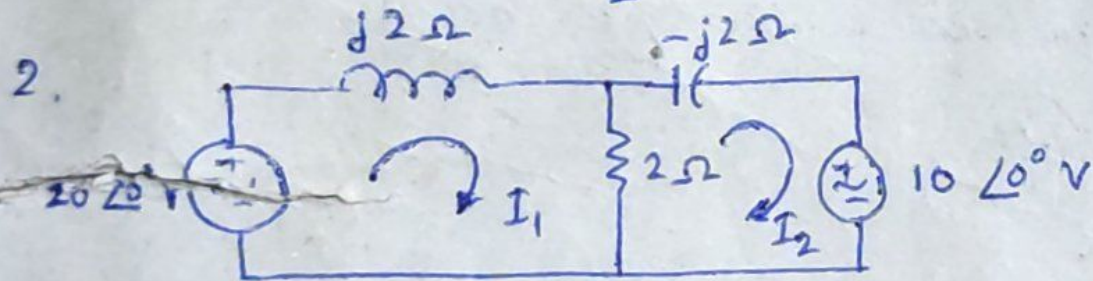$\therefore P = \frac{1}{2} \cdot 29 \cdot 8 = 116 \text{ W}$.



$\underline{I}_1 = 5 - j10 = 11.18 \angle -63.45^\circ$

$\underline{I}_2 = 5 - j5 = 7.07 \angle -45^\circ$

$\underline{I}_{2\Omega} = \underline{I}_1 - \underline{I}_2 = -j5 = 5 \angle -90^\circ$

$\therefore I_m = 5$ $P_R = \frac{1}{2} I_m^2 R = \frac{1}{2} 5^2 \cdot 2 = 25 \text{ W}$.

$P_{\text{left}} = -\frac{1}{2} (20) (11.18) \cos(0^\circ + 63.45^\circ) = -50 \text{ W}$

$P_{\text{right}} = \frac{1}{2} (10) (7.07) \cos(0^\circ + 45^\circ) = 25 \text{ W}$.

Maximum power transfer theorem: For a Thevenin source V_s , impedance $Z_{th} = R_{th} + jX_{th}$ connected to load $Z_L = R_L + jX_L$,

Avg. power is maximum when $R_L = R_{th}$, $X_L = -X_{th}$ i.e. $Z_L = Z_{th}^*$.

Some nonperiodic fns.:

$$i(t) = \sin t + \sin \pi t \rightarrow (\text{ratio of periods} \rightarrow \text{irrational})$$

* Note: $i(t) = \sin t + \sin 3.14 t$ is periodic

$$\boxed{2\pi n = \frac{2\pi m}{3.14}} \text{ is solvable } T = 1000 \text{ s.}$$

delivered to 1Ω resistor
 $p = i^2 R = 1t$
 $\tau \rightarrow \infty$

$$\frac{1}{\tau} \int_{-\tau/2}^{\tau/2} (\sin^2 t + \sin^2 \pi t + 2 \sin t \sin \pi t) dt$$

(cos A - cos B)

$$\left(\frac{1}{2} - \frac{1}{2} \cos 2t\right) \quad \left(\frac{1}{2} - \frac{1}{2} \cos 2\pi t\right)$$

$$\text{avg. } P = \frac{1}{2} + \frac{1}{2} + 0 = 1 \text{ W.}$$

Thus $i(t) = I_{m1} \cos \omega_1 t + \dots + I_{mN} \cos \omega_N t$


$$P = \frac{1}{2} (I_{m1}^2 + I_{m2}^2 + \dots + I_{mN}^2) R \text{ delivered to resistance } R.$$

* So when $\omega_1 \neq \omega_2 \neq \omega_3 \dots \neq \omega_N$, superposition holds for power.

$$i_1 = 2 \cos 10t - 3 \cos 20t \text{ A} \rightarrow 26 \text{ W to } 4\Omega \text{ resistor}$$

$$\text{while } i_2 = 2 \cos 10t - 3 \cos 10t \text{ A} \rightarrow 2 \text{ W avg. power to } 4\Omega \text{ resistor.}$$

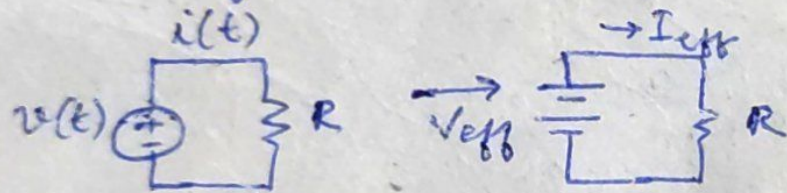Effective values of current and voltage; measure of effectiveness of a (voltage) source in delivering power to a resistive load.



Resistor receives same average power

I_{eff} of any periodic current is equal to the value of the direct current which, flowing through an R -ohm resistor, delivers same power to the resistor as does the periodic current.

$$\therefore P = I_{\text{eff}}^2 R = \frac{1}{T} \int_0^T i^2 R dt$$

$$\Rightarrow I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} \rightarrow \text{rms.}$$

~ by for V_{eff} .

For sinusoidal waveform, $i(t) = I_m \cos(\omega t + \phi)$ $T = \frac{2\pi}{\omega}$

$I_{\text{eff}} = I_m / \sqrt{2}$. \rightarrow real qty. independent of phase angle

$\therefore i(t) = \sqrt{2} \cos(\omega t + \phi) \text{ A} \rightarrow I_{\text{eff}} = 1 \text{ A} \rightarrow$ same power delivered to resistive load.

For sawtooth waveform, $I_{\text{eff}} = I_m / \sqrt{3}$.

$$\therefore P = \frac{1}{2} I_m^2 R$$

avg. power delivered to $R \Omega$ resistor by sinusoidal current.

$$= I_{\text{eff}}^2 R$$

$$* = V_{\text{eff}} \cdot I_{\text{eff}} \cos(\theta - \phi)$$

$$= \frac{V_{\text{eff}}^2}{R}$$

Note: V & I may be represented as $V_m \angle \phi$ or $V_{\text{eff}} \angle \phi$ — reqd. to check.
 waveform composed of a

For a sum of a no. of sinusoids of diff. frequencies (periodic or nonperiodic)

$$P = \frac{1}{2} (I_{m1}^2 + I_{m2}^2 + \dots + I_{mN}^2) R$$

$$= (I_{\text{eff}1}^2 + I_{\text{eff}2}^2 + \dots + I_{\text{eff}N}^2) R$$

$$\therefore I_{\text{eff}} = \sqrt{\sum I_{i\text{eff}}^2}$$

Ex. Say sinus. current of 5A rms at 60Hz. flows thru a 2Ω resistor
Avg. power of 50W absorbed ($=5^2 \times 2$). 2nd current of 3A rms
at 120Hz. absorbed power $= 50 + 3^2 \cdot 2 = 68\text{W}$

But if 3A rms at 60Hz., then $3 < P < 128\text{W}$ depending on
phase. $[(5-3)^2 \cdot 2 \text{ to } (5+3)^2 \cdot 2]$

$$I_{\text{eff}} = \sqrt{I_{1\text{eff}}^2 + I_{2\text{eff}}^2} = 5.83\text{A} \text{ (1st case) else bet. 2 to 8 A.}$$

Apparent power : due to electric power industry : efficiency of energy transfer related to cost of elec. energy.

Customer provides load ~~of~~ ^{results} \rightarrow in poor transmission efficiency.
 \rightarrow greater price for each kWh of elec. energy he actually receives & uses.

$$v(t) = V_m \cos(\omega t + \theta) \quad i(t) = I_m \cos(\omega t + \phi)$$

v leads i by $\cos(\theta - \phi)$

$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi) = V_{\text{eff}} I_{\text{eff}} \cos(\theta - \phi)$$

For dc applied voltage & currents, $P = V_{\text{eff}} I_{\text{eff}} = V \cdot I$

Absorbed power is 'apparently' $V_{\text{eff}} I_{\text{eff}} = P_{\text{apparent}}$

$$\text{Power factor } PF = \frac{\text{avg. power}}{\text{apparent power}} = \frac{P}{V_{\text{eff}} I_{\text{eff}}} = \cos(\theta - \phi) \text{ for sine waves.}$$

Note : Purely resistive & $X_L = X_C$ loads, $PF = 1$.


Purely reactive $PF = 0 \rightarrow$ worst case.

$PF \rightarrow$ leading or lagging in terms of phase of current wrt. voltage.

$\therefore X_L \rightarrow$ voltage leads current, PF lagging.

Ex

60 $\angle 0^\circ$ V
rms

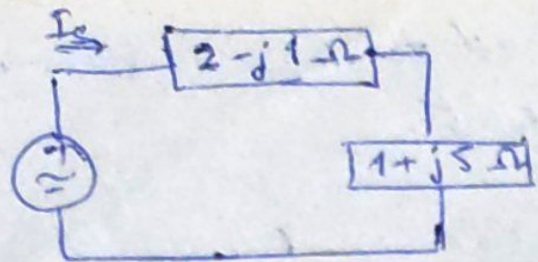

$$I_s = \frac{60}{3+j4} \text{ A} = 12 \angle -53.1^\circ \text{ A rms.}$$

Source supplies apparent power

$$60(12) = 720 \text{ V.A}$$

Avg. power : $720 \cos(0 + 53.1^\circ) = 432 \text{ W}$

[$0-\phi$ or $\phi-0$
→ no difference]

Avg. power received by $(2-j1) \Omega = 12^2 \cdot 2 \text{ W} = 288 \text{ W}$

$(1+j5) \Omega = 12^2 \cdot 1 \text{ W} = 144 \text{ W.}$

PF of combined loads = $\frac{P}{V_{\text{eff}} I_{\text{eff}}} = \frac{432}{720} = 0.6.$

$Z_{\text{eq}} = 3+j4 = 5 \angle 53.1^\circ \Omega \therefore \text{PF} = \cos 53.1^\circ = 0.6.$

Combined load inductive \therefore lagging PF.

Ex. Practical importance:

Generator produces 200V rms at 60Hz, max. power of 1kW.

\therefore rms current of 5A deliverable to load.

But if load req. 1kW at lagging PF = 0.5 connected to generator

then $200 \cdot I_{\text{eff}} \cdot 0.5 = 1000 \Rightarrow I_{\text{eff}} = 10\text{A}$ reqd.

ex Avg. power of 11kW at unity PF and 220V rms. $R_{\text{lines}} = 0.2\Omega$.

$\therefore \frac{50}{220} \frac{11000}{220}$ A rms current flows in load and in lines \therefore loss of $50^2 \times 0.2$
 $= 500\text{W}$.

\therefore Reqd. to generate 11.5kW to send 11kW to customer.

Say req. 11kW at PF \angle of 60° lagging \therefore 100A forced \therefore loss $= 100^2 \times 0.2$
 $= 2\text{kW} \therefore$ 13kW to be generated.

Complex power:

$$P = V_{\text{eff}} I_{\text{eff}} \cdot \text{Re} [e^{j(\theta - \phi)}] = \text{Re} [V_{\text{eff}} I_{\text{eff}} e^{j(\theta - \phi)}]$$

$$= \text{Re} [\vec{V}_{\text{eff}} \vec{I}_{\text{eff}}^*]$$


$$\vec{V}_{\text{eff}} = V_{\text{eff}} \angle \theta, \quad \vec{I}_{\text{eff}} = I_{\text{eff}} \angle \phi$$

$$\text{or} = \text{Re} [\underline{\vec{V}}_{\text{eff}} \underline{\vec{I}}_{\text{eff}}^*]$$


Complex power $\vec{S} = \vec{V}_{\text{eff}} \cdot \vec{I}_{\text{eff}}^* = P + jQ \rightarrow$ real power + reactive power

Apparent power = $|\vec{S}|$ units var (voltampere reactive)

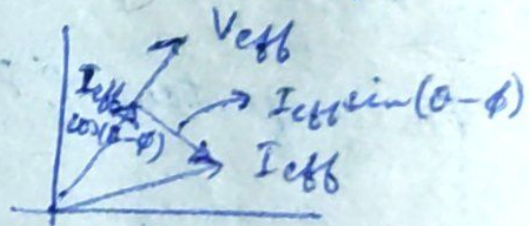$Q = V_{\text{eff}} I_{\text{eff}} \sin(\theta - \phi) \rightarrow$ quadrature power


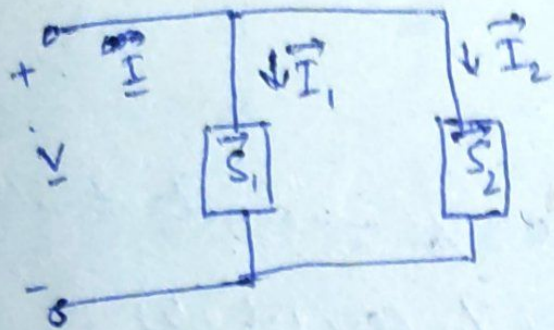
$$\vec{S} = \vec{V} \vec{I}^* = \vec{V} (\vec{I}_1 + \vec{I}_2)^* = \vec{V} (\vec{I}_1^* + \vec{I}_2^*)$$



Industrial consumer operating

~~50~~ 50 kW induction motor at lagging PF 0.8.

connect $S_2 = ?$ to raise PF to 0.95 lagging.

by adding purely reactive load [cost effective].

\vec{V} same $\therefore \vec{S}_2 \parallel \vec{S}_1$.

$$V = 230 \angle 0^\circ \text{ V rms.}$$

$$* \underline{S}_1(0.8) = 50 \frac{1}{\cos^{-1}(0.8)} \text{ kVA (real part of } \underline{S}_1 = \frac{P_1}{\cos \theta}$$

$$\therefore \underline{S}_1 = 50 + j 37.5 \text{ kVA.}$$

$$\text{to achieve PF } 0.95, \quad \underline{S} = \frac{50}{0.95} \frac{1}{\cos^{-1}(0.95)} = 50 + j 16.43 \text{ kVA.}$$

$$\therefore \underline{S}_2 = -j 21.07 \text{ kVA [Complex power drawn by corrective load]}$$

$$\underline{I}_2^* = \frac{\underline{S}_2}{V} = \frac{-j 21070}{230} = -j 91.6 \text{ A.}$$

$$\therefore \underline{I}_2 = j 91.6 \text{ A.}$$

$$\therefore \underline{Z}_2 = \frac{V}{\underline{I}_2} = \frac{230}{j 91.6} \Omega = -j 2.51 \Omega \text{ (Capacitive load)}$$

At 60 Hz operating freq., 1056 μF capacitor reqd.

* ~~✓~~

$$50 = \operatorname{Re} \underline{S}_1$$

$$= |\underline{S}_1| \cdot \cos(\theta - \phi)$$

$$y = |\underline{S}_1| \cdot \sin(\theta - \phi)$$

$$= |\underline{S}_1| \cdot \sin(\cos^{-1} 0.8)$$

$$= \frac{50}{0.8} \cdot \sin(\cos^{-1} 0.8)$$

$$\underline{S}_1 = \frac{50}{0.8} \cdot \cos(\cos^{-1} 0.8) + j \frac{50}{0.8} \sin \cos^{-1}(0.8)$$

$$= \frac{50}{0.8} \angle \cos^{-1}(0.8)$$