

Complex frequency:

Damped sinusoid: $v(t) = V_m e^{\sigma t} \cos(\omega t + \theta)$

Sp. cases: $\sigma = 0, \omega = 0$ ~~sinusoid~~ $v(t) = V_m \cos \theta = V_0$ — constant voltage

$\sigma = 0$, general sinusoid $v(t) = V_m \cos(\omega t + \theta)$

$\omega = 0$, exponential voltage $v(t) = V_m e^{\sigma t} \cos \theta = V_0 e^{\sigma t}$

Any fn. may be written in general as

$$\underline{f(t)} = \underline{K} e^{\underline{s}t} \quad \underline{s} = \text{complex frequency} = \sigma + j\omega$$

$$\therefore \cos(\omega t + \theta) \Rightarrow \frac{1}{2} (e^{j(\omega t + \theta)} + e^{-j(\omega t + \theta)})$$

$$\text{so } v(t) = V_m \cos(\omega t + \theta) = \underline{K}_1 e^{s_1 t} + \underline{K}_2 e^{s_2 t} = \left(\frac{1}{2} V_m e^{j\theta}\right) e^{j\omega t} + \left(\frac{1}{2} V_m e^{-j\theta}\right) e^{-j\omega t}$$

$$\left[\text{s.t. } K_2 = K_1^*, s_2 = s_1^* \right] = K_1 e^{s_1 t} + (K_1 e^{s_1 t})^*$$

\sim by for $v(t) = V_m e^{\sigma t} \cos(\omega t + \theta)$ \rightarrow

So, voltages

$$v(t) = 100$$

$$v(t) = 5e^{-2t}$$

$$v(t) = 2 \sin 500t$$

$$v(t) = 4e^{-3t} \sin(6t + 10^\circ)$$

associated
complex frequencies

$$s = 0$$

$$s = -2 + j0$$

$$s_{1,2} = \pm j500$$

$$s_{1,2} = -3 \pm j6$$


(complex conjugate
understood for a physical system)

Damped sinusoid forcing fn.:

$$v(t) = V_m e^{\sigma t} \cos(\omega t + \theta) = \text{Re} (V_m e^{\sigma t} e^{j(\omega t + \theta)})$$

$$= \text{Re} (V_m e^{j\theta} e^{st})$$

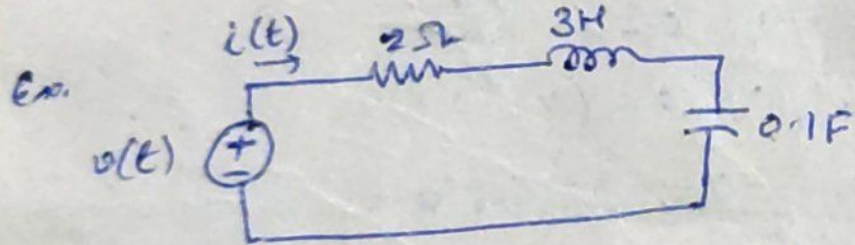\therefore Omit Re and suppress e^{st} as in sinusoidal ss response.



$$v(t) = 60 e^{-2t} \cos(4t + 10^\circ).$$

$$\text{Req. } i(t) = I_m e^{-2t} \cos(4t + \phi).$$

$$\text{Now } v(t) = \text{Re} (60 e^{j10^\circ} e^{(-2+j4)t})$$

$$= \text{Re} (\underline{V} e^{st})$$

$$\therefore \underline{V} = 60 \angle 10^\circ \quad s = -2 + j4$$

$$\text{Dropping Re, } 60 \angle 10^\circ e^{st} = 2 \underline{I} e^{st} + 3s \underline{I} e^{st} + \frac{1}{0.1s} \underline{I} e^{st}$$

$$\therefore 60 \angle 10^\circ = 2 \underline{I} + 3s \underline{I} + \frac{10}{s} \underline{I}$$

$$\therefore \underline{I} = \frac{60 \angle 10^\circ}{2 + 3s + 10/s}$$


Substitute for $s = -2 + j4$ and solve.

$$\underline{I} = 5.37 \angle -106.6^\circ$$

$$\therefore i(t) = 5.37 e^{-2t} \cos(4t - 106.6^\circ).$$

	R	L	C
$\underline{Z}(s)$	R	sL	1/sC
$\underline{Y}(s)$	1/R	1/sL	sC

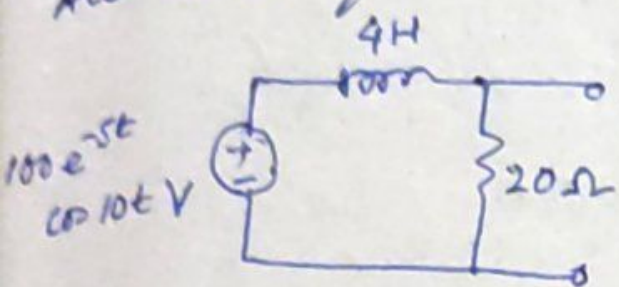All techniques as discussed in ss analysis usable.



$$s = -5 + j10 \quad \underline{V}_s = 100 \angle 0^\circ$$

$$\underline{Z}_L(s) = 4(-5 + j10) = -20 + j40$$


$$\underline{Z}_R(s) = 20$$

$$\therefore \underline{Z}_{th} = \underline{Z}_L \parallel \underline{Z}_R = 20 + j10$$



$$\underline{V}_{oc} = 100 \angle 0^\circ \cdot \frac{20}{20 - 20 + j40} = -j50$$

Then for some specific load, desired response found in freq. domain then transformed back to time domain.





Complex frequency plane:

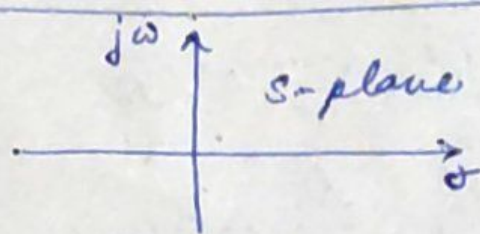

Responses:

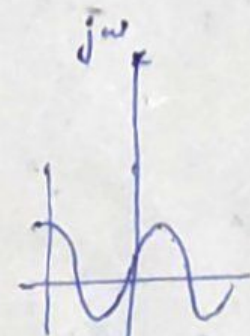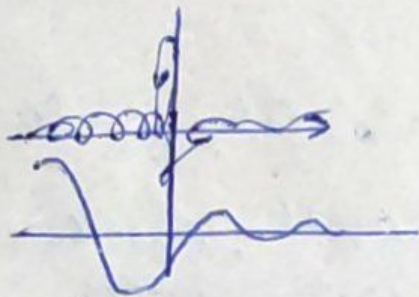

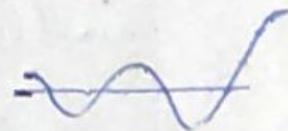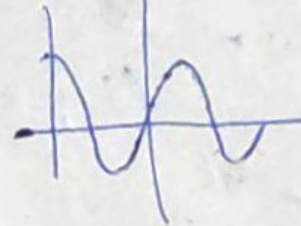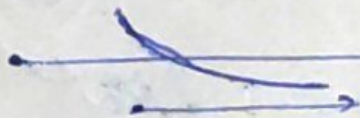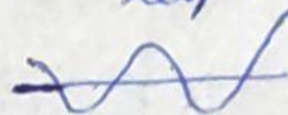
s-plane and corres. time domain responses



$$Y(s) = \frac{1}{s+3} \quad \therefore |Y(s)| = \frac{1}{\sqrt{(\sigma+3)^2 + \omega^2}}$$

So for particular ω , σ -response may be obtained & vice versa.

Natural response and the s-plane

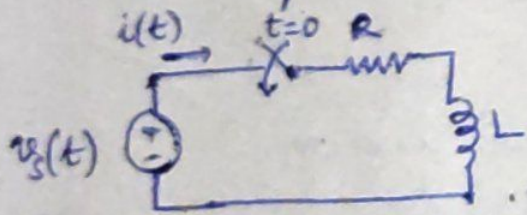

$$i(t) = i_x(t) + i_f(t)$$

$$\underline{I}(s) = \frac{\underline{V}_s}{R + sL}$$

Transfer function $\underline{H}(s) = \frac{\underline{I}(s)}{\underline{V}_s} = \frac{1}{L(R/L + s)}$

Natural response when $\underline{V}_s = 0$ but only when operating at a pole of $\underline{H}(s)$ is it possible to have nonzero $\underline{I}(s)$.

So say $\underline{I}(s) = A$ at $\underline{s} = -R/L + j0 \longrightarrow$ Natural response.

$$\therefore i_x(t) = \operatorname{Re} \left(A e^{-Rt/L} \right) = A e^{-Rt/L}$$


$$\therefore i(t) = i_x(t) + i_f(t) \dots$$

General network: say $\frac{V_2(s)}{V_s} = \underline{H}(s) = k \frac{(s-s_1)(s-s_3)\dots}{(s-s_2)(s-s_4)\dots}$

So poles at s_2, s_4, \dots $\therefore v_{2H}(t) = A_2 e^{s_2 t} + A_4 e^{s_4 t} + \dots$


Important: location of virtual source for evaluating natural response.

Say

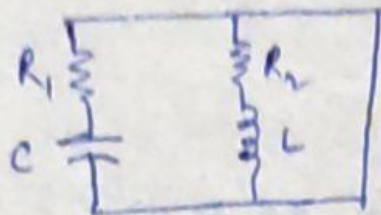

\therefore virtual source on R, C limb would yield $\underline{H}(s) = 0$ since it produces no s.s. i in R, L limb.

Ex. 1.

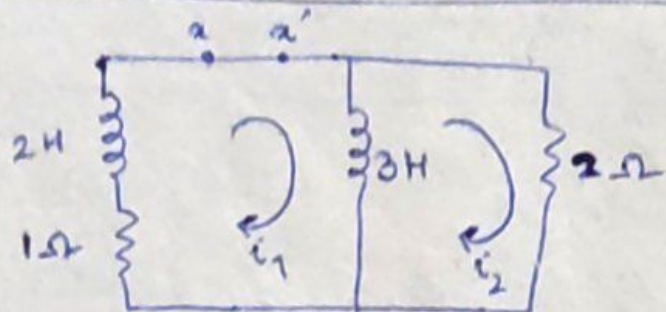

$$i_1(0) = i_2(0) = 11 \text{ A.}$$

$$\underline{H}(s) = \underline{I}_1(s) / \underline{V}_s$$

$$\underline{I}_1(s) = \frac{\underline{V}_s}{2s + 1 + \frac{6s}{3s + 2}} = \frac{3s + 2}{6s^2 + 13s + 2} \underline{V}_s$$

$$\therefore \underline{H}(s) = \frac{\frac{1}{2} (s + 2/3)}{(s + 2)(s + 1/6)}$$

$$\therefore i_1(t) = A e^{-2t} + B e^{-t/6} \dots \textcircled{1}$$

$$i_2(t) = 8 e^{-2t} + 3 e^{-t/6} \quad \therefore \frac{di_1}{dt} = -2A e^{-2t}$$

$$i_2(t) = 12 e^{-2t} - e^{-t/6} \quad -\frac{1}{6} B e^{-t/6} \dots \textcircled{1'}$$


Then using i.c. as earlier.

KVL @ perimeter $1i_1 + 2\frac{di_1}{dt} + 2i_2 = 0 \dots \textcircled{2}$

Ex 2. Solve for $\frac{di_1}{dt} \Big|_{t=0} = -2A - \frac{1}{6}B = -\frac{22+11}{2} \dots \textcircled{2'}$

Ex 2. Solve for $\frac{dy}{dt} \Big|_{t=0} = -2A - \frac{1}{6}B = -\frac{2L+1}{2} \dots$

$v(t) = v_f(t) + v_n(t)$

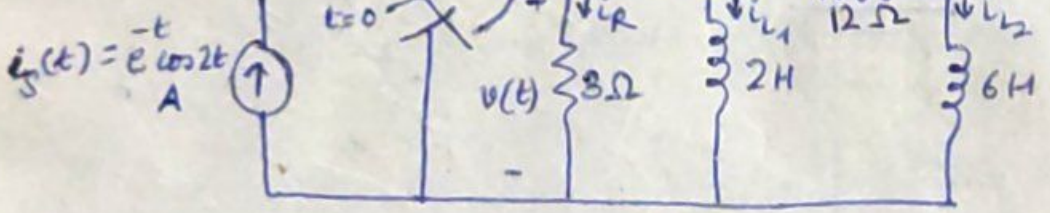

$$\underline{V}(s) = \frac{\underline{I}_s}{\frac{1}{3} + \frac{1}{2s} + \frac{1}{6s+12}}$$

$$\therefore \underline{H}(s) = \frac{\underline{V}(s)}{\underline{I}_s} = \frac{3s(s+2)}{(s+1)(s+3)}$$

$$\therefore v_n(t) = Ae^{-t} + Be^{-3t}$$

To find forced response $\underline{I}_s(s) = 1$ at $s = -1 + j2$ multiplied by impedance at $s = -1 + j2$

$$\Rightarrow \underline{V}(s) = \underline{I}_s(s) \underline{H}(s) \Big|_{s=-1+j2} = 1.875\sqrt{2} \angle 45^\circ = 3 \frac{(-1+j2)(1+j2)}{j2(2+j2)}$$

$$\therefore v_f(t) = 1.875\sqrt{2} e^{-t} \cos(2t + 45^\circ)$$

Then use i.c.s. $i_{L1}(0) = i_{L2}(0) = 0$. $\therefore 1$ A through 3Ω resistor.

$$\therefore v(0) = 3 = A + B + \frac{1.875\sqrt{2}}{\sqrt{2}}$$

$$v(t) = 3i_R = 3i_s - 3i_{L1} - 3i_{L2} \quad \therefore \frac{dv}{dt} = 3 \frac{di_s}{dt} - 3 \frac{di_{L1}}{dt} - 3 \frac{di_{L2}}{dt}$$

at $t=0$, $RHS = 3(-3) - 3 \cdot \left(\frac{3}{2}\right) - 3 \cdot \left(\frac{1}{2}\right) = -9 = -5.625 - A - 3B$

$$\therefore A = 0, B = 1.125$$

$$\therefore v(t) = 1.125 e^{-3t} + 1.875\sqrt{2} e^{-t} \cos(2t + 45^\circ)$$

