

Laplace transform techniques:

$$\underline{V}(s) = \int_{-\infty}^{\infty} e^{-st} v(t) dt = \int_{0^-}^{\infty} e^{-st} v(t) dt$$

One sided Laplace trans.
since most fns. do not
exist forever in time,
so consider that initiated
at $t=0$.

$t=0^-$ taken to take care of initial conditions.

$$v(t) = \frac{1}{2\pi j} \int_{\sigma_0 - j\infty}^{\sigma_0 + j\infty} e^{st} \underline{V}(s) ds$$

$$\therefore \mathcal{L}[v(t)] = \underline{V}(s) \quad \text{or} \quad v(t) = \mathcal{L}^{-1}[\underline{V}(s)]$$

Some basic formulae.

$$\mathcal{L}[u(t)] = \frac{1}{s}$$

$$\mathcal{L}[\delta(t)] = 1$$

$$\mathcal{L}[t u(t)] = \frac{1}{s^2}$$

$$\mathcal{L}[e^{-\alpha t} u(t)] = \frac{1}{s + \alpha}$$

$$\mathcal{L}[\sin \omega t u(t)] = \frac{\omega}{s^2 + \omega^2}$$

$$\mathcal{L}[\cos \omega t u(t)] = \frac{s}{s^2 + \omega^2}$$

$$\mathcal{L}[f_1(t) + f_2(t)] = \underline{F}_1(s) + \underline{F}_2(s)$$

$$\mathcal{L}[k v(t)] = k \underline{V}(s)$$

$$\mathcal{L}\left[\frac{dv}{dt}\right] = s \underline{V}(s) - v(0^-)$$

$$\mathcal{L}\left[\frac{d^2v}{dt^2}\right] = s^2 \underline{V}(s) - s v'(0^-) - v''(0^-)$$

$$\mathcal{L}\left[\int_{0^-}^t v(x) dx\right] = \frac{\underline{V}(s)}{s}$$

$$\mathcal{L}\left[\int_{-\infty}^t v(x) dx\right] = \frac{1}{s} \underline{V}(s) + \frac{1}{s} \int_{-\infty}^{0^-} v(x) dx$$

$$\mathcal{L}[f(t-a)u(t-a)] = e^{-as} \underline{F}(s) \quad a \geq 0$$

Convolution: $\int_{-\infty}^{\infty} f_1(\lambda) f_2(t-\lambda) d\lambda = f_1(t) * f_2(t)$

Let $\underline{F}_1(s) = \mathcal{L}[f_1(t)]$, $\underline{F}_2(s) = \mathcal{L}[f_2(t)]$

then $\mathcal{L}[f_1(t) * f_2(t)] = \underline{F}_1(s) \cdot \underline{F}_2(s)$

$$\mathcal{L}\left[\frac{t^{n-1}}{(n-1)!} e^{-\alpha t} u(t), n=1,2,\dots\right] = \frac{1}{(s+\alpha)^n}$$

$$\mathcal{L}\left[\frac{1}{\beta-\alpha} (e^{-\alpha t} - e^{-\beta t}) u(t)\right] = \frac{1}{(s+\alpha)(s+\beta)}$$

$$\mathcal{L}[e^{-\alpha t} \sin \omega t u(t)] = \frac{\omega}{(s+\alpha)^2 + \omega^2}$$

$$\mathcal{L}[e^{-\alpha t} \cos(\omega t) u(t)] = \frac{(s+\alpha)}{(s+\alpha)^2 + \omega^2}$$

$$\begin{aligned} \mathcal{L}[\sin(\omega t + \theta) u(t)] &= \mathcal{L}[(\sin \omega t \cos \theta + \cos \omega t \sin \theta) u(t)] \\ &= \frac{\omega \cos \theta + s \sin \theta}{s^2 + \omega^2} \end{aligned}$$

$$\mathcal{L}[f(t) e^{-\alpha t}] = \underline{F}(s+\alpha)$$

$$\mathcal{L}[-t f(t)] = \frac{d\underline{F}(s)}{ds}$$

$$\mathcal{L}\left[\frac{f(t)}{t}\right] = \int_s^{\infty} \underline{F}(s) ds$$

$$\mathcal{L}[f(at)] = \frac{1}{a} \underline{F}\left(\frac{s}{a}\right)$$

$$\mathcal{L}[f(0^+)] = \lim_{s \rightarrow \infty} s \underline{F}(s)$$

$$\mathcal{L}[f(\infty)] = \lim_{s \rightarrow 0^+} s \underline{F}(s)$$

(provided all poles of $\underline{F}(s)$ in LHP)


* For a periodic fn.

$$f(t) = f(t+nT) \quad n=1,2,\dots$$

$$\text{Say } \underline{F}_1(s) = \int_0^T f(t) e^{-st} dt$$

$$\mathcal{L}[f(t)] = \frac{1}{1-e^{-Ts}} \underline{F}_1(s)$$

Ex. 1.

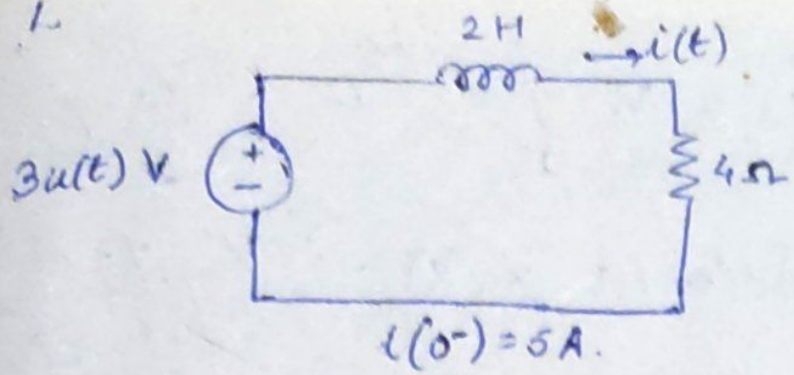

$$\therefore 2 \frac{di}{dt} + 4i = 3u(t)$$

Taking \mathcal{L} -transform of both sides.

$$\text{or } 2[sI(s) - i(0^-)] + 4I(s) = \frac{3}{s}$$

$$\therefore (2s + 4) I(s) = \frac{3}{s} + 10$$

$$\therefore I(s) = \frac{3}{2s(s+2)} + \frac{5}{s+2} = \frac{A}{s} + \frac{B}{s+2}$$

At $s=0$, $sI(s) = \frac{1.5}{2} + \frac{5s}{2} = A + \frac{Bs}{s+2}$

$$\therefore A = 0.75$$


At $s=-2$, $(s+2)I(s) = \frac{3}{2s} + 5 = \frac{A(s+2)}{s} + B$

$$= \frac{-3}{4} + 5 = 4.25$$

$$\therefore I(s) = \frac{0.75}{s} + \frac{4.25}{s+2}$$

$$\therefore i(t) = 0.75u(t) + 4.25e^{-2t}u(t)$$

Ex 2.

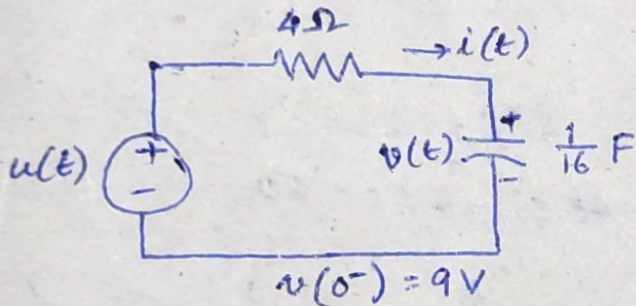

$$u(t) = 4i(t) + 16 \int_{-\infty}^t i(t) dt$$

$$= 4i(t) + v(0^-) + 16 \int_{0^-}^t i(t) dt$$

Note $\mathcal{L}[v(0^-)]$

$= \mathcal{L}[v(0^-)u(t)]$ since one-sided \mathcal{L} -transform.

Taking Laplace transform of both sides.

~~$$\frac{1}{s} = 4I(s) + \frac{9}{s} + \frac{16}{s} I(s)$$~~

$$\Rightarrow -8 = 4(s+4)I(s)$$

$$\Rightarrow I(s) = \frac{-2}{s+4}$$

$$\Rightarrow i(t) = -2e^{-4t}u(t)$$

If $v(t)$ had been desired, write nodal eqn.

$$\frac{v(t) - u(t)}{4} + \frac{1}{16} \frac{dv}{dt} = 0$$

Take Laplace.

$$\frac{V(s)}{4} - \frac{1}{4s} + \frac{1}{16} [sV(s) - v(0^-)] = 0$$

$$\Rightarrow V(s) \left[1 + \frac{s}{4} \right] = \frac{1}{s} + \frac{9}{4}$$

$$\Rightarrow V(s) = \frac{4}{s(s+4)} + \frac{9}{s+4} = \frac{1}{s} - \frac{1}{s+4} + \frac{9}{s+4} = \frac{1}{s} + \frac{8}{s+4}$$

$$\Rightarrow v(t) = u(t) + 8e^{-4t}u(t) = (1 + 8e^{-4t})u(t)$$

$$\frac{4}{s(s+4)} = \frac{A}{s} + \frac{B}{s+4}$$

$$A(s+4) + Bs = 4$$


$$\Rightarrow A+B=0$$

$$4A=4 \Rightarrow A=1 \therefore B=-1$$

check

$$\frac{1}{16} \frac{dv}{dt} = \frac{1}{16} [-32e^{-4t}] = -2e^{-4t} = \frac{-(v(t) - u(t))}{4} \therefore \text{correct.}$$

Ex 3

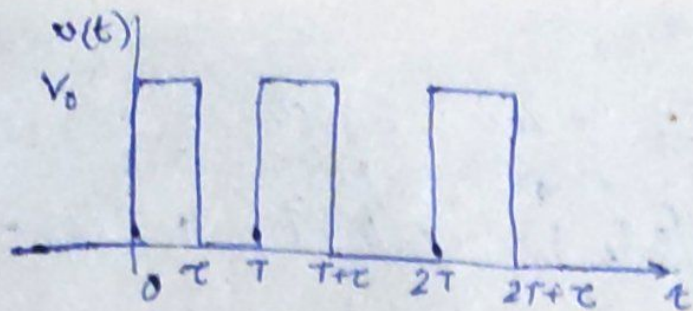

$$* \therefore \underline{v}_1(\underline{s}) = V_0 \int_0^{\tau} e^{-st} dt = \frac{V_0}{\underline{s}} (1 - e^{-\underline{s}\tau})$$


$$\therefore \mathcal{L}[v(t)] = \underline{V}(\underline{s}) = \frac{V_0}{\underline{s}} \frac{1 - e^{-\underline{s}\tau}}{1 - e^{-\underline{s}T}}$$

denominator : due to periodicity,


$e^{-\underline{s}\tau}$: due to time delay of negative eq. wave that turns off pulse.

$\frac{V_0}{\underline{s}}$: $\mathcal{L}[V_0 u(t)]$.

Ex 4

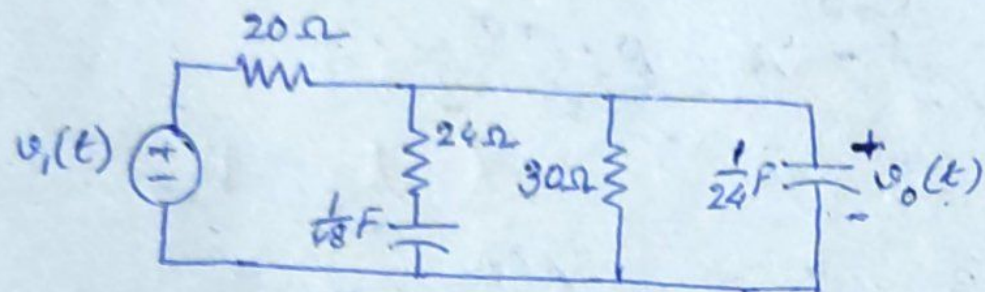

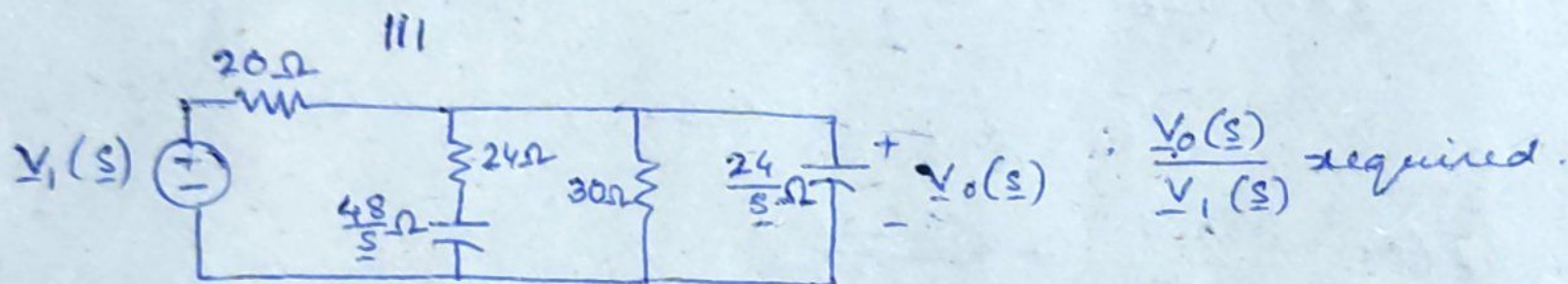Assume no initial ^{energy} storage in network.



impedance of 3 parallel branches.

$$\underline{Z}_i(s) = \frac{1}{\frac{s}{24} + \frac{1}{30} + \frac{1}{24 + 48/s}} = \frac{120(s+2)}{5s^2 + 19s + 8}$$

$$\therefore \frac{\underline{V}_0(s)}{\underline{V}_1(s)} = \frac{\underline{Z}_i(s)}{20 + \underline{Z}_i(s)} = \frac{6(s+2)}{5s^2 + 25s + 20}$$

$$\therefore \underline{H}(s) = \frac{1.2(s+2)}{(s+1)(s+4)} = \frac{A}{s+1} + \frac{B}{s+4} = \frac{0.4}{s+1} + \frac{0.8}{s+4}$$

$$\therefore h(t) = (0.4e^{-t} + 0.8e^{-4t})u(t)$$

So, for $v_i(t) = 5(t)$. $v_o(t) = R(t)$

Say $v_i(t) = 50 \cos 2t u(t)$ V.


$$\begin{aligned}\therefore \underline{V}_o(s) &= \underline{H}(s) \cdot \underline{V}_i(s) = \underline{H}(s) \cdot \mathcal{L}[50 \cos 2t u(t)] \\ &= \underline{H}(s) \frac{50s}{s^2 + 4} = \frac{12(s+2)}{(s+1)(s+4)} = \frac{50s}{s^2 + 4}\end{aligned}$$

$$= \frac{A}{s+1} + \frac{B}{s+4} + \underbrace{\frac{C}{s+j2} + \frac{D}{s-j2}}_{\frac{Cs+D}{s^2+4}}$$

$$= \frac{-4}{s+1} - \frac{8}{s+4} + \frac{12s+24}{s^2+4}$$

$$\therefore v_o(t) = (-4e^{-t} - 8e^{-4t} + 12 \cos 2t + 12 \sin 2t) u(t)$$

Ex 5

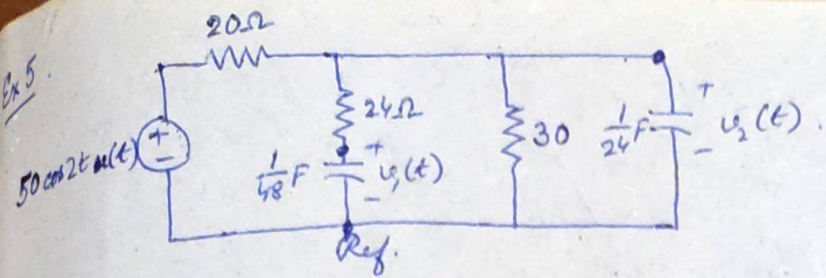

Let $v_1(0^-) = 10V$
 $v_2(0^-) = 25V$

At ①, $\frac{1}{48} \frac{dv_1}{dt} + \frac{v_1 - v_2}{24} = 0$

$\Rightarrow 2v_2 = 2v_1 + \frac{dv_1}{dt}$... ①

At ②, $\frac{1}{24} \frac{dv_2}{dt} + \frac{v_2}{30} + \frac{v_2 - v_1}{24} + \frac{v_2 - 50 \cos 2t u(t)}{20} = 0$

$\Rightarrow v_1 = \frac{dv_2}{dt} + 3v_2 - 60 \cos 2t u(t)$... ②

Eliminate v_1 and $\frac{dv_1}{dt}$ by taking derivative of ② [Note $\frac{du(t)}{dt} = \delta(t)$]

$\therefore v_1' = v_2'' + 3v_2' + 120 \sin 2t u(t) - 60 \delta(t)$... ③

Substituting ② & ③ in ①

$v_2'' + 5v_2' + 4v_2 = (120 \cos 2t - 120 \sin 2t)u(t) + 60 \delta(t)$

Taking Laplace transform

$$\left[\underline{s}^2 \underline{V}(\underline{s}) - 5v_2(0^-) - v_2'(0^-) \right] + \left[5\underline{s} \underline{V}_2(\underline{s}) - 5v_2(0^-) \right] + 4\underline{V}(\underline{s})$$

$$= \frac{120\underline{s} - 240}{\underline{s}^2 + 4} + 60$$

$\Rightarrow (\underline{s}^2 + 5\underline{s} + 4) \underline{V}(\underline{s}) = \underline{s}v_2(0^-) + v_2'(0^-) + 5v_2(0^-) + \frac{120\underline{s} - 240}{\underline{s}^2 + 4} + 60$

~~Let~~ $v_2(0^-) = 25$.

To evaluate $v_2'(0^-)$, use (2),

$$v_1(0^-) = v_2'(0^-) + 3v_2(0^-) = 0.$$

$$\Rightarrow v_2'(0^-) = -65. \quad \text{while } v_2(0^-) = 25.$$

$$\therefore V_2(s) = \frac{25s^3 + 120s^2 + 220s + 240}{(s+1)(s+4)(s^2+4)}$$

$$= \frac{A}{s+1} + \frac{B}{s+4} + \frac{Cs+D}{s^2+4}$$

$$= \frac{23/3}{s+1} + \frac{16/3}{s+4} + \frac{12s+24}{s^2+4}$$

$$\therefore v_2(t) = \left(\frac{23}{3} e^{-t} + \frac{16}{3} e^{-4t} + 12 \cos 2t + 12 \sin 2t \right) u(t).$$