

Electrical circuit: an interconnection of simple electrical devices in which there is at least one closed path in which current may flow.

Analysis: a (mathematical) study of a complex entity and the interrelationship of its parts.


All matter \rightarrow fundamental building blocks - ATOMS - e^- , protons and neutrons \rightarrow charged particles. Ref. Millman Halkias (tran. at low freq.)

Coulomb (C): Fund. unit
 Q or q : symbol — (Difference?) — TI vs. instantaneous
 \sim by $i_c, i_C, I_e, I_C \rightarrow$ different quantities. a) max., avg (dc) & rms by uppercase
 b) lowercase
 c) Avg (dc) & inst. total - uppercase subscript
 d) varying comp. from some quiescent

Current: $\frac{dq}{dt} = i$ I or i Amperes (A)

Charge transferred bet. t_0 and t : $q|_{t_0}^t = \int_{t_0}^t i dt$

Total charge transferred over all time

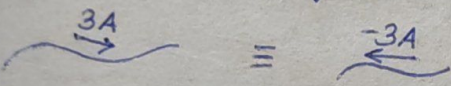


$i_1(t)$

$$\int_{t_0}^t i dt + q(t_0) = q$$

Types: dc or ac (sinusoid) or exponential or damped sinusoid.

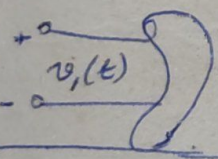Any circuit is a system composed of several elements through which i flows when v is applied across it.




Voltage v or V : Volts (V). work reqd. to move charge through element.
 $\therefore E = qv$

Let $v(t) = 100 \cos 250t$ Find a) $v(1ms)$ b) $v(8ms)$

(c) energy reqd. to move $4C$ from lower to upper terminal at $t = 4ms$
 $96.89V, -41.6V, -216J$

Power absorbed by any ckt. element in terms of voltage across it and current through it: P or p Watts (W)

$p = vi$

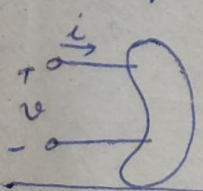

Passive sign convention: ^{power or} energy absorbed +ve


Physical device \neq mathematical model of device \rightarrow CKT. ELEMENT

General ckt. element composed of one or more than one simple ckt. element (cannot be further subdivided).

CLASSIFICATION acc. to reln. bet. i & v

- a) Independent sources: v totally independent of i or vice versa.
- b) Dependent (controlled) sources: Source v or i depends on i or v elsewhere in ckt.

Independent voltage source
(Ideal)

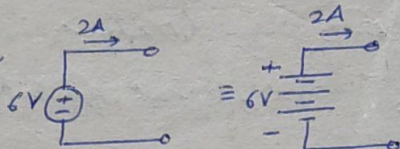

d.c. battery

For currents less than 20A or so, ord. household electrical outlet approx. an independent voltage source $v_s = 220\sqrt{2} \cos 2\pi 50t$ V.


Independent current source



used in electronic ckt.

Independent dc current source represents very closely the proton beam of a cyclotron operating at constant beam current of @ $1\mu A$

Dependent sources

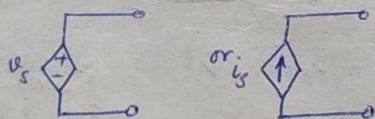


Sources: ACTIVE ELEMENTS. — capable of delivering power to some external device.

All others: PASSIVE ELEMENTS: receive power. (can store too \therefore deliver)

Electric NETWORK: interconnection of two/more simple ckt. elements.
CKT. : if at least one closed path so i can flow through.

PASSIVE ckt. elements: Resistor, inductor, capacitor and pair of mutually coupled inductors.

Power absorbed by each element:

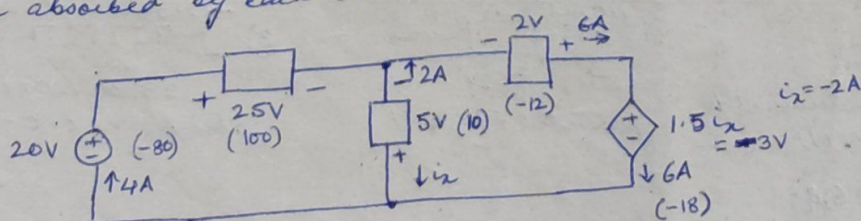

Notation summarized


Inst. total value	v_b	i_b
Resistant	V_b	I_b
Inst. value of varying component	v_b	$i_b = i_b - I_b$
Effective value of varying component	V_b	I_b
Supply voltage	V_{BB}	

Source: Hillman Hallies
Transistor at low frequencies.

Resistive circuits


Ohm's law: LINEAR resistor: voltage across many types of conducting materials is directly prop. to the current flowing through the material.

$$v = Ri$$

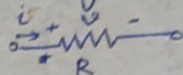

R : constant of proportionality - Resistance

unit: Ω (ohms) = $1V/A$.

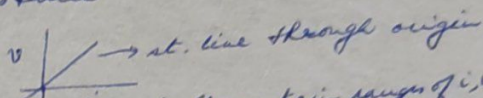

provided temp. & other environmental factors are held constant (for certain ranges of $i, v, power$) normally +ve quantity.

* (-ve resistances simulated with op. cktry.)

Actual resistors: nonlinear. - ex. zener diodes, tunnel diodes, fuses.

Absorbed power dissipated totally as heat (always +ve) - no power delivering or storing capacity. $p = vi = Ri \cdot i = i^2 R = \frac{v^2}{R}$

Wattage essential: connect 100Ω , $2W$ carbon resistor across $110V$ source - flame, smoke, breakage.

Ratio of current to voltage: $\frac{i}{v} = \frac{i}{Ri} = \frac{1}{R} = G$ (conductance)

unit: mho, \mathcal{S} or Siemen (S)

same ckt. symbol.

Absorbed power: $vi = v^2 G = \frac{i^2}{G}$

charge across resistor $\therefore i$ & v varies with time

All in terms of instantaneous values. $\therefore i$ & v varies with time in same manner.

$R = 10 \Omega$, $v = 2 \sin 100t V \Rightarrow i = \frac{v}{R} = 0.2 \sin 100t A$

power: $0.4 \sin^2 100t V \rightarrow$ diff. variation with time. (always +ve)

Short circuit: $R = 0 \Omega \rightarrow v = 0V$, i any value

Open circuit: $R = \infty \Omega \rightarrow v$ any value, $i = 0A$

a) R if $v = -8V$, $i = -5mA = 1.60k \Omega$

b) absorbed power, if $i = -5A$, $R = 2.2 \Omega = 55W$

c) i if $R = 8 \Omega$, $p_{absorbed} = 200mW = \pm 158.1mA$

d) G if $v = 2.5V$ and $i = 100mA = 40mS$

Kirchhoff's laws


Consider simple networks in which two/more simple ckt. elements are interconnected by electrical conductors (leads) with 0 resistance
 → perfectly conducting

∴ Lumped constant network.


Actual: distributed constant network.

So, ckt. leads kept small

Node: A pt. at which two or more elements have a common connection

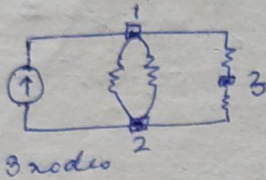

not 4

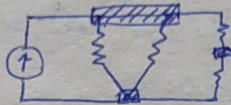

Path: Start at one node in network, through element to another node, through another element to 3rd node and so on w/o encountering a node more than once.


Closed path: if start at node & back to node through a path.
 or
 Loop

Branch: Single path in network composed of one element & nodes at either end of element. 5 branches.

Kirchhoff's Current Law (KCL)

Algebraic sum of ~~the~~ the currents entering any node is zero.

[∴ charge cannot accumulate at any node]

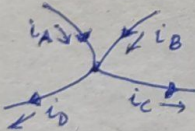

$$i_A + i_B - i_C - i_D = 0 \quad \text{currents entering a node.}$$

$$\textcircled{1} \quad \sum_{n=1}^N i_n = 0.$$


Equally valid for currents leaving the node: $-i_A - i_B + i_C + i_D = 0.$

Water: junction of several pipes → node; ^{mass} flow rate

KVL

Algebraic sum of voltages @ any closed path in a ckt. is zero.

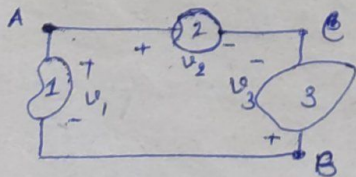[∴ Energy reqd. to move a charge from one pt. to another is independent of path taken.]




Path bet A & B

clockwise with - encountered

$$V_1 = V_2 - V_3$$

$$\text{i.e. } -V_1 + V_2 - V_3 = 0.$$
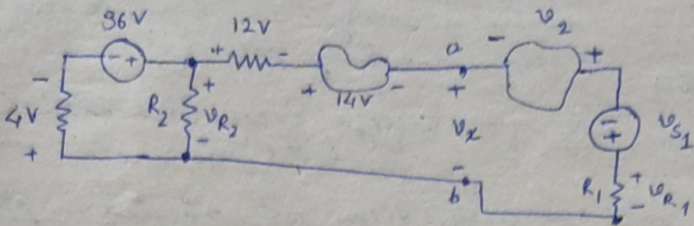
$$\sum_{n=1}^N v_n = 0. \quad (\text{Conservation of energy})$$




$$V_{R2} : 4 - 36 + V_{R2} = 0$$

$$V_{R2} = 32V$$

$$V_x : -32 + 12 + 14 + V_x = 0$$


$$V_x = 6V$$

or $4 - 36 + 12 + 14 + V_x = 0$

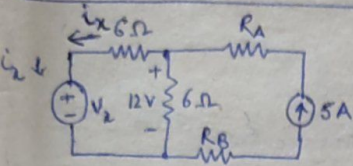


a)

Branches	6
Nodes	5
i_x	3 A
V_x	-6 V

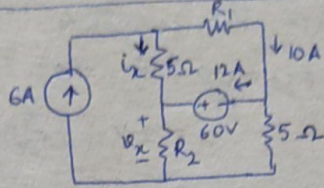

b)


Branches	6
Nodes	4
i_x	-4 A
V_x	50 V

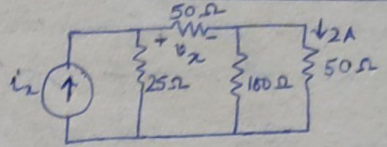

c)

Branches	5
Nodes	3
i_x	13 A
V_x	150 V

Analysis of single loop circuit:

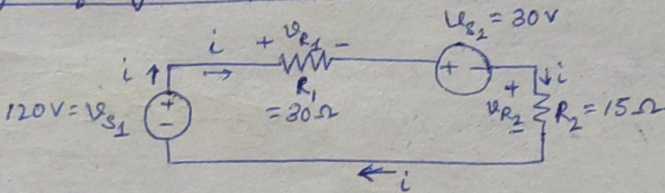

KCL: same i through whole of ckt.

All elements that carry same current are in series (not equal but same)
 $V = Ri$ assumes i enters terminal at which $+V$ ref. located $\therefore p + v$

KVL: $-V_{S1} + V_{R1} + V_{S2} + V_{R2} = 0$

$\Rightarrow -V_{S1} + R_1 i + V_{S2} + R_2 i = 0$

$i = \frac{V_{S1} - V_{S2}}{(R_1 + R_2)}$


~~original~~ $i = \frac{120 - 30}{30 + 15} \text{ A} = 2 \text{ A}$. $V_{30} = 2 \cdot 30 = 60 \text{ V}$, $V_{15} = 2 \cdot 15 = 30 \text{ V}$

$P_{120V} = 120(-2) = -240 \text{ W}$ (delivered \therefore)

$P_{30} = 30(2) = 60 \text{ W}$ and so on.


Power balance exists.

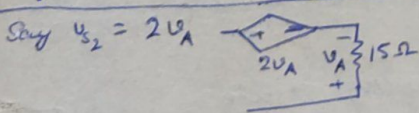If i considered in opp. direction \rightarrow check. $i_2 = -i$.




$\therefore -120 + V_{30} + 2V_A - V_A = 0$. $V_A = -15i$, $V_{30} = 30i$

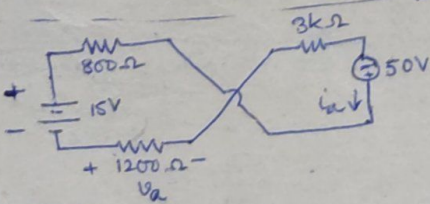$\therefore i = 8 \text{ A}$
 Dependent source.



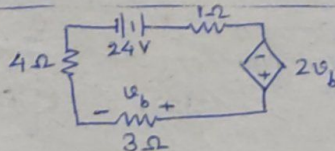$i_a = 7 \text{ mA}$, $V_x = 8.4 \text{ V}$,
 power supplied by 15V battery: -105 mW .




Power absorbed by each element.

$P_{4\Omega} = 576$ $P_{24V} = -288$, $P_{1\Omega} = 144$

$P_{2V_b} = -864$ $P_{3\Omega} = 432 \text{ W}$

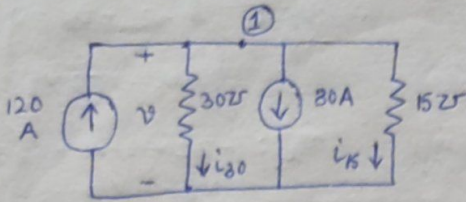Single-node-pair circuit → Companion (dual) of single loop ckt.



Assume a voltage across any element
= assign arbitrary polarity.

KVL → voltage across each branch identical.

All elements having common voltage across them are connected in parallel


Passive sign convention → select two currents.

$$\text{KCL at node 1: } -120 + i_{30} + 30 + i_{15} = 0$$

$$i_{30} = 30 \text{ V}, \quad i_{15} = 15 \text{ V}, \quad v = 2 \text{ V}, \quad i_{30} = 60 \text{ A}, \quad i_{15} = 30 \text{ A}$$

$$P_{30} = 120 \text{ W}, \quad P_{15} = 60 \text{ W}, \quad P_{120 \text{ A}} = -240 \text{ W}, \quad P_{30 \text{ A}} = 60 \text{ W}$$

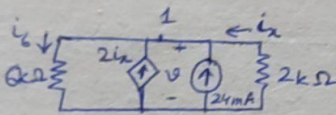~~EXACT~~ DUALS → same elements & values same, else DUALS




$$\text{Node 1 (KCL): } -i_x + 24 \times 10^{-3} = 2i_6 + i_6 = 0$$

$$i_6 = \frac{v}{6000}, \quad i_x = -\frac{v}{2000}$$

$$\frac{v}{6000} - 0.024 + \frac{3v}{2000} = 0$$


$$10v = 24 \times 6 = 144 \text{ V} \quad \therefore v = 14.4 \text{ V}; \quad i_x = -0.0072 \text{ A}$$
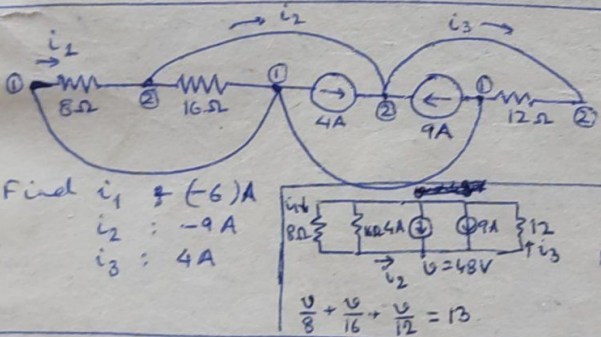
$$P_{24} = 14.4 (0.024) = 0.346 \text{ W}$$



$$\text{Find } i_1 = (-6) \text{ A} \\ i_2 = -9 \text{ A} \\ i_3 = 4 \text{ A}$$

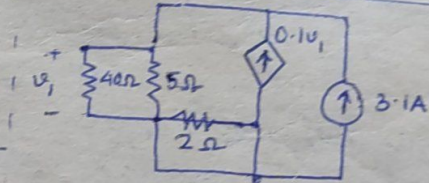
$$\frac{v}{8} + \frac{v}{16} + \frac{v}{12} = 13 \\ v = 48 \text{ V}$$



$$\text{L-R power absorbed} \\ 15.4 \text{ W}; 123 \text{ W}; 0 \text{ W}; -61.5 \text{ W}; -76.9 \text{ W}$$


Equivalent resistances:


Series combination of N resistors:

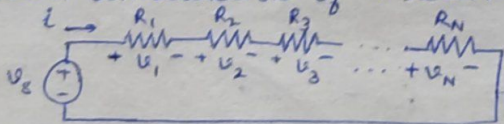

$$\text{KVL: } v_S = v_1 + v_2 + \dots + v_N = i(R_1 + R_2 + \dots + R_N) \\ R_{eq} = \sum_{i=1}^N R_i = i R_{eq}$$

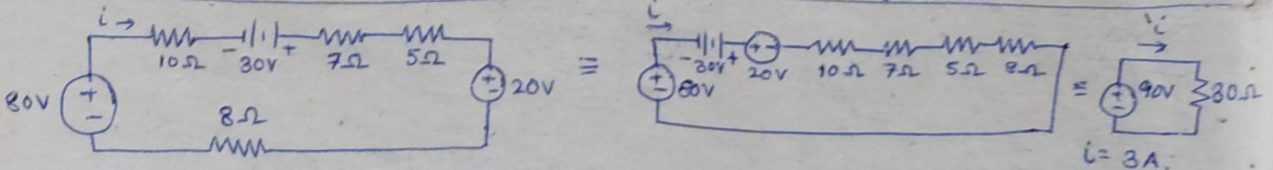1. Condu: Not specifically require i, v or p associated with indiv. resistor.
2. Order of elements not important
3. Sev. voltage sources may be replaced by eq. voltage source




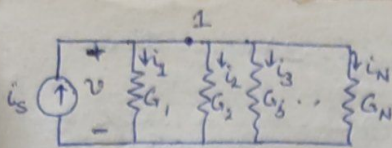

KCL at node 1: $i_s = i_1 + i_2 + i_3 + \dots + i_N$
 $= (G_1 + G_2 + \dots + G_N)v = G_{eq} \cdot v$

$\therefore G_{eq} = \sum_{i=1}^N G_i \Rightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N}$

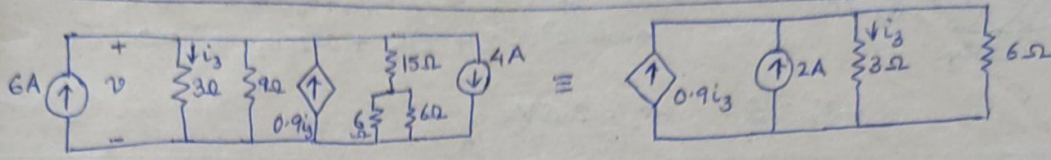For two resistors, $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$



$\therefore -0.9i_3 - 2 + i_3 + \frac{v}{6} = 0 \Rightarrow 0.1i_3 + \frac{v}{6} = 2 \Rightarrow \frac{v}{30} + \frac{v}{6} = \frac{v}{5} = 2$
 $\Rightarrow v = 10V \therefore i_3 = \frac{v}{3} = 3.33A$



$0.9i_3 = \frac{9}{10} \times \frac{10}{3} = 3A$

\therefore Power delivered = $3 \times 10W = 30W$


Power dissipated in 15 ohm resistor: $\rightarrow v = 10V$
 $i = ? \rightarrow$ power.

Parallel of two voltage sources / series of two current sources \rightarrow not physically possible. (KVL/KCL) \rightarrow only permissible when terminal voltage identical at each instant

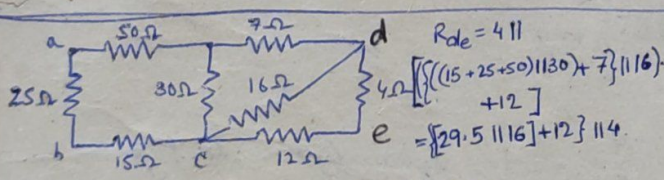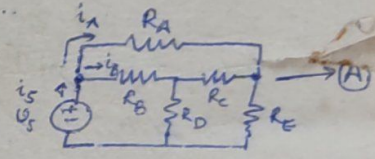Single loop \rightarrow in series as well as in parallel.
 All ckt. may not have elements in series / parallel




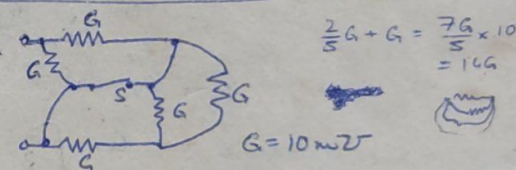$R_{ab} = 18.75 \Omega, R_{ac} = 24 \Omega, R_{bc} = 12.75 \Omega$




terminal conductance if (i) open 14mS
 (ii) closed 20mS (iii) replaced by G: 16.25mS


Voltage and current division:

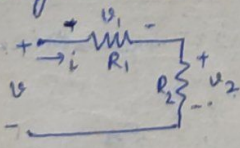

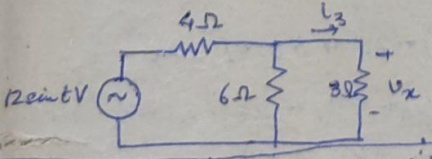$v_2 = R_2 \cdot i = R_2 \cdot \frac{v}{R_1 + R_2} = \frac{R_2}{R_1 + R_2} \cdot v$; $v_1 = \frac{R_1}{R_1 + R_2} \cdot v$
 $i = \frac{v}{\sum_{i=1}^N R_i}$ for resistances in series.



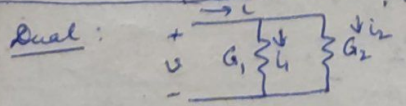$\equiv v$ (source) in series with 4 ohm resistor and 2 ohm resistor in parallel. $\therefore v_2 = \frac{2}{6} \times v = 4 \sin t V$



$i_2 = G_2 \cdot v = \frac{G_2}{G_1 + G_2} v = \frac{R_1}{R_1 + R_2} i$
 $i_1 = \frac{R_2}{R_1 + R_2} i$, $i_i = \frac{G_i}{\sum_{i=1}^N G_i} i$

$i_2 = \frac{6}{9} \cdot 4 \sin t A = \frac{8}{3} \sin t A$
 $i_3 = \frac{6}{9} \cdot i = \frac{6}{9} \cdot \frac{12}{4+2} = \frac{v}{9} = \frac{12}{9} \sin t = \frac{4}{3} \sin t A$

* Not always applicable \rightarrow say for (A) — only for || branches (same pair of nodes)