

Magnetically coupled circuits: TRANSFORMERS

$$v = L \frac{di}{dt} \quad \text{due to (i) magnetic flux produced by current } (\phi \propto i)$$


(ii) prod. of voltage by time varying magnetic field
 $(v \propto \frac{d\phi}{dt})$

Mutual inductance: same concept: current flowing in one coil establishes magnetic flux about that coil and a second coil in its vicinity and thus voltage produced in 2nd coil.

$$v_2 = M_{21} \frac{di_1}{dt}$$


M_{21} : coeff. of mutual inductance.


units: H (henry).

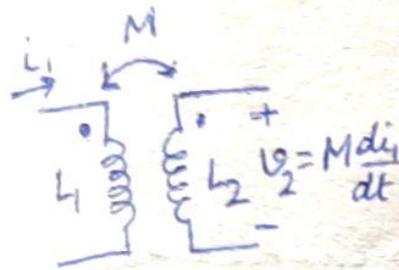

Dot convention: Current entering dotted terminal of one coil produces ~~an~~ an open ckt. voltage

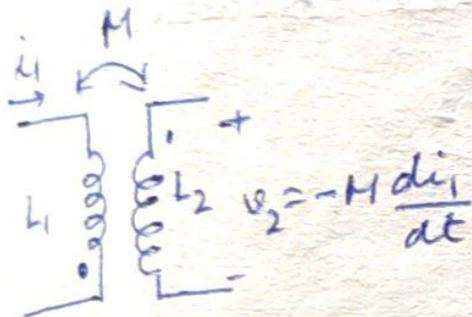bet. the terminals of the second coil which is sensed in the direction indicated by a positive voltage reference at the dotted terminal of this second coil.



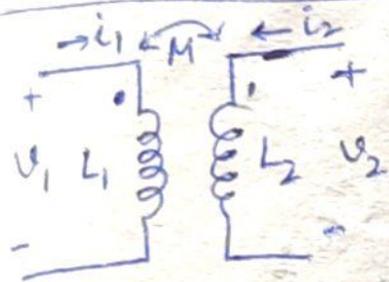


$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$\underline{v}_1 = \underline{L}_1 \underline{I}_1 + \underline{M} \underline{I}_2$$

$$v_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

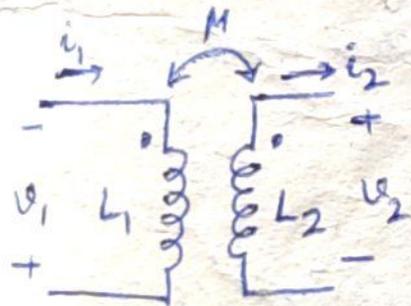
$$\underline{v}_2 = \underline{L}_2 \underline{I}_2 + \underline{M} \underline{I}_1$$



$$-v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} \Rightarrow v_1 = -L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$v_2 = -L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

Physically: At. hard core

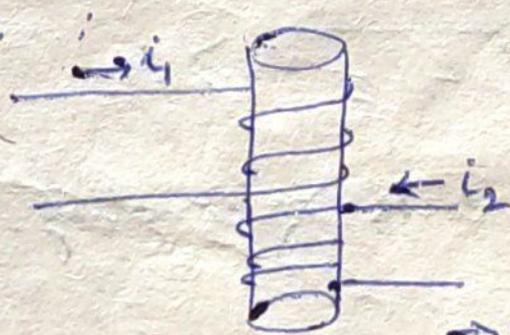


Assume i_1, i_2 +ve and \uparrow with time.
downward flux for both.

\therefore Additive fluxes.

$\Rightarrow i_1, i_2$ entering dot marked terminals

Ex. 1

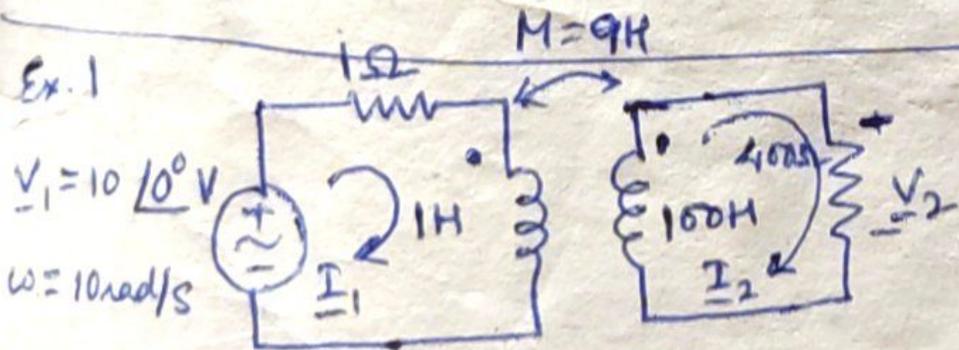

$$\underline{I}_1 (1 + j10) - j90 \underline{I}_2 = 10$$

$$\underline{I}_2 (400 + j1000) - j90 \underline{I}_1 = 0$$


$$\therefore \underline{I}_2 = 0.1724 \angle -16.7^\circ$$

$$\therefore \frac{\underline{V}_2}{\underline{V}_1} = \frac{400 (0.1724 \angle -16.7^\circ)}{10} = 6.90 \angle -16.7^\circ$$

General expression for $\underline{I}_2(\underline{s}) = \frac{9 \underline{s} \underline{V}_1}{19 \underline{s}^2 + 500 \underline{s} + 400}$

$$\therefore \frac{\underline{V}_2}{\underline{V}_1} = 189.5 \frac{\underline{s}}{(\underline{s} + 0.826)(\underline{s} + 25.5)}$$

Ex 2

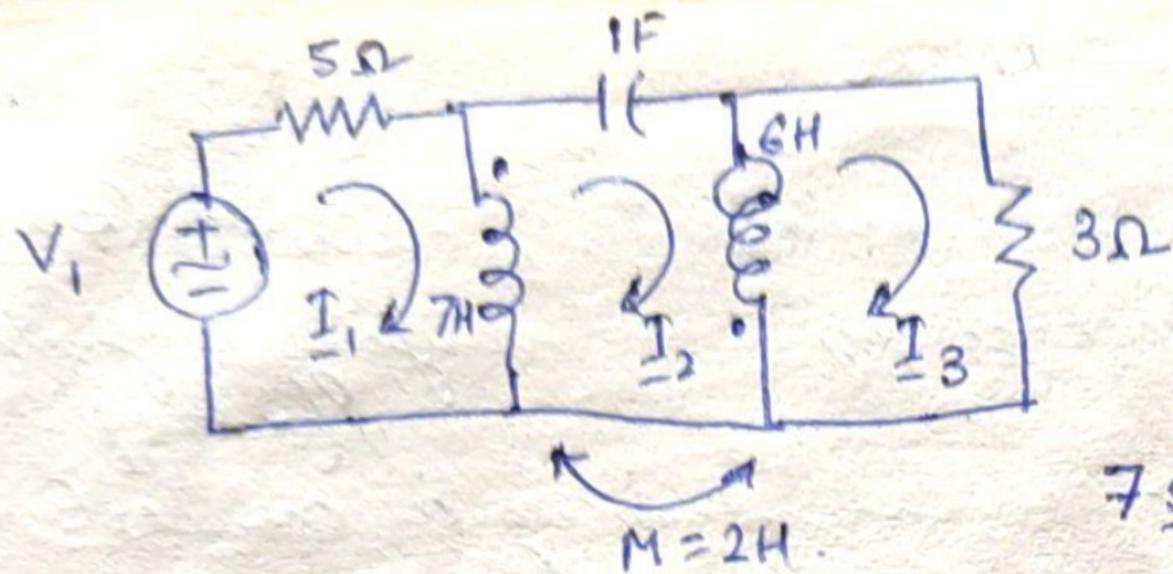

~~(5 Ohm) I_1~~

$$5 \underline{I}_1 + 7 \underline{S} (\underline{I}_1 - \underline{I}_2) + 2 \underline{S} (\underline{I}_3 - \underline{I}_2) = \underline{V}_1$$


$$7 \underline{S} (\underline{I}_2 - \underline{I}_1) + \frac{1}{\underline{S}} \underline{I}_2 + 6 \underline{S} (\underline{I}_2 - \underline{I}_3)$$

$$+ 2 \underline{S} (\underline{I}_2 - \underline{I}_3) + 2 \underline{S} (\underline{I}_2 - \underline{I}_1) = 0$$

* (current leaving dot terminals)

$$6 \underline{S} (\underline{I}_3 - \underline{I}_2) + 3 \underline{I}_3 + 2 \underline{S} (\underline{I}_1 - \underline{I}_2) = 0$$

Energy considerations:

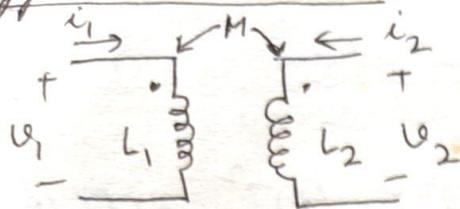

1. Let all i & v be zero.

\therefore 0 initial energy storage

2. o.c. at terminal pair

$i_1 \rightarrow 0$ to I_1 in time $t = t_1$

\therefore power entering network from left

instantaneously $\therefore v_1 i_1 = L_1 \frac{di_1}{dt} \cdot i_1$

from it. $\therefore v_2 i_2 = 0 \quad \therefore i_2 = 0$.

Energy stored w/i the network when $i_1 = I_1$

$$\int_0^{t_1} v_1 i_1 dt = \int_0^{I_1} L_1 i_1 di_1 = \frac{1}{2} L_1 I_1^2$$

3. i_1 cons. at I_1 , change $i_2 \rightarrow 0$ to I_2 in time $t_1 \rightarrow t_2$

\therefore Energy delivered from it. source is

$$\int_{t_1}^{t_2} v_2 i_2 dt = \int_0^{I_2} L_2 i_2 di_2 = \frac{1}{2} L_2 I_2^2$$

Energy delivered by left source

$$\int_{t_1}^{t_2} v_1 i_1 dt = \int_{t_1}^{t_2} M_{12} \frac{di_2}{dt} \cdot i_1 dt = M_{12} I_1 I_2$$

\therefore Total energy stored when i_1 & i_2 reach constant values


$$W_{\text{total}} = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M_{12} I_1 I_2$$

\sim by starting from it. $= \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M_{21} I_1 I_2$

i.c. & final condus. same \therefore Total energy same $\therefore M_{12} = M_{21} = M$

$$\therefore W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M I_1 I_2$$

Energy considerations:

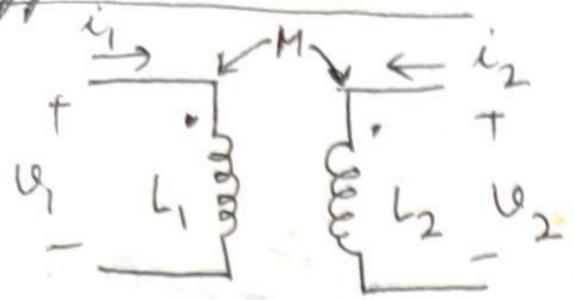

1. Let all i & v be zero.

\therefore 0 initial energy storage

2. o.c. at terminal pair

$i_1 \rightarrow 0$ to I_1 in time $t = t_1$

\therefore power entering network from left

instantaneously $\therefore v_1 i_1 = L_1 \frac{di_1}{dt} \cdot i_1$

from it. $\therefore v_2 i_2 = 0 \therefore i_2 = 0.$

Energy stored w/i the network when $i_1 = I_1$

$$\int_0^{t_1} v_1 i_1 dt = \int_0^{I_1} L_1 i_1 di_1 = \frac{1}{2} L_1 I_1^2$$

3. i_1 cons. at I_1 , change $i_2 \rightarrow 0$ to I_2 in time $t_1 \rightarrow t_2$.

\therefore Energy delivered from it. source is

$$\int_{t_1}^{t_2} v_2 i_2 dt = \int_0^{I_2} L_2 i_2 di_2 = \frac{1}{2} L_2 I_2^2$$

Energy delivered by left source

$$\int_{t_1}^{t_2} v_1 i_1 dt = \int_{t_1}^{t_2} M_{12} \frac{di_2}{dt} \cdot i_1 dt = M_{12} I_1 I_2$$

\therefore Total energy stored when i_1 & i_2 reach constant values

$$W_{\text{total}} = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M_{12} I_1 I_2$$

\sim by starting from it. $= \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M_{21} I_1 I_2$.

i_1 & final condus. same \therefore Total energy same $\therefore M_{12} = M_{21} = M$.

$$\therefore W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M I_1 I_2$$

Say i_1 enters • terminal, i_2 leaves • terminal, then

$$W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 - M I_1 I_2$$

$$\therefore \text{Instantaneously: } w(t) = \frac{1}{2} L_1 [i_1(t)]^2 + \frac{1}{2} L_2 [i_2(t)]^2 \pm M [i_1(t)] [i_2(t)]$$

For upper lt. on M , ~~note~~ assume i_1 & i_2 both +ve or -ve

\therefore only case when $w(t)$ can be -ve is

$$w(t) = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 - M i_1 i_2$$

$$= \frac{1}{2} (\sqrt{L_1} i_1 - \sqrt{L_2} i_2)^2 + \sqrt{L_1 L_2} i_1 i_2 - M i_1 i_2$$

\downarrow

≥ 0


\therefore since $w(t) \geq 0$

$$\therefore \sqrt{L_1 L_2} - M \geq 0 \quad \therefore M \leq \sqrt{L_1 L_2}$$

$$\text{coeff. of coupling } k = \frac{M}{\sqrt{L_1 L_2}}, \quad 0 \leq k \leq 1$$

The linear transformer: Φ vs. i linear

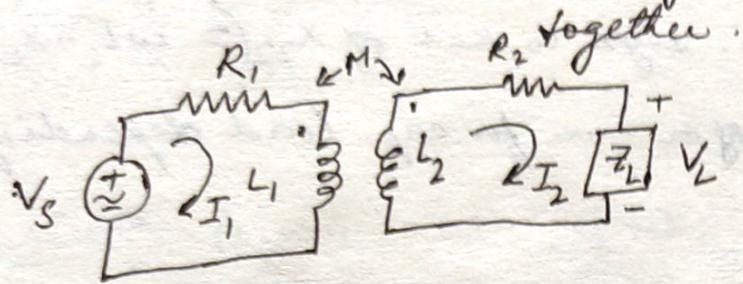network containing two or more coils deliberately coupled



Core: usually iron alloy.

Primary, Secondary (has load connected)

R_1, R_2 : winding resistance & other losses.

Usually secondary: resonant (tuned)
also primary tuned - ideal voltage source replaced by
current source + // large R & C.

Mesh eqns.

$$\underline{V}_S = \underline{I}_1 (R_1 + sL_1) - \underline{I}_2 sM \quad \dots (11)$$

$$0 = -\underline{I}_1 sM + \underline{I}_2 (R_2 + sL_2 + \underline{Z}_L) \quad \dots (12)$$

Let, $\underline{Z}_{11} = R_1 + sL_1$ $\underline{Z}_{22} = R_2 + sL_2 + \underline{Z}_L$

$$\therefore \underline{V}_S = \underline{I}_1 \underline{Z}_{11} - \underline{I}_2 sM \quad \dots (13)$$

$$0 = -\underline{I}_1 sM + \underline{I}_2 \underline{Z}_{22} \quad \dots (14)$$

Solve (14) for \underline{I}_2 & replace in (13)

$$\therefore \underline{Z}_{in} = \frac{\underline{V}_S}{\underline{I}_1} = \underline{Z}_{11} - \frac{s^2 M^2}{\underline{Z}_{22}} \quad \dots (15)$$

Note: 1. independent of dot placement

2. reduce coupling (M) to 0, then $\underline{Z}_{in} = \underline{Z}_{11}$

as M inc., \underline{Z}_{in} changes from \underline{Z}_{11} by $\left(-\frac{s^2 M^2}{Z_{22}}\right) \rightarrow$ reflected impedance.

Under s.s. sinusoidal oper. $s = j\omega$

$$\therefore \underline{Z}_{in}(j\omega) = \underline{Z}_{11}(j\omega) + \frac{\omega^2 M^2}{R_{22} + jX_{22}}$$

$$= \underline{Z}_{11} + \frac{\omega^2 M^2 R_{22}}{R_{22}^2 + X_{22}^2} + \frac{-j\omega^2 M^2 X_{22}}{R_{22}^2 + X_{22}^2}$$

3: Presence of sec. inc. losses in pri. ckt. $\therefore \frac{\omega^2 M^2 R_{22}}{R_{22}^2 + X_{22}^2}$ is +ve.

4. Reactance reflected into pri. load, opp. sign to that of $X_{22} (= \omega L_2 + X_L)$

$\& X_{22}'$ is (+ve) for inductive X_L & +ve or -ve for cap. load depending on mag. of X_L .

Sp. case : 1. pri. has C in series added.

2. pri. & sec. are identical series resonant ckt's,

$$R_1 = R_2 = R, \quad L_1 = L_2 = L, \quad \underline{Z}_L = C.$$

$$\therefore \omega_0 = \frac{1}{\sqrt{LC}} \quad \therefore \underline{Z}_{11} = R_{11}, \quad \underline{Z}_{22} = R_{22}$$

\underline{Z}_{in} is purely resistive, no reflected reactance.

\therefore resonant condn.

3. Say $\omega = \omega_0 + \delta$ \therefore \underline{X}_{11} & \underline{X}_{22} both inductive

\therefore reflected reactance is capacitive (associated -ve sign)


if k is large, then \underline{Z}_{in} may again be resistive \therefore 2nd resonant condn.

vice versa for $\omega = \omega_0 - \delta$.

Useful in communications sys. \rightarrow AM & FM radio, TV, radar, telemetry etc.


\therefore allow large sec. allowed over a band of frequencies from slightly below to slightly above ω_0 . \therefore Max. response over wider range of freq.

Equivalent T & π networks: Say ckt.

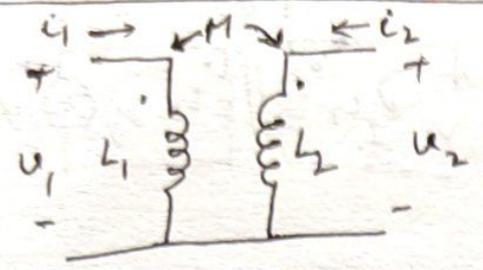

$$\therefore v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \quad \dots (16)$$
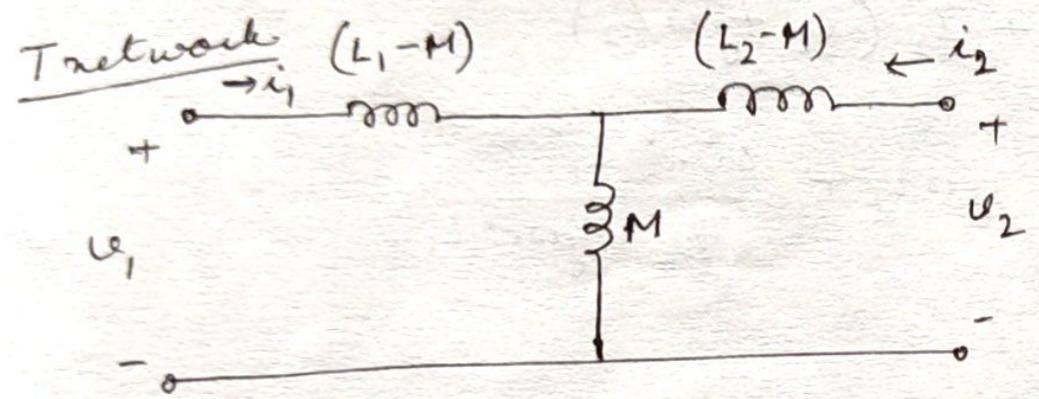
$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \quad \dots (17)$$



If dot changed, then replace M by $(-M)$ all through

Note: Equi. ckt. may have (-ve) inductance.
 - useful in network synthesis where such is reqd. by using appropriate transformer.

π network req. nodal eqns.

\therefore Solve (17) for $\frac{di_1}{dt}$ & substitute in (6)

$$\therefore v_1 = L_1 \frac{di_1}{dt} + M \left(\frac{1}{L_2} \right) \left[v_2 - M \frac{di_1}{dt} \right]$$


$$\text{or } \frac{di_1}{dt} = \frac{L_2}{4L_2 - M^2} v_1 - \frac{M}{4L_2 - M^2} v_2$$

Integrate from 0 to t \rightarrow current source.

$$\therefore i_1 - i_1(0)u(t) = \frac{L_2}{4L_2 - M^2} \int_0^t v_1 dt - \frac{M}{4L_2 - M^2} \int_0^t v_2 dt$$

$$\text{~ by } i_2 - i_2(0)u(t) = \frac{-M}{4L_2 - M^2} \int_0^t v_1 dt + \frac{L_1}{4L_2 - M^2} \int_0^t v_2 dt$$

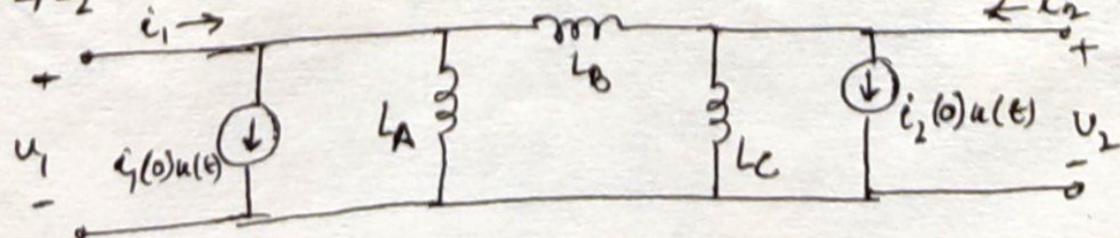
$$\therefore \frac{1}{L_B} = \frac{M}{4L_2 - M^2}, \text{ coeff. of } \int_0^t v_1 dt = \frac{1}{L_A} + \frac{1}{L_B} \therefore \frac{1}{L_A} = \frac{L_2 - M}{4L_2 - M^2}$$



$$\text{~ by } \frac{1}{L_C} = \frac{L_1 - M}{4L_2 - M^2}$$

Ideal transformer: $k=1$
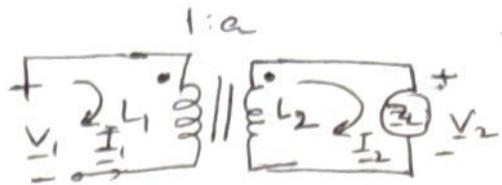
$$\therefore \frac{L_2}{L_1} = \frac{N_2^2}{N_1^2} = a^2 \quad \text{where} \quad \frac{N_2}{N_1} = a.$$



sinusoidal s.s. $\underline{V}_1 = \underline{I}_1 j\omega L_1 - \underline{I}_2 j\omega M$

$$0 = -\underline{I}_1 j\omega M + \underline{I}_2 (\underline{Z}_L + j\omega L_2)$$

$$\therefore \underline{Z}_{in} = j\omega L_1 + \frac{\omega^2 M^2}{\underline{Z}_L + j\omega L_2} = j\omega L_1 + \frac{\omega^2 a^2 L_1^2}{\underline{Z}_L + j\omega a^2 L_1}$$

$$= \frac{j\omega L_1 \underline{Z}_L}{\underline{Z}_L + j\omega a^2 L_1}$$

If $L_1 \rightarrow \infty$, then $\underline{Z}_{in} = \frac{\underline{Z}_L}{a^2}$ for finite \underline{Z}_L

Note ~~the~~ Z_{22} = Reflected impedance is $a^2 [a, L_1]$

$\therefore Z_{in}$ show diff. from cancellation of Z_{11} & reflected Z_{22} .

$$N_1 I_1 = N_2 I_2$$

$$\frac{V_2}{V_1} = a^2 \frac{I_2}{I_1} = a = \frac{N_2}{N_1} \quad \& \quad V_2 I_2 = V_1 I_1 \rightarrow \text{AZL for condus.}$$

when L_1, L_2 large compared to Z_L

Can be represented as Th. / Norton's equivalent on pri. / sec. side as req.

