



Response as fn. of ω :

3. Consider series RL ckt.

$$\therefore I = \frac{V_s}{R + j\omega L} \quad \therefore Y = \frac{1}{R + j\omega L}$$

$$\therefore |Y| = \frac{1}{\sqrt{R^2 + \omega^2 L^2}}$$
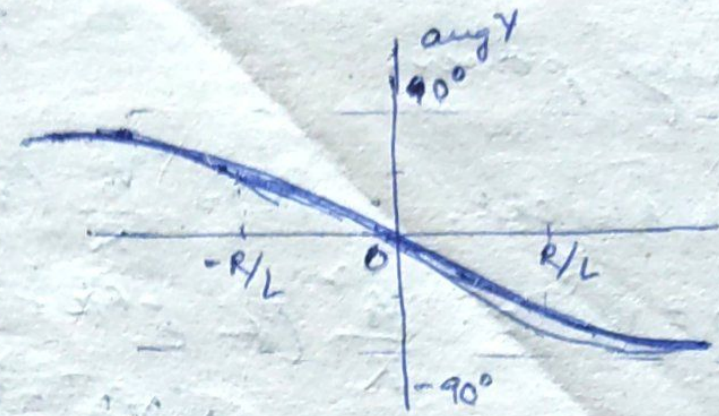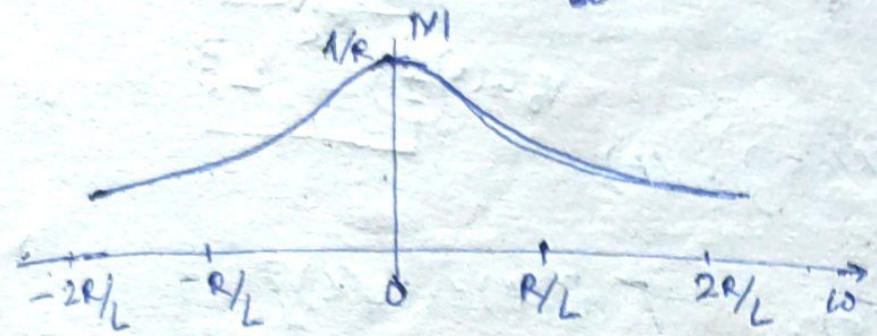
$$\text{ang. } Y = -\tan^{-1} \frac{\omega L}{R}$$



$$\omega = 100 \text{ rad/s} \Rightarrow v(t) = 50 \cos(\omega t + 30^\circ)$$

$$v(t) = 50 \cos(-100t + 30^\circ)$$

at $\omega = \pm R/L = \pm 1/\tau \rightarrow |Y| = 0.707 |Y|_{\text{max}}$, $\text{ang } Y = 45^\circ$.


Half power frequency. \rightarrow avg power = 0.5 max. power.

\therefore For same V , $I = \frac{1}{\sqrt{2}} I_{\text{max}}$



avg. power = $(0.707)^2 P_{\text{max}} = 0.5 P_{\text{max}}$

only due to R

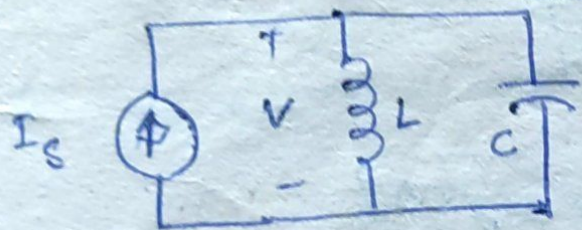2. Parallel LC ckt. driven by sinusoidal source:


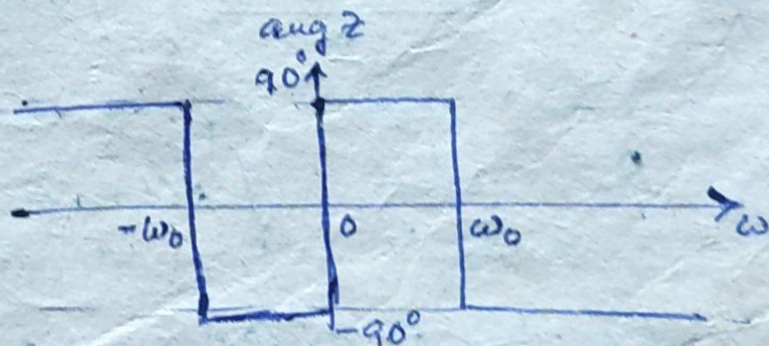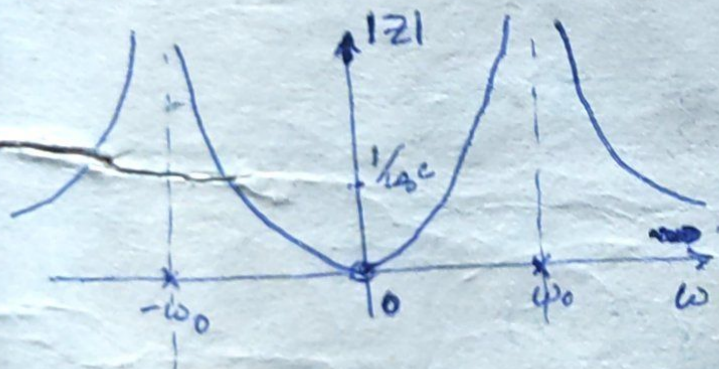
$$V = I_s \cdot \frac{(j\omega L) \cdot (1/j\omega C)}{j\omega L - j(1/\omega C)}$$



$$Z = \frac{L/C}{j(\omega L - 1/\omega C)} = -j \cdot \frac{1}{C} \cdot \frac{\omega}{\omega^2 - 1/LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{Critical frequencies}$$

$$\therefore |Z| = \frac{1}{C} \frac{|\omega|}{|(\omega - \omega_0)(\omega + \omega_0)|}$$


at which responses
0 or ∞.

zeros (o) → poles (x)

note: $\omega = \pm \infty$ is a zero

Frequency Response: Parallel resonance.

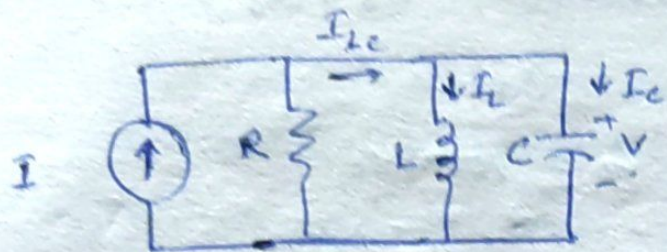A network is in resonance when the voltage and current at the network input terminals are in phase.




$$\underline{Y}(s) = \frac{1}{R} + \frac{1}{sL} + sC = C \frac{s^2 + s/RC + 1/LC}{s}$$

$$= C \frac{(s + \alpha - j\omega_d)(s + \alpha + j\omega_d)}{s}$$


As seen resonance occurs when $\omega C - \frac{1}{\omega L} = 0$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$
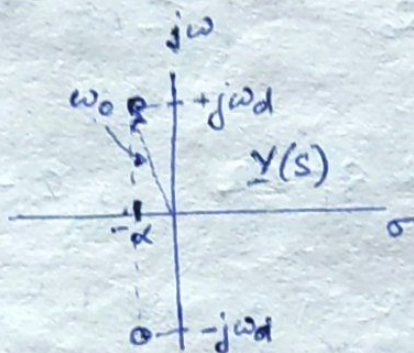
$$\underline{Y} = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$


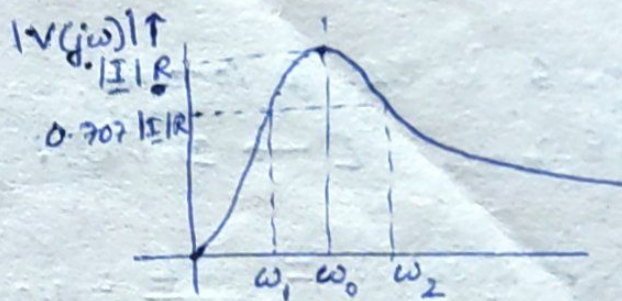
$$\alpha = 1/2RC, \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$



Ht. of response curve depends only on R for constant amplitude excitation but width & steepness depend on L & C too.

Quality factor $Q = 2\pi \frac{\text{maximum energy stored}}{\text{total energy lost per period.}}$

$$= 2\pi \frac{[\omega_L(t) + \omega_C(t)]_{\text{max}}}{\frac{P}{R} T}$$

↓
avg. power dissipation

Say $i(t) = I_m \cos \omega_0 t$ $v(t) = R i(t) = R I_m \cos \omega_0 t$.

$$w_C(t) = \frac{1}{2} C v^2 = \frac{I_m^2 R^2 C}{2} \cos^2 \omega_0 t$$

$$w_L(t) = \frac{1}{2} L i^2 = \frac{1}{2} L \left(\frac{1}{L} \int_0^t v dt \right)^2$$

$$= \frac{I_m^2 R^2 C}{2} \sin^2 \omega_0 t$$

$$\therefore w(t)_{\max} = \frac{I_m^2 R^2 C}{2}$$

$$P_R T = \frac{1}{2} I_m^2 R \cdot T = \frac{1}{2 f_0} I_m^2 R$$

$$\therefore Q_0 = \omega_0 R C = R \sqrt{\frac{C}{L}} = \frac{R}{X_{C_0}} = \frac{R}{X_{L_0}} \quad (\text{dimensionless})$$

$$d = \frac{1}{2(Q_0/\omega_0 C) C} = \frac{\omega_0}{2Q_0} ; \quad w_d = \omega_0 \sqrt{1 - \left(\frac{1}{2Q_0}\right)^2}$$

$$\xi = \frac{1}{2Q_0}$$

$$\text{Bandwidth} = \omega_2 - \omega_1 = B$$

* Half power freq.: since for cons. I, $V = \frac{1}{\sqrt{2}} V_{\text{max}}$
 \therefore power dissipated in R = V^2/R is $\frac{1}{2} P_{\text{max}}$

$$\underline{Y} = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right) = \frac{1}{R} + j\frac{1}{R} \left[\frac{\omega \cdot \omega_0 RC}{\omega_0} - \frac{\omega_0 R \cdot C}{\omega \cdot \omega_0 L} \right]$$

$$= \frac{1}{R} \left[1 + j Q_0 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right] \quad \text{Now, } |\underline{Y}| = \sqrt{2}/R \text{ only when } \left| Q_0 \left(\frac{\omega_1}{\omega_0} - \frac{\omega_0}{\omega_2} \right) \right| = 1$$

$$\therefore \omega_{1,2} = \omega_0 \left[\sqrt{1 + \left(\frac{1}{2Q_0} \right)^2} \mp \frac{1}{2Q_0} \right] \quad \therefore B = \frac{\omega_0}{Q_0}, \quad \omega_0 = \sqrt{\omega_1 \omega_2}$$

$$\therefore d = \frac{1}{2} B$$

Similarly analyze series resonance ckt.

$$\omega_0 = \sqrt{1/LC}$$

$$Q_0 = \omega_0 L / R$$


$$\omega_{1,2} = \omega_0 \left[\sqrt{1 + \left(\frac{1}{2Q_0} \right)^2} \mp \frac{1}{2Q_0} \right] \approx \omega_0 \mp \frac{1}{2} B \quad B = \frac{\omega_0}{Q_0}$$

Ex. Dr. Noe gave Pat $R = 20 \Omega$, $L = 20 \mu\text{H}$, $C = 1 \mu\text{F}$ (nominal)

connect variable freq. voltage source to series combination

& meas. resultant V_R as fn. of freq. then calculate ω_0 , Q_0 , B

& predict them

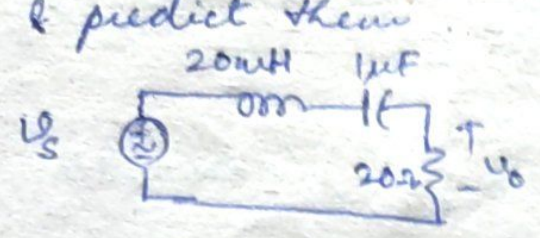

Theo.

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = 1125 \text{ Hz}$$

$$Q_0 = \frac{\omega_0 L}{R} = 7.07$$

$$B = \frac{f_0}{Q_0} = 159 \text{ Hz}$$

Prac.

$$f_0 = 1000 \text{ Hz}$$

$$Q_0 = 0.625$$

$$B = 1600 \text{ Hz}$$

check on Q-meter @ 1000 Hz:

$R = 18 \Omega$, $L \rightarrow 21.4 \mu\text{H}$ with $Q = 1.2$, $C \rightarrow 1.4 \mu\text{F}$ with $1/Q = 0.123$

$\therefore L$ with R series $= \frac{\omega L}{Q} = 112 \Omega$



C with series $R = \frac{1}{\omega C Q} = 13.9 \Omega$

$\therefore f_0 = 916 \text{ Hz}$, $Q_0 = \frac{2\pi \times 916 \times 21.4 \times 10^{-3}}{143.9} = 0.856$, $B = \frac{916}{0.856} = 1070 \text{ Hz}$

Further, off impedance of voltage source 50Ω .

$\therefore Q_0 = 0.635$, $B = 1442 \text{ Hz}$.

$\Delta \rightarrow Y$ transformation

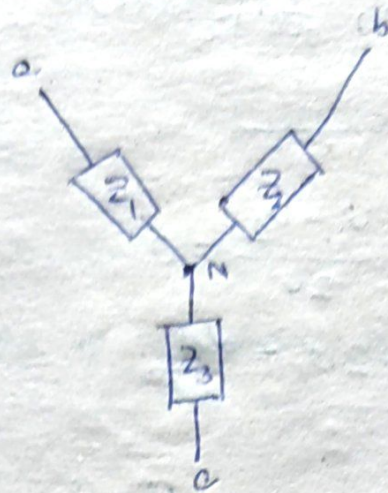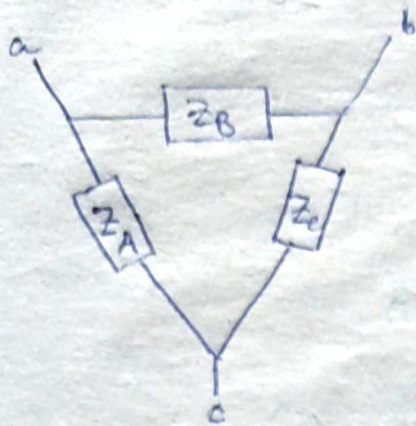

Between a & b:

$$\bar{z}_B \parallel (\bar{z}_A + \bar{z}_C) = \frac{\bar{z}_B (\bar{z}_A + \bar{z}_C)}{\bar{z}_A + \bar{z}_B + \bar{z}_C} = \bar{z}_1 + \bar{z}_2$$

$$\bar{z}_1 = \frac{\bar{z}_A \bar{z}_B}{\bar{z}_A + \bar{z}_B + \bar{z}_C} ; \bar{z}_2 = \frac{\bar{z}_B \bar{z}_C}{\bar{z}_A + \bar{z}_B + \bar{z}_C} ; \bar{z}_3 = \frac{\bar{z}_A \bar{z}_C}{\bar{z}_A + \bar{z}_B + \bar{z}_C}$$

Short a and b.

Admittance bet. a(b) & c:

$$\frac{1}{\bar{z}_A} + \frac{1}{\bar{z}_C} = \frac{1}{(\bar{z}_1 \parallel \bar{z}_2) + \bar{z}_3} = \frac{\bar{z}_1 + \bar{z}_2}{\bar{z}_1 \bar{z}_2 + \bar{z}_2 \bar{z}_3 + \bar{z}_3 \bar{z}_1}$$

$$\bar{z}_A = \frac{\sum_{i=1}^3 \bar{z}_i \bar{z}_j}{\bar{z}_2} ; \bar{z}_B = \frac{\sum \bar{z}_i \bar{z}_j}{\bar{z}_3} ; \bar{z}_C = \frac{\sum \bar{z}_i \bar{z}_j}{\bar{z}_1}$$

and thus the voltage V_{ab} may be found, with an eye on the subscripts:

$$\begin{aligned} V_{ab} &= V_{an} + V_{nb} = V_{an} - V_{bn} \\ &= 100 \angle 0^\circ - 100 \angle -120^\circ \\ &= 100 - (-50 - j86.6) \\ &= 173.2 \angle 30^\circ \end{aligned}$$

The three given voltages and the construction of the phasor V_{ab} are shown on the phasor diagram of Fig. 11-3.

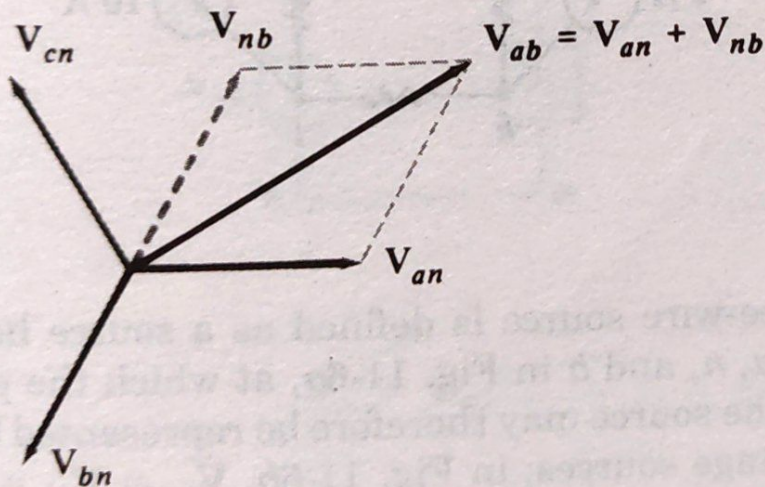


Figure 11-3

This phasor diagram illustrates the graphical use of the double-subscript voltage convention to obtain V_{ab} for the network of Fig. 11-2.

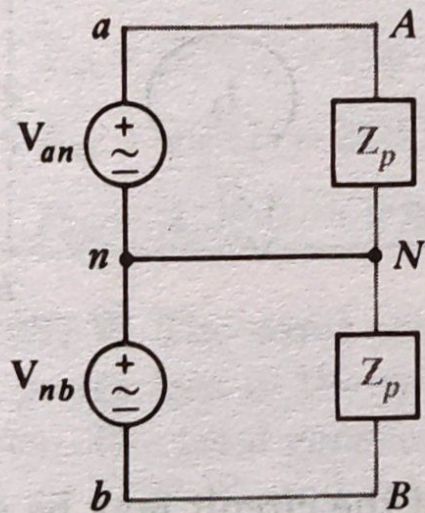


Figure 11-7

A simple single-phase three-wire system. The two loads are identical, and the neutral current is zero.

Since

$$V_{an} = V_{nb}$$

then,


$$I_{aA} = \frac{V_{an}}{Z_p} = I_{Bb} = \frac{V_{nb}}{Z_p}$$

and therefore

$$I_{nN} = I_{Bb} + I_{Aa} = I_{Bb} - I_{aA} = 0$$

Figure 11-8

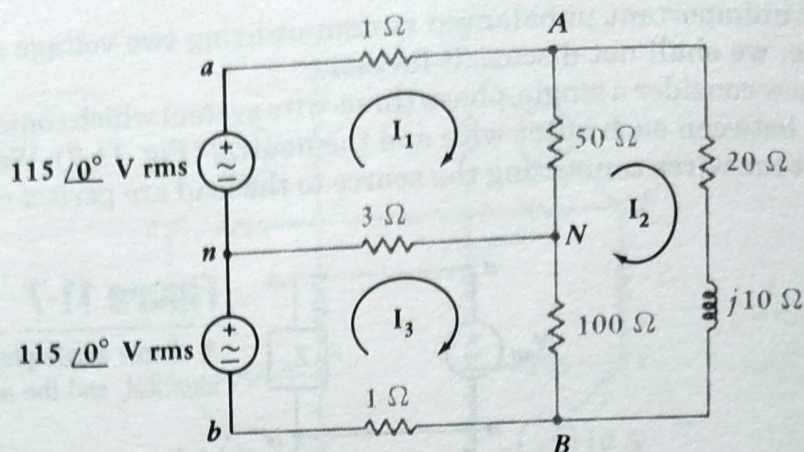A typical single-phase three-wire system.



Solution: The analysis of the circuit may be achieved by assigning mesh currents and writing the appropriate equations. The three mesh currents are

$$\mathbf{I}_1 = \frac{\begin{vmatrix} 115 & -50 & -3 \\ 0 & 170 + j10 & -100 \\ 115 & -100 & 104 \end{vmatrix}}{\begin{vmatrix} 54 & -50 & -3 \\ -50 & 170 + j10 & -100 \\ -3 & -100 & 104 \end{vmatrix}} = 11.24 / -19.83^\circ \text{ A rms}$$

$$\mathbf{I}_2 = \frac{\begin{vmatrix} 54 & 115 & -3 \\ -50 & 0 & -100 \\ -3 & 115 & 104 \end{vmatrix}}{\text{denom}} = 9.39 / -24.47^\circ$$

$$\mathbf{I}_3 = \frac{\begin{vmatrix} 54 & -50 & 115 \\ -50 & 170 + j10 & 0 \\ -3 & -100 & 115 \end{vmatrix}}{\text{denom}} = 10.37 / -21.80^\circ$$

The currents in the outer lines are thus

$$\mathbf{I}_{aA} = \mathbf{I}_1 = 11.24 / -19.83^\circ \text{ A rms}$$

$$\mathbf{I}_{bB} = -\mathbf{I}_3 = 10.37 / 158.20^\circ$$

and the smaller neutral current is

$$\mathbf{I}_{nN} = \mathbf{I}_3 - \mathbf{I}_1 = 0.946 / -177.7^\circ \text{ A rms}$$

The power drawn by each load may be determined:

$$P_{50} = |\mathbf{I}_1 - \mathbf{I}_2|^2(50) = 206 \text{ W}$$

which could represent two 100-W lamps in parallel. Also,

$$P_{100} = |\mathbf{I}_3 - \mathbf{I}_2|^2(100) = 117 \text{ W}$$

which might represent one 100-W lamp. Finally,

$$P_{20+j10} = |\mathbf{I}_2|^2(20) = 1763 \text{ W}$$

which we may think of as a 2-hp induction motor. The total load power is 2086 W. The loss in each of the wires is next found:

$$P_{aA} = |\mathbf{I}_1|^2(1) = 126 \text{ W}$$

$$P_{bB} = |\mathbf{I}_3|^2(1) = 108 \text{ W}$$

$$P_{nN} = |\mathbf{I}_{nN}|^2(3) = 3 \text{ W}$$

giving a total line loss of 237 W. The wires are evidently quite long; otherwise, the relatively high power loss in the two outer lines would cause a dangerous temperature rise. The total generated power must therefore be $206 + 117 + 1763 + 237$, or 2323 W, and this may be checked by finding the power delivered by each voltage source:

$$P_{an} = 115(11.24) \cos 19.83^\circ = 1216 \text{ W}$$

$$P_{bn} = 115(10.37) \cos 21.80^\circ = 1107 \text{ W}$$

or a total of 2323 W. The transmission efficiency for this system is

$$\text{Eff.} = \frac{2086}{2086 + 237} = 89.8\%$$

A phasor diagram showing the two source voltages, the currents in the outer lines, and the current in the neutral is constructed in Fig. 11-9. The fact that $I_{aA} + I_{bB} + I_{nN} = 0$ is indicated on the diagram. ■

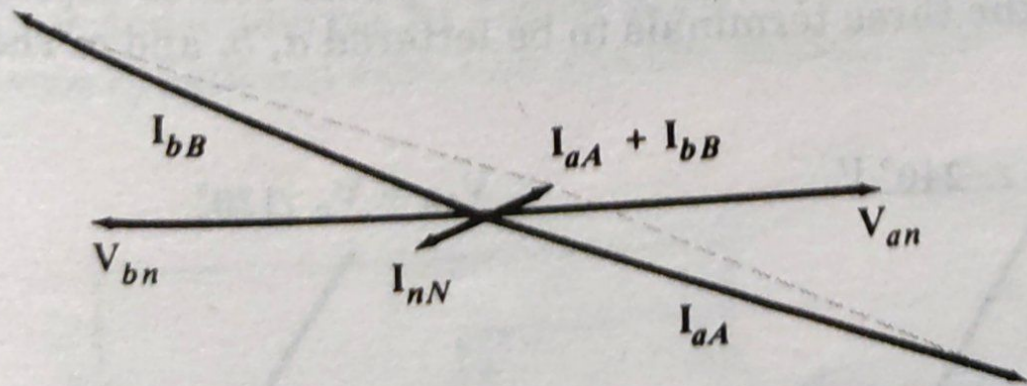


Figure 11-9

The source voltages and three of the currents in the circuit of Fig. 11-8 are shown on a phasor diagram. Note that $I_{aA} + I_{bB} + I_{nN} = 0$.

$$\mathbf{V}_{an} = V_p \angle 0^\circ$$

where we shall consistently use V_p to represent the rms *amplitude* of any of the phase voltages, then the definition of the three-phase source indicates that either


$$\mathbf{V}_{bn} = V_p \angle -120^\circ \quad \mathbf{V}_{cn} = V_p \angle -240^\circ$$

or

$$\mathbf{V}_{bn} = V_p \angle 120^\circ \quad \mathbf{V}_{cn} = V_p \angle 240^\circ$$

Figure 11-10

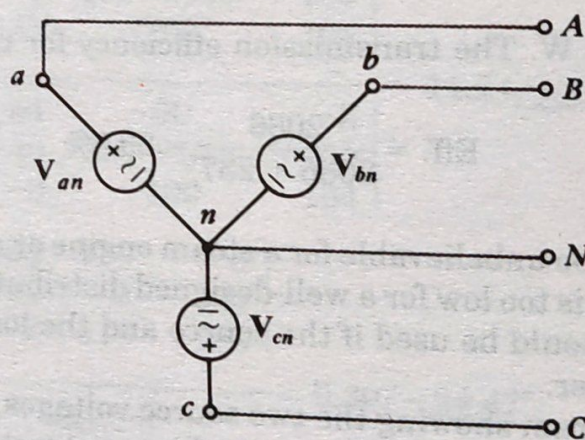
A Y-connected three-phase four-wire source.



The former is called *positive phase sequence*, or *abc* phase sequence, and is shown in Fig. 11-11a; the latter is termed *negative phase sequence*, or *cba* phase sequence, and is indicated by the phasor diagram of Fig. 11-11b. It is apparent that the phase sequence of a physical three-phase source depends on the arbitrary choice of the three terminals to be lettered *a*, *b*, and *c*. They may always

Figure 11-11

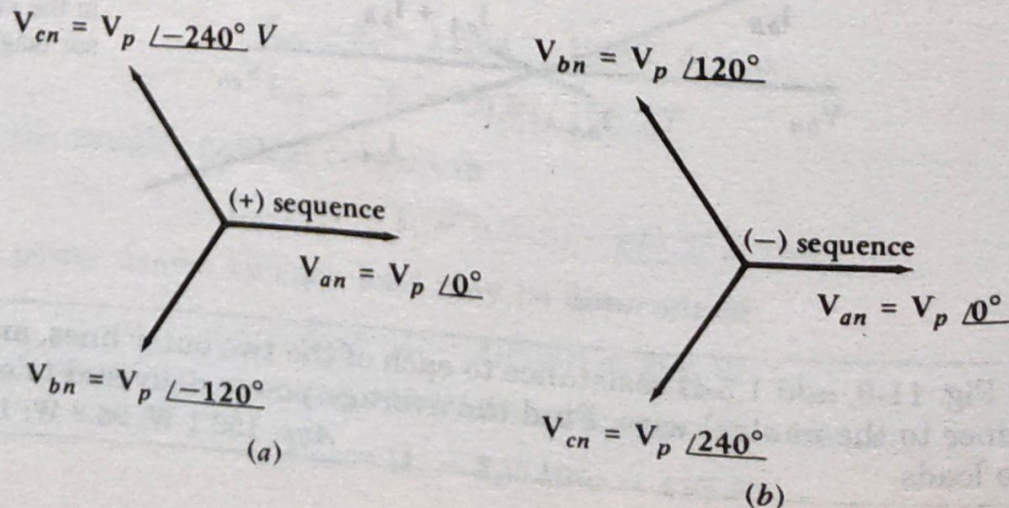- (a) Positive, or *abc*, phase sequence.
 (b) Negative, or *cba*, phase sequence.



$$\mathbf{V}_{ab} = \sqrt{3}V_p \angle 30^\circ$$

$$\mathbf{V}_{bc} = \sqrt{3}V_p \angle -90^\circ$$

$$\mathbf{V}_{ca} = \sqrt{3}V_p \angle -210^\circ$$

Kirchhoff's voltage law requires the sum of these three voltages to be zero, and it is zero.


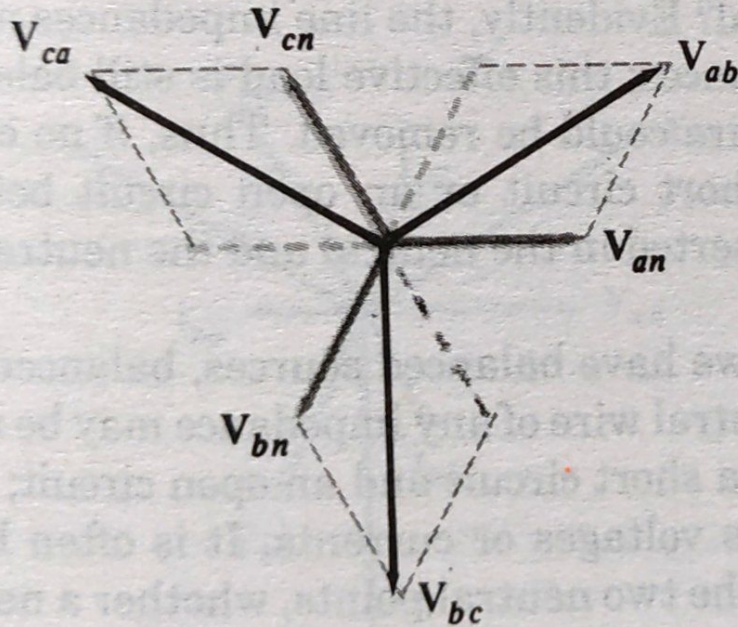


Figure 11-12

A phasor diagram which is used to determine the line voltages from the given phase voltages.

Three phase Y-Y connection:

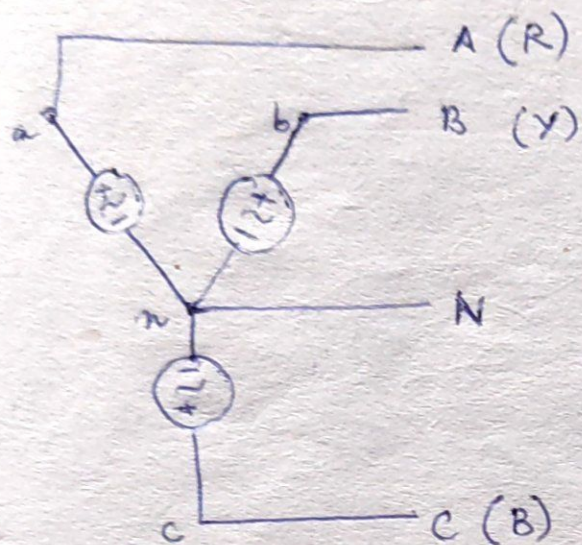

All in rms

3-phase 4 wire system with 4th wire from common or neutral pt.


In balanced 3-phase systems,

$$|V_{an}| = |V_{bn}| = |V_{cn}| \quad [V_{an} = V_a - V_n]$$

$$\text{and } \underline{V}_{an} + \underline{V}_{bn} + \underline{V}_{cn} = 0.$$

→ PHASE VOLTAGES.

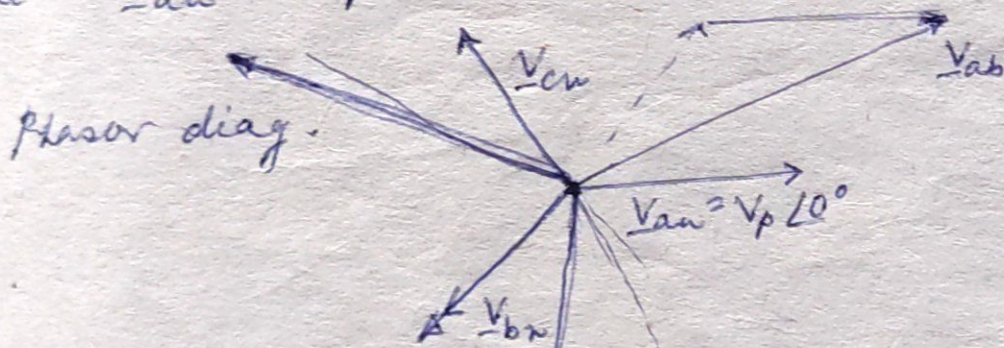Let $\underline{V}_{an} = V_p \angle 0^\circ$, then $\underline{V}_{bn} = V_p \angle -120^\circ$, $\underline{V}_{cn} = V_p \angle -240^\circ$ POSITIVE PHASE SEQUENCE



For line voltages:


$$\underline{V}_{ab} = \underline{V}_{an} - \underline{V}_{bn} = \sqrt{3} V_p \angle 30^\circ = V_L \angle 30^\circ$$

$$\sqrt{3} V_p \angle -90^\circ = V_L \angle -90^\circ$$

$$\sqrt{3} V_p \angle -210^\circ = V_L \angle -210^\circ$$

Similarly $\underline{V}_{bc} =$
 $\underline{V}_{ca} =$

$$\therefore V_L = \sqrt{3} V_p$$

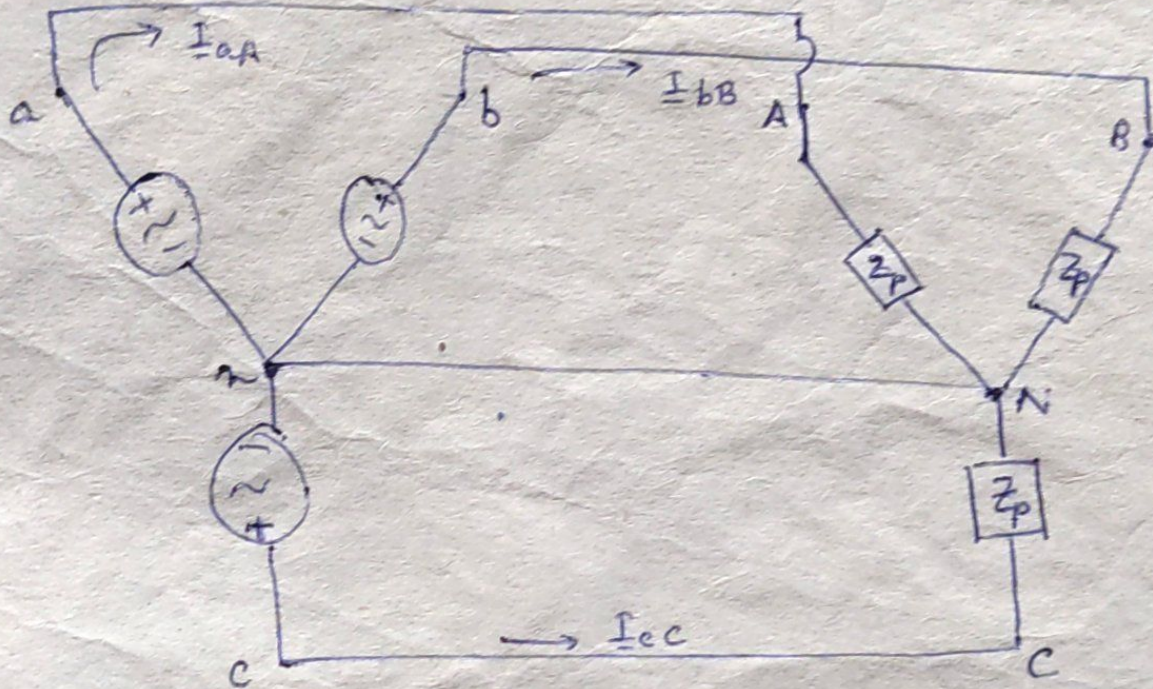

Balanced Y-connected load to Y-connected source.

$$\underline{I}_{aA} = \frac{V_{an}}{Z_p} = I_L \angle 0^\circ; \quad \underline{I}_{bB} = \frac{V_{bn}}{Z_p} = \underline{I}_{aA} \angle -120^\circ = I_L \angle -120^\circ$$

$$\underline{I}_{cC} = \frac{V_{cn}}{Z_p} = \underline{I}_{aA} \angle -240^\circ = I_L \angle -240^\circ$$

$$\therefore \underline{I}_{NN} = \underline{I}_{aA} + \underline{I}_{bB} + \underline{I}_{cC} = 0 \quad \therefore \text{no current in neutral for balanced load.}$$

For Balanced $\left\{ \begin{array}{l} \text{source} \\ \text{load} \\ \text{line impedances} \end{array} \right.$, a neutral wire of ANY impedance may be replaced by any other including short/open ckt. — system remains unaffected.

$$\text{For } nN \text{ open, } I_L = I_p \quad [\because I_{NN} = 0]$$

$$V_L = |\mathbf{V}_{ab}| = |\mathbf{V}_{bc}| = |\mathbf{V}_{ca}|$$

or known phase voltages

$$V_p = |\mathbf{V}_{an}| = |\mathbf{V}_{bn}| = |\mathbf{V}_{cn}|$$

where

$$V_L = \sqrt{3}V_p \quad \text{and} \quad \mathbf{V}_{ab} = \sqrt{3}V_p \angle 30^\circ$$

and so forth, as before. Since the voltage across each branch of the Δ is known, the *phase currents* are found:

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{ab}}{\mathbf{Z}_p} \quad \mathbf{I}_{BC} = \frac{\mathbf{V}_{bc}}{\mathbf{Z}_p} \quad \mathbf{I}_{CA} = \frac{\mathbf{V}_{ca}}{\mathbf{Z}_p}$$

and their differences provide us with the line currents, such as

$$\mathbf{I}_{aA} = \mathbf{I}_{AB} - \mathbf{I}_{CA}$$

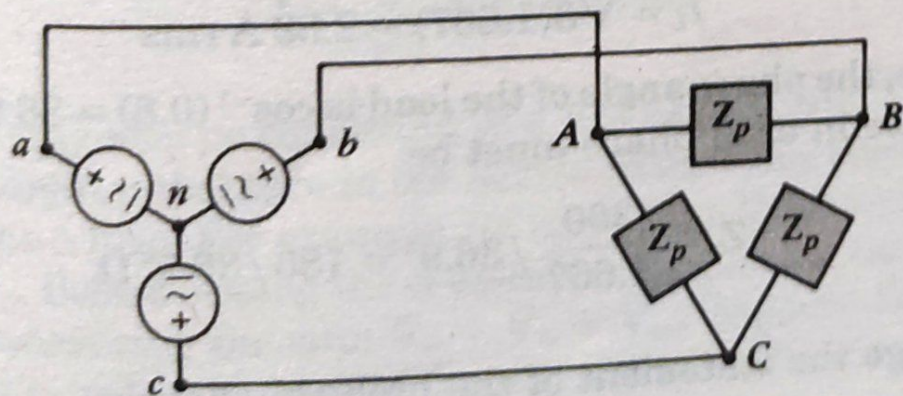


Figure 11-17

A balanced Δ -connected load is present on a three-wire three-phase system. The source happens to be Y-connected.