
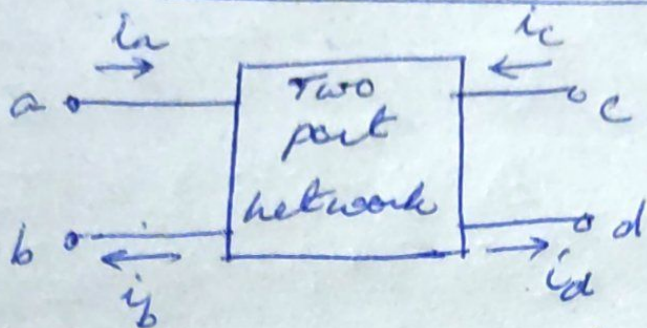


## Two port networks

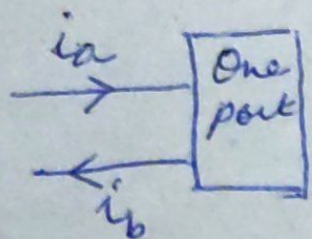

Loop eqns. for a  $N$  by  $N$  passive network:

$$Z_{11} I_1 + Z_{12} I_2 + \dots + Z_{1N} I_N = V_1$$


$$Z_{21} I_1 + Z_{22} I_2 + \dots + Z_{2N} I_N = V_2$$

$$Z_{N1} I_1 + Z_{N2} I_2 + \dots + Z_{NN} I_N = V_N$$

$$\Rightarrow \underline{Z} \underline{I} = \underline{V}$$

$$\Rightarrow \begin{bmatrix} Z_{11} & Z_{12} & \dots & Z_{1N} \\ Z_{21} & Z_{22} & \dots & Z_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ Z_{N1} & Z_{N2} & \dots & Z_{NN} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix}$$
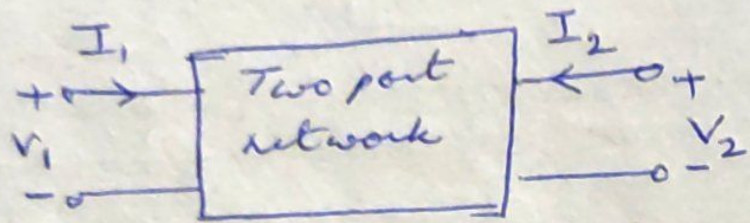
$$\text{so } I_1 = \frac{\Delta_{11}}{\Delta_2} V_1 ; Z_{in} = \frac{V_1}{I_1} = \frac{\Delta_2}{\Delta_{11}} \text{ (reciprocal)}$$



Short circuit admittance parameters  $y_{ij}$

$$\begin{cases} I_1 = y_{11} V_1 + y_{12} V_2 \\ I_2 = y_{21} V_1 + y_{22} V_2 \end{cases} \Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \Rightarrow \underline{I} = \underline{Y} \underline{V}$$

$$\therefore y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} \text{ ; } y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} \text{ , } y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} \text{ , } y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

i/p admittance
transfer admittances
o/p admittances

Open circuit impedance parameters  $z_{ij}$

$$\begin{cases} V_1 = z_{11} I_1 + z_{12} I_2 \\ V_2 = z_{21} I_1 + z_{22} I_2 \end{cases} \Rightarrow \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \Rightarrow \underline{V} = \underline{Z} \underline{I}$$

$$\Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \underline{Z}^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \Rightarrow \begin{aligned} I_1 &= \frac{z_{22}}{\Delta_2} V_1 - \frac{z_{21}}{\Delta_2} V_2 = \frac{\Delta_{11}}{\Delta_2} V_1 - \frac{\Delta_{12}}{\Delta_2} V_2 \\ I_2 &= -\frac{z_{12}}{\Delta_2} V_1 + \frac{z_{11}}{\Delta_2} V_2 = -\frac{\Delta_{21}}{\Delta_2} V_1 + \frac{\Delta_{22}}{\Delta_2} V_2 \end{aligned}$$


Voltage gain  $G_V = \frac{V_2}{V_1}$

Current gain  $G_I = \frac{I_2}{I_1}$

Power gain  $G_P = -G_V G_I = \frac{P_{out}}{P_{in}} = \frac{\operatorname{Re}[-\frac{1}{2} V_2 I_2^*]}{\operatorname{Re}[-\frac{1}{2} V_1 I_1^*]}$

Input impedance  $Z_{in} = \frac{V_1}{I_1}$ , output impedance  $Z_{out}$  = Thevenin impedance

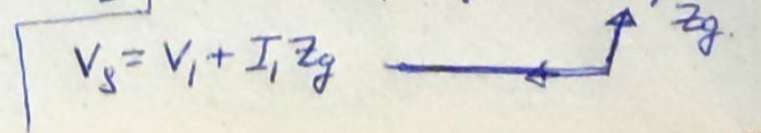$= \frac{V_2}{I_2} = Z_{22} - \frac{Z_{12} Z_{21}}{Z_{11} + Z_g}$  for generator impedance



## Hybrid parameters $h_{ij}$

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned} \quad \left| \quad \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \underline{h} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} \right.$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = \text{s.c. i/p impedance}; \quad h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \text{o/p ckt. reverse voltage gain}$$


$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = \text{s.c. fwd current gain}; \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \text{o/p ckt. o/p admittance}$$

For bilateral network,  $h_{12} = -h_{21}$
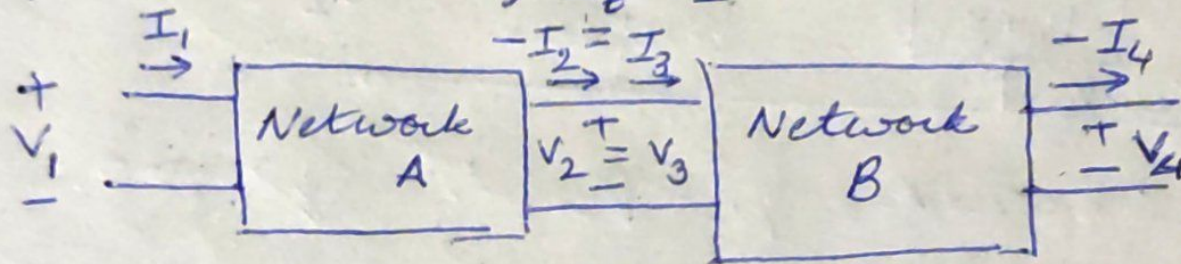
## Transmission parameters $t_{ij}$ ABCD parameters.

$$\begin{aligned} V_1 &= t_{11} V_2 - t_{12} I_2 \\ I_1 &= t_{21} V_2 - t_{22} I_2 \end{aligned} \quad \Rightarrow \quad \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} t_{11} & t_{12} \\ t_{21} & t_{22} \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

For reciprocal networks,  $\Delta_t = 1$ .





Cascade connections

$$\text{For bilateral, } \Delta_t = t_{11} t_{22} - t_{12} t_{21} = 1$$

Ex 15-1, 15-2,  
15-3

Single  
port  
network

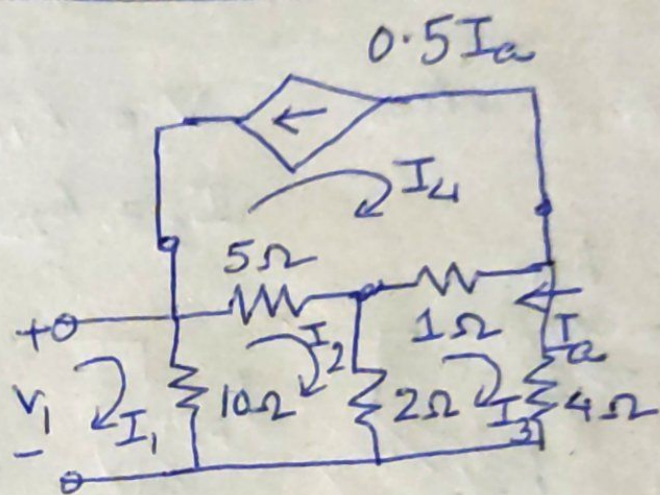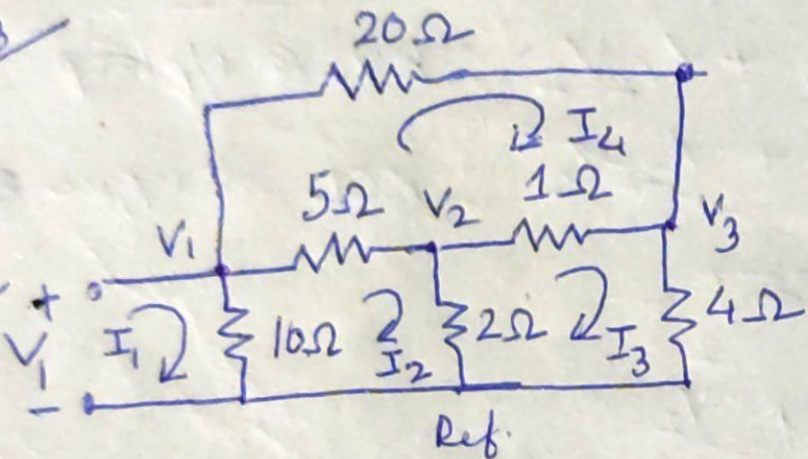

$$V_1 = 10I_1 - 10I_2$$

$$0 = -10I_1 + 17I_2 - 2I_3 - 5I_4$$

$$0 = -2I_2 + 7I_3 - I_4$$

$$0 = -5I_2 - I_3 + 26I_4$$

Mesh  
equations

$$V_1 = 10I_1 - 10I_2$$

$$0 = -10I_1 + 17I_2 - 2I_3 - 5I_4$$

$$0 = -2I_2 + 7I_3 - I_4$$

$$I_4 = -0.5I_a = -0.5(I_4 - I_3)$$

$$\Rightarrow 0 = +0.5I_3 - 1.5I_4$$



BILATERAL  
ELEMENTS

$$\Delta_2 = \begin{bmatrix} 10 & -10 & 0 & 0 \\ -10 & 17 & -2 & -5 \\ 0 & -2 & 7 & -1 \\ 0 & -5 & -1 & 26 \end{bmatrix}$$

$$\Delta_2 = \begin{bmatrix} 10 & -10 & 0 & 0 \\ -10 & 17 & -2 & -5 \\ 0 & -2 & 7 & -1 \\ 0 & 0 & 0.5 & -1.5 \end{bmatrix}$$

Ex 15.1, 15.2,  
15.3

Single  
port  
network

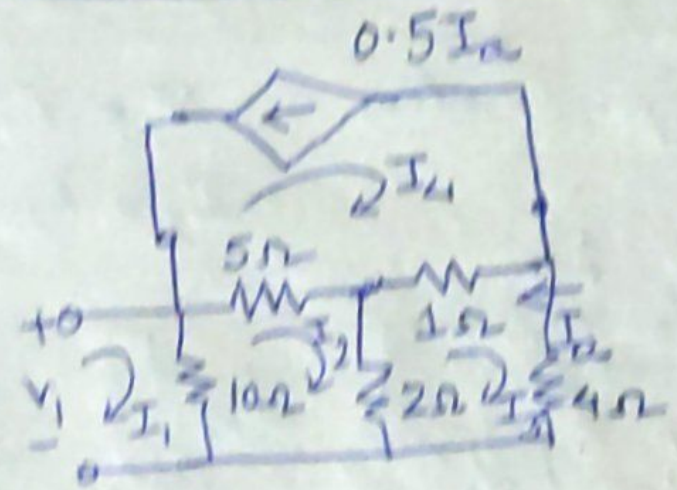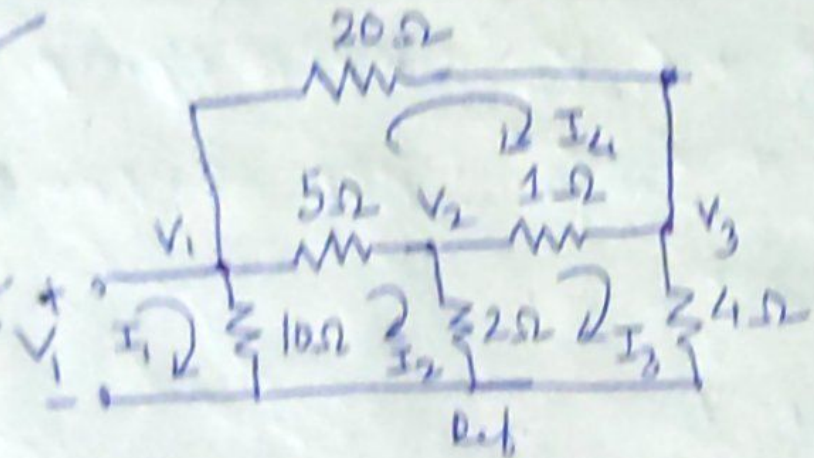

Nodal  
for  $\Delta y$

$$V_1 \left( \frac{1}{10} + \frac{1}{5} + \frac{1}{20} \right) - 0.2V_2 - 0.05V_3 = 0$$


$$-0.2V_1 + V_2 \left( \frac{1}{5} + \frac{1}{2} + 1 \right) - V_3 = 0$$

$$-0.05V_1 - V_2 + V_3 \left( \frac{1}{20} + 1 + \frac{1}{4} \right) = 0$$

$$\Delta y = \begin{bmatrix} 0.35 & -0.2 & -0.05 \\ -0.2 & 1.7 & -1 \\ -0.05 & -1 & 1.3 \end{bmatrix}; Y_{in} = \frac{\Delta y}{\Delta_{11}}$$

Ex 15-5

Two port network

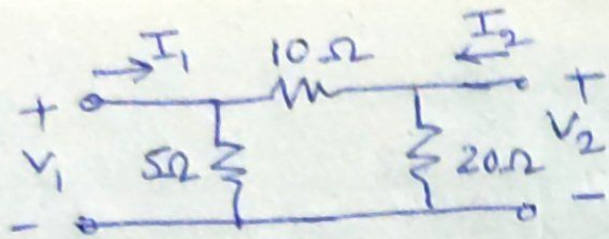

$$I_1 = V_1 \left( \frac{1}{5} + \frac{1}{10} \right) - 0.1 V_2$$

$$I_2 = -0.1 V_1 + V_2 \left( \frac{1}{10} + \frac{1}{20} \right)$$

$$\Rightarrow I_1 = 0.3 V_1 - 0.1 V_2$$

$$I_2 = -0.1 V_1 + 0.15 V_2$$

$$\Rightarrow \underline{[Y]} = \begin{bmatrix} 0.3 & -0.1 \\ -0.1 & 0.15 \end{bmatrix}$$





$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

$$I_2 = y_{12}V_1 + y_{22}V_2 + (y_{21} - y_{12})V_1$$

for bilateral network form.
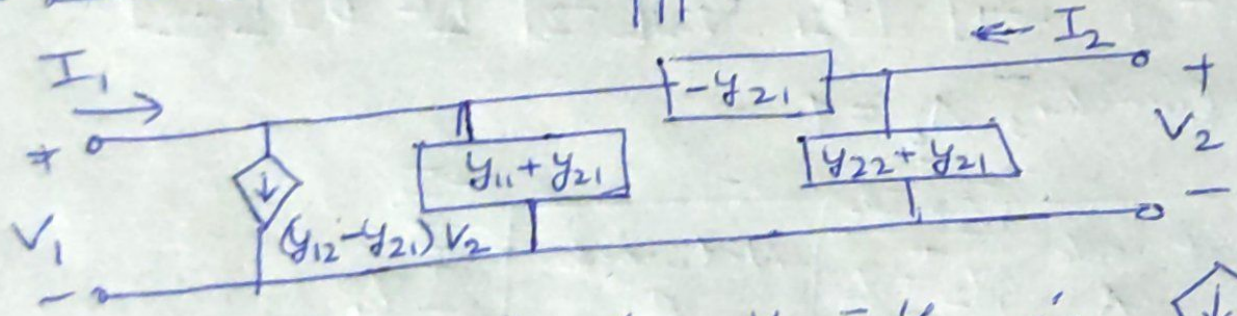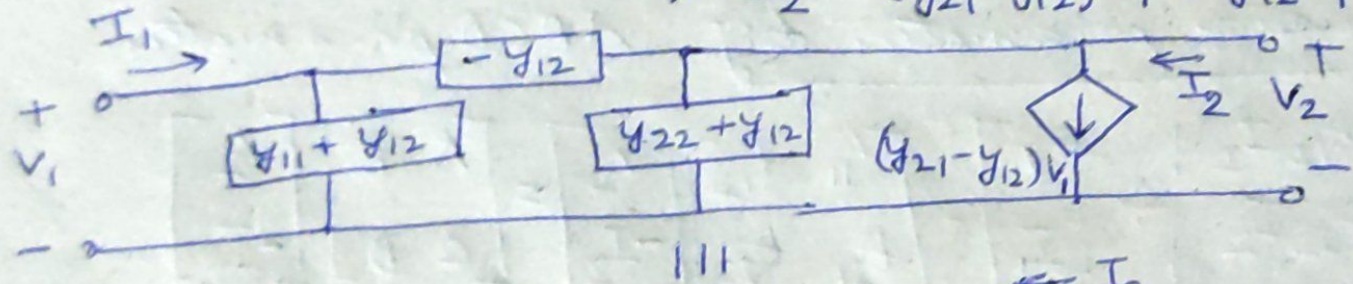
$$\Rightarrow I_2 - (y_{21} - y_{12})V_1 = y_{12}V_1 + y_{22}V_2$$




For bilateral network,  $y_{12} = y_{21} \therefore \diamond \rightarrow 0$ .

Also  $\nabla \rightarrow Y$  conversion possible.

For  $h$ -parameters


$$V_1 = h_{11} I_1 + h_{12} V_2 \quad ; \text{KVL @ } i_p \text{ loop}$$
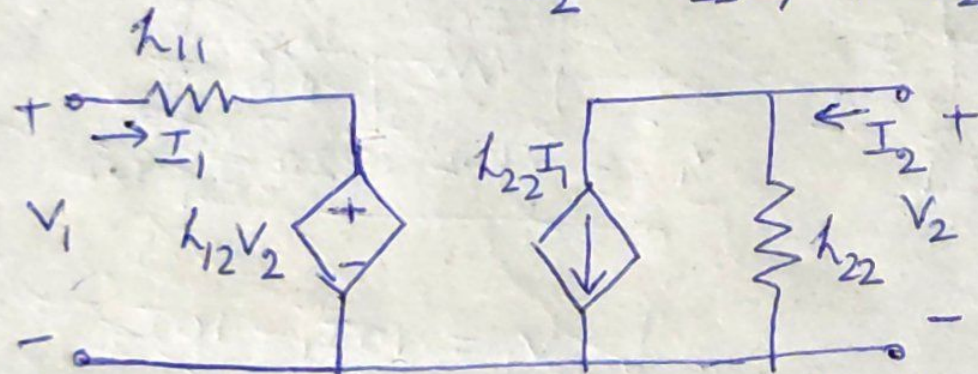
$$I_2 = h_{22} I_1 + h_{21} V_2 \quad ; \text{KCL at upper o/p node}$$



Transistor equivalent circuit

For  $t$ -parameters

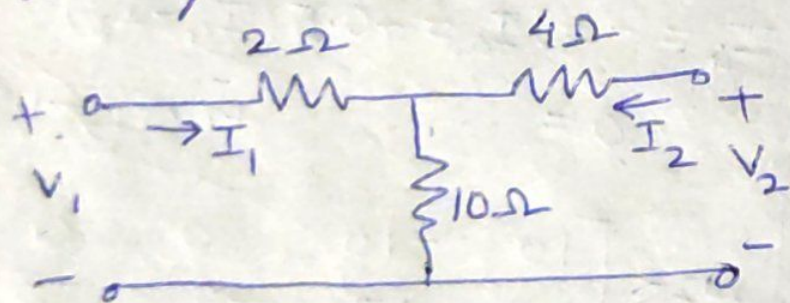

$$V_1 = 12I_1 + 10I_2$$

$$V_2 = 10I_1 + 14I_2 \rightarrow I_1 = \underset{t_{21}}{0.1} V_1 - \underset{t_{22}}{1.4} I_2$$

$$V_1 = \underset{t_{11}}{1.2} V_1 - \underset{t_{12}}{6.8} I_2$$

$$V_1 = t_{11} V_2 - t_{12} I_2$$

$$I_1 = t_{21} V_2 - t_{22} I_2$$