
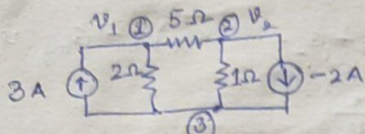


Nodal analysis:

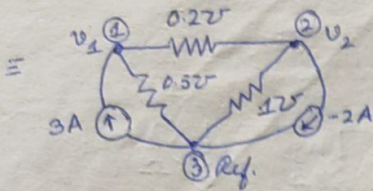N node ckt: $(N-1)$ voltages and $(N-1)$ equations.





Let reference node be ③ → node to which largest no. of branches connected.
If ref. marked, then signs of v_1, v_2 need not be marked.



KCL at node ①: $-3 + 0.2(v_1 - v_2) + 0.5v_1 = 0$
node ②: $-2 + 1v_2 + 0.2(v_2 - v_1) = 0$

$\therefore v_1 = 5V; v_2 = 2.5V$

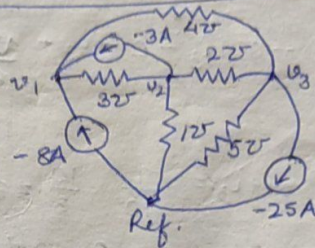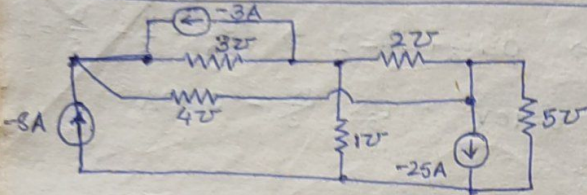

KCL at node ①: $+8 + 3 + 3(v_1 - v_2) + 4(v_1 - v_3) = 0$
②: $-3 + 3(v_2 - v_1) + 1v_2 + 2(v_2 - v_3) = 0$
③: $-25 + 5v_3 + 2(v_3 - v_2) + 4(v_3 - v_1) = 0$


$\Rightarrow 7v_1 - 3v_2 - 4v_3 = -11$
 $-3v_1 + 6v_2 - 2v_3 = 3$
 $-4v_1 - 2v_2 + 11v_3 = 25$

Cramer's rule: $v_1 = \frac{\begin{vmatrix} -11 & -3 & -4 \\ 3 & 6 & -2 \\ 25 & -2 & 11 \end{vmatrix}}{\begin{vmatrix} 7 & -3 & -4 \\ -3 & 6 & -2 \\ -4 & -2 & 11 \end{vmatrix}} = 1V$

$v_2 = 2V, v_3 = 3V$

Conductance matrix: $G = \begin{bmatrix} 7 & -3 & -4 \\ -3 & 6 & -2 \\ -4 & -2 & 11 \end{bmatrix}$: symmetrical about pivot axis.
all elements on diag: +ve rest

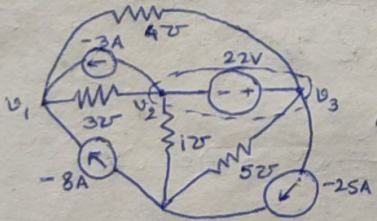Consider that a voltage source bet. v_2 and v_3 in place of 2Ω conductance.



If sum of i leaving v_2 or $v_3 = 0$, then sum of i leaving supernode $(v_2, v_3) = 0$.


KCL at node (v_2, v_3) :
 $\therefore 3(v_2 - v_1) - 3 + 4(v_3 - v_1) - 25 + 5v_3 + 1v_2 = 0$
 $-7v_1 + 4v_2 + 9v_3 = 28$

$7v_1 - 3v_2 - 4v_3 = -11$

Rela. bet. v_2 & v_3 : $-v_2 + v_3 = 22$

$v_1 = \frac{\begin{vmatrix} 28 & 4 & 9 \\ -11 & -3 & -4 \\ 22 & -1 & 1 \end{vmatrix}}{\begin{vmatrix} 7 & -3 & -4 \\ -3 & 6 & -2 \\ 0 & -1 & 1 \end{vmatrix}} = -4.5V$

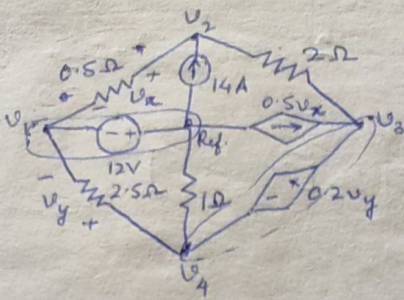- Comments:
- No conductance matrix
 - No symmetry @ diag.
 - KCL to no. of nodes reduced by 1 for a voltage source + voltage reln.



~~KCL~~ $v_1 = -12V$

KCL at (2): $-14 + \frac{v_2 - v_1}{0.5} + \frac{v_2 - v_3}{2} = 0$

at supernode (3,4):

$$-0.5v_x + \frac{v_3 - v_2}{2} + \frac{v_4}{1} + \frac{v_4 - v_1}{2.5} = 0$$

$$v_3 - v_4 = 0.2v_y = 0.2(v_4 - v_1)$$

Also $v_x = v_2 - v_1$

$$-14 + \frac{12}{0.5} + 2.5v_2 - 0.5v_3 = 0$$

$$-2v_1 + 2.5v_2 - 0.5v_3 = 14$$

$$v_1 = -12$$

$$0.1v_1 - v_2 + 0.5v_3 + 1.4v_4 = 0$$



$$0.2v_1 + v_3 - 1.2v_4 = 0$$

$$v_1 = -12V, v_3 = 0, v_2 = -4V, v_4 = -2V$$

Mesh analysis: Applicable only to planar networks.

Planar: If the diag. of a ckt. can be drawn on a plane surface s.t. no branch passes over or under any branch.

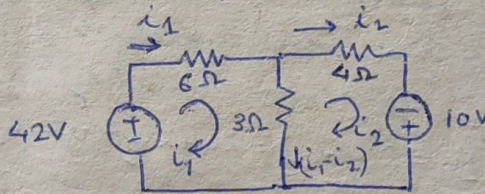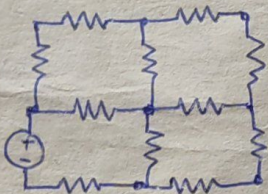Mesh: A loop which does not contain any other loops w/in it.




KVL for LH mesh: $-42 + 6i_1 + 3(i_1 - i_2) = 0$

RH: $4i_2 - 10 - 3(i_1 - i_2) = 0$

$$i_1 = 6A, i_2 = 4A, i_1 - i_2 = 2A$$

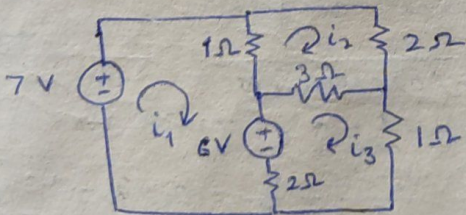M-meshes: M branch currents & M independent eqns.



$$3i_1 - i_2 - 2i_3 = 1$$


$$-i_1 + 6i_2 - 3i_3 = 0$$

$$-2i_1 - 3i_2 + 6i_3 = 6$$

$$i_3 = 3A, i_1 = 3A, i_2 = 2A$$

Resistance matrix $R = \begin{bmatrix} 3 & -1 & -2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{bmatrix}$

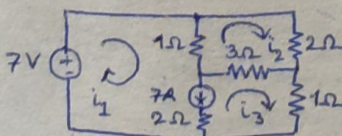Consider current source in place of voltage source of 6V.
- Supernode whose interior is that of meshes 1 & 3.




KVL: $-7 + 1(i_1 - i_2) + 3(i_3 - i_2) + 1i_3 = 0$

KVL @ 1: $1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$

Current source reln: $i_1 - i_3 = 7$

$$i_3 = 2A, i_1 = 9A, i_2 = 2.5A$$

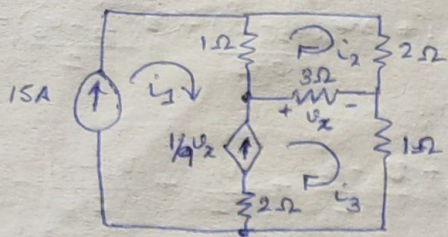For both dependent and independent source:



only one KVL for mesh 2: $1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$

$$i_1 = 15A$$

$$i_3 - i_1 = \frac{1}{9}v_2 = \frac{1}{9}[3(i_3 - i_2)]$$

$$i_1 = 15, i_2 = 11, i_3 = 17A$$

Linearity and Superposition:

Linear element: Passive element that has a linear voltage-current relationship

Linear: satisfies principle of superposition - v. useful practically.

HOMOGENEITY ① $a \cdot kb = k(ab)$

SUPERPOSITION ② $d(a+b) = da + db$

$$f(ax_1 + a_2x_2) = a_1f(x_1) + a_2f(x_2)$$

$$y = ax + b \quad \text{violates (2)}$$

$$y = ax + b \cdot 2$$

$$2y = a \cdot 2x + b \cdot 2$$

or linear current-voltage reln. \rightarrow multiplication of ~~time~~ varying i through element by constant k results in multiplication of v across element by same constant k .

$$[v = iR \therefore (ki) \cdot R = k(iR) = k \cdot v]$$

Principle of superposition: the response at any pt. in the linear ckt. having more than one independent source can be obtained as a sum of the responses caused by each independent source acting alone.

$$[v = R(i_1 + i_2) = Ri_1 + Ri_2 = v_1 + v_2]$$


Resistor, inductor, capacitor, mutually coupled inductor - all linear

Linear dependent source: Dependent current or voltage source whose v or i \propto only to first power of some i or v variable in the circuit or to the sum of such quantities.

$$v_s = 0.6i_1 - 14v_2 \quad \text{linear} \quad \text{NOT} \quad v_s = 0.6i_1^2 \quad \text{or} \quad v_s = 0.6i_1v_2$$

$$\Rightarrow \alpha v_s = 0.6(\alpha i_1) - 14(\alpha v_2) \quad \alpha v_s \neq 0.6(\alpha i_1)^2 \quad \alpha v_s \neq 0.6(\alpha i_1)(\alpha v_2)$$

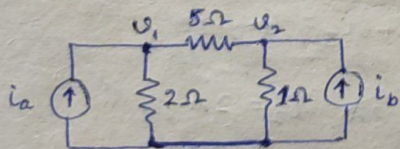Linear circuit: ckt. composed entirely of independent sources, linear dependent sources and linear elements.



Sources \rightarrow FORCING FNS.

Voltages produced \rightarrow RESPONSE FNS.

$$\text{KCL at } \textcircled{1}: i_a = \frac{v_1 - v_2}{5} + \frac{v_1}{2} = 0.7v_1 - 0.2v_2$$

$$\textcircled{2}: i_b = -0.2v_1 + 1.2v_2$$

changing sources to $i_{ax}, i_{bx} \rightarrow v_{1x}, v_{2x}$ and then $i_{ay}, i_{by} \rightarrow v_{1y}, v_{2y}$ then add or superpose:


$$i_{ax} + i_{ay} = 0.7(v_{1x} + v_{1y}) - 0.2(v_{2x} + v_{2y})$$

$$i_{bx} + i_{by} = -0.2(v_{1x} + v_{1y}) + 1.2(v_{2x} + v_{2y})$$

\therefore Responses can be taken independently and simply added.

Superposition Theorem:

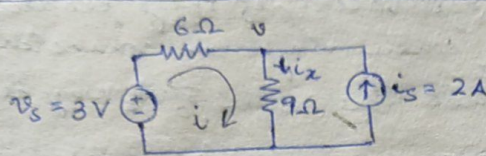In any linear resistive network containing several sources, the voltage across or the current through any resistor or source may be calculated by adding algebraically all the individual voltages or currents caused by each independent source acting alone, with all the other independent voltage sources replaced by short ckt. & all other independent current sources replaced by open circuits.




Reqd.: expression for i_x .

1. Current source = 0 \therefore open ckt.

$$\therefore i_x = \frac{3V}{15\Omega} = \frac{1}{5} A = 0.2 A.$$

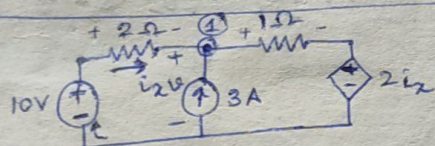2. Voltage source = 0, short ckt.

$$\therefore i_x = \frac{6}{15} \times 2 A = \frac{12}{15} A = \frac{4}{5} A = 0.8 A \quad \therefore \text{Total } i_x = 1 A.$$



Seek i_x

$$\textcircled{1} \frac{10-3}{2} + \frac{V}{1} = 2 \Rightarrow \frac{7}{2} = \frac{V}{1} \Rightarrow V = 3.5 \Rightarrow i_x = \frac{3.5}{1} = 3.5 A$$

$$\textcircled{2} -3 + 6i_x + 9(i_x + 2) = 0 \Rightarrow 15i_x + 15 = 0 \Rightarrow i_x = -1 \therefore i_x = i_x + 2 = 1 A$$

1. Open ckt. 3A source.

$$\therefore -10 + 5i_x' = 0 \therefore i_x' = 2 A.$$

2. Short ckt. 10V source. KCL at node $\textcircled{1}$: $\frac{V''}{2} + \frac{V'' - 2i_x''}{1} = 3$

short ckted left branch: $V'' = -2i_x''$

$$\therefore i_x'' = -0.6 A$$

$$\therefore i_x = 2 - 0.6 = 1.4 A.$$

Limitation of Superposition: $\textcircled{1}$ not much time saved if dependent sources present since then at least two sources to be considered each time.

$\textcircled{2}$ applicable only to linear responses: power/energy not subject to superposition.

Source transformations:


Practical source \equiv ideal source only as long as relatively small currents/power drawn.

Automobile start with headlights on: starter current of 100 A \therefore headlights perceptibly dimmed.

Say, for no current flow, battery terminal voltage = 12V
 — do — = 11V.

\therefore Practical voltage source: 12V in series with 0.01Ω

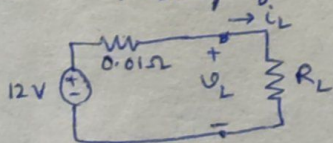\therefore drop of 1V across 0.01Ω when 100A flows.




V_L : practical voltage $\frac{i_L}{1200}$

$$V_{100} = r_i i_L + V_L$$

$$12 = 0.01 i_L + V_L$$


$$\therefore i_L = 1200 - 100 V_L$$

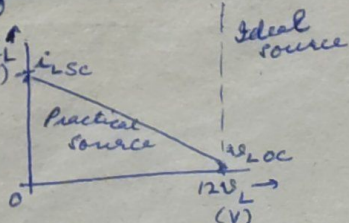

So, each pt. on line \rightarrow diff. R_L , when $V_L = \frac{1}{2} V_{100}$, $R_L = r_i = 0.01\Omega$

$$\frac{V_{100}}{i_L} = 2r_i$$



General practical voltage source

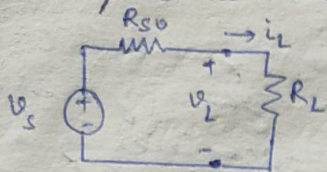

$$V_L = V_s - R_{SV} i_L$$


$$V_{Loc} = V_s$$

$$i_{Lsc} = \frac{V_s}{R_{SV}}$$

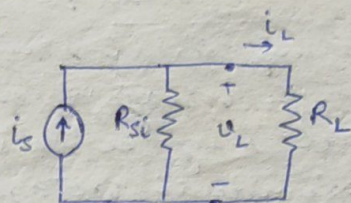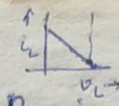

$$i_L = i_s - \frac{V_L}{R_{Si}}$$

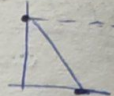
$$i_{Lsc} = i_s, \quad V_{Loc} = R_{Si} i_s$$




Equivalent sources: Two sources are equivalent if they produce identical values of \$V_L\$ and \$i_L\$ when they are connected to identical values of \$R_L\$, ^{no matter} what the value of \$R_L\$ may be.

\$\therefore R_L = \infty, R_L = 0 \rightarrow\$ Equivalent sources provide same open ckt. voltage and short circuit current.
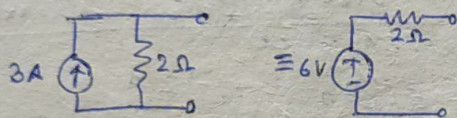
$$\therefore V_{Loc} = V_s = R_{Si} i_s, \quad i_{Lsc} = \frac{V_s}{R_{SV}} = i_s \quad \therefore R_{Si} = R_{SV} = R_S \text{ \& } V_s = i_s R_S$$



Maximum Power Theorem

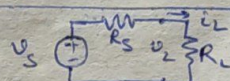

For a practical voltage source, power delivered to the load is

$$P_L = i_L^2 R_L = \left(\frac{V_s}{R_S + R_L} \right)^2 R_L \quad \frac{v \, dv - v \, dv}{v^2} = \frac{d}{dv} \left(\frac{v}{v} \right)$$

To find value of \$R_L\$ that absorbs max. power from given practical source, differentiate \$P_L\$ wrt \$R_L\$ and equate to zero

$$\frac{dP_L}{dR_L} = \frac{(R_S + R_L)^2 \cdot V_s^2 - V_s^2 R_L \cdot 2(R_S + R_L)}{(R_S + R_L)^4} = 0$$


$$\Rightarrow (R_S + R_L) - 2R_L = 0 \Rightarrow R_S = R_L$$

Diff. again: $\frac{d^2 P_L}{dR_L^2} \Rightarrow$ -ve for \$R_S = R_L\$
check.

\$R_L = 0 \text{ \& } R_L = \infty \rightarrow\$ both give min. \$P_L = 0 \therefore\$ proved.





Max. power theorem: An independent voltage source in series with a resistance \$R_S\$ or an independent current source with a resistance \$R_S\$ in parallel delivers maximum power to that load resistance \$R_L\$ for which \$R_L = R_S\$.

Drill Problems

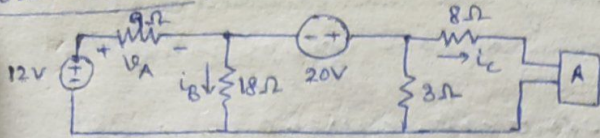


Find V_A if A is

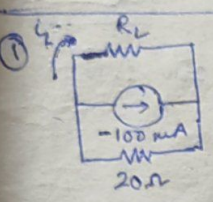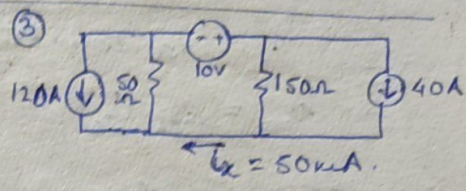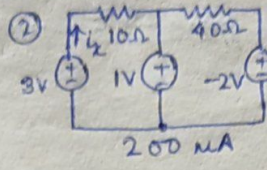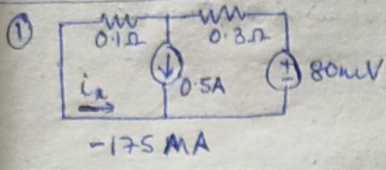- ① 4V voltage source \uparrow 4V 23.7V
- ② 9Ω ... 23.6V
- ③ 600mA \downarrow 23.9V



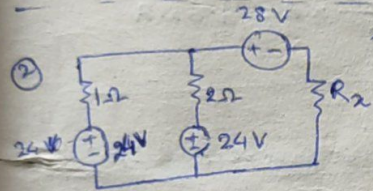
- a) $R_L = 80\Omega$, $i_L = ?$
 - b) transform to prac. voltage source,
 - c) Power supplied by ideal source in each case?
 - d) value of R_L for maxm. power, maxm. power = ?
- 20mA; 20mA; 160mW, 40mW; 20Ω, 50mW.




a) transform both 24V sources to prac. current sources, combine resistors & ideal current sources, transform prac. current source back to prac. voltage source, combine ideal voltage sources.

- a) if $R_x = 2\Omega$, power delivered to $R_x = ?$
 - b) maxm. power delivered to any $R_x = ?$
 - c) what two values of $R_x \rightarrow$ exactly 5W delivered to them?
- 4.5W; 6W; 0.280 & 1.587Ω.

Thevenin's Theorem

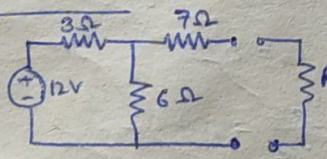

Source transformations

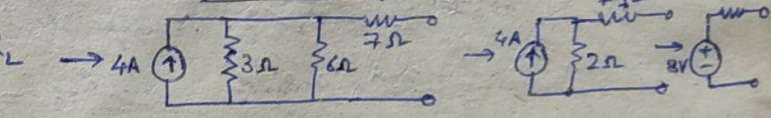


Prob.: ① more complicated the ckt., more the transformations needed.
 ② dependent sources \rightarrow usually inapplicable.

THEVENIN'S THEOREM: Given that any linear ckt., rearrange it in the form of two networks A and B that are connected together by two resistanceless conductors. If either network contains a dependent source, its control variable must be in the same network. Define a voltage V_{oc} as the open ckt. voltage which would appear across the terminals of A if B were disconnected so that no current is drawn from A. Then all the currents and voltages in B will remain unchanged if A is killed (all inde. voltage \rightarrow shorts, & sources \rightarrow open) and an independent voltage source V_{oc} is connected, with proper polarity in series with the dead (inactive) A network.

Disconnect $R_L \therefore V_{oc} = V_{6\Omega} = \frac{6}{9} \times 12V = 8V$.

Kill A; Replace 12V by short. \therefore = Equivalent resistance R_{th}

\therefore Result.

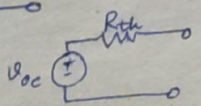


Only restriction → ① linear ckt. — original ckt. composed of A & B.
 ② dependent sources in A have control variables in A.


Dual: Norton's Theorem: Define short ckt. current i_{sc} if B were short ckt. ed so that no voltage is provided by A.
 $\therefore i_{sc}$ connected in parallel with dead A network.

$$V_{oc} = R_{th} i_{sc}$$

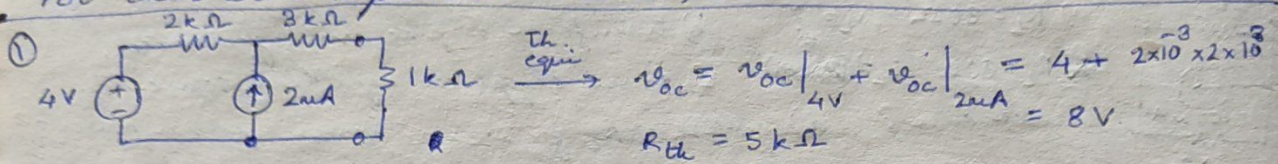For ckt's with dependent sources, evaluate V_{oc} , i_{sc} , then R_{th} .



Norton equi. $i_{sc}|_{4V} + i_{sc}|_{2mA} = \frac{4}{5} mA + 2 \cdot \frac{2}{5} mA = 1.6 mA$

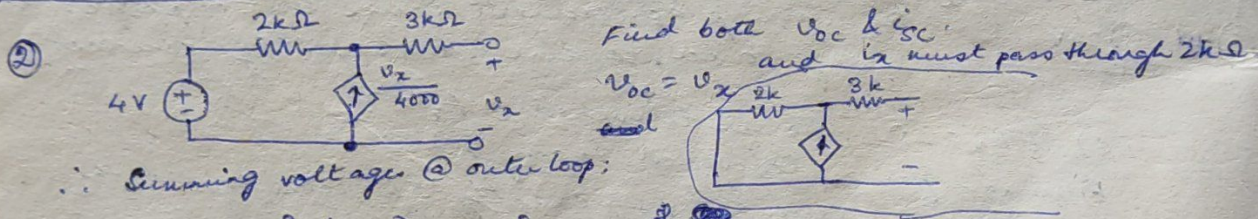


\therefore KVL @ outer loop:

$$-4 + 2 \times 10^3 \times \left(\frac{-v_x}{4000} \right) + 3 \times 10^3 \times 0 + v_x = 0$$

$$\therefore v_x = 8 = V_{oc}$$

i_{sc} , short opp. $v_x = 0$. \therefore dependent $i_x = 0$.
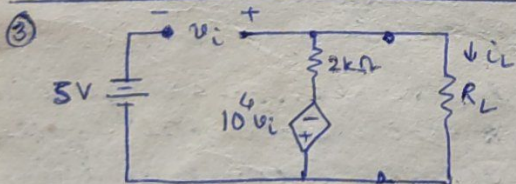
$$\therefore i_{sc} = \frac{4}{5} mA = 0.8 mA \quad \therefore R_{th} = \frac{V_{oc}}{i_{sc}} = 10k\Omega$$



$V_{Loc}, R_L = \infty$
 \therefore no current through $2k\Omega$

$$\therefore V_{Loc} = -10^4 v_i$$

$$v_i = V_{Loc} - 5$$

$$\therefore V_{Loc} = \frac{10^4}{10001} \times 5 \approx 5V$$

i_{Lsc} : R_L by short. KVL for right mesh.


$$10^4 v_i + 2000 i_{Lsc} = 0$$

KVL @ perimeter: $-5 - v_i = 0$

$$\therefore 10^4 (-5) + 2000 i_{Lsc} = 0 \quad \therefore i_{Lsc} = 25A$$

$$\therefore R_{th} = \frac{V_{Loc}}{i_{Lsc}} = 0.2\Omega$$

(4)

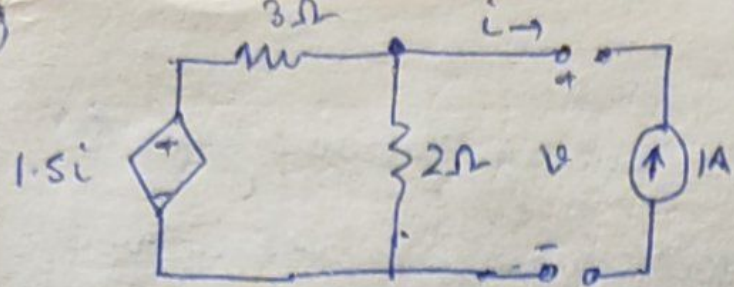
 $V_{oc} = 0$ ∵ no inde. source.

∴ ~~Apply~~ Apply 1-A source externally,
measure resultant voltage, then set

$$R_{th} = \frac{V}{1}$$

$$\therefore i = -1, \quad \frac{V - 1.5i}{3} + \frac{V}{2} = 1. \quad (\text{KCL at node})$$

$$\therefore V = 0.6V$$

$$R_{th} = 0.6\Omega$$

∴ Th. equi. 