


Inductance and Capacitance:

Active element: Capable of furnishing an average power greater than zero to some external device, where the average is taken over an infinite time interval.

Passive element: One that cannot supply an average power that is greater than zero over an infinite time interval.

Practical circuits: Both forcing fns. & responses usually T Varying.

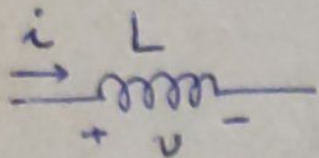Inductor: Capable of ^{storing and} delivering finite amounts of energy — both LLC.
but not unlimited amount of energy
or finite avg. power over infinite time interval



Early 1800s, Oersted — current carrying conductor affected compass needles (produced magnetic field)

Ampere — Mag. field \propto i producing it

Faraday & Henry — changing magnetic field induced voltage in neighbouring circuit.

Math. model:

$$v = L \frac{di}{dt}$$

i produced the mag. field.

Henry (H) — Vs/A

Henry (H) — Vs/A

Physical inductor: winding length of coil wire into coil effectively
 $\rightarrow L$ increases \uparrow causing the mag. field
 + inc. "no." of neighbouring ckt. in which Faraday's voltage may be induced.

$$L = \mu N^2 A / l \quad \text{for long helix of v. small pitch.}$$

A: cross sectional area of l : axial length of helix

N: no. of complete turns of wire

μ : permeability (constant) μ_0 (vacuum \approx air) = $4\pi \times 10^{-7}$ H/m.

① For $i = \text{constant}$ $v = 0$ \therefore short ckt. to dc.

② $i = i_1$ to $i = i_2$ abruptly $\rightarrow v = \infty$ across L also $p = vi = \infty$.




So to avoid ∞ v or p , i is not allowed to jump instantaneously from one value to another.

eg \rightarrow open ckt. a physical inductor through which i flowing causes "arcing" across switch. — stored energy \rightarrow ionizes

air in path of arc.

of automobile ignition where i through spark coil is interrupted by distributor.

3 H inductor.

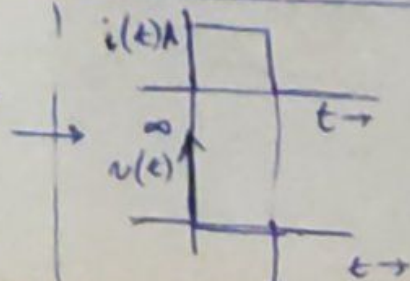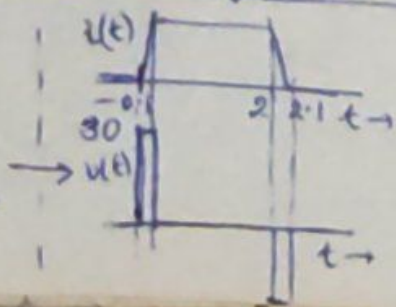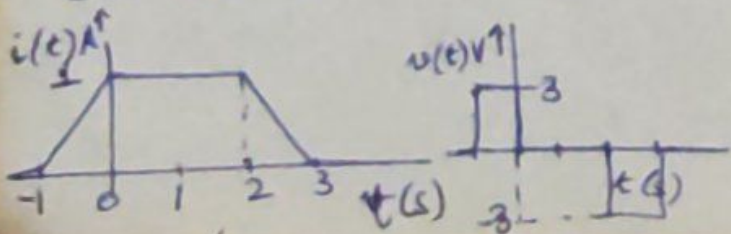

$$i(t) = \frac{1}{L} \int_{t_0}^t v dt + i(t_0) = \frac{1}{L} \int_{-\infty}^t v dt.$$

So say if $L = 2H$, $v(t) = 6 \cos 5t$, then $i(t) = 0.6(\sin 5t - \sin 5t_0) + i(t_0)$.

Say if i is $1A$ at $t = -\pi/2$ s $\Rightarrow t_0 = -\pi/2$, $i(t_0) = 1$.

$$\therefore i(t) = 0.6 \sin 5t + 1.6.$$

$p = v i = L i \frac{di}{dt}$ W \rightarrow $\begin{cases} \frac{di}{dt} +ve, p+ve \rightarrow \text{absorbed} \\ \frac{di}{dt} -ve, p-ve \rightarrow \text{released} \end{cases}$ \therefore need for $v = -L \frac{di}{dt}$


$$\text{energy } w_L = \int_{t_0}^t p dt = \int_{t_0}^t L i \frac{di}{dt} dt = \int_{t_0}^t L i di = \frac{L i^2}{2} \Big|_{t_0}^t \text{ J.}$$

$$w_L = \frac{1}{2} L i^2$$

Assuming energy = 0 at time $t = t_0$
 $\Rightarrow i = 0$

\therefore Whenever there is finite i through inductor, energy is stored.
 \therefore Power is delivered to & recovered from ideal inductor - all energy may be recovered.

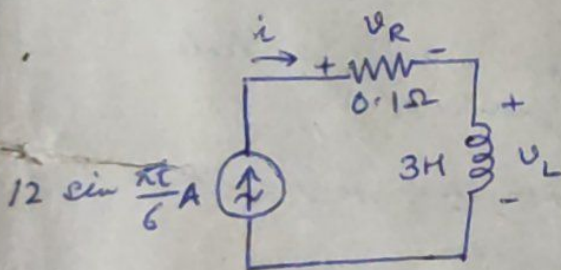Practical L : associated R \therefore lossless storage / recovery not possible



$$v_R = iR = 1.2 \sin \frac{\pi t}{6} \text{ V.}$$

$$v_L = L \frac{di}{dt} = 3 \cdot \frac{d}{dt} (12 \sin \frac{\pi t}{6}) = 6\pi \cos \frac{\pi}{6} t \text{ V}$$

$$w_L = \frac{1}{2} L i^2 = 216 \sin^2 \frac{\pi}{6} t \text{ J}$$

$$\sin^2 \theta = \frac{1 - \cos 2\theta}{2}$$

\therefore period: 2θ .

$$2 \cdot 2(\pi/6) = 2\pi$$

$\therefore t=0, w_L=0$; $t=3, w_L=216$. and so on.


power dissipated in resistor = $p_R = i^2 R = 14.4 \sin^2 \frac{\pi}{6} t$ W

$$\therefore w_R = 14.4 \int_0^6 \sin^2 \frac{\pi}{6} t dt \quad \text{in 6-s}$$

$$= \frac{14.4}{2} \int_0^6 (1 - \cos \frac{\pi}{3} t) dt = 43.2 \text{ J.} = 20\% \text{ of max. stored energy.}$$

For $L = 100 \mu H$ typically 2-3% heating losses.

Capacitor :

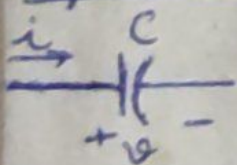

$$i = C \frac{dv}{dt}$$

farad (F) : C/V or AS/V

Physically: two conducting surfaces on which charge may be stored, separated by thin insulating layer having very large resistance.

Assuming $R = \infty$, no path for charges to combine within capacitor plates or cap. plates. ^{equal & opp.}

Say i source connected to C so positive i into one plate of capacitor and out through other. — equal currents. In interior of capacitor, +ve charges accumulate on +ve plate as $i = \frac{dq}{dt}$


Maxwell hypothesized a "displacement i " present whenever i or v varies with time s.t. conduction current at leads = $i_{disp} = i = C \frac{dv}{dt}$.

Physical model: $C = \epsilon A/d$ ϵ : permittivity $\epsilon_0 = 8.854 \text{ pF/m}$
 A : area of c.s. d : plate sepr. distance

- ① open circuit to dc since constant voltage \Rightarrow ^{requires} zero current.
 ② sudden jump in voltage req. infinite i

$$v(t) = \frac{1}{C} \int_{t_0}^t i dt + v(t_0) = \frac{1}{C} \int_{-\infty}^t i dt$$

$$\therefore q = Cv$$

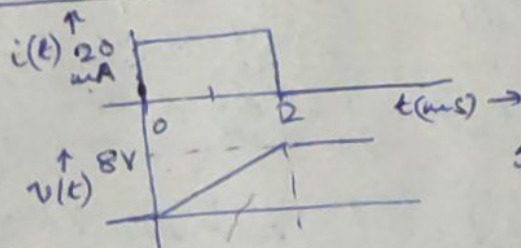


5 μF capacitor

$$\therefore v(t) = \begin{cases} 0 & t \leq 0 \\ 4000t & 0 \leq t \leq 2 \text{ ms} \\ 8 & t \geq 2 \text{ ms} \end{cases}$$

$$p = vi = Cv \frac{dv}{dt}$$

$$w_c = \frac{1}{2} Cv^2$$

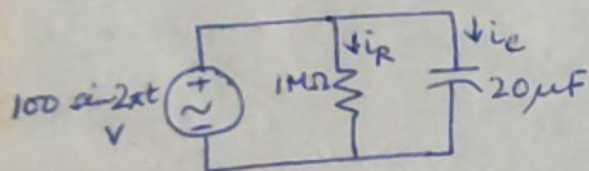

// resistor: resis. of insulator/dielectric bet. plates of cap.

$$i_R = \frac{v}{R} = 10^{-4} \sin 2\pi t \text{ A}$$

$$i_C = C \frac{dv}{dt} = 4\pi \times 10^{-3} \cos 2\pi t \text{ A}$$


$$w_c = \frac{1}{2} Cv^2 = 0.1 \sin^2 2\pi t \text{ J}$$

$$t=0 \quad w_c = 0$$

$$t=1/4 \text{ s} \quad w_c = 0.1 \text{ J}$$

$$w_R = \int_0^{0.5} p_R dt = 2.5 \text{ mJ} \rightarrow 2.5\% \text{ of max. stored energy of C. is lost in the process of storing \& removing the energy.}$$


Inductance and capacitance combinations:

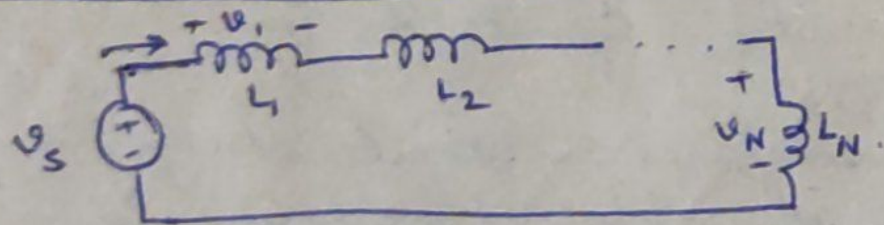

$$v_s = v_1 + \dots + v_N$$

$$= L_1 \frac{di}{dt} + \dots + L_N \frac{di}{dt}$$
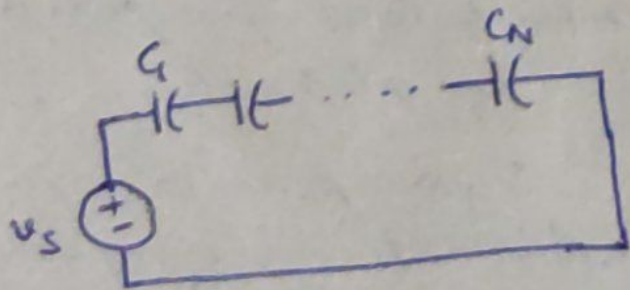
$$= \sum_n L_n \frac{di}{dt} = L_{eq} \frac{di}{dt}$$





$$v_s = v_1 + \dots + v_N$$

$$= \sum_n \left[\frac{1}{C_n} \int_{t_0}^t i dt + v_n(t_0) \right]$$


$$= \sum_n \frac{1}{C_n} \int_{t_0}^t i dt + v_s(t_0)$$

$$\therefore \frac{1}{C_{eq}} = \frac{\sum_n (1/C_n)}{n}$$

~ def for || ckt.

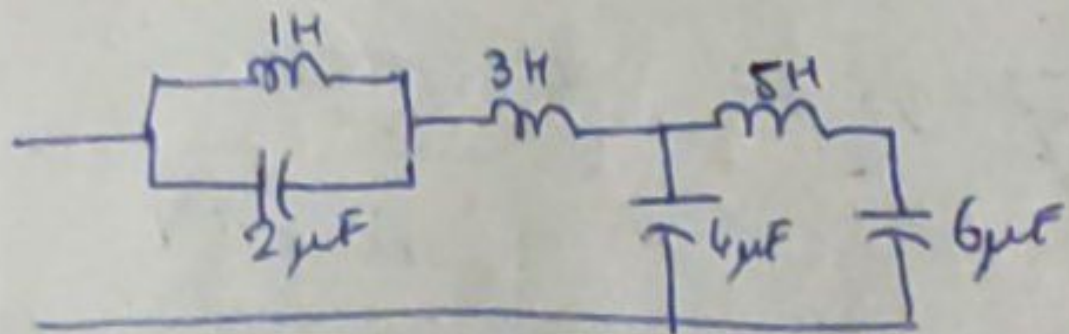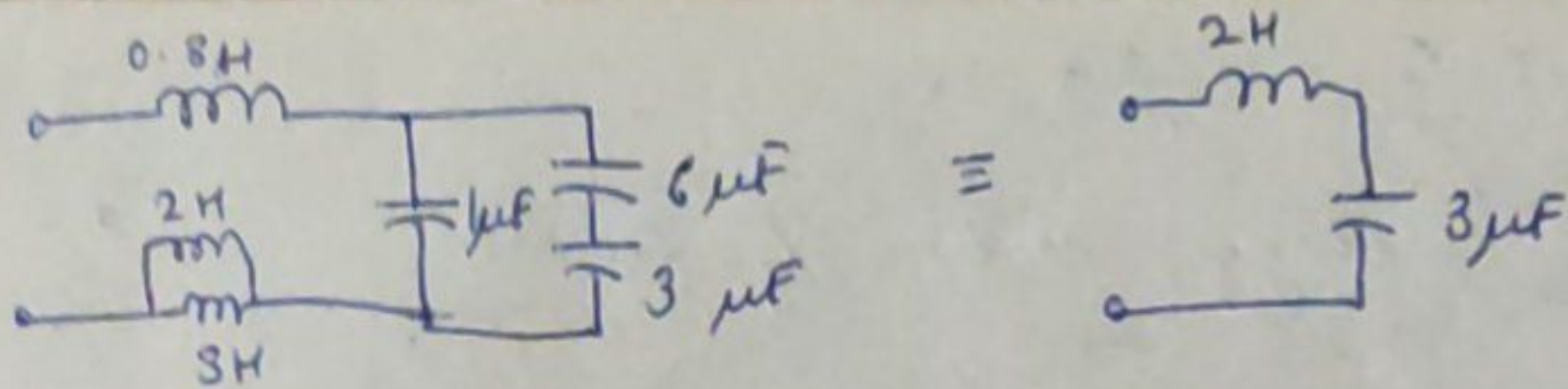

no series/|| combinations possible

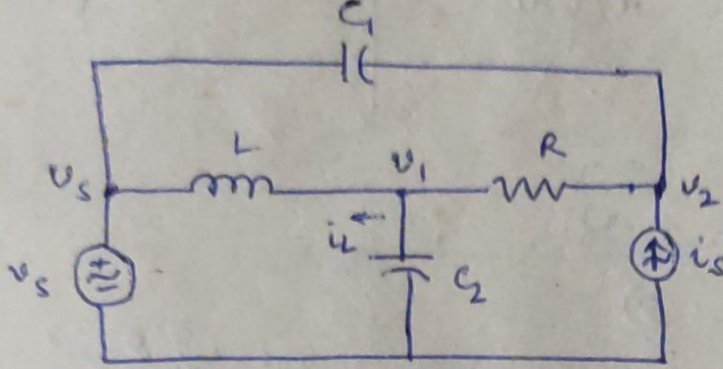

KCL at ①,

$$\frac{1}{L} \int_{t_0}^t (v_1 - v_s) dt + i_2(t_0) + \frac{v_1 - v_2}{R} + C_2 \frac{dv_1}{dt} = 0.$$

KCL at ②,

$$C_1 \frac{d(v_2 - v_1)}{dt} + \frac{v_2 - v_1}{R} - i_s = 0.$$


$$\therefore \frac{v_1}{R} + C_2 \frac{dv_1}{dt} + \frac{1}{L} \int_{t_0}^t v_1 dt - \frac{v_2}{R} = \frac{1}{L} \int_{t_0}^t v_s dt - i_2(t_0).$$

$$-\frac{v_1}{R} + \frac{v_2}{R} + C_1 \frac{dv_2}{dt} = C_1 \frac{dv_s}{dt} + i_s$$

→ INTEGRO DIFFERENTIAL EQNS.

- ① v_s - source voltage enters as integral as well as derivative (but not as v_s . → R not connected to it)
- ② $i_2(t_0)$ → acts as a (constant) source current at node ①.
- ③ For sinusoidal forcing fns. v_s & i_s , will be possible to define impedance / admittance for each of the 3 passive elements.

Ques :

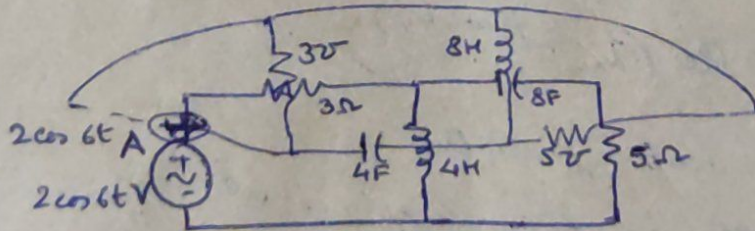

$$3i_1 + 4 \frac{di_1}{dt} - 4 \frac{di_2}{dt} = 2 \cos 6t \quad \text{Ⓐ}$$

$$-4 \frac{di_1}{dt} + 4 \frac{di_2}{dt} + \frac{1}{8} \int_0^t i_2 dt + 5i_2 = -10.$$

STAR DELTA CONVERSION

13 Refer to the network shown in Fig. 3-30 and find (a) R_{eq} if each element is a 10- Ω resistor; (b) L_{eq} if each element is a 10-H inductor; and (c) C_{eq} if each element is a 10-F capacitor.

14 In Fig. 3-31, let elements A, B, C, and D be (a) 1-H, 2-H, 3-H, and 4-H inductors, respectively, and find the input inductance with $x-x'$ first open-circuited and then short-circuited; (b) 1-F, 2-F, 3-F, and 4-F capacitors, respectively, and find the input capacitance with $x-x'$ first open-circuited and then short-circuited.

Figure 3-30

See Prob. 13.


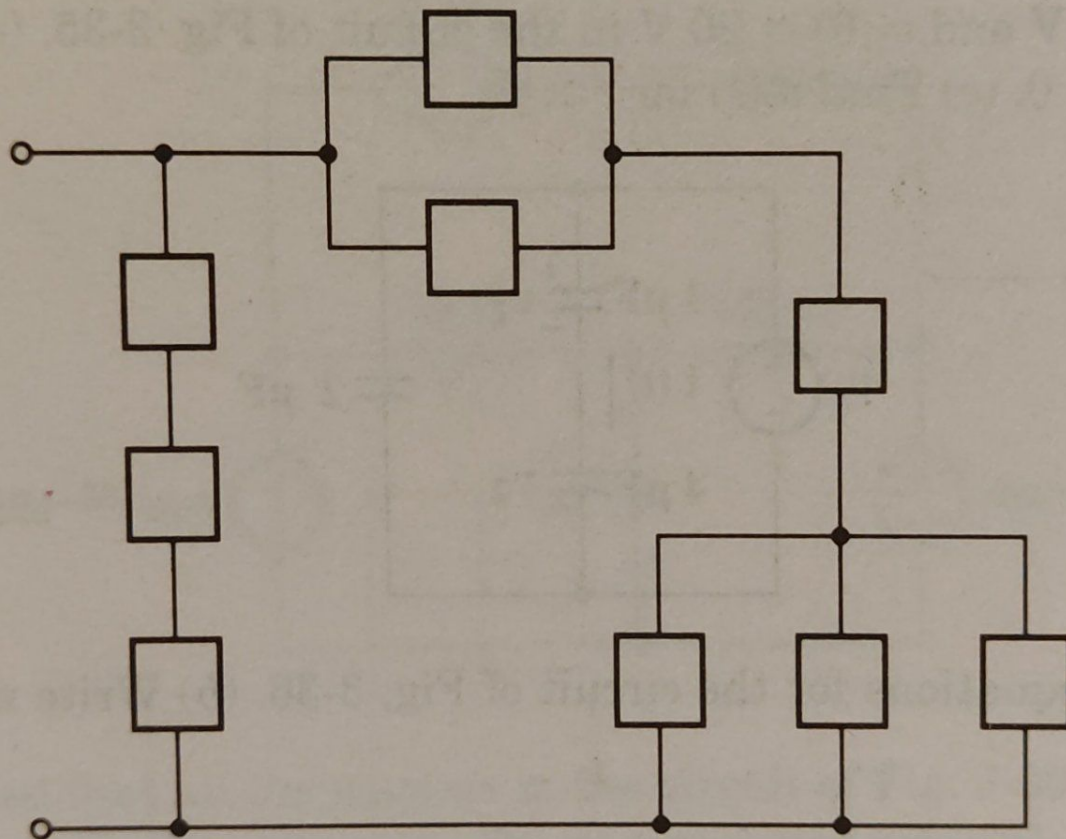


Figure 3-31


See Prob. 14.

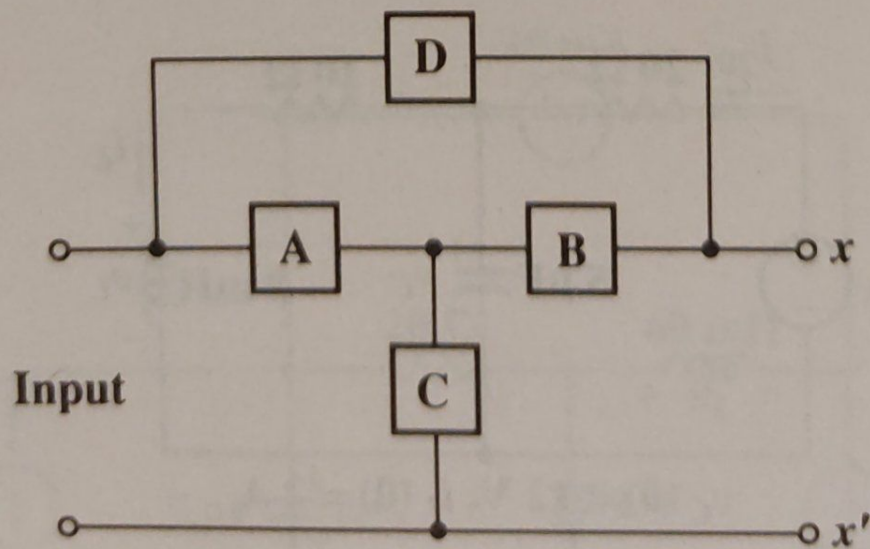

- 20 (a) Write nodal equations for the circuit of Fig. 3-36. (b) Write mesh equations for the same circuit.

Figure 3-36

See Probs. 20 and 21.

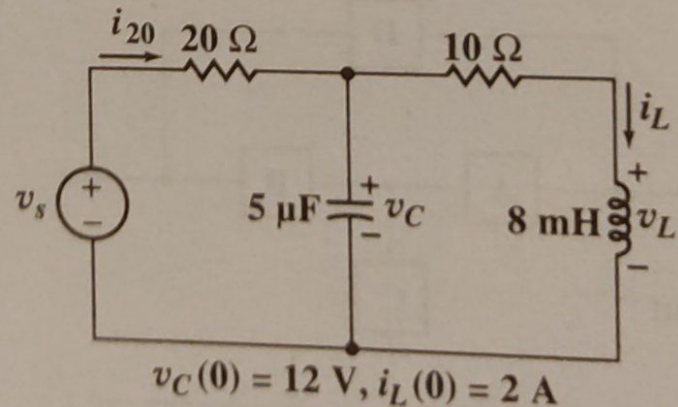

- 21 (a) Draw the exact dual of the circuit shown in Fig. 3-36. Specify the dual variables and the dual initial conditions. (b) Write nodal equations for the dual circuit. (c) Write mesh equations for the dual circuit.