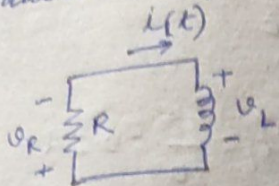


Simple RL and RC circuits:

(A)

A Source Free ckt.: only stored energy considered.

Natural response / Transient response / Complementary fr.



$$v_R + v_L = Ri + L \frac{di}{dt} = 0 \Rightarrow \frac{di}{i} = -\frac{R}{L} dt \dots$$


Assume $i(t) = Ae^{s_1 t}$

$$\therefore As_1 e^{s_1 t} + \frac{R}{L} A e^{s_1 t} = 0 \Rightarrow \left(s_1 + \frac{R}{L}\right) A e^{s_1 t} = 0$$

\therefore Possible soln. $s_1 = -R/L$. $\therefore A = 0$ or $s_1 = -\infty \Rightarrow$ no response.

$$\therefore i(t) = A e^{-Rt/L} \quad \text{at } t=0, i = I_0 \therefore A = I_0 \Rightarrow i(t) = I_0 e^{-Rt/L}$$
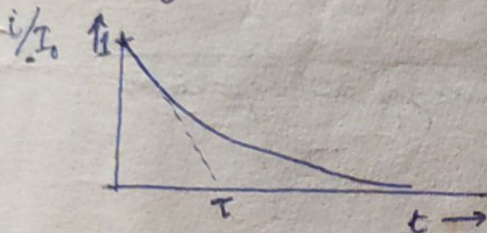
$$W_R = \int_0^{\infty} P_R dt = I_0^2 R \int_0^{\infty} e^{-2Rt/L} dt = \frac{1}{2} L I_0^2 \quad \text{dissipated through resistor}$$



$$\text{initial rate of decay} = \left. \frac{d}{dt} \frac{i}{I_0} \right|_{t=0} = -R/L$$

$$\therefore \text{ini rate of decay} = -(-R/L) = R/L$$


$$\tau : \text{Time constant} = L/R$$

\therefore time taken for i/I_0 to drop from unity to zero assuming constant rate of decay. $\boxed{\frac{R}{L} \tau = 1}$

$$i(\tau) = e^{-1} I_0 = 0.368 I_0$$

3 to 5 time constants later $\rightarrow i(t) \ll I_0$ ($0.0498 I_0 \rightarrow 0.0067 I_0$)

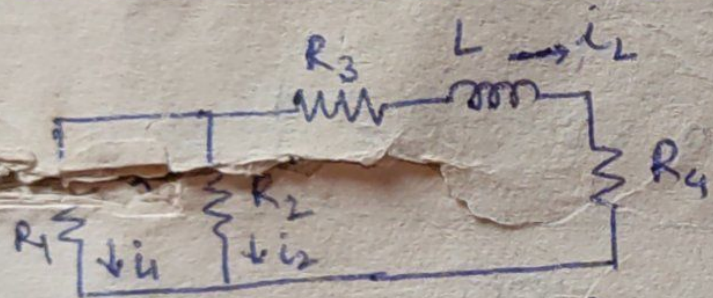Larger $L/R \Rightarrow$ response decays more slowly \rightarrow greater energy storage and/or power flowing into R less for same I_0 . \therefore time more.



$$R_{eq} = R_3 + R_4 + \frac{R_1 R_2}{R_1 + R_2}$$

$$\tau = L/R_{eq}$$

$$i_L = i_L(0) e^{-t/\tau}$$

Say req. $i_2 = \left(\frac{R_1}{R_1 + R_2} \right) (-i_L)$


Say know $i_1(0^+) \therefore i_2(0^+) = i_1(0^+) \cdot \frac{R_1}{R_2}$

$$\therefore i_2(0^+) = - [i_1(0^+) + i_2(0^+)] = - \frac{R_1 + R_2}{R_2} i_1(0^+)$$

$$\therefore i_2 = i_1(0^+) \cdot \frac{R_1}{R_2} e^{-t/\tau}$$

OR Say $i_2 = A e^{-t/\tau}$, $\tau = L/R_{eq}$
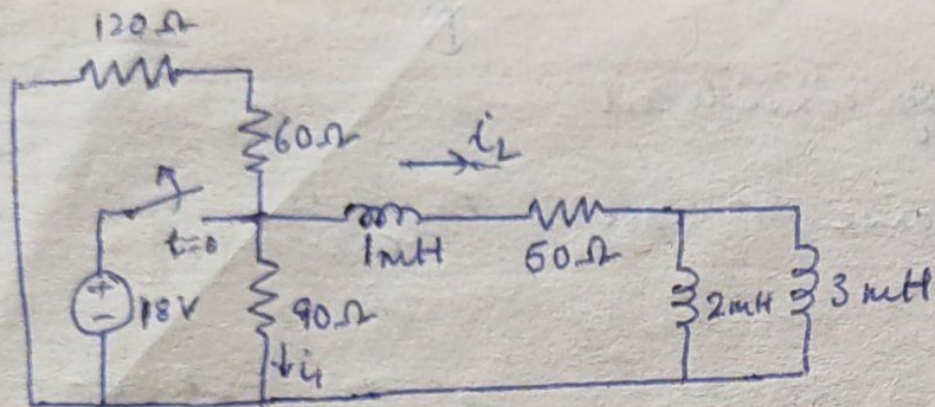
$$i_2(0^+) = A = i_1(0^+) \cdot \frac{R_1}{R_2}$$



$$\tau = \frac{L_{eq}}{R_{eq}} = \frac{2.2 \times 10^{-3}}{110} = 20 \mu s.$$

$$\therefore i_L = A e^{-50000t}$$

For $t < 0$ (source connected), $i_L = \frac{18}{50} = 0.36 A$; $i_1 = \frac{18}{90} = 0.2 A$

$t = 0^+$ $i_L = 0.36 A$ (through inductor cannot change instantaneously).

$$i_1(0^+) = -i_L(0^+) \cdot \frac{180}{270} \quad (\text{Current division}) = -0.24 A$$

$$\therefore \left. \begin{aligned} i_L &= 0.36 & t < 0 \\ &= 0.36 e^{-50000t} & t > 0 \end{aligned} \right\} \quad \left. \begin{aligned} i_1 &= 0.2 & t < 0 \\ &= -0.24 e^{-50000t} & t > 0 \end{aligned} \right\}$$

Current through inductors 2 & 3 mH cons. current at $t \rightarrow \infty$.

$$i_2 = A_1 + A_2 e^{-t/\tau}$$




$v(0) = v_0$ → initial stored energy in capacitor.

$$C \frac{dv}{dt} + \frac{v}{R} = 0. \quad (\text{node})$$

$$v(t) = v(0) e^{-t/RC} = v_0 e^{-t/RC}. \quad \tau = RC.$$

Larger R & C → slower dissipation. ∴ $\left(\frac{v^2}{R}\right)$ → given voltage less dissipation.

Ex (Prob 6.27)

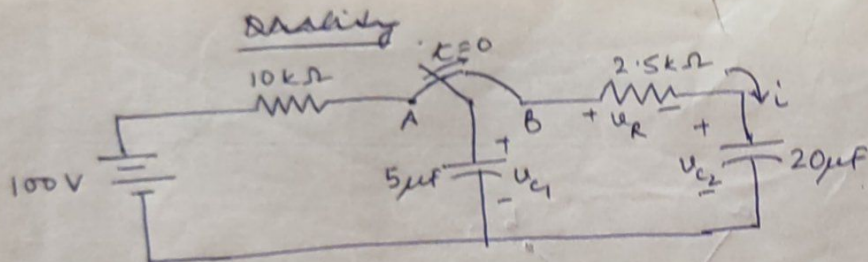

$$\textcircled{3} R_{eq} = 2.5 \times 10^3 \Omega$$

$$C_{eq} = 4 \frac{20 \times 5 \times 10^{-6} \times 10^{-6}}{25 \times 10^{-6}} = 4 \times 10^{-6} \text{ F}$$

$$\therefore \tau = R_{eq} C_{eq} = \frac{1}{100} \text{ s.}$$

$$\textcircled{5} v_{C1}(t) = \frac{1}{C_1} \int (-i) dt + K.$$

$$= \frac{10^6}{5} \times \left(\frac{-4}{100}\right) \cdot \left(\frac{1}{-100}\right) \cdot e^{-100t} + K. \quad \text{why}$$

$$\text{At } t=0^+, \quad 100 = 80 e^{-100t} \Big|_{0^+} + K = 80 + K.$$

$$\therefore K = 20$$

⑦ Energy balance: Initial

$$\frac{1}{2} C_1 v_{C1}^2(0^-) + \frac{1}{2} C_2 v_{C2}^2(0^-) = \frac{1}{2} \times 25 \times 10^{-6} \times 10^6 + 0 = 25 \text{ mJ} + 0 \text{ mJ}.$$

$$\text{Final dissipated: } \frac{1}{2} C_1 v_{C1}^2 + \frac{1}{2} C_2 v_{C2}^2 + \int_0^{\infty} \frac{v^2}{R} dt = \frac{1}{2} \times 25 \times 10^{-6} \times (20)^2 + \frac{10^6}{2.5 \times 10^3} \int_0^{\infty} e^{-200t} dt$$

$$= 5 \times 10^{-3} + \frac{41}{200} = 5 \times 10^{-3} + 20 \times 10^{-3}$$

$$= 25 \text{ mJ.}$$

$$\textcircled{1} v_{C1}(0^-) = 100 \text{ V (open ct.)}$$

$$v_{C2}(0^-) = 0 \text{ V}$$

$$\textcircled{2} v_{C1}(0^+) = 100 \text{ V}$$

$$v_{C2}(0^+) = 0 \text{ V}$$

$$v_R(0^+) = 100 \text{ V.}$$

$$\textcircled{4} i(t) = \frac{v_R(t)}{R} = \frac{100 e^{-100t}}{2.5 \times 10^3} = 0.04 e^{-100t} \text{ A.}$$

$$\textcircled{6} v_{C2}(t) = 20 - 20 e^{-100t}$$


Note at $t=\infty$, $v_{C2}(\infty) = 20$.

why $v_{C1}(\infty) = 20$.

TANK CIRCUIT



Application of Unit Step Forcing Function:

Forced response

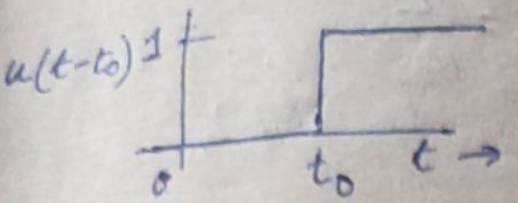


$$u(t-t_0) = \begin{cases} 0 & t < t_0 \\ 1 & t > t_0 \end{cases}$$

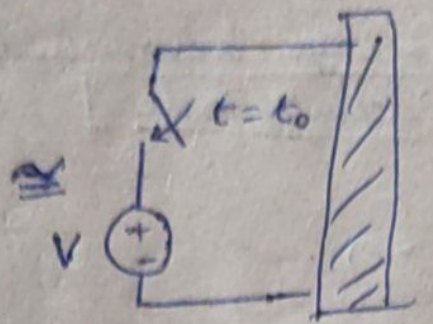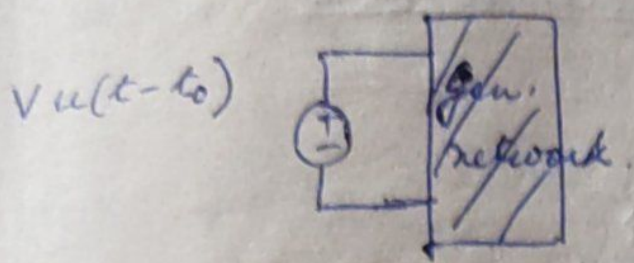
Unit step ^{fn.}
 * Not necessarily of $u(x-x_0)$ say




i.e. may not be met.

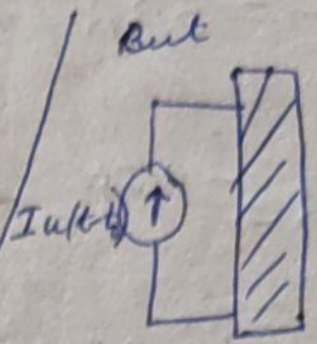



But

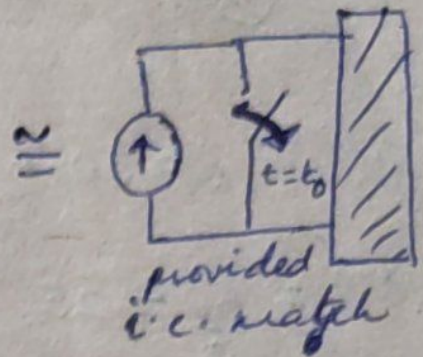

Note:

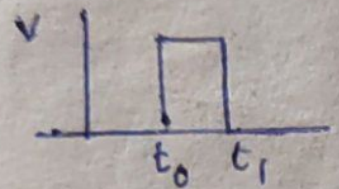

$$= V [u(t-t_0) - u(t-t_1)]$$

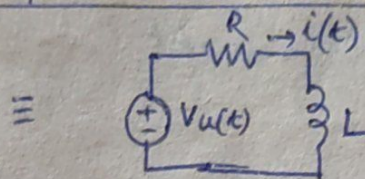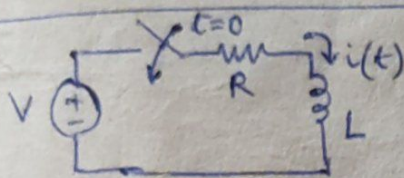

KVL

$$Ri + L \frac{di}{dt} = Vu(t)$$

$$i(t) = 0 \quad t < 0$$

$$t > 0 \quad Ri + L \frac{di}{dt} = V \Rightarrow L \frac{di}{dt} + Ri = V$$

Form $\frac{di}{dt} + Pi = Q \Rightarrow di + P i dt = Q dt$

Multiply by $e^{\int P dt} = e^{Pt}$ [P being constant]

$$\therefore d(i e^{Pt}) = Q e^{Pt} dt$$

Integrate \int & transpose $i = e^{-Pt} \int Q(t) e^{Pt} dt + A e^{-Pt}$

↓
Particular sol.
or forced response i_f

→ Natural response i_n

For constant Q, $i_f = \frac{Q}{P}$


$$\therefore i(t) = \frac{Q}{P} + A e^{-Pt} = i_f + i_n$$

$$\therefore i(t) = \frac{V}{R} + A e^{-Rt/L}$$

$$0 = A + \frac{V}{R} \therefore A = -\frac{V}{R}$$


* (not necessarily
ini. value of
response).
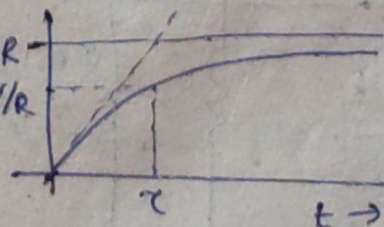
$$\therefore i(t) = \frac{V}{R} (1 - e^{-Rt/L}) u(t)$$



Finally as R & L in series with battery \therefore L short to dc $\therefore V/R = i(\infty)$

Ex

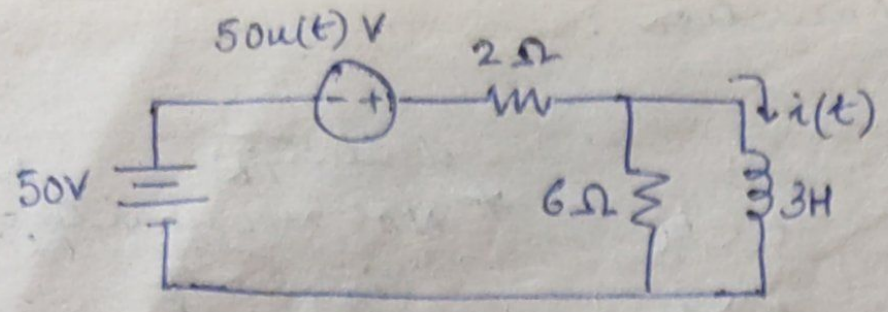


$$i = i_f + i_n$$

$$i_n = A e^{-t/2} \quad \therefore \tau = \frac{L}{R_{eq}} = \frac{3}{1.5} = 2$$

$t > 0.$

$(6/1/2)$


$i_f =$  $\frac{100}{2} = 50A$ [no voltage across inductor at $t=0$. \therefore short to de]

$\therefore i = 50 + A e^{-0.5t} \quad t > 0$


$i_L(0^-) = \frac{50}{2} = 25. \quad \therefore 25 = 50 + A \quad \therefore A = -25.$

$\therefore i = 50 - 25 e^{-0.5t} \text{ A } t > 0$
 $= 25 \text{ A} \quad t < 0.$

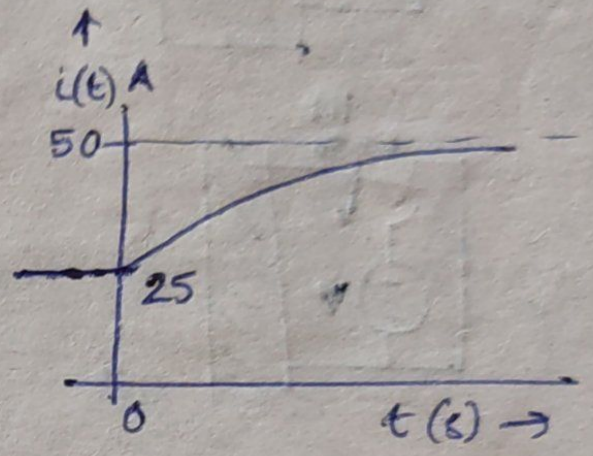or $i(t) = 25 + 25(1 - e^{-0.5t})u(t) \text{ A}$



Say apply

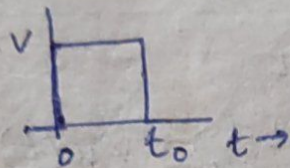

to RL series ckt.

$$v(t) = V u(t) - V u(t - t_0)$$

$$i(t) = i_1(t) + i_2(t)$$



$$i_1(t) = \frac{V}{R} (1 - e^{-Rt/L}) \quad t > 0$$

$$i_2(t) = -\frac{V}{R} (1 - e^{-R(t-t_0)/L}) \quad t > t_0$$

$$\therefore i(t) = \frac{V}{R} (1 - e^{-Rt/L}) \quad 0 < t < t_0$$


$$= \frac{V}{R} (1 - e^{-Rt/L}) - \frac{V}{R} (1 - e^{-R(t-t_0)/L}) \quad t > t_0$$
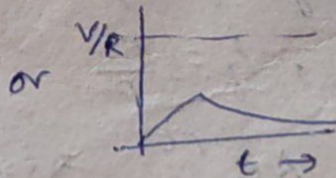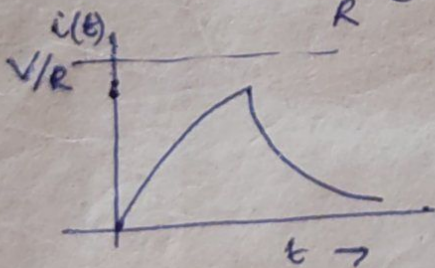
$$= \frac{V}{R} e^{-Rt_0/L} (e^{Rt_0/L} - 1)$$



depending on τ

Ex RC ckt.

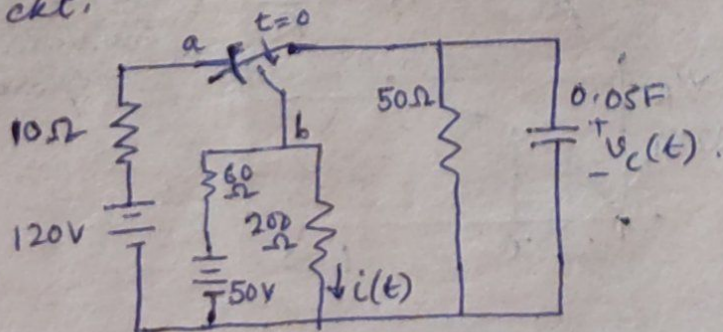

$$v_c(0^+) = v_c(0^-) = \frac{50}{50+10} \times 120 = 100V$$

$$v_c = v_{cf} + v_{cn}$$

$$v_{cn} = A e^{-t/Req C}$$

$$Req = \frac{1}{\frac{1}{50} + \frac{1}{200} + \frac{1}{60}} = 24 \Omega$$


$$\therefore v_{cn} = A e^{-t/1.2}$$

$$\therefore v_c = (20 + A e^{-t/1.2}) V$$

$$v_{cf} = \frac{50 \times (50 \times 200) / 250}{60 + \frac{50 \times 200}{250}} = 20V$$

So $100 = 20 + A \quad \therefore A = 80$

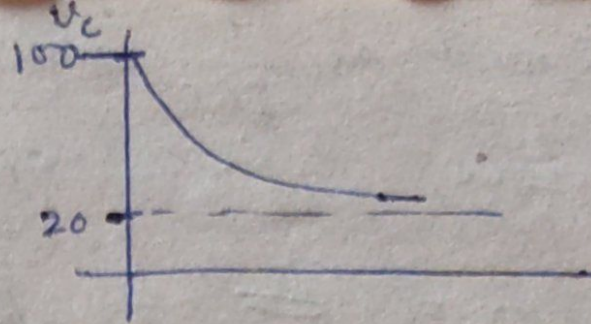$\therefore v_c = 20 + 80 e^{-t/1.2} \quad V \quad t > 0$



say req. $i(t)$

$i(0^-) = \frac{50}{260} A = 0.192 A$

$i_b = \frac{50}{200+50} \times \frac{50}{60 + \frac{50 \times 200}{250}} = 0.1 A$

$i = 0.1 + A e^{-t/1.2}$

req. $i(0^+) \rightarrow v_c(0^+) = 100 V \quad i(0^+) = \frac{100}{200} A = 0.5 A$ (all with cap. ^{200 Ω resistance})

$\therefore A = 0.4$ ~~$0.5 + 0.192 = 0.1 + A$
 $A = 0.592?$~~

$\therefore i(t) = 0.192 A \quad t < 0$

$= 0.1 + 0.4 e^{-t/1.2} \quad t > 0$

or $i(t) = 0.192 + (-0.092 + 0.4 e^{-t/1.2}) u(t) A$

