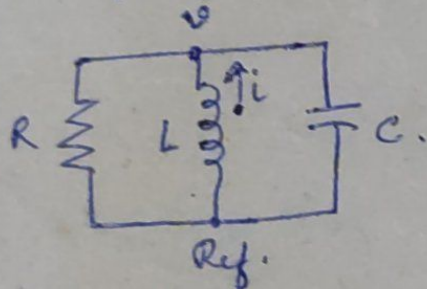


RLC circuits

Second order ~~ckt~~ system. \therefore two arbit. constants to be evaluated.

Source free parallel ckt.



\equiv physical inductor + capacitor in parallel.

— analogous to mass-spring-damper system
— vertical motion of automobile,
~~pendulum (torsional or simple)~~

— useful in communications networks
— part of electronic amplifiers in radio receivers. — frequency selectivity.

— also in multiplexing filters, harmonic suppression filters etc.

$$\frac{v}{R} + \frac{1}{L} \int_{t_0}^t v dt - i(t_0) + C \frac{dv}{dt} = 0. \quad i(0^+) = I_0, \quad v(0^+) = V_0.$$

Differentiating,

$$C \frac{d^2 v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v = 0. \quad \dots \quad (a)$$

Assume $v(t) = A e^{st}$

$$\therefore A e^{st} \left(C s^2 + \frac{1}{R} s + \frac{1}{L} \right) = 0. \quad \Rightarrow \quad C s^2 + \frac{1}{R} s + \frac{1}{L} = 0.$$

CHARACTERISTIC EQN. / AUXILIARY EQN.

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$v = v_1 + v_2 = A_1 e^{s_1 t} + A_2 e^{s_2 t}$ is the form of the natural response.

$s_{1,2}$ as well as $\frac{1}{2RC}$ and $\frac{1}{\sqrt{LC}}$ must have units s^{-1} for s, t to be dimensionless. \therefore → FREQUENCIES

$$\omega_0 = \frac{1}{\sqrt{LC}} \triangleq \text{RESONANT FREQUENCY}$$

$$\alpha = \frac{1}{2RC} \triangleq \text{EXPONENTIAL DAMPING COEFFICIENT OR NEPER FREQUENCY}$$

s_1, s_2 : COMPLEX FREQUENCIES.

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \quad ; \quad \alpha = \frac{1}{2RC} \quad , \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\zeta = \frac{\alpha}{\omega_0} \triangleq \text{DAMPING RATIO} = \frac{1}{2R} \sqrt{\frac{L}{C}} \quad A_1, A_2 \text{ obtained from i.c.s.}$$

(zeta)

Note : $i_{L,R,C}$ are also of similar forms

$\zeta >, =, < 1$ determines 3 kinds of responses.


Overdamped || RLC ckt. : $\alpha > \omega_0 \Rightarrow \frac{1}{2RC} > \frac{1}{\sqrt{LC}} \Rightarrow LC > 4R^2C^2$

$\therefore s_{1,2}$ both real and $\sqrt{\alpha^2 - \omega_0^2} < \alpha$

$\therefore s_1, s_2 < 0$

$\therefore v(t) \rightarrow A_1 e^{s_1 t} \rightarrow 0$ as $t \rightarrow \infty$

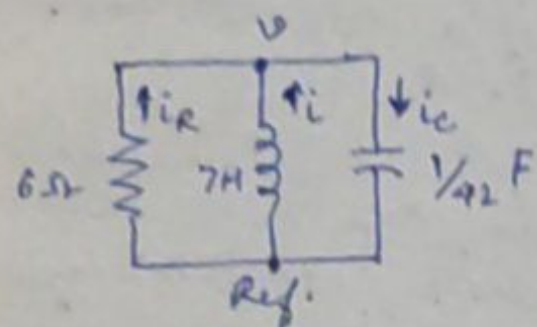(s_2 being more negative, $A_2 e^{s_2 t}$ dies out faster)



$$v(0) = 0, i(0) = 10 \text{ A}$$

$$\alpha = 3.5 \text{ s}^{-1}, \omega_0 = \sqrt{6} \text{ s}^{-1}, s_1 = -1 \text{ s}^{-1}, s_2 = -6 \text{ s}^{-1}$$

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\dots \textcircled{1} = A_1 e^{-t} + A_2 e^{-6t}$$

$$v(0) = 0 = A_1 + A_2$$


Take derivative of $\textcircled{1}$, $\therefore \frac{dv}{dt} = -A_1 e^{-t} - 6A_2 e^{-6t}$

$$\therefore \left. \frac{dv}{dt} \right|_{t=0} = -A_1 - 6A_2$$

$$i_C = C \frac{dv}{dt} \quad \therefore \frac{i_C(0)}{C} = \left. \frac{dv}{dt} \right|_0 = \frac{i(0) + i_R(0)}{C} = \frac{i(0)}{C} = 420 \text{ V/s}$$

$$\therefore A_1 = 84, A_2 = -84$$
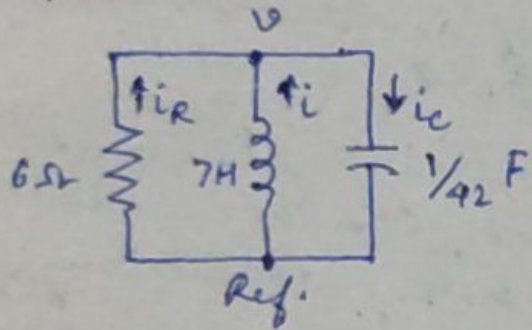
$$\therefore v(t) = 84 (e^{-t} - e^{-6t})$$



$$v(0) = 0, \quad i(0) = 10 \text{ A}$$

$$\alpha = 3.5 \text{ s}^{-1}, \quad \omega_0 = \sqrt{6} \text{ s}^{-1}, \quad s_1 = -1 \text{ s}^{-1}, \quad s_2 = -6 \text{ s}^{-1}$$

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \dots \quad \textcircled{1} = A_1 e^{-t} + A_2 e^{-6t}$$

$$v(0) = 0 = A_1 + A_2$$

Take derivative of $\textcircled{1}$, $\therefore \frac{dv}{dt} = -A_1 e^{-t} - 6A_2 e^{-6t}$

$$\therefore \left. \frac{dv}{dt} \right|_{t=0} = -A_1 - 6A_2$$

$$i_C = C \frac{dv}{dt} \quad \therefore \frac{i_C(0)}{C} = \left. \frac{dv}{dt} \right|_0 = \frac{i(0) + i_R(0)}{C} = \frac{i(0)}{C} = 420 \text{ V/s}$$

$$\therefore A_1 = 84, \quad A_2 = -84$$

$$\therefore v(t) = 84 (e^{-t} - e^{-6t})$$


Note:
 $\textcircled{1} \tau_1 = 1 \text{ s}, \quad \tau_2 = \frac{1}{6} \text{ s}$

$\textcircled{2} \Rightarrow \frac{v}{v_0} = e^{-t} - e^{-6t}$ \therefore Both exponential terms with unity amp. but 2nd term dies out faster

$\textcircled{3}$ Total response never negative $\textcircled{3}$ as $t \rightarrow \infty$, both $\rightarrow 0$.

$\textcircled{3}$ Eqn. $\textcircled{2}$ yields maxima, after differentiating, $0 = -e^{-t_m} + 6e^{-6t_m}$
 $\ln[e^{-t_m}] = \ln[6e^{-6t_m}] \quad \therefore \frac{\ln 6}{5} = t_m = 0.358 \text{ s}, \quad v(t_m) = 48.9 \text{ V}$

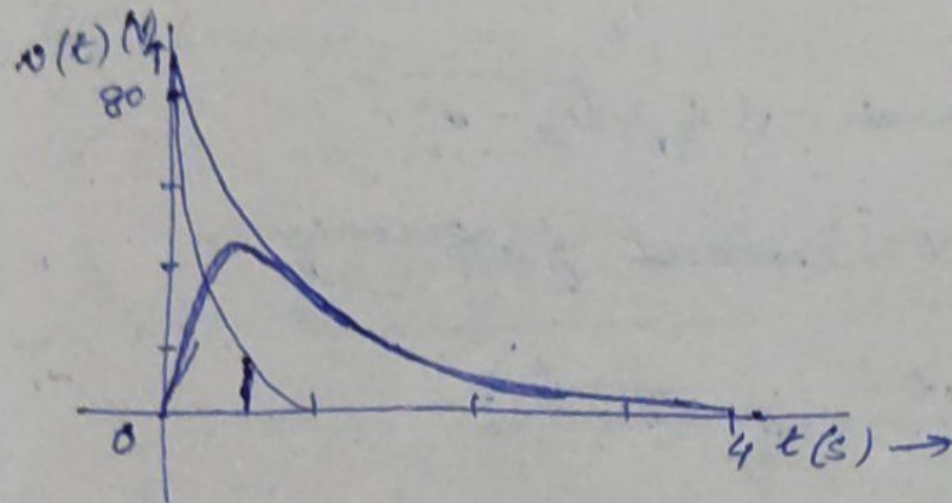④ Plot by taking difference of two curves.



⑤ Settling time (t_s): length of time it takes for transient part of response to die out.

→ 1% or 2% or even 5% level.

when $v \leq x\%$ of 10_{out} .

For 1% → $t_s = 5.15s$

Critical damping: $\alpha = \omega_0$ Practically impossible.

$$\therefore LC = 4R^2C^2$$

$$\therefore R = \frac{\sqrt{L}}{2C}$$

Say change R to obtain critical damping $\therefore R = 7\sqrt{6}/2 \Omega$.

$$\therefore \alpha = \omega_0 = \sqrt{6}, \quad s_{1,2} = -\sqrt{6}.$$

$\therefore v(t) = A e^{-\sqrt{6}t}$ \longrightarrow but then only one i.c. would be satisfied. $\therefore v(t)$ has another form.

Note: For $\alpha = \omega_0$, equ. (a) becomes.

$$\frac{d^2v}{dt^2} + 2\alpha \frac{dv}{dt} + \alpha^2 v = 0.$$

has soln. of form $v(t) = e^{-\alpha t} (A_1 t + A_2)$.

$$v_s = A_1 t e^{-\sqrt{6}t} + A_2 e^{-\sqrt{6}t}$$

$$v(0) = 0 \therefore A_2 = 0$$

$$\frac{dv}{dt} = A_1 t (-\sqrt{6}) e^{-\sqrt{6}t} + A_1 e^{-\sqrt{6}t} \quad [\because A_2 \text{ is } 0]$$

$$\therefore \left. \frac{dv}{dt} \right|_{t=0} = A_1 = \frac{i_c(0)}{C} = \frac{i(0)}{C} = 420 \text{ A}$$


$$\therefore v(t) = 420 t e^{-2.45t}$$

$$\text{As } t \rightarrow 0, v(t) = 0 \text{ and, at } t = \infty, v(t) = 420 \frac{t}{e^{2.45t}} = 420 \frac{t}{t} \frac{1}{2.45e^{2.45t}} = 0$$

(\therefore Hôpital's rule)

$$v_m \text{ (at } t_m = 0.408 \text{ s)} = 63.1 \text{ V} \rightarrow \text{larger than overdamped case.}$$
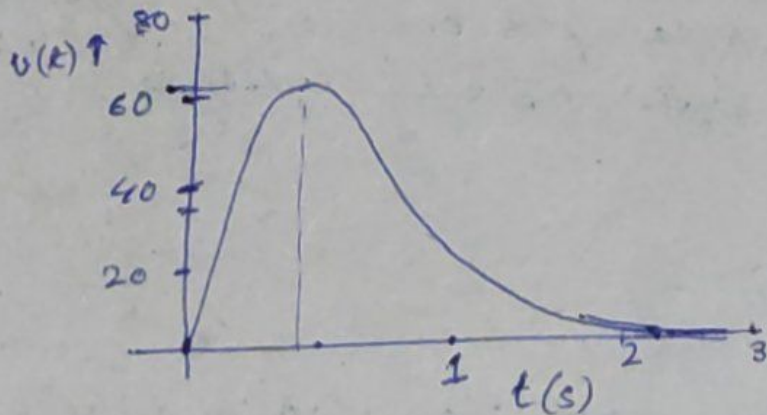
$$\frac{v_m}{100} = 420 t_s e^{-2.45 t_s} \text{ yields } t_s = 3.12 \text{ s.}$$



Underdamped // RLC ckt. $\alpha < \omega_0$

$$\therefore s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \triangleq \text{natural resonant frequency.}$$

$$\therefore v(t) = e^{-\alpha t} (A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t})$$

$$= e^{-\alpha t} \left[(A_1 + A_2) + \left(\frac{e^{j\omega_d t} + e^{-j\omega_d t}}{2} \right) + j(A_1 - A_2) \left[\frac{e^{+j\omega_d t} - e^{-j\omega_d t}}{j2} \right] \right]$$

$$= e^{-\alpha t} \left[(A_1 + A_2) \cos \omega_d t + j(A_1 - A_2) \sin \omega_d t \right]$$

$$= e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t].$$

Note : Since $v(t)$ must be real $\therefore B_2$ is real.

Let $R = 10.5 \Omega$ $\therefore \alpha = 2$, $\omega_0 = \sqrt{6}$, $\omega_d = \sqrt{2}$ (rad/s all)

$$\therefore v(t) = e^{-2t} (B_1 \cos \sqrt{2} t + B_2 \sin \sqrt{2} t)$$

For $v(0) = 0$, $B_1 = 0$ $\therefore v(t) = B_2 e^{-2t} \sin \sqrt{2} t$

$$i(0) = 10 \quad \therefore \left. \frac{dv}{dt} \right|_{t=0} = \left(\sqrt{2} B_2 e^{-2t} \cos \sqrt{2} t - 2 B_2 e^{-2t} \sin \sqrt{2} t \right) \Big|_{t=0}$$

$$= \sqrt{2} B_2 = 420$$

$$\therefore B_2 = 210\sqrt{2} \quad \therefore v(t) = 210\sqrt{2} e^{-2t} \sin \sqrt{2} t$$

Note : ① $v(0) = 0$, $v(\infty) = 0$ [$\because e^{-2t} \rightarrow 0$
 $\therefore \sin t = 0$]

② t_m is before $\sin \sqrt{2} t$ attains max.

when $t = \pi/\sqrt{2}$, $\sin \sqrt{2} t = 0 \therefore v(t) = 0$.

$\pi/\sqrt{2} < t < \sqrt{2}\pi \rightarrow v(t)$ is negative

Thus $v(t)$ is an oscillatory fn. of time and crosses the real axis for all $t = n\pi/\sqrt{2}$.

More noticeable for $d \ll \omega_0$.

For $d = 0$, $v(t)$ is an undamped sinusoid $\therefore \omega_0 =$ ~~resonant~~ ^{resonant} frequency oscillating with constant amplitude.

$$V_{m1} = 71.8 \text{ V at } t_{m1} = 0.435 \text{ s}$$


$$V_{m2} = -0.845 \text{ V at } t_{m2} = 2.657 \text{ s}$$

$t_5 = 2.92 \text{ s} \rightarrow$ slightly lower than that for critical damping

Observations:

1. As ζ decreases, $V_m \uparrow$.
2. $\zeta < 1 \rightarrow$ oscillatory response.
3. $t_{s \text{ min}}$ for slight underdamping.

Prob.
2-5
Pg 210

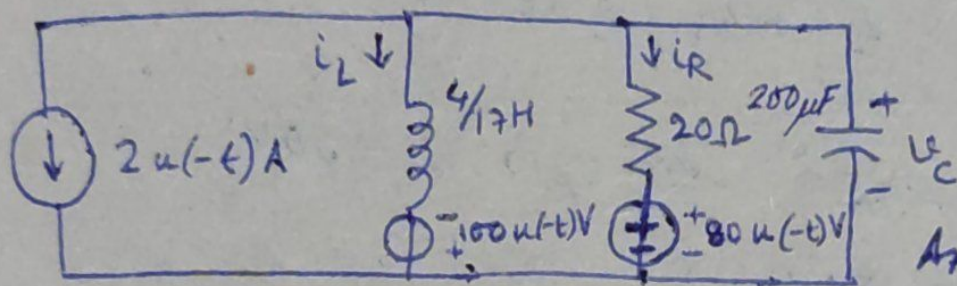


All sources turn off at $t=0$.


$v_C(0)$, $i_L(0)$, $i_R(0^+)$, $i_L(10\text{ms})$

Ans: -100V , 7A , -5A , 2.64A .

Source free series RLC ckt:

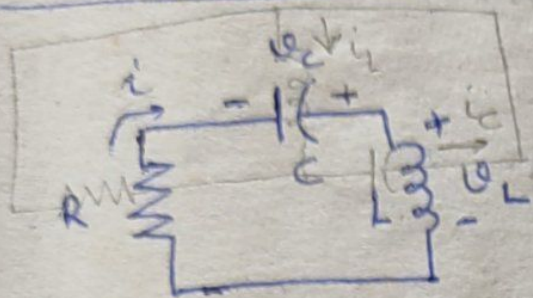

dual of

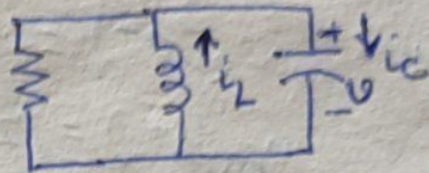

overdamped:

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_{1,2} = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$= -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

critically damped case, $i(t) = e^{-\alpha t} (A_1 t + A_2)$

Under damped: $i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$

$$\text{where } \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$


Ex: $R = 2\text{k}\Omega$, $C = 1/401\ \mu\text{F}$, $L = 1\text{H}$, $i(0) = 2\text{mA}$, $v_C(0) = 2\text{V}$

$\beta_0 \alpha = 1000$, $\omega_0 = 20025$, $\omega_d = 20000$

$i(t) = e^{-1000t} (\beta_1 \cos 20000t + \beta_2 \sin 20000t)$

$\beta_1 = 0.002$, $\beta_2 = 0$

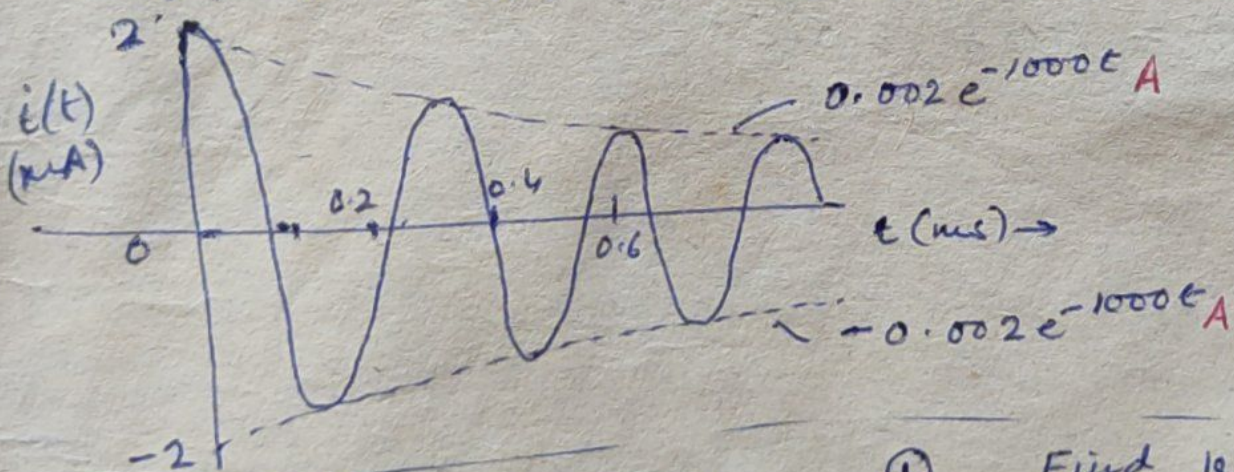$i(t) = 2e^{-1000t} \cos 20000t\ \mu\text{A}$




$20,000t = \pi/2$

or $t = 0.07854\ \mu\text{s}$

$t_s = 461\ \mu\text{s}$

Prob.
7-6, 7-7
Pg 213

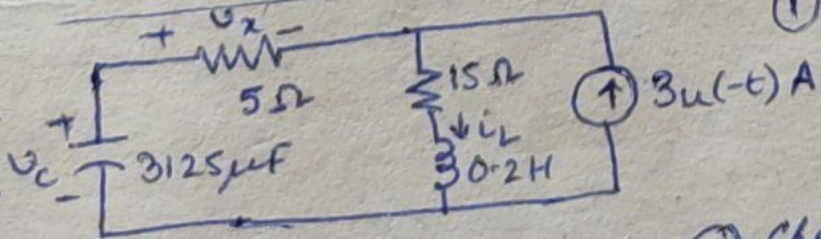


① Find $v_C(0)$, $i_L(0)$, $v_x(0^-)$, $v_x(0^+)$, $v_C(0^+)$

Ans: 45V, 3A, 0, 15V, 29.7V

② change 15 ohm resistor to 4.6 ohm & repeat

Ans: 13.8V, 3A, 0, 15V, -0.412V

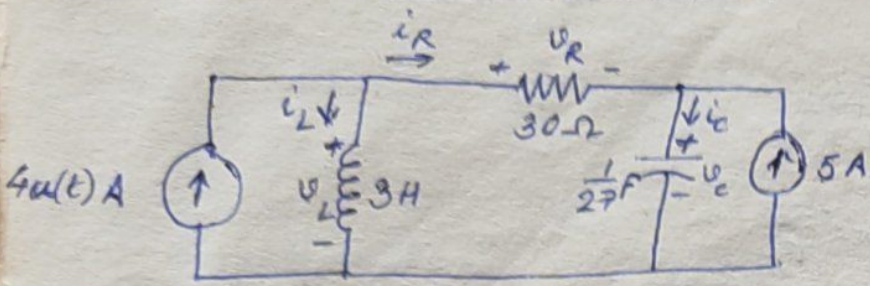

$$v(t) = V_f + A e^{s_1 t} + B e^{s_2 t}$$

$$\frac{dv}{dt} = 0 + s_1 A e^{s_1 t} + s_2 B e^{s_2 t}$$

$v_L(0^-) = 0$ [s.s. voltage across L has to be 0 - short to dc - else unrealistic infinite value of i_L or v_C at $t=0^-$]

~ by $i_C(0^-) = 0$

KCL to right node: $i_R(0^-) = -5A \Rightarrow v_R(0^-) = -150V$

KVL @ central mesh: $v_C(0^-) = 150V$

KCL at left node: $i_L(0^-) = 5A$

At $t=0^+$, $v_C(0^+) = v_C(0^-) = 150V$, ~ by $i_L(0^+) = 5A$

$\therefore i_R(0^+) = -1A$, $v_R(0^+) = -30V$

$\therefore i_C(0^+) = 4A$, $v_L(0^+) = 120V$

$v_L = L \frac{di_L}{dt} \therefore \left. \frac{di_L}{dt} \right|_{t=0^+} = \frac{v_L(0^+)}{L} = 40 A/s$

~ by $\left. \frac{dv_C}{dt} \right|_{t=0^+} = \frac{v_C(0^+)}{C} = 108 V/s$

For other derivatives, KCL at left node: $4 - i_L - i_R = 0 \quad t > 0$

$\Rightarrow -\frac{di_L}{dt} - \frac{di_R}{dt} = 0 \Rightarrow \left. \frac{di_R}{dt} \right|_{t=0^+} = -40 A/s$

~ by $\left. \frac{dv_R}{dt} \right|_{t=0^+} = -1200 V/s$, $\left. \frac{dv_L}{dt} \right|_{t=0^+} = -1092 V/s$, $\left. \frac{di_C}{dt} \right|_{t=0^+} = -40 A/s$

$[v_R + v_C = v_L]$

$[i_R + 5 = i_C]$

For dead network, series RLC : $s_1 = -1, s_2 = -9$

$V_{oc} = 150V$ (from dc equivalent of ckt.)

$$V_c(t) = 150 + Ae^{-t} + Be^{-9t} \quad \left| \frac{dV_c}{dt} = -Ae^{-t} - 9Be^{-9t} \right.$$

$$V_c(0^+) = 150 = 150 + A + B$$

$$\left. \frac{dV_c}{dt} \right|_{t=0^+} = 108 = -A - 9B$$

$$\therefore A = 13.5 = -B$$

$$\therefore V_c(t) = 150 + 13.5(e^{-t} - e^{-9t})$$