
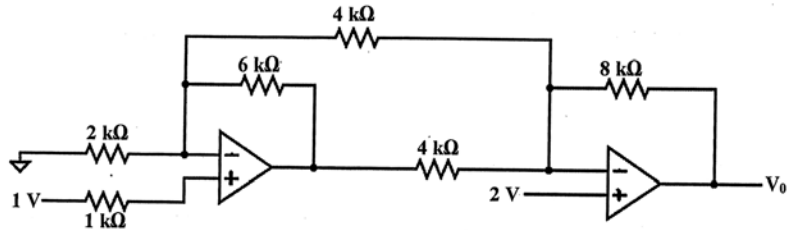


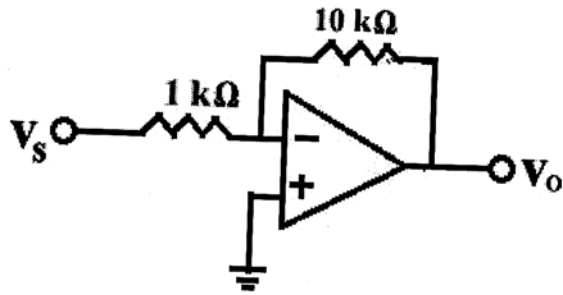5. a) Find V_0 in circuit shown in figure below.



b) Find the closed loop gain of the inverting op-amp circuit provided below when open loop gain is (i) 100 and (ii) 100000. Give your comment.



5+5

6. a) Write down the rule of op-amp in open loop configuration.
 b) Draw the circuit diagram and explain the operating principle of a zero cross detector.
 c) Draw circuit diagram of a square wave oscillator.
 d) For a 8 bit ADC, reference voltage is 5 V. What will be the output bit pattern if $V_{in} = 4V$. 2+3+2+3

BACHELOR OF SCIENCE EXAMINATION, 2022

(2nd Year, 2nd Semester)

PHYSICS

[ANALOG SYSTEMS AND APPLICATIONS]

PAPER – CORE 10


Time : Two hours

Full Marks : 40

Answer any four questions.

Each question carries equal mark.

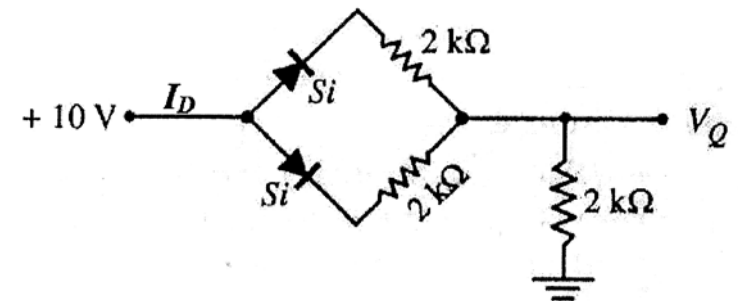1. a) Why the band energy positions of p-type Silicon is higher than n-type Silicon?
- b) How the barrier potential depends on junction temperature?
- c) Calculate the ripple factor of full wave and half wave rectifier.
- d) Find the voltage (V_0) and current (I_D) in the network shown in the Figure.




2+2+3+3

[Turn over

[2]

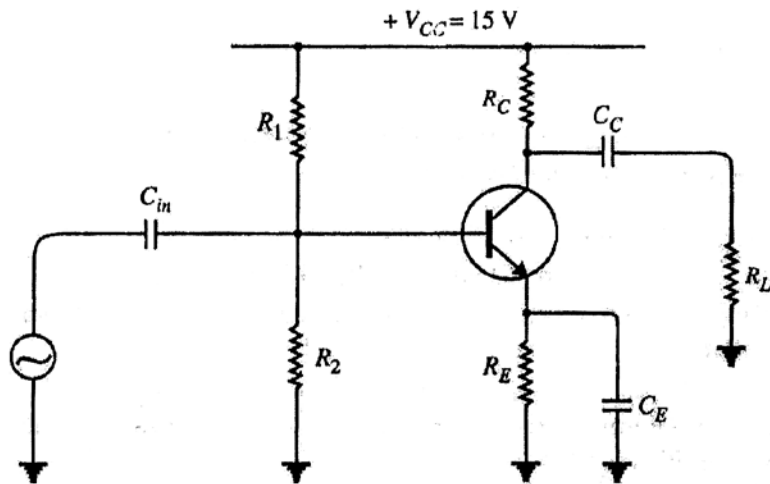2. a) What is the reason of making base layer thin for a BJT?
- b) Transistor amplifies a signal – does it violate energy conservation principle? Justify your answer.
- c) In Emitter Bias configuration, how stability of biasing is improved compared to Fixed Bias configuration?
- d) For the transistor amplifier shown in the Figure below, $R_1 = 10\text{ k}\Omega$, $R_2 = 5\text{ k}\Omega$, $R_C = 1\text{ k}\Omega$, $R_E = 2\text{ k}\Omega$ and $R_L = 1\text{ k}\Omega$.

Draw d.c. load and determine the operating point




$1\frac{1}{2} + 1\frac{1}{2} + 3 + 4$


[3]

3. a) Explain the difference in working principle of Light Emitting Diode (LED) and Photodiode?
- b) Design a circuit to get the following output from the given input.

Input

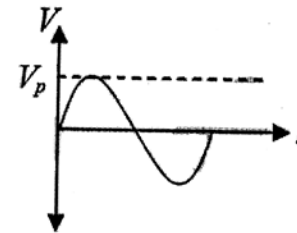

Output

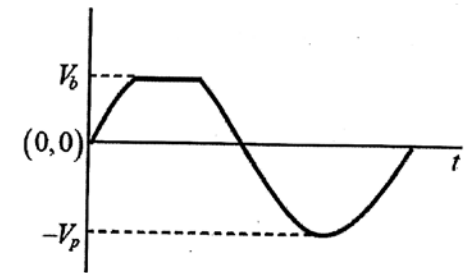

- c) In Oscillator although there is no supply of continuous ac signal in the input, how will we get the ac signal in the output?
- d) What is Barkhausen criterion for oscillation?
- e) For an oscillator, calculate the resonance frequency of a LC tank circuit. $1\frac{1}{2} + 2\frac{1}{2} + 2 + 2 + 2$
4. a) Draw circuit diagram of a differential amplifier working in common mode configuration. Draw its suitable equivalent r_e model circuit and calculate the gain of circuit.
- b) Explain the virtual ground concept of operational amplifier (op-amp). $7 + 3$

[Turn over