B.E. MECHANICAL ENGINEERING FIRST YEAR FIRST SEMESTER - 2022

SUBJECT: BASIC ELECTRICAL ENGINEERING

Time: Three Hours

Full Marks: 100

8

8

(50 Marks for each part)


Use a separate Answer-Script for each part

Two marks for neat and well-organized answers

Question No.	Part-I	Marks
110.		

Answer any three questions

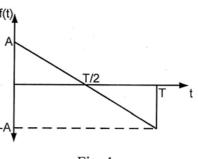1. (a) Calculate Form factor and Peak factor for the periodic waveform as shown in Fig. 1.




- Fig. 1.
- (b) Three branches, possessing resistance of 50Ω , an inductance of 0.15H and a capacitance of $100\mu F$, respectively are connected in parallel across a 100V, 50Hz supply. Calculate: (i) the current in each branch, (ii) the supply current and (iii) the phase angle between the supply current and the supply voltage.
- 2. (a) Discuss about the current characteristics of a parallel combination of R-C 3+2+3 components under pure sinusoidal voltage. What do you mean by instantaneous power? Calculate instantaneous power for the parallel combination of R-C components under pure sinusoidal voltage.
 - (b) In a circuit, the equation for instantaneous voltage and current is given by $v=141.4sin(\omega t-2\pi/3)V$ and $i=7.07sin(\omega t-\pi/2)A$, where $\omega=314rad/s$.
 - (i) Sketch a neat phasor diagram for the circuit.
 - (ii) Calculate the impedance with phase angle.
 - (iii) Calculate the average power and power factor
 - (iv) Calculate the instantaneous power at the instant t=0.

[Turn over

Ref No.: Ex/ME(M2)/ES/B/EE/T/114/2022

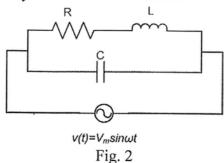3. (a) Calculate the impedance of the circuit in Fig.2. Also deduce the expression of frequency at resonance condition.



(b) Describe the transfer of electrical power from generating station to the service mains using single line diagram.

- 4. (a) What do you mean by active and passive transducer? With proper example, discuss about the operation of primary and secondary transducer
 - (b) Discuss about the selection criteria of a transducer. Also discuss about the 5+5 advantages and disadvantages of transducer.
- 5. Write short notes on the following topics

(i) Active and reactive power

- (ii) Average and RMS value of ac signal
- (iii) Thermocouple
- (iv) Electrical transducer

7

 4×4

B.E. MECHANICAL ENGINEERING FIRST YEAR FIRST SEMESTER EXAMINATION, 2022

SUBJECT: BASIC ELECTRICAL ENGINEERING

Full Marks -100

Time: Three hours

Use a separate Answer-Script for each part

No. of question	Part II (50 Marks)	Marks
question	Answer any three questions(2 marks reserved for neat and well-organized answer)	
1. a)	Three resistors of 20Ω resistances are connected in star. Find the equivalent delta resistances. If a dc voltage source of 230 V is connected across any two terminals of the equivalent delta connected resistances, find the current drawn from the source.	8
b)	Correct or Justify: An ideal current source and an ideal voltage source have internal resistances of infinite and zero value, respectively.	4
c)	State and explain Norton's theorem.	4
2. a)	Using superposition theorem, find the voltage drop across 15 Ω resistor in the figure below.	8
	$ \begin{array}{c c} \hline 15\Omega \\ \hline 10\Lambda \end{array} $ $ \begin{array}{c c} \hline 10\Lambda \end{array} $ $ \begin{array}{c c} \hline 40\Omega \end{array} $	
b)	Find out the Thevenin and Norton's equivalents at AB.	8
	10v + 22 = 3 0 B + 40v	
3.a)	In the magnetic circuit shown below, calculate the required current (<i>I</i>) to be passed in the coils in order to establish a flux of 0.5 mWb <i>in the air gap</i> . Relative permeability of the ferromagnetic core is 1200. Neglect magnetic leakage and fringing.	12

Ref. No.

Ex/ME(M2)/ES/B/EE/T/114/2022

B.E. MECHANICAL ENGINEERING FIRST YEAR FIRST SEMESTER EXAMINATION, 2022

SUBJECT: BASIC ELECTRICAL ENGINEERING

Full Marks -100

Time: Three hours

Use a separate Answer-Script for each part

