

B. CIVIL ENGG. 1<sup>ST</sup> YEAR 1<sup>ST</sup> SEM. SUPPLEMENTARY EXAMINATION-2017

## Subject: BASIC ELECTRICAL &amp; ELECTRONICS ENGINEERING


Time: Three Hours

Full Marks: 100

Use a separate Answer-Script for each Part

Part I: (50 marks)Answer any Five questions taking at least Two from each SectionSection A

- Q1 (a) State Norton and Thevenin's theorem. 4  
 (b) For the circuit, shown in Fig P-1(b), find the Thevenin and Norton equivalent circuits. 6

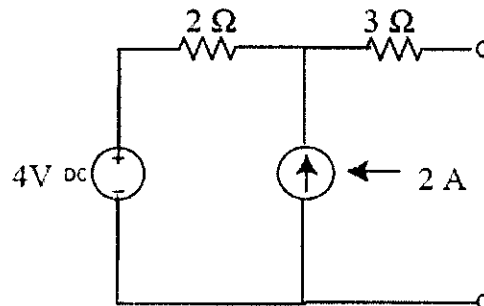Fig. P-1(b)

- Q2 (a) Define and find the expression for Reluctance of a magnetic circuit. 1+3  
 (b) Consider a toroid with the mean length of 20 cm, the cross section of 2 cm<sup>2</sup>, and the relative magnetic permeability of 6700. What will be the magnetic flux and the magnetic flux density if the coil has 10 turns and the current is 2 amperes? 6
- Q3 (a) Explain how voltage builds up in a d.c. shunt generator. 4  
 (b) An 8-pole d.c. generator has 960 conductors and a flux/pole of 20 mwb. Calculate the emf generated when running at 500 rpm for (i) lap, and, (ii) wave connected armature winding. 6
- Q4 (a) What is synchronization? Discuss the conditions that must be satisfied to achieve synchronization? 2+4  
 (b) A three-phase synchronous generator has a per phase synchronous reactance of 10  $\Omega$  and delivers a load consisting of a 15  $\Omega$  pure capacitive reactance. Determine the ratio of induced emf and terminal voltage. 4
- Q5 Write short notes on: 5+5  
 (a) Hysteresis Loss;  
 (b) Maximum Power Transfer Theorem.

Section B

- Q6 (a) Define the r.m.s. and average values of an alternating sinusoidal current waveform. 4
- (b) A resistance of  $7 \Omega$  is connected in series with a pure inductance of 31.8 mH and the circuit is connected to a 100 V, 50 Hz, sinusoidal supply. Calculate: (i) the circuit current; (ii) the phase angle. 6
- Q7 (a) Show that two wattmeters are sufficient for measuring the active power of a balanced three-phase system. 4
- (b) The input power to a three-phase motor was measured by the two wattmeter method. The readings were 5.2 kW and  $-1.7$  kW, and the line voltage was 400 V. Calculate: (i) the total active power; (ii) the power factor; (iii) the line current. 6
- Q8 (a) Explain the principle of generating rotating magnetic field in three-phase induction motors. 6
- (b) The frequency of the emf induced in the stator winding of an 8-pole induction motor is 50 Hz and that in the rotor is 1.5 Hz. Determine the (i) speed, and, (ii) slip of the motor. 4
- Q9 (a) Write down the assumptions of an ideal transformer. 4
- (b) A 250 kVA, 11000 V/400 V, 50 Hz single-phase transformer has 80 turns on the secondary. Calculate: 6
- (i) the approximate values of the primary and secondary currents;
- (ii) the approximate number of primary turns;
- (iii) the maximum value of the flux.
- Q10 Write short notes on: 5+5
- (a) Starting of Squirrel-Cage Induction Motors;
- (b) Open Circuit test on Transformers.

**B.CIVIL ENGG. 1ST YEAR 1ST SEM. SUPPLEMENTARY EXAM. 2017  
BASIC ELECTRICAL & ELECTRONICS ENGINEERING**

**Time: 3Hrs**

**Full Marks: 50**

**Part II**

*Use Separate Answer scripts for each Group  
Answer any five (05) of the following questions.*

- 1) Answer any five (any 02) briefly. [05x2=10]
  - i) What is a semiconductor? Explain different types.
  - ii) What is Atomic Energy Level and define the unit of energy in joules and electron-volts.
  - iii) What are charged particles? Define work-function of a metal.
- 2) What is a diode? Draw a neat sketch of its symbol, structure and characteristics for the different types. [10]
- 3) Describe the Energy Band in crystals with appropriate figures and equations. Explain Fermi-Dirac Distribution Function with appropriate figures and equations. [05+05=10]
- 4) Add 17 and 19 after converting them to binary value. Express the same in hexa-decimal and octal notations. [10]
- 5) Draw the schematic diagram and show the k-map operation table for a) AND gate b) OR gate c) NAND gate d) NOR gate. [10]
- 6) As system of particles obeys Fermi-Dirac distribution function. Show that the probability of vacancy of an energy level  $\Delta E$  above the Fermi level  $E_F$  is the same as the probability of occupancy of an energy level  $\Delta E$  below  $E_F$ . [10]
- 7) Why the field - effect transistor is called unipolar? Draw schematically the structure of an n-channel JFET and explain the terms source, drain, gate and channel. What is the significance of the term field-effect? Draw the circuit symbol of the JFET. [10]
- 8) A diode has a forward resistance of which is  $50\Omega$ , supplies power to a load resistance  $1200\Omega$  for a 20V (rms) source. Calculate,
  - a) The DC load current.
  - b) The AC load current.
  - c) The % regulation. [10]