

**B. ELECTRICAL ENGINEERING 2<sup>ND</sup> YEAR 1<sup>ST</sup> SEMESTER SUPPLE EXAMINATION, 2017**

**ELECTRONICS-II**

**Time: 3 Hours**

**Full Marks: 100**

**Use separate Answer - Script for each Part**

**50 marks for each part**

**PART - I**

Answer any **Five (5)** Questions from the followings: 10×5

1. Give the circuit diagram of a *Wien-bridge oscillator* using *OPAMP*, Explain how oscillation principle is satisfied in this circuit? How the frequency of oscillation is determined for such oscillator?  
(2+3+5)
2. Explain the operation of *Monostable multivibrator* using *555 IC* with necessary circuit diagram. Write down expression of expressions of width (*W*), time period (*T*), frequency (*f*) and duty cycle (*D*) of output waveform.  
(3+3+4)
3. Describe with a suitable circuit diagram how a *transistorized shunt voltage regulator* provides a stable dc output voltage against the input voltage fluctuation?  
(4+6)
4. Give the circuit diagram of IC 7805 voltage regulator. Explain the operation of this circuit.  
(4+6)
5. Give the circuit diagram of integrated *current mirror circuit* using two *BJTs*. Clearly explain why this circuit is called the *current mirror circuit*.  
(5+5)
6. What do you meant by constant current sources? Explain with suitable circuit diagram how a *BJT* circuit provides a constant current?  
(2+3+5)
7. Give the circuit diagram of complementary *MOSFET (CMOS) NAND* circuit. Explain how the logic of *NAND* Gate is verified with this circuit.  
(5+5)
8. Write short note (any two of the followings): 2×5
  - a. Darlington transistor
  - b. Schmitt trigger circuit
  - c. TTL circuit
  - d. Bootstrap circuit

[ Turn over

**B. ELE ENGG. 2<sup>ND</sup> YEAR 1<sup>ST</sup> SEMESTER SUPPLE EXAMINATION-2017****Subject: ELECTRONICS – II      Time: 3 Hours      Full Marks: 100****PART-II****Answer Q.1 and any FOUR from the rest.****All parts of the same question must be answered at one place only.**

- 1.(a) Fill in the blank:  $(243.62)_7 = (?)_9$   
(b) What is the advantage of Gray code?  
(c) Implement XNOR function using minimum number of NOR gates. 3+3+4=10
  
2. Explain the functionality of a carry look-ahead adder. 10
  
3. Design a priority encoder and explain its operation 10
  
4. Design a 4-bit full adder-subtractor circuit. 10
  
5. Explain the operation of a TTL NAND gate indicating the significance of the totem-pole arrangement. 10
  
6. Explain how a master-slave configuration helps to eliminate the race-around problem. 10
  
7. Design a self-correcting 4-bit ring counter. 10
  
8. Design a 4-bit universal shift register. 10