

**B. ETCE 2<sup>ND</sup> YEAR 1<sup>ST</sup> SEMESTER SUPPLEMENTARY EXAMINATION 2017**  
**Subject: ANALOG CIRCUITS-I                      Time: 3 Hours                      Full Marks: 100**

**All parts of the same question must be answered at one place only**  
**Use separate answer script for each PART**

**PART- I**

**(Answer any Five Questions)**

1. Explain the working principle of a voltage multiplier with proper circuit diagram. [Marks: 10]
2. Explain the working principle of a half wave rectifier. Find  $V_{dc}$ ,  $V_{rms}$  and efficiency( $\eta$ ) of a half wave rectifier. [Marks: 10]
3. Find the output voltage  $V_o$  of the diode circuit shown below and plot the output voltage for a temperature range 0 to 100°C. [All diodes are real and identical] [Marks: 6+4=10]

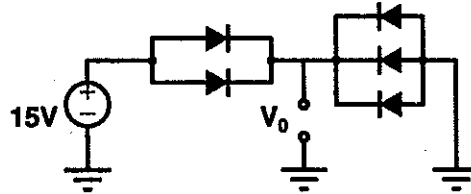


Figure 1

4. A) Draw the output waveform of the circuit shown below. ( $V_{B1} = 2V$ ,  $V_{B2} = 3V$  and diodes are real)
- B) Determine the minimum or maximum value of  $V_{B1}$  and  $V_{B2}$  to avoid the clipping of output waveform. [Marks: 6+4=10]

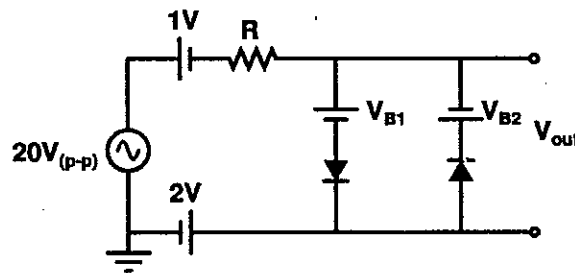


Figure 2

5. Determine the expression of stability factor  $S(I_{co})$  for a voltage divider network. [Marks: 10]
6. Explain the function of a current mirror circuit. Design one current mirror with  $1\mu A$  current in primary branch and  $0.75\mu A$  in secondary branch. (Available transistors are identical with  $\beta = 1000$  and  $V_{BE} = 0.7V$ . Supply voltage 3V)

7. One CE amplifier with proper biasing arrangement is shown below. Find the following parameters: [ $\beta = 100$ ,  $C_E = C_C = C_B = 1 \mu F$  and neglect  $r_o$ ]

- A) All low frequency poles and zeros due to coupling capacitor and lower cut-off frequency.
- B) Gain versus frequency plot (for very low to mid frequency range) [Marks: 7+3=10]

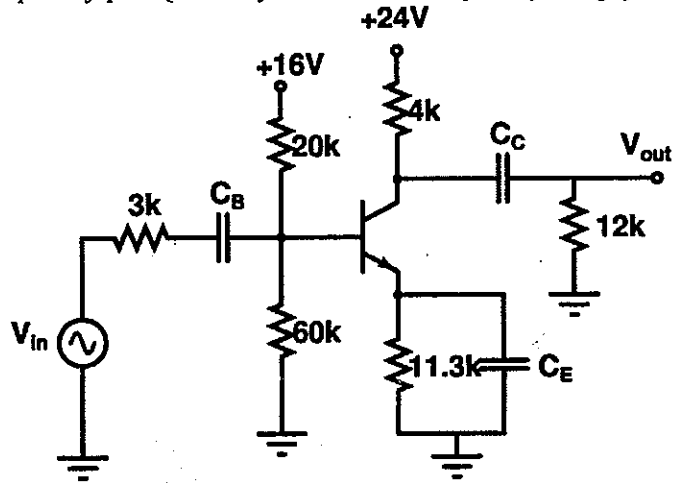


Figure 3

B. ETCE 2<sup>ND</sup> YEAR 1<sup>ST</sup> SEMESTER SUPPLEMENTARY EXAMINATION-2017


Subject: ANALOG CIRCUITS – I Time: 3 Hours Full Marks: 100

PART-II


Answer any FIVE.

All parts of the same question must be answered at one place only.

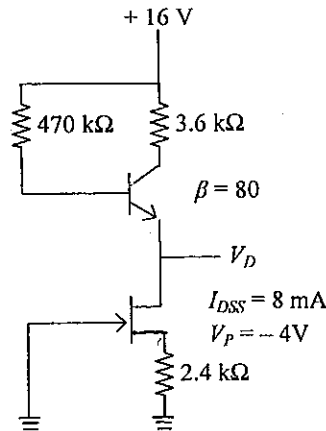
1. Explain the operation of an n-channel JFET. 10
2. Determine  $V_D$ . 10



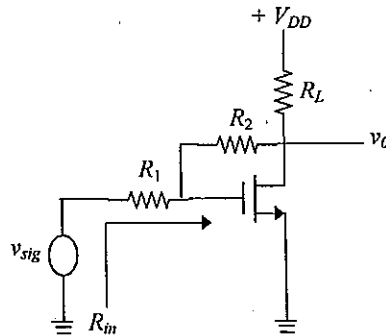
3. Find  $v_o/v_{sig}$  and  $R_m$  of the following circuit with  $g_m = 1 \text{ mA/V}$ ,  $r_o = 100 \text{ k}\Omega$ ,  $R_L = 10 \text{ k}\Omega$ ,  $R_1 = 500 \text{ k}\Omega$ ,  $R_2 = 1 \text{ M}\Omega$ . 10



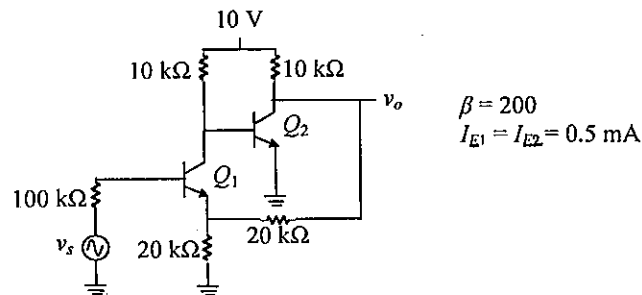4. Determine the feedback configuration of the following circuit and hence quantitatively explain how the feedback connection helps in improving the behavior of the circuit as an ideal source. 10



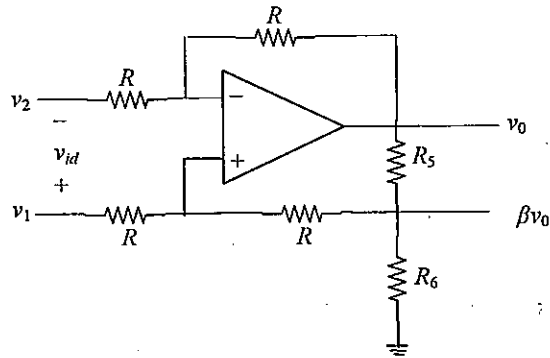5. Explain how a differential amplifier with active load and Wilson current mirror can achieve a near ideal value of CMRR. 10
6. Assume that  $R_5$  and  $R_6$  of the following circuit are much smaller than  $R$  so that the current through  $R$  is much lower than the current in the voltage divider, so that  $\beta = R_6/(R_5 + R_6)$ . Show that the differential gain is given by  $A_d = 1/(1 - \beta)$ . Also design the circuit to obtain  $A_d = 10$ ,  $R_{id} = 2 \text{ M}\Omega$  by selecting  $R$ ,  $R_5$  and  $R_6$  such that  $(R_5 + R_6) \leq R/100$ . 10



7. Explain the operation of a monostable multivibrator. 10