


B. E. T. C. E. 2ND YEAR Supplementary Examination 2017
First Semester
Network Synthesis

Time: 3 hours

Full Marks : 100

Answer any five questions
All questions carry equal marks

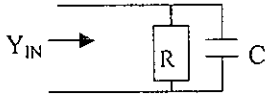- 1(a) Define PR function? From your definition prove that the input admittance function of the following circuit is PR



10

- 1(b) If $Z_1(S)$ and $Z_2(S)$ are PR functions then using your definition in part(a) prove that
- $Z_1(S) + Z_2(S)$ is a PR function
 - $1/Z_1(S)$ is a PR function.
 - $Z_1(Z_2(S))$ is a PR function.

10

- 2(a) If $P(S)$ is a strictly Hurwitz polynomial, show that $P(S)/P'(S)$ is PR,
 where $P'(S) = dP(S)/dS$

10

- 2(b) If $P(s)$ is a Hurwitz polynomial show that $\phi(s) = M(s)/N(s)$ is a PR function where, $M(s)$ is the even part of $P(s)$ and $N(s)$ is the odd part of $P(s)$.

10

- 3(a) Assume that $Z(S)$ is a PR function and $\text{Re}[Z(S)] = 0$. Show that $Z(S)$ can be expressed either as $M(S)/N(S)$ or as $N(S)/M(S)$ where $M(S)$ and $N(S)$ respectively represent even and odd polynomials in S .

08

- 3(b) From the result proved in part (a) obtain the general expression for an LC driving point impedance function. Hence derive the Foster I and Foster II realization technique for LC impedance function

06

- 3(c) Find the Foster I and Foster II realization for the following LC function

$$Z_{LC}(S) = \frac{S(S^2 + 2)}{(S^2 + 1)(S^2 + 3)}$$

06

- 4 Obtain two Cauer and two Foster realizations for the following RC driving point admittance function.

$$Y(S) = \frac{S(S+3)}{(S+1)(S+4)}$$

5+5+5+5

- 5(a) Describe a constant K low pass filter. Derive the expression for L and C used in this filter in terms of its cut off frequency and the $Z_1 Z_2$ product. 10
- 5(b) What are the disadvantages of the above filter? Show how these disadvantages may be overcome in an m-derived filter. Find the expression for m and f_∞ for such filter. 10
- 6(a) Derive the expression $\sinh \frac{\gamma}{2} = \sqrt{\frac{Z_1}{4Z_2}}$ for a symmetric T network. Assume the usual meanings of the symbols used. 10
- 6(b) Show how the above expression is used to find the qualitative filter characteristics of a reactive T network. Use a constant K high pass filter as an example to explain your answer. 10
- 7 Design a state variable low pass filter described by the following voltage transfer function. 20
- $$\frac{V_o(S)}{V_i(S)} = \frac{\omega_o S}{S^2 + a\omega_o S + \omega_o^2}$$
- where, $\omega_o = 1000$ rad/sec and $a = \sqrt{2}$
- 8 Find the voltage transfer functions for the circuits shown in Fig 2(a) and 2(b).. Also comment on their applications. 10+10

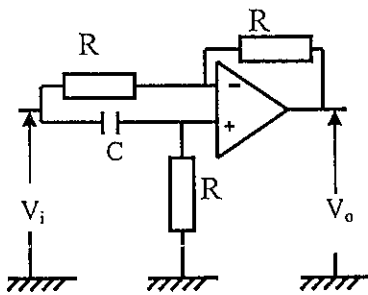


Fig 2(a)

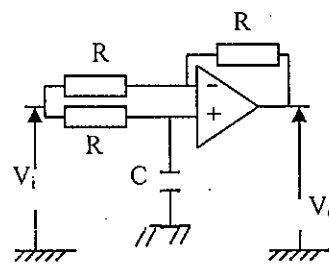


Fig 2(b)