

B.E.ELECTRONICS & TELECOMMUNICATION ENGINEERING

FOURTH YEAR SECOND SEMESTER (old)-2017

INDUSTRIAL ELECTRONICS

Full Marks =100

Time : 3 Hours

Answer Q.1 and any FOUR from the rest
(Assume all rectifiers AC-mains operated ; unless stated otherwise)

1. Indicate True(T)/ False(F) : 10x2
- i. A single-phase HW-rectifier uses 1:4 step-up transformer with a diode (D); the PIV across D is 2.1 KV
 - ii. Efficiency of a HW-rectifier is 12% if load $R_L = 1K\Omega$ and r (diode) = 600Ω
 - iii. A HW-rectifier uses a transformer with 2KVA rating ; DC power to a resistive load without overheat is 573 W
 - iv. Depth of penetration in Induction Heating is $\delta = (\rho / \mu^2) @ 15MHz$
 - v. Heat power on a non-magnetic load surface is $\Delta p = 160 (\beta^2 \sqrt{\rho}) @ 16MHz$
 - vi. For a $6-\Phi$ rectifier $I_{dc} = 20.1$ mA if $R_L = 1K\Omega$
 - vii. In a $m-\Phi$ rectifier dc output voltage is $E_{dc} = 230 \sin(\pi/m)$
 - viii. A programmable logic controller is essentially a Multiplexer
 - ix. A relaxation oscillator using UJT($\eta=0.5$), $C=14.5$ nF and $R=1K\Omega$ generates pulse-waves of period = 1.5 ms.
 - x. A FW-rectifier with LC-filter becomes unstable if $L=25mH$ and $C=100\mu F$
2. a. Explain operation of a full-wave (FW) rectifier with a neat circuit diagram 6+8+6
b. Derive an expression for Ripple-Factor (γ) with RC-filter
c. Desired $\gamma = 2\%$ with $R=1K\Omega$ and diode conduction angle = 10° . Determine $C(\mu F)$
3. a. What is a Multiphase rectifier 4+4+12
b. Define : (i) Efficiency (ii) P_{dc}
c. Determine P_{dc} and E_{dc} for a $4-\Phi$ rectifier assuming $R_L=10K\Omega$
4. a. Explain the characteristics of a silicon controlled rectifier (SCR) 6+6+8
b. How the operation of a TRIAC differs from the SCR
c. A SCR operates on AC-mains line to get $I_{dc} = 5$ mA @ load $R_L=10K\Omega$. Determine Firing Angle
5. a. Explain operation of Push-Pull Power Inverter (PPPI) 8+12
Given for a PPPI : $A = 4cm^2$, $B=4K.gauss$, $f=3.6KHz$, $V_{cc}=15V_{dc}$ and $V_{be}=2v$ (winding) and secondary $N = 50$ turns.
Determine (i) Peak output voltage (ii) Total number of Primary turns.

[Turn over

6. a. What is a PLC 6+14
 b. A process system involves four variables (A, B, C, D) controlled by a PLC : Show a logic control diagram for 'ENERGIZE' Alarm Signal (Y) if $A=0$ and
Either $B=1$ AND $C=0$ OR $D=1$
7. a. Define 8+6+6
 (i) 'Resistance' for a liquid level system
 (ii) Time constant of a Thermal system
 b. Consider a typical first-order Thermal system wherein liquid in a tank is heated by heat input (H_i) resulting to temperature rise (θ_o) of the liquid. Formulate the transfer function $F = \theta_o / H_i$.
 c. Sketch response of $\theta_o(t)$ assuming a sudden step-change in H_i applied at $t = 0$. Calculate value of $\theta_o(t) \Big|_{t=\tau}$ as percent of steady state θ_o .
8. Write Short Note (Any Two) : 10+10
- Bridge Rectifier
 - Induction Heating
 - LC-commutation for SCR turn-Off
 - Resistance Weld
 - Function XOR by Relay ladder logic.
 - Cycloconverter