

B Mechanical 1st year 1st sem EXAMINATION, 20 17

(1st/2nd Semester/Regular/Repeat/Supplementary/Spl. Supplementary/Old/Annual/Bi-Annual)

SUBJECT Basic Electrical Engineering
(Name in full)

PAPER

Time : Two hours/Three hours/Four hours/Six hours

Full Marks 30/ 100
(15/50 marks for each part)

Use a separate Answer-Script for each part

No. of questions	Part I / Part II	Marks
<u>Answer any three questions (16 × 3) + 2 marks for well organized answer</u>		
1. a)	State and explain Thevenin's Theorem with suitable example.	8
b)	Find the power delivered by the energy sources individually in the following circuit	8
2. a)	Deduce the expression for maximum power transfer in a DC Network. Find efficiency for this condition	8
b)	Find the current flowing in branch AB in the network shown below, when this branch has a resistance of i) 5Ω and ii) 0.1Ω	8
3. a)	Deduce the expression for conversion from Star to Delta connected resistance network.	8
b)	In a single phase AC Circuit derive the expression for power, power factor and reactive power. Show representative circuit and phasor diagram	8
4. a)	Explain the phenomenon of resonance in a series RLC circuit and deduce the expression for Band Width	8
b)	An AC voltage $v(t) = 220\sqrt{2}(\sin 314t + 30^\circ)$ is applied across a series circuit of $R=10\Omega$ and $C=1mF$. Find resultant current through the circuit and also find the power delivered by the source.	8
5. a)	For a pure sinusoidal waveform derive the expression for Crest Factor and Form Factor.	8
b)	Find the values of a) current b) V_1 and V_2 and c) Reactive power in the following circuit. Draw a phasor diagram for the circuit indicating voltage drops across the components	8

Form A: Paper-setting Blank

Ref. No. ME/EE/T/114/2017(S).

B. Mechanical 1st year, 1st semester Supplementary... EXAMINATION, 20 17
 (1st/2nd Semester/Repeat/Supplementary/Annual/Bi-Annual)

SUBJECT... Basic Electrical Engineering

(Name in full)

PAPER.....

Time : Two hours/Three hours/Four hours/Six hours

Full Marks 100
(50 marks for each part)

Use a separate Answer-Script for each part

No. of questions	<u>Part-I/Part-II</u> Answer any three questions, two marks for organized answer (16 X 3=48 +2=50)	Marks
1. a)	What is the relation between permeability of a material and reluctance of the magnetic circuit?	5
b)	Explain the Hysteresis Curve (B-H) of a magnetic material from Domain-Theory of Magnetism point of view.	6
c)	An iron ring of mean length 30 cm has an air gap of 2 mm and winding of 200 turns. If the permeability of the iron core is 300 when a current of 1A flows through the coil, find the flux density.	5
2. a)	Compare the Electric Circuit with Magnetic Circuit.	5
b)	A steel magnetic circuit has a uniform cross-sectional area of 20 cm ² and a length of 200cm. A coil of 1000 turns is wound uniformly over the magnetic circuit. When the current in the coil is 4A, the total flux is 1mWb, when the current is 6A, the total flux is 1.2 mWb. For each value of current, calculate the (a) magnetic field strength and (b) relative permeability of the steel.	7
c)	Derive the expression of mutual inductance (M) for a bilateral magnetic circuit as a function of coefficient of coupling (k) and self-inductances (L ₁ & L ₂) of the coils.	4

Form A: Paper-setting Blank

Ref. No. ME/EE/T/1.14/2017.(S)

B. Mechanical 1st year, 1st semester Supplementary... EXAMINATION, 20 17
 (1st/2nd Semester /Repeat/Supplementary/Annual/Bi-Annual)

SUBJECT... Basic Electrical Engineering.....
 (Name in full)

PAPER.....

Time : Two hours/Three hours/Four hours/Six hours

Full Marks 100
 (50 marks for each part)

No. of questions		Marks
3. a)	Explain the working principles of Moving Coil & Moving Iron type instruments? Also mention, how those two types of meters can be differentiated by visual inspection. How can you classify measuring instruments?	8
b)	In the shown Schering Bridge find out the expressions of capacitance C_1 & its resistance R_1 as the functions of other bridge parameters with the help of phasor diagram . Hence, also find the loss angle δ .	8
a)	What are the fundamental parameters generally considered while characterizing a measuring instrument?	6
b)	Write a Note on: Classes of Protection in a Thermal Power Station.	5
c)	How a Circuit Breaker works along with Relay in a Protection Scheme?	5

Pg 307 3

Form A: Paper-setting Blank

Ref. No. ME/EE/T/1.14/20.17(S)

B. Mechanical 1st year, 1st semester Supplementary

EXAMINATION, 20 17

(1st/2nd Semester /Repeat/Supplementary/Annual/Bi-Annual)

SUBJECT... Basic Electrical Engineering

(Name in full)

PAPER.....

Time : ~~Two hours~~/Three hours/~~Four hours~~/Six hours

Full Marks 100
(50 marks for each part)

No. of questions		Marks
5. a)	What are the fundamental components of power system?	3
b)	Discuss how the electrical power is evacuated from a generating station to the distributor, with the help of a schematic diagram.	13