



3. The input voltage to a series  $RL$  circuit is  
 $e(t) = 180 \sin(314t + 10^\circ) + 56 \sin(942t + 35^\circ) + 18$   
 The values of  $R$  and  $L$  are  $18 \Omega$  and  $0.0413 \text{ H}$ . Determine (i) the expression for current (ii) rms values of voltage and current. (iii) average power dissipation in the circuit and (iv) the power factor of the circuit.

14

4. Discuss the even function symmetry of a periodic function with suitable example. Hence show that Fourier Series of an even periodic function contains only cosine terms plus a constant.

4 + 10

5. (a) State and explain Thevenin's Theorem with suitable example.

4

(b) Find the current through the  $1.0 \Omega$  resistance connected between the terminals  $a$  and  $b$  for the network as shown in fig. 5.(b) using Thevenin's Theorem.

10

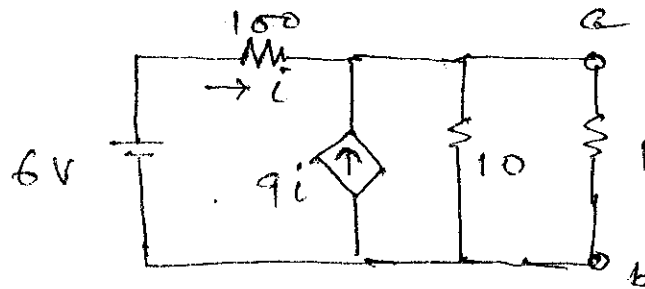


Fig. 5(b)

6. (a) State and explain Maximum Power Transfer Theorem with suitable example.

4

(b) For the network shown as shown in fig. 6.(b) below,  $E_1 = 240 \text{ V}$ .  
 (i) If  $E_2 = 50 \text{ V}$ , find the value of  $R_L$  which results in maximum power absorbed in it. What is the value of maximum power? (ii) If  $E_2$  is variable, what should be its value to limit the maximum power dissipation in  $R_L$  to  $10 \text{ W}$ ?

10

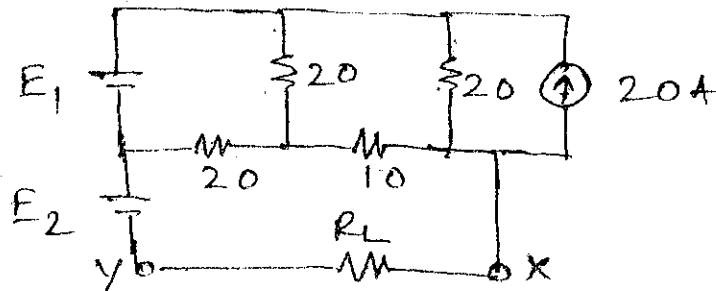


Fig. 6.(b)

7. (a) Determine the current through  $5 \Omega$  resistor for network shown in fig. 7.(a) by nodal analysis.

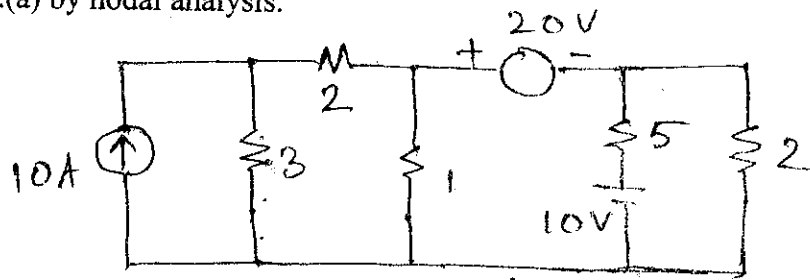


Fig. 7(a)

- (b) Determine the current through  $5 \Omega$  resistor for network shown in fig. 7.(b) by loop analysis.

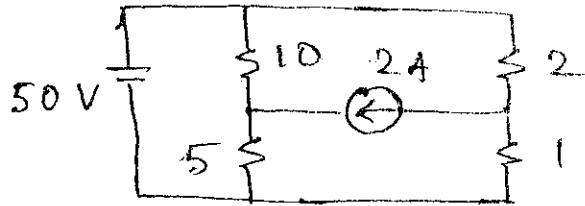


Fig. 7(b)

8. (a) Find the response current of a series  $RLC$  circuit with  $R = 5 \Omega$ ,  $L = 1 H$  and  $C = 0.25 F$  when each of the following driving force is applied. (i)  $12 r(t-2)$  and (ii)  $3 u(t-3)$

- (b) A pulse of width  $b$  and magnitude  $10 V$  is applied at time  $t$  to a series  $RC$  circuit with  $R = 1.0 \Omega$  and  $C = 0.25 F$ . Find current flowing through the circuit assuming zero net charge across the capacitor.

9. Consider the circuit as shown in fig. 9. The input to the circuit is  $24 V$ . The output of the circuit, the voltage across the capacitor, is given to be

$$v_o(t) = 16 - 12e^{-0.6t} \text{ V when } t > 0$$

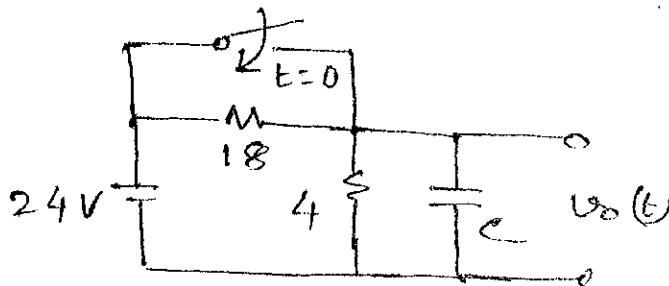


Fig. 9

Determine the value of the capacitance  $C$ .

10. (a) Derive the condition for reciprocity and symmetry of hybrid parameters ( $h$ -parameters) representation of a two port network.

(b) Find the z-parameters for network as shown in fig.10. (b) below.

7

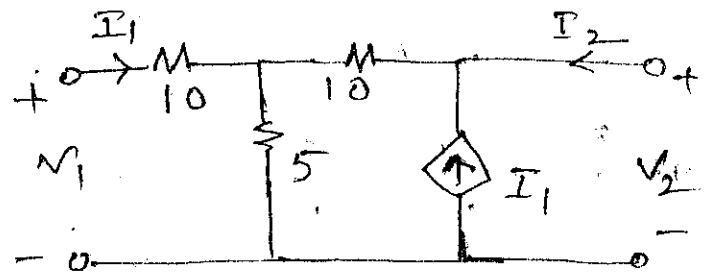


fig. 10(b)