

BACHELOR PRINTING ENGINEERING EXAMINATION, 2017
(1st Year, 2nd Semester)

Electronics

Time : Three hours

Full Marks : 100

Instruction :

1. Answer any *five* questions out of 8 questions.
2. Answers of sub questions of any questions should be written in one place. Do not be haphazard.

- 1) a) Define mobility and it's SI unit. Why mobility of electron is greater than that of hole in a semiconductor ?

Find Resistivity of an intrinsic Si-bar with following data :

Intrinsic carrier concentration = 1.5×10^3 /cc

Electronic Charge = 1.6×10^{-19} C

Electron Mobility = $1400 \text{ cm}^2 / \text{V.Sec.}$

Hole Mobility = $450 \text{ cm}^2 / \text{V.Sec.}$

(1+1+3+5 = 10)

- b) A Si-diode is applied with a forward bias voltage V. Draw tentative characteristic (FB) curves of it, if it be (1) real diode, (2) approximate model diode (3) ideal model diode. (2x3 = 6)

- c) Calculate (with argument) the net voltage and current in the circuit in fig.-I of APPENDIX. (4)

- 2) a) Define rectification efficiency (η) of a diode rectifier deduce an expression for (η) of a half wave rectifier in terms of circuit parameters and show that its maximum value may be 40.5%. (2+6+2 = 10)

- b) Draw the equivalent circuit of the Si-rectifier given in fig.- II of APPENDIX where $r_f = 10 \Omega$ and $V_b = 0.7\text{V}$ Hence calculate peak current in the circuit and peak O/P voltage. What will be these values if the diode be an ideal one. (2+2x2+2x2 = 10)

- 3) a) Draw circuit diagram of a bridge-rectifier and briefly explain its action. Also show the nature of O/P voltage if its I/P voltage be sinusoidal. (2+4+2 = 8)

- b) Discuss temperature dependence of characteristic curve of a diode. (6)

- c) What is a clipper circuit ? Draw a combination clipper circuit using two real diodes showing the nature of its O/P with a sinusoidal I/P voltage. (2x3 = 6)

- 4) a) Why NPN transistor is more useful than PNP ? Draw double diode analogy circuit of a NPN transistor and write down the transistor equations from the circuit. (2x3 = 6)


- b) Draw I/P and O/P characteristic curves of a NPN transistor (CE Configuration) and discuss their similarities with diode characteristics. Define I/P and O/P resistance of transistor from these curves. (2x2+3+2 = 9)

- c) Copy fig.- III of APPENDIX and calculate I_B , I_C , I_E and V_{CE} .

(5)

- 5) Draw a neat diagram of single stage amplifier circuit using a single battery (self bias). Mention the phasal nature of O/P voltages at its two O/P ends. Also briefly discuss the functions of various capacitors present in the circuit. (4+2+3 = 9)
- b) Draw the DC and AC equivalent circuits of the above amplifier. (3+3 = 6)
- c) Referred to the DC equivalent circuit as above, deduce the equation of DC load line of the amplifier. (5)
- 6) a) Define lower cut-off and upper cut-off frequency of an amplifier. Why are they also called 3dB frequencies ? What is dB power gain ? Calculate dB power gain of an amplifier with 59% amplification. (2x2+3+2+2 = 11)
- b) In an amplifier the max. power gain = 90dB at 2KHz and gain falls to 87dB at 200Hz and 3.5KHz. What is the band width of the amplifier ? Answer with reasons. (2)
- c) A Zener diode of unregulated power supply has the following ratings : $V_z = 6.8V$, $r_z = 2\Omega$ at $I_z = 50mA$. If maxm. source current = 150mA and load current varies from $I_L(\min) = 10mA$ to $I_L(\max) = 120mA$, what would be the variation of load voltage and % regulation ? (7)
- 7) a) Write down fundamental equation of feedback amplifier (No deduction). Hence define positive and negative feedback. Also establish the statement – “Negative Feedback improves bandwidth at the cost of gain”. (1+2+3 = 6)
- b) From fundamental equation of feedback show that % variation of gain with feedback is less than the same without feedback if the feedback be negative. (7)
- c) An amplifier has a open loop gain = 400 and negative feedback = 10%. If open loop gain changes by 20%, find the % change in closed loop gain and sacrifice factor (7)
- 8) a) Why an OPAMP is named as OPAMP ? Mention 4 special features of an ideal OPAMP . (2+4 = 6)
- b) Discuss the functions of two I/P ideal OPAMP as :
- 1) Inverting amplifier and unit inverter (3+1 = 4)
 - 2) Voltage Subtractor (5)
 - 3) Inverting Summing Amplifier (5)

APPENDIX

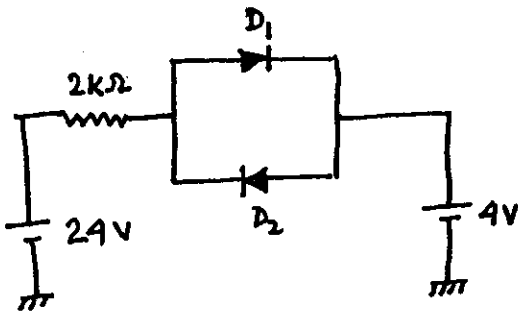

D₁ - D₂ are Si Diodes
r_f negligible. V_t = 0.7V.

Fig-I


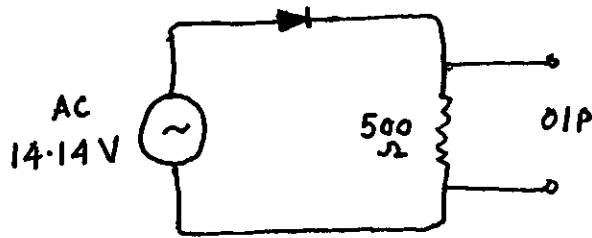


Fig-II

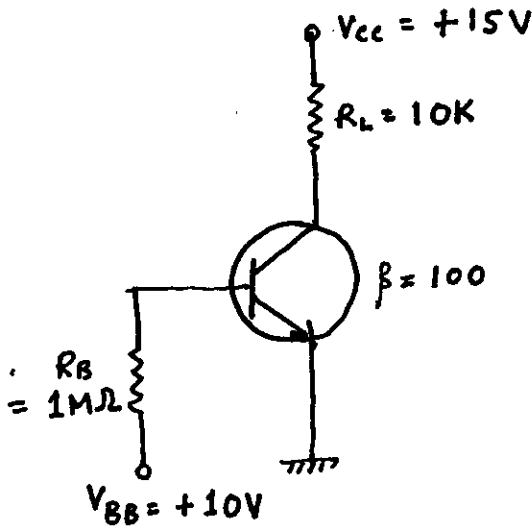

V_{BE} negligible

Fig-III.