

**B.E. ELECTRONICS AND TELE-COMMUNICATION ENGINEERING SECOND YEAR  
FIRST SEMESTER EXAM, 2023**

**ANALOG CIRCUITS- I**

**Time: Three hours**

**Full Marks: 100**




*(All parts of the same question must be answered together)*

**Module I [Answer any one (1×20=20)]**

1. a) Write names and briefly explain the operations of the circuits (i, ii, iii, and iv) . [10+10]

b) Sketch the output waveforms of the following circuits for

  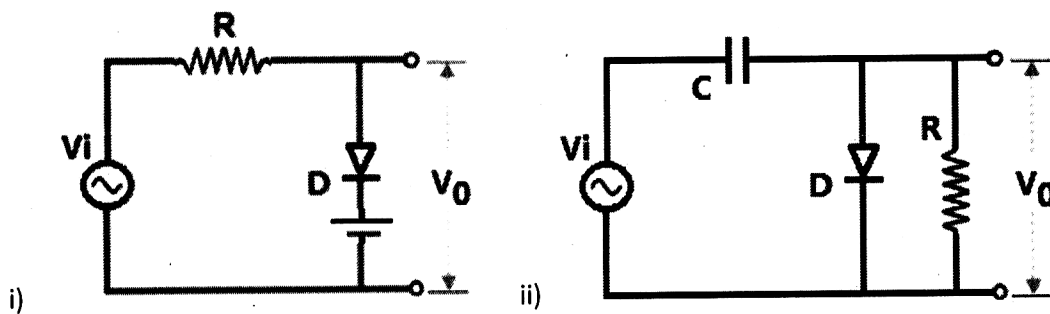- i. Sinusoidal input (consider diode drop)
- ii. Square input (consider diode drop)
- iii. Sinusoidal input (ideal diode)
- iv. Amplitude modulated input (ideal diode)



[ Turn over

**B.E. ELECTRONICS AND TELE-COMMUNICATION ENGINEERING SECOND YEAR  
FIRST SEMESTER EXAM, 2023**

ANALOG CIRCUITS- I

Time: Three hours

Full Marks: 100

2. a) A Zener voltage regulator has input voltage  $V_{in}=20V$  and  $R_S= 500\Omega$ . The Zener voltage at breakdown voltage is  $6V$ . The Zener current at breakdown ( $I_{zk}$ ) is  $0.1mA$  and maximum Zener current ( $I_{zm}$ ) is  $0.1 A$ . The dynamic resistance is  $20\Omega$ . Find the range of load resistance can be used. [ 10]
- b) Explain the output of a RC high pass filter for a pulse input. A pulse of amplitude  $10 V$  and width  $t_p =10 \mu s$  is applied to a high-pass RC circuit. Sketch the output waveforms indicating the voltage levels for (i)  $RC =t_p$ , (ii)  $RC =0.5t_p$  and (iii)  $RC= 2t_p$ . [10]

**Module II [Answer any two (2×15=30)]**

3. a) Draw a capacitive coupled CE mode npn BJT amplifier with an un-bypassed emitter resistance. With the help of small signal equivalent circuit (any one) find the expression for the voltage gain, input resistance and output resistance. [12]
- b) Explain the effect of coupling capacitances on voltage gain. [3]
4. a) Draw a collector to base feedback biasing of npn CE mode BJT to obtain  $S(I_{C0})=10$  and collector current of  $1mA$ . Assume Supply voltage as  $10 V$ . Set operating point at the mid of the load line. [10]
- b) Draw and explain the Darlington pair circuit using npn BJT. [5]
5. a) In a zero bias JFET determine the values of  $R_D$  and  $R_S$  to achieve maximum output voltage swing. Given that  $V_{DD}=10 V$ ,  $I_{DSS}=12mA$  and  $V_{GSoff}= -6V$ . [5]
- b) Explain Miller effect associated with CS mode FET amplifier with the help of small signal model. Why are source follower circuits free from Miller effect? [7+3]

**Module III [Answer any one (1×10=10)]**

6. Define Op-amp. Write down six characteristics of an ideal OP-Amp. Explain origins of input offset voltage, input bias current and slew rate of a practical op-amp. [2+3+5]
7. Draw basic differential amplifier using npn BJT. Find out the common mode and difference mode voltage gain for double input balanced mode configuration. [2+8]

**B.E. ELECTRONICS AND TELE-COMMUNICATION ENGINEERING SECOND YEAR  
FIRST SEMESTER EXAM, 2023**

ANALOG CIRCUITS- I

Time: Three hours

Full Marks: 100

**Module IV[Answer any two (2×20=40)]**

8. a) Define line and load regulation of a voltage regulator. Explain the short circuit protection circuit in a series voltage regulator. [4+6]
- b) Design a 10 V regulated power supply with a series voltage regulator. (Properly choose the values of resistances, input voltage range and Zener voltage). Assume Zener resistance is as  $0\Omega$  and Zener current range is 0.1 mA to 100 mA. [10]
9. a) Draw an inverting amplifier using OP-Amp. Determine the expression for voltage gain, input and output resistances considering a practical OP-Amp. [10]
- b) With the help of proper circuit diagram, input and output waveforms explain the operation of an integrator circuit using OP-Amp. [10]
- 10 a) Explain the super diode using OP-Amp. Draw a negative clipper circuit using OP-Amp and sketch the output for a rectangular input of 5V peak. [10]
- b) Draw an op-amp circuit to solve  $y = 5xy + 10x^2$  [10]