

B. ETCE 2ND YEAR 1ST SEMESTER SUPPLEMENTARY EXAMINATION, 2023
CIRCUIT ANALYSIS AND SYNTHESIS

Time: 3 Hours

Full Marks: 100

Part I: 30 MarksAnswer any **One (1)** Question from the followings: 30×1

- What do you mean by passive and active elements? Give examples. 4
 - What is a complex frequency? Explain its significance. 4
 - Explain how Q acts as an amplification factor in resonant circuits? 4
 - State the advantage offered by graph theory as applied to electric circuit problems. Explain the terms: branch, link, tree, co-tree and loop. 3+5
 - Explain what you mean by critical frequencies of driving point admittance function. What are the different properties of a driving point reactance function? 2+3
 - What are the properties of the R - L driving point impedance and R - C admittance function? 5
- The voltage waveform $v(t)$ across a capacitor C is shown in Fig. 1. Plot the current through C as a function of time t . 10
 - In the circuit of Fig. 2, determine the voltage V_0 using source transformation. 10
 - In the circuit of Fig. 3, $L_1 = 1500 \mu\text{H}$, $L_2 = 200 \mu\text{H}$ and $C_1 = 0.001 \mu\text{F}$. If free oscillations are set up in the circuit by some means, at what frequencies would they occur? 10

Part II: 60 MarksAnswer any **Four (4)** Question from the followings: 15×4

- For the network shown in Fig. 4, draw the graph, tree and obtain a cut-set schedule and equilibrium node equations and solve for node voltages and branch currents. 15
- Using nodal analysis, find the current and voltages in all the branches of the network for the circuit shown in Fig. 5. 7
 - Find the voltage V across 12Ω resistance using Norton's theorem for the circuit shown in Fig. 6. 8
- Find Y -parameters for the network shown in Fig. 7. 8
 - Find the value of L for which the circuit of Fig. 8 is resonant at a frequency $\omega = 10,000$ rad/sec. 7
- A filter section is to have design impedance of 500Ω , a cut-off frequency of 5 KHz and a frequency of infinite attenuation of 4 KHz . Determine the value of components if the section is to be m -derived π -filter. 8
 - Design a active notch filter for $f_0 = 2 \text{ KHz}$, $Q = 10$. Assume $C = 500 \text{ pF}$. 8
- The driving point impedance across the terminal 1, 2 in the network of Fig. 9 is $Z_D(s) = (2s^2 + 2)/(s^3 + 2s^2 + 2s + 2)$. If $Z(s)$ is an LC network, synthesize it in the first Foster form. Also find R . 8
 - The polynomial form of driving point impedance is $Z_D(s) = (2s^2 + 8s + 6)/(s^2 + 6s + 8)$. Determine the First Cauer form of network. 7
- Find the Laplace Transform of the functions
 - $f(t) = e^{-at} \sin \omega t u(t)$ 2
 - $f(t) = t \cos \omega t u(t)$ 2
 - Using the convolution theorem evaluate the inverse Laplace Transform for the following function

[Turn over

B. ETCE 2ND YEAR 1ST SEMESTER SUPPLEMENTARY EXAMINATION, 2023
CIRCUIT ANALYSIS AND SYNTHESIS

Time: 3 Hours

Full Marks: 100

$$F(s) = 1/(s+a)^2 \quad 3$$

(c) Find the $i(t)$ in the circuit (Fig. 10) when the switch "k" is closed at $t = 0$ (using Laplace Transform). 8

7. (a) Suppose that a periodic voltage is expressed as

$$v(t) = V_0 + \sum_{n=1}^{\infty} V_n \cos(n\omega_0 t - \alpha_n)$$

then calculate the average power and plots power spectra. 7

(b) In Fig. 11 $v_i(t) = 10 \text{sgn}(t)$ volt. Using Fourier Transform method find $v_c(t)$ and plot $v_c(t)$ versus t . 8

Part III: 10 Marks

Answer any **One (1)** Question from the followings: 10×1

1. Make a comparative study between Laplace and Fourier Transform.
2. Make a comparative study between LPF, HPF, BPF and BEF
3. Make a comparative study between Driving point and Transfer impedance

B. ETCE 2ND YEAR 1ST SEMESTER SUPPLEMENTARY EXAMINATION, 2023
CIRCUIT ANALYSIS AND SYNTHESIS

Time: 3 Hours

Full Marks: 100

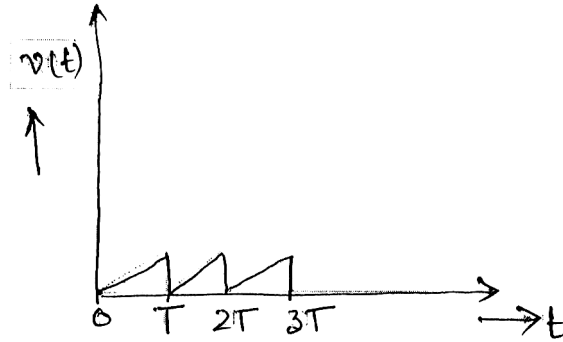


Fig. 1

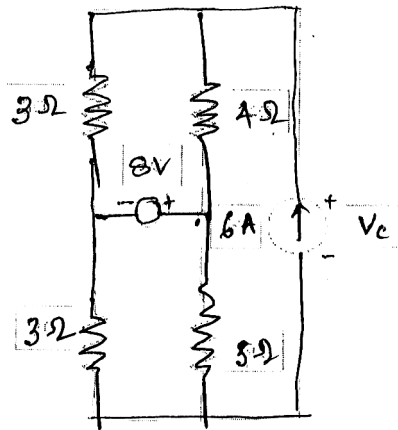


Fig. 2

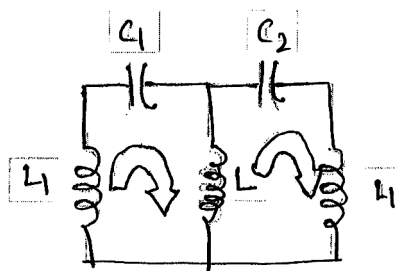


Fig. 3

B. ETCE 2ND YEAR 1ST SEMESTER SUPPLEMENTARY EXAMINATION, 2023
CIRCUIT ANALYSIS AND SYNTHESIS

Time: 3 Hours

Full Marks: 100

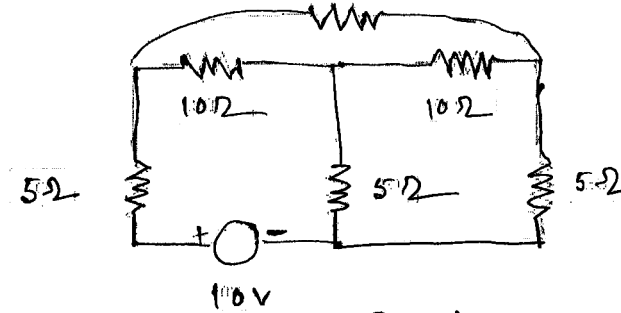


Fig. 4

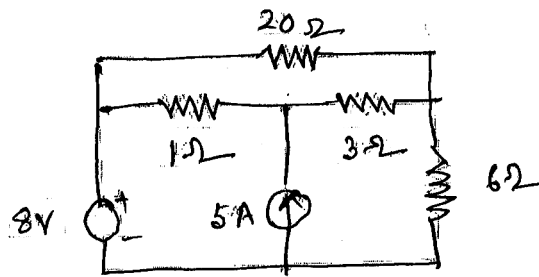


Fig. 5

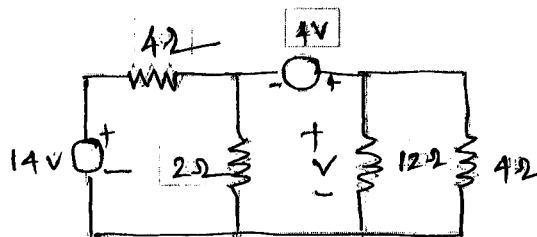


Fig. 6

B. ETCE 2ND YEAR 1ST SEMESTER SUPPLEMENTARY EXAMINATION, 2023
CIRCUIT ANALYSIS AND SYNTHESIS

Time: 3 Hours

Full Marks: 100

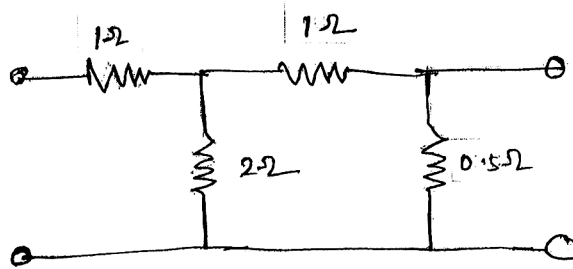


Fig. 7

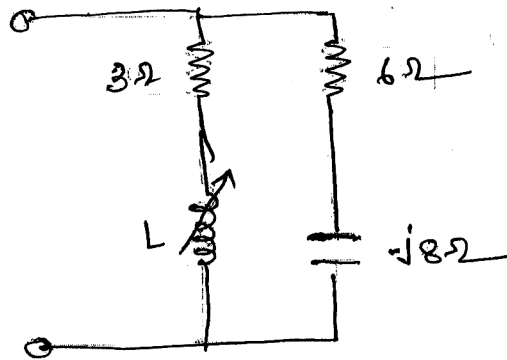


Fig. 8

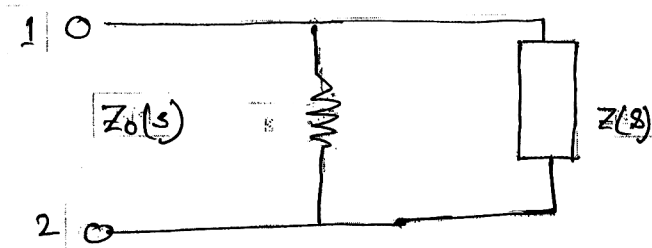


Fig. 9

B. ETCE 2ND YEAR 1ST SEMESTER SUPPLEMENTARY EXAMINATION, 2023
CIRCUIT ANALYSIS AND SYNTHESIS

Time: 3 Hours

Full Marks: 100

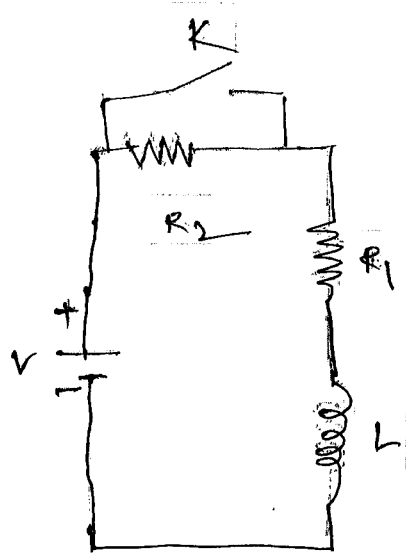


Fig. 10

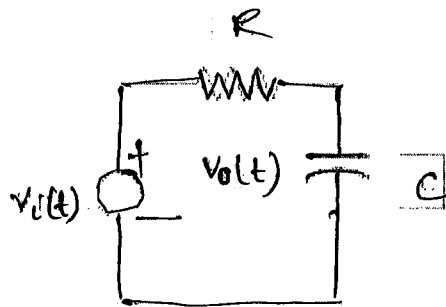


Fig. 11