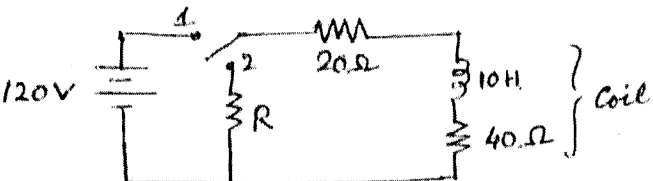
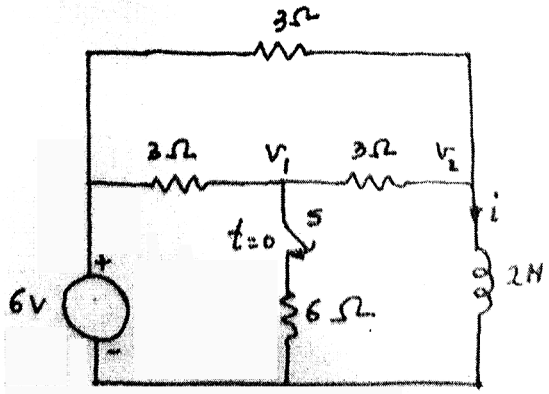
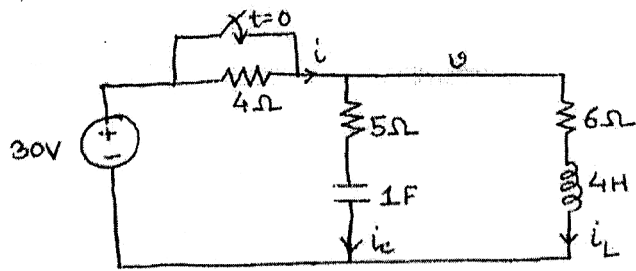


| Q.No. | | Marks |
|-------|--|------------------------------|
| 3. | <p>a) Derive the natural response $i(t)$ for the underdamped series RLC circuit and draw detailed response. State from derivation and indicate the following in the figure: (i) starting value (ii) upper and lower envelopes with their maximum values (iii) maximum overshoot and (iv) peak time and (v) 5% tolerance band.</p> <p>b) (i) A $50 \mu\text{F}$ capacitor is discharged through a $100 \text{ k}\Omega$ resistor. If the capacitor was charged to 400V initially, then (i) find initial energy stored W_0, (ii) time constant τ, (iii) expression for energy stored in capacitor $w_C(t)$ in terms of W_0, t and τ and (iv) energy stored after 600ms. How long will it take for the capacitor to discharge to 0.072 J?</p> <p style="text-align: center;">OR</p> <p>(ii) For the RL circuit in Fig. below, the switch is moved from position 1 to 2 at $t=0$. a) Find the voltage across the coil at the instant of changeover for $R=500\Omega$. b) What is the value of R for this voltage to be 120V? c) For the value of R as in b), determine the time taken to dissipate 95% of the stored energy.</p> <div style="text-align: center;">  </div> | <p>10</p> <p>5</p> <p>5</p> |
| 4. | <p>a) The circuit for a spark gap ignition system consists of an electrolytic capacitor of $0.01 \mu\text{F}$, in series with the ideal resistanceless spark gap, a 1mH inductance, a $1.25\text{k}\Omega$ resistance and a test object of $4\text{k}\Omega$. At the instant of spark gap breakdown, a surge generator has the capacitor charged to 200 kV. Find the current in the circuit and the voltage across the $4\text{k}\Omega$ test object. What is the time to reach the peak test voltage? Also find the initial rate of rise of voltage.</p> <p style="text-align: center;">OR</p> <p>b) An iron plunger is drawn into a solenoid of resistance 50Ω against a spring. 2.5A current flows into it nominally for a 250V, 50Hz supply. This drops to 1A when the plunger is drawn into the solenoid. Calculate i) impedance, ii) reactance, iii) inductance of solenoid and iv) stored energy for both positions of the solenoid.</p> | <p>10</p> <p>10</p> |
| 5. | <p>a) On applying 100V at 50Hz, 8A current flows and 120W power is consumed in coil A while 10A current and 500W power is consumed in coil B. If this supply is applied to the series connection of coils A and B, determine the resultant current and power consumed.</p> <p>b) (i) The voltages across a resistor, an inductor coil and a capacitor of a series RLC circuit are 170, 150 and 100V resp. and the current is 4A when 200V is applied across it. Consider the inductor as a coil with associated coil resistance. The capacitor can be considered to be ideal. Determine power factors of the inductor and the circuit.</p> <p style="text-align: center;">OR</p> <p>(ii) A capacitance C of $20\mu\text{F}$ is connected in series to a resistance R and an iron cored inductor L. The current through the circuit is 0.345A. The drops across the R, L and C elements are 25V, 40V, 55V while the drop across the R and L elements is 50V. Find (i) the applied voltage, (ii) frequency and (iii) loss in L.</p> | <p>5</p> <p>10</p> <p>10</p> |

| Q.No. | | Marks |
|-------|---|-------|
| 8. | <p>a) Draw the Laplace equivalent circuit with initial conditions represented as sources. Determine the initial conditions at $t=0+$ when the switch S is closed. Using Laplace transform, write the nodal equations and determine $I(s)$. Calculate $i(t)$. The resistance between the 6V source and V_1 is 3Ω.</p>  | 10 |
| OR | | 10 |
| | <p>b) Using Laplace transform, calculate $i(t)$. Determine the initial conditions i_L, v_C and i_C at $t=0+$.</p>  | |