

Bachelor of Instrumentation and Electronics Engineering, 2023
2nd year, 1st semester
DIGITAL ELECTRONICS

Time : Three hours

Full Marks : 100

ANSWER ALL MODULES

Module – I (4 Marks)

Q1. What decimal number corresponds to the binary pattern **10100110**, when it is in

- (a) **Excess-3 BCD** format, (b) **2's complement** format, (c) **sign-magnitude** format, and
(d) **Gray** format. (4)

Module – II (6 Marks)

Q2. Perform the following arithmetic operations :

- (a) **(-25) + (-121)** using **8-bit 2's complement** number system.
(b) **(963) + (3086)** using **Excess-3 BCD** numbers.

Represent the final results in decimal.

(3+3)

Module – III (40 Marks)

(Answer Q3 and ANY ONE from Q4 and Q5)

Q3. (a) Why are **CMOS transmission gates** preferred over both **n-MOS** and **p-MOS pass transistors** for connecting signals to a bus ?

(b) Draw the circuit of a **2-input TTL NOR** gate with totem-pole output.

(c) Draw the CMOS circuit to realize a **Full-Subtractor**. (5 + 5 + 10)

Q4. (a) Use **Karnaugh Map** technique to obtain the minimized expressions for the following functions as indicated :

(i) $F(W, X, Y, Z) = W'Y'Z' + WX'Y' + XY'Z + W'X'Y' + WX'Z + W'XZ' + WXYZ'$;
using **only NAND** gates

(ii) $F(A, B, C, D) = \prod M(2, 5, 7, 8, 13, 15) + d(0, 1, 4, 10)$; in **minimized SOP** form

(iii) $F(A, B, C, D) = \sum m(3, 4, 5, 7, 9, 13, 14, 15)$; in **minimized POS** form

[Turn over

(b) In **Positive Logic** certain logic circuit corresponds to the function

$$f = AB'C + A'BC + AB'$$

What will be the expression of the output from the same logic circuit in **Negative Logic** ?

(3 x 5 + 5)

Q5. (a) Using **one 8:1 Multiplexer** and **one 2:1 Multiplexer (if needed)**, realize the following function :

$$F(W, X, Y, Z) = W'X'Z' + WX' + WX'Y' + X'Y$$

(b) Realize a **3-input Priority Encoder** using a suitable **PROM** of minimal configuration and necessary **logic gates** in **minimum number**. Explicitly mention the priority order chosen for the inputs and corresponding output codes. **Draw the necessary diagram.** (10 + 10)

Module – IV (50 Marks)

(Answer Q6 and and ANY ONE from Q7 and Q8)

Q6. (a) The circuit shown in **Fig. P6(a)** represents a certain **3-bit counter**. Initial state of this counter is $Q_2Q_1Q_0 = 000$. Draw the **state transition diagram** for this counter. What is the **modulus** of this counter ? Can this counter face **lock-out problem** ? Establish your answer. (10 + 1 + 4)

 


Fig. P6(a)

(b) For the circuit shown in **Fig. P6(b)** realize and draw the **State Transition Diagram**. Input to the circuit is **A** and the output is **Z**. Is it a **Moore machine** or a **Mealy machine** ? (9+1)

 


Fig. P6(b)

Q6. (c) Design a **2-bit synchronous binary down counter**. Use **T-FFs** as memory elements. (5)

Q7. Design a **Sequence detector** which detects the presence of input sequence **"11"** and **sets the output to logic 1 state**. The output is **reset again** by the presence of a **"00"** sequence. Use **D-FFs** as memory elements. Is there **any lock-out possibility** in your design ? Justify.
(18 + 2)

Q8. (a) Design a sequence generator which generates the sequence **"100110"** repeatedly. Use minimum number of **D-FFs**.
(b) Using **SR-FF** as memory element, realize a sequential **Gray to Binary** code converter. The input Gray bits are **coming serially starting from the MSB**. (10 + 10)

----- * -----