

**B.E. INSTRUMENTATION AND ELECTRONICS
ENGINEERING EXAMINATION, 2023
(3rd Year, 2nd Semester)**

POWER ELECTRONICS (HONS)

Time : Three hours

Full Marks : 100

CO1: Describe the working principles and usability of different power electronic devices:-

Answer any two questions:-

- 1.(a) What is meant by the reverse recovery time of a power electronic diode? On what factors does its value depend? How does this parameter affect the performance of the device? 10
- (b) For a power electronic diode, the reverse recovery time is 5 microsecond and the rate of fall of the diode current is 70 Amp/microsecond. If the softness factor of the diode is 0.40, determine,
i) the storage charge Q_{RR} ,
ii) the peak reverse current I_{RR} .
Deduce necessary relations. 10
2. (a) What is meant by the overdriving of a power transistor? How does it affect the switching characteristics of the device? 6
- (b) For a power electronic switch using a BJT, deduce the expression for the total power loss during switching. 14
3. (a) Explain the static characteristics of a four layer device using a two-transistor model. 12
- (b) What is meant by a TRIAC? Explain some applications of such a device. 8

CO2: Explain the working principle of single phase and polyphase converter and inverter circuits.

Answer any two questions:-

[Turn over

4. (a) With the help of circuit and waveform diagrams explain the operation of a three phase bridge rectifier. 8
- (b) For a three phase bridge rectifier with a purely resistive load , determine,
 i) the transformer utilization factor,
 ii) the peak inverse voltage of each diode,
 iii) the peak current through a single diode . 12
5. (a) With the help of necessary derivations explain the operation of a step-up dc-dc converter. How can this principle be applied to transfer energy from one voltage source to another ? 10
- (b) For a step-up dc-dc converter with a resistive load, find out the output ripple current. 10
6. (a) With the help of circuit and waveform diagrams, describe the function of a single phase half-bridge inverter with an inductive load. Calculate the performance parameters of such a circuit. 14
- (b) How can the above mentioned circuit be converted into a full-bridge inverter? 6

CO3: Describe the speed control techniques of AC and DC motors.

7. Describe, some methods of controlling the speed of dc series motors. 10

CO4: Explain the working principle of SMPS and UPS.

8. With the help a block diagram describe the function of a static switch. Write down, in tabular form, the differences between an SMPS and an UPS. 10