MASTER OF ELECTRICAL ENGINEERING EXAMINATION, 2018

(1st Year, 2nd Semester)

HIGH VOLTAGE MEASUREMENTS

Time: Three Hours Full Marks: 100

Answer any Five Questions

- 1. a) Draw the circuit diagram of a peak voltmeter that contain a bleeder resistance. Describe the principle of operation of such a peak voltmeter and discuss about the errors associated with peak voltage measurement.
 10
 - b) Explain how a sphere gap can be used to measure the peak value of high voltage. What are the parameters and factors that influence such voltage measurement?
- 2. a) Briefly explain the operation of Klydonograph with suitable diagram. What is the significance of 'Lichtenberg figures' in lightning impulse voltage measurement.
 - Explain the techniques of impedance matching for the measurement of high voltage surge with respect to both divider end and oscilloscope end.
- 3. Explain what you mean by apparent charge. Why the concept of apparent charge has to be introduced in measuring partial discharge? Describe an experimental setup for partial discharge measurement from a sample?
 20
- 4. a) Briefly explain the construction and the working principle of Generating voltmeter with a neat diagram. Also mention the advantage and limitations of this voltmeter.
 - b) A generating voltmeter is read 250 kV with an indicating meter having a range of (0 20) μA.
 Calculate the capacitance of the generating voltmeter when the driving motor rotates at a constant speed of 1500 RPM.
- Briefly explain the operation of Schering Bridge for both grounded and ungrounded test object.
 - b) An AC Schering bridge was made up as follows:
 Arm AB, a capacitor of 0.00125 μF in parallel with 3.18 kΩ resistance, BC a resistance of 636 Ω, arm CD an unknown capacitor C_x and R_x in series, arm DA a capacitance of 100 pF. Determine the value of capacitance C_x, resistance R_x and dissipation factor.
- 6. a) Explain the different types of divider are used in high voltage measurement. Discuss their advantage and limitations.
 - b) Describe the measurement procedure of high impulse current by a Rogowski Coil. 08

7. Write short notes on:

10×2

- (i) Capacitive Voltage Transformer (CVT)
- (ii) Electrostatic voltmeter.

--0-