

**B.C.S.E. 1<sup>st</sup> Year, 1<sup>st</sup> Semester Supplementary Examination, 2018**  
**Digital Logic**

Full Marks: 100

Time : 3 Hr

**Answer all questions (Q1 - Q3). Write answers to the point and state all the assumptions (wherever required).**

**ALL PARTS OF THE QUESTION SHOULD BE ANSWERED TOGETHER**

Q 1) Attempt all questions (1a - 1k) (40)

- (a) Convert the following  $(1100101010)_2$  to octal, decimal and hexadecimal format (3)
- (b) Convert the following decimal number,  $(347)_{10}$  to binary, octal and hexadecimal formats (3)
- (c) Perform the following addition:  $(FFF)_{16} + (A34)_{16}$  (2)
- (d) Perform the following subtraction using two's complement  $(1101011)_2 - (111010)_2$  (2)
- (e) Represent  $(28)_{10}$  in binary form using :  $(2 \times 2 = 4)$   
 (i) BCD Code (ii) Excess-3 Code
- (f) Describe about the standard representation for logical functions. (4)
- (g) Explain the operation of NAND and NOR gates using figures and truth-tables. Why are these gates important in digital electronics (5)
- (h) Design 3 to 8 line decoder. (4)
- (i) What is Race-around problem? How can you rectify it? (5)
- (j) Compare combinational and sequential logic circuit. (4)
- (k) Explain the operation of a JK flip-flop. (4)

Q 2) Answer any two questions  $(2 \times 20 = 40)$

- (a) (i) Make a K-Map for the following function and consequently minimize it:  
 (10)  

$$f = AB + A\bar{C} + C + AD + A\bar{B}C + ABC$$
- (ii) Design the full subtractor using NOR gates only. (5)
- (iii) Explain the working of bi-directional shift registers. (5)
- (b) (i) Convert the following  $30_{16}$  to binary. Show each step clearly. (3)

[ Turn over

- (ii) Perform the following:  $555 - 332$  using 9's complement Binary Coded Decimal (BCD) subtraction. (4)
- (iii) A four-variable Boolean function is given by

$$F = A.B.C + B.C.D + A.\bar{C}.D$$

and

$$\phi = \{A.B.\bar{C}.\bar{D}, A.\bar{B}.C.D, \bar{A}.\bar{B}.C.D\}$$

is a **don't-care** function. Using a Karnaugh map or otherwise :

- (I) Find the simplest sum of products expression for  $F$ . (5)
- (II) Design a circuit to implement  $F$  using NAND gates only (4)
- (III) Design a circuit to implement  $F$  using NOR gates only. (4)
- (c) (i) State the logic circuit, truth table and derive the equivalent logic expression from the truth table of the following Boolean expression  $Y = A\bar{B} + \bar{B}C$   
(3 + 4 + 3 = 10)
- (ii) Explain the operation of a left/right shift register. Use diagrams to explain the operation. (10)

Q 3) Answer any **two** question (2 × 10 = 20)

- (a) Solve the following using Quine-McCluskey Method

$$F(A, B, C, D) = \Sigma(23, 7, 9, 11, 13) + \Sigma\phi(1, 10, 15)$$

- (b) Design a 3 bit binary DOWN counter.
- (c) Design a digital circuit for generating a sequence  $1 - 3 - 5 - 7 - 1 - 3 - 5 - \dots$ . Give its corresponding timing diagram