

B.E. POWER ENGINEERING, SECOND YEAR, FIRST SEMESTER - 2019

Subject : ELECTRONICS

Time : Three Hours

Full Marks : 100

- Instructions :
- 1) This paper contains **eight** questions and an **APPENDIX**. Answer any **five** questions
 - 2) Answers of sub-questions of any question to be written in **one place**. Do not be haphazard.
 - 3) Write 'Answer' beside the final answer of numerical problem.
 - 4) Justified marks will be given for neat presentation.

- Q1.**
- a) Segregate the following elements into Active and Passive groups: PN-diode, Capacitor, Inductor, BJT, Transformer, FET, IC741, Zener diode. (4)
 - b) Copy the circuit of the Fig.-I of APPENDIX. Apply Thevenin's Theorem to find current (value and direction) in the branch AB. Also find the same if the polarity of 12V battery be reversed? (6+4)
 - c) Each Amplifier of Group A is **Closely related** with **One** of the terms of Group - B. Find out the **best** matches. (No Explanations) **Group - A** : Voltage Amplifier, Power Amplifier, Audio Frequency Amplifier, Radio Frequency Amplifier, R-C Coupled Amplifier, Transformer Coupled Amplifier.
Group - B : 10Hz to 20kHz, Handles large I/P signal, Good impedance matching, Handles small I/P signal, 300kHz to 30MHz, Almost flat frequency response. (1x6=6)
- Q2.**
- a) Define α -cut-off frequency, f_T frequency of BJT .
 What is the value of h_{FB} at f_T frequency? (1x3=3)
 - b) Draw neat circuit diagram of a Bridge Rectifier showing proper direction of current at each half cycle of the I/P signal.(no detailed description) (4)
 - c) A 2-diode fullwave rectifier uses **Si-diodes** of $r_f=10\Omega$ with a load of 200Ω . I/P AC voltage across the half secondary winding is 35.4V, 50Hz. Draw the circuit. Calculate DC O/P Voltage, % efficiency, O/P frequency. (2+3+1+1=7)
 - c) Fig-II of APPENDIX shows the O/P waveform of a half wave rectifier with I/P Voltage: $V = V_0 \sin \omega t$ ($0 \leq t \leq T$, $\omega T=2\pi$). Determine the dc-value and ac-value of the O/P. Show your mathematical steps. (3+3=6)
- Q3.**
- a) Draw circuit of a negative clipper. Show the I/P, O/P and explain the typical nature of the "clipped O/P" (i.e. How it forms?) (2+3=5)
 - b) How do you use a Clipper Circuit to estimate 'turn on voltage' (barrier potential) of a real diode? —describe briefly. You may be provided with a CRO. (5)
 - c) How do you differentiate between Si-diode and Ge-diode by their FB/RB characteristics ? Which is more stable device? – Si or Ge? Why? (1+1+1=3)

- d) Deduce that forward dynamic resistance (r_e) of a PN-diode is inversely proportional to the FB current. Estimate the value of r_e for a forward current of 5mA. (4+1=5)
- e) What are two specification parameters of PN-diode? (2)
- Q4.**
- a) It is well known that an Emitter follower has voltage gain less than unity. Can you call it an amplifier? Justify. State two major uses of emitter follower (3+2=5)
- b) Copy the circuit of Fig.-III which consists of a Si-BJT. Find out its' voltage gain (A_v); hence justify that it is truly an emitter follower. (7+2=9)
- c) Convert decimal 75.9296875 to Octal, then to binary. (2+2=4)
- d) What is the full form of the term "Bit". (2)
- Q5.**
- a) Take $V_{CE} - I_C$ axes. Draw an arbitrary load line and graphically present the operations of Class-A, Class-B, Class-C amplifiers. Use three separate diagrams. No detail descriptions. Only neat drawings needed. (2x3=6)
- b) one of the above three classes provides "amplification as well as rectification". __ Which one? (2)
- c) Define Stabilization factor (S). Draw a simple voltage stabilizer circuit using a series resistance (R_S), Zener resistance (r_z) and load resistance (R_L). Deduce an expression for "S" in terms of above resistances. Express 'S' in its' simplest form by approximation. Hence, establish a simple relation between I/P (E_i) and O/P (E_o) voltages. (1+2+4+2=9)
- d) In the same circuit, as above, $r_z = 5\Omega$; $V_z = 10V$, $R_S = 100\Omega$, $R_L = 1k\Omega$ and E_i varies within the range 20V – 25V. Find % regulation. (3)
- Q6.**
- a) You are given three **NAND** gates. Using them construct a circuit with OR as O/P. What would be the O/P if you replace all the **NAND** gates by **NOR** gates? (2+2=4)
- b) Copy the Fig.-IV of **APPENDIX**. Find the O/P (X) for A and B both are grounded. (4)
- c) Copy the Fig.- V of **APPENDIX**. It is a Si-BJT with β -value ranging 100 to 120 for temperature range 25°C - 75°C. Calculate % variations of I_C and V_{CE} ? What is the change in Power dissipation of BJT? (5+5+2=12)
- Q7.**
- a) Draw neat circuit diagram of a practical BJT amplifier with single battery potential divider bias. Name the various capacitors therein. Draw its' DC and AC equivalent circuits. Write down the expression of voltage gain (A_v) and briefly explain the effect of a particular capacitor on A_v (3x2+2x2+1x2=12)
- b) Write equation of DC load line of the amplifier, as above, with proper chosen axes. Shade the area representing the power dissipation of BJT. What is Q-point? Where it should be located for maximum Power dissipation? (1x4=4)

c) $X = 1\ 0\ 1\ 1\ 1\ 0\ 1$, $Y = 1\ 1\ 1\ 1\ 1\ 0$. Perform the operation $(X-Y)$ using 1's Complement and 2's complement.






(2+2=4)

Q8. a) Suppose A, B are two I/Ps. Construct a logic circuit using **only** NAND gates with $A \oplus B$ as O/P. Derive the O/P. (3+2=5)

b) Write down Truth Table of a Full Adder and derive Boolean expressions for "Sum" and "Carry-Out". Draw logic circuit of Full Adder. (2+4+3=9)

c) Carefully copy the Truth Table of Fig.-VI of APPENDIX. Express the O/P (X) as a Boolean function of A, B, C. Simplify X and finally draw the logic circuit using the most minimum number of logic gates. (1+3+2=6)

APPENDIX

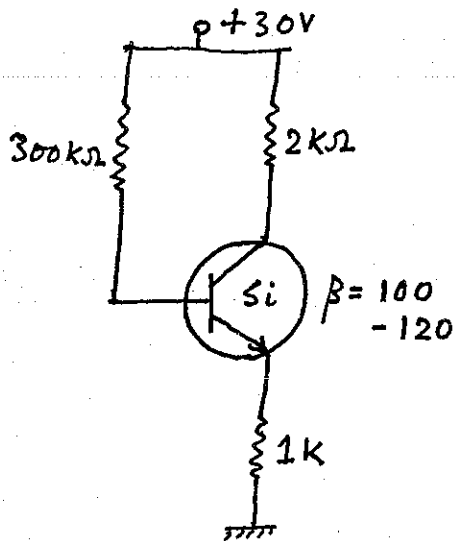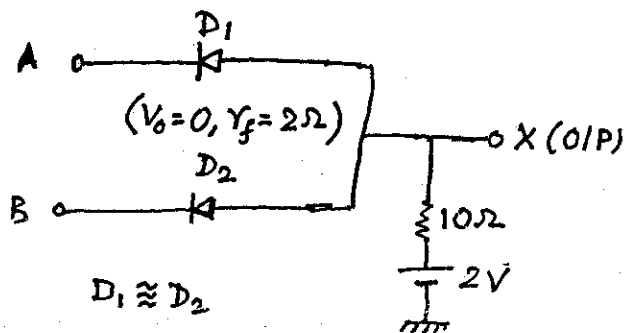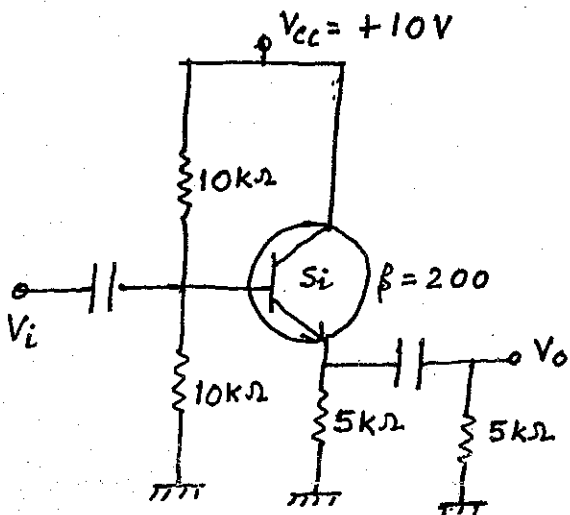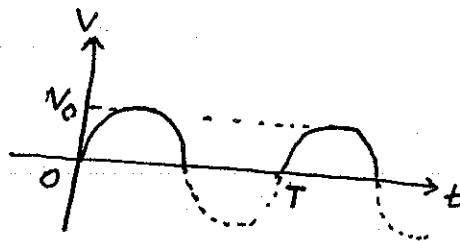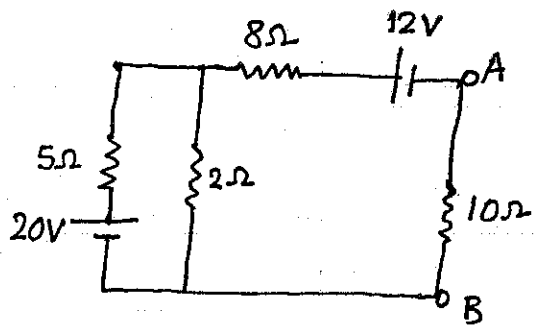

| A | B | C | X |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 |

fig-VI