

B. E. ELECTRICAL ENGINEERING 2ND YEAR 1ST SEMESTER EXAMINATION, 2018

SUBJECT: - ELECTRICAL MEASUREMENT & MEASURING INSTRUMENTS

Time: Three hours

**Full Marks 100
(50 marks for each part)**

Use a separate Answer-Script for each part

PART-I

Question No. 1 (carries 20 marks) is compulsory and attempt two more (15 marks each) from the rest.

1. a) The sensitivity of Wheatstone bridge is defined as ratio of 1
- (i) Deflection of the galvanometer to the unit fractional change in the value of unknown resistance
 - (ii) Square of the deflection of the galvanometer to the unit fractional change in the value of unknown resistance
 - (iii) Deflection of the galvanometer to the twice of the unit fractional change in the value of unknown resistance
 - (iv) Unit fractional change in the value of unknown resistance to the deflection of the galvanometer
- b) The dielectric loss of a capacitor can be measured by 1
- i) Owen bridge
 - ii) Schering bridge
 - iii) Wien bridge
 - iv) Maxwell bridge
- c) The *Gauge Factor* and *Transverse sensitivity* of a strain gauge should be 1
- i) High and Low respectively
 - ii) High and High respectively
 - iii) Low and Low respectively
 - iv) Low and High respectively
- d) In a Kelvin's double bridge two sets of readings are taken when measuring a low resistance, one with the current in one direction and the other with direction of current reversed. This is done to 1
- i) eliminate the effect of contact resistance
 - ii) eliminate the effect of resistance of leads
 - iii) correct for changes in battery voltage
 - iv) eliminate the effect of thermo-electric emfs
- e) The bridge sensitivity for Wheatstone bridge based strain measurement using one active and one dummy strain gauge is 1
- i) 1
 - ii) 0.5
 - iii) 0.25
 - iv) none of these
- f) What is **phantom loading** in the context of calibration of wattmeter? 3
- g) Define **gauge factor** of a strain gauge. How is it related to **Poisson's ratio**, μ ? 3
- h) What do you mean by "**standardization**" of a dc potentiometer? 3
- i) How do iron losses in a specimen of magnetic material depend on excitation frequency? 3
- j) Why is reference (cold) junction compensation used for thermocouple? 3


B. E. ELECTRICAL ENGINEERING 2ND YEAR 1ST SEMESTER EXAMINATION, 2018**SUBJECT: - ELECTRICAL MEASUREMENT & MEASURING INSTRUMENTS**

Time: Three hours

Full Marks 100
(50 marks for each part)

Use a separate Answer-Script for each part

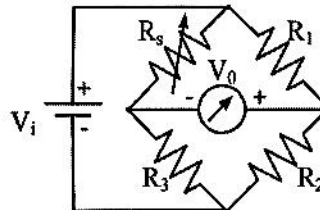2. a) What are the precautions to be taken in a high voltage Schering Bridge? 3
- b) A standard cell of 1.0186V used with a dc potentiometer balances at 50 cm. Calculate (i) emf of a cell that balances at 70 cm; (ii) The percentage error of a voltmeter measuring a voltage which balances at 65 cm when reading 1.35V; (iii) The percentage error in an ammeter that reads 0.45A when balance is secured at 43.5 cm while measuring potential difference across a 2 ohm resistor in the ammeter circuit. 5
- c) Derive the expression of measurement sensitivity for a Wheatstone bridge method based strain measurement with four active gauges. 7
3. a) A capacitor with an electrostatic voltmeter of infinite resistance and 10 μF capacitance connected across it, is charged to a potential of 100 volts. After disconnecting from charging source the potential falls from 100 V to 50 V in 20.8 seconds. When an additional 50 μF air capacitor is connected in parallel with the test capacitor, the voltage falls from 100 V to 50 V in 55.5 seconds, what is the leakage resistance of the test capacitor? 5
- b) A Crompton potentiometer has a coarse dial with 15 steps, where each step represents 0.1 V and each dial resistance is 10 ohms. The fine dial is 11 ohms with 200 divisions. How can it be transformed into a dual range potentiometer with multiplying factors X1 and X 0.1. 5
- c) A strain gauge forms one arm of the bridge shown in the figure below and has a nominal resistance without any load as $R_s = 1\text{k}\Omega$. Other bridge resistances are $R_1 = R_2 = R_3 = 1\text{k}\Omega$. During certain measurement of strain, when the bridge is excited by voltage source (V_i) of 10 V, the strain gauge resistance increases by 1Ω . Find the voltage V_0 across the detector. 5



4. a) The total iron loss in a sample is 300 watts at 50 Hz, with a loss component due to eddy current 5 times of that due to hysteresis. At what frequency will the iron loss double itself, if the peak flux density is kept the same? 4
- b) Comment on relative merits and demerits of Ring specimens and square shaped specimens for magnetic tests. 4
- c) Why is it difficult to measure low resistances using Wheatstone's bridge? Explain how the problem is overcome in measuring low resistance by the use of Kelvin's double bridge. 7
5. Write Short Notes on:
- a) Insulation Megger 7.5
- b) Series and Shunt type ohmmeters 7.5

B.E. ELECTRICAL ENGINEERING 2ND YEAR 1ST SEMESTER EXAMINATION, 2018**SUBJECT: - ELECTRICAL MEASUREMENT & MEASURING INSTRUMENTS**

Full Marks 100

(50 marks for each part)

Time: Three hours

Use a separate Answer-Script for each part

No. of Questions	PART- II	Marks
	<i>Answer any Five only.</i>	
1.	<p>Answer any <i>Two</i> from the following:</p> <p>a) "Universal shunt is used to alter the full scale current only for a PMMC meter." – Justify in favour of or against the statement.</p> <p>b) "Logarithmic decrement is an indirect measure of the settling time of an under damped instrument." – Justify in favour of or against the statement.</p> <p>c) "Reading of a moving iron instrument is subjected to waveform error." – Justify in favour of or against the statement.</p>	2x5=10
2.	<p>a) A resistance of 50 ohm is connected in series with one rectifying device, one permanent magnet moving coil ammeter and one electro-dynamometer type ammeter. The entire circuit is connected across a sinusoidal ac supply of 100 V. The resistance of rectifying device is 50 ohm in one direction and 250 ohm in other direction. Calculate the readings of two ammeters.</p> <p>b) What happens to the reading of a PMMC voltmeter if one of its control springs snaps?</p>	7+3
3.	<p>a) A moving iron instrument has full scale current of 100mA. It is converted to a 250V voltmeter by using series resistance made of a material having negligible resistance temperature coefficient. The meter has a resistance of 300 ohm at 20°C and an inductance of 100mH. After carrying a current steadily for a long time, the resistance of the coil increases to 369 ohm due to self heating. Calculate the error due to self heating when the meter is subjected to a voltage of</p> <p>(i) 250V at 50Hz (ii) 250V at 60Hz.</p> <p>b) Why does the inductance of a moving iron instrument vary with deflection?</p>	7+3

4.	<p>a) A correctly adjusted, single phase, 240V induction watt-hour meter has a constant of 600 revolutions per kWh. Determine the speed of the disc, for a current of 10A at a power factor of 0.8 lagging. If the lag adjustment is altered so that the phase angle between voltage coil flux and applied voltage is 86°, calculate the error introduced at</p> <p>(i) unity power factor (ii) 0.5 power factor lagging</p> <p>b) "Series coil is used to compensate the friction torque in an induction type watt-hour meter." – State clearly whether the statement is true or false and justify your comment.</p>	7+3
5.	<p>a) A Current Transformer has a bar primary and 200 turns secondary. An ammeter of resistance 1.3Ω and reactance of 0.8Ω is connected as burden across the secondary winding having a resistance of 0.4Ω and reactance of 0.7Ω. The magnetizing and loss ampere turns are 80 and 40, respectively. Find the primary current, the ratio-error and phase angle when secondary current is 8A.</p> <p>b) State three differences between a measuring CT and a protection CT.</p>	7+3
6.	<p>a)</p> <div style="text-align: center;"> <p style="text-align: center;">Figure-1</p> </div> <p>An electro-dynamometer type wattmeter with ideal current coil (CC) and pressure coil (PC) has been inserted in a circuit, as shown in Figure-1. What will the wattmeter read?</p> <p>b) How do you compensate the effect of inductance of the pressure coil of an electro-dynamometer type wattmeter? Justify your solution.</p>	7+3
7.	<p>Write short note on any <i>One</i>:</p> <p>a) Measurement of power at high current and high voltage</p> <p>b) Tuning of vibration galvanometer</p>	10