

**BACHELOR OF ELECTRICAL ENGINEERING 3RD YR 1<sup>ST</sup> SEMESTER EXAMINATION, 2018**(1<sup>st</sup> / 2<sup>nd</sup>-Semester/Repeat/Supplementary/Annual/Bi-Annual)**SUBJECT: - ELECTRICAL INSTRUMENTATION**

Time: Two hours/Three hours/ Four hours/ Six hours

Full Marks 100  
(50 marks for each part)

Use a separate Answer-Script for each part

PART I		Marks
1.	<p><b>Answer Question:1 and any TWO from the rest:</b></p> <p><b>Answer any four :</b></p> <p>a) For LVDT, the PSD converts the AC signal into bipolar DC signal -Justify.</p> <p>b) Why differential capacitive sensor can produce linear output?</p> <p>c) Why piezoelectric sensor can be used only for vibrating load condition but not for steady load condition?</p> <p>d) Explain in brief how the signal conditioning circuit used with accelerometer can produce outputs as vibration , velocity and acceleration components.</p> <p>e) Why lifting gate control valve is used for flow control of fluid containing solid matters?</p> <p>f) What is the difference in operation of ultrasonic sensor operating in Doppler frequency shift and pulse echo modes?</p>	4 X 5=20
2.	<p>a) Draw equivalent circuit of a LVDT, whose output is connected to meter. Also derive the expression for frequency domain transfer function.</p> <p>b) Illustrate a scheme for measurement of displacement by LVDT under dynamic condition.</p> <p>c) Draw the reactive AC bridge circuit for capacitive sensor Also derive the expression of bridge output for change in capacitance in null and direct method.</p>	5+5+5

[ Turn over

**BACHELOR OF ELECTRICAL ENGINEERING 3RD YR 1<sup>ST</sup> SEMESTER EXAMINATION, 2018**  
(1<sup>st</sup> / 2<sup>nd</sup>-Semester/Repeat/Supplementary/Annual/Bi-Annual)

**SUBJECT: - ELECTRICAL INSTRUMENTATION**

Full Marks 100

Time: Two hours/Three hours/ Four hours/ Six hours

(50 marks for each part)

3.	a) Discuss in brief about the working principle of diaphragm type capacitive sensor.  b) Draw the equivalent circuit of a piezoelectric sensor and derive the expression of frequency domain transfer function considering voltage as output and displacement as input.	7+8
4.	a) Illustrate a scheme for liquid level measurement in a tank by ultrasonic sensor following pulse-echo method.  b) Illustrate a scheme for liquid flow rate measurement for bi-directional flow using ultrasonic sensor.	8+7
5.	<p><b>Write short notes on any three:</b></p> i) Thickness measurement by capacitive sensor. ii) Humidity measurement by capacitive sensor. iii) Force and Torque measurement. iv) Hot wire anemometer. v) Electromagnetic type velocity sensor. vi) Servo type accelerometer.	3X5


**B.E.E. (EVENING) 3<sup>RD</sup> YEAR 1<sup>ST</sup> SEMESTER**  
**SUPPLEMENTARY EXAMINATION, 2018**

**SUBJECT: - ELECTRICAL INSTRUMENTATION**

**Time: Three hours**

**Full Marks 100**  
**(50 marks for each part)**

Use a separate Answer-Script for each part

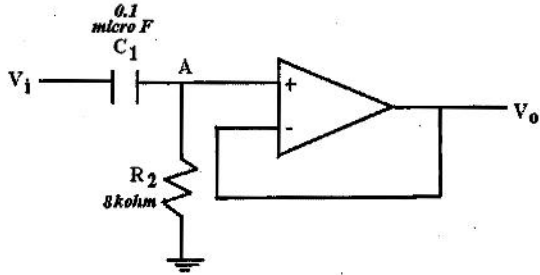No. of Questions	PART-II	Marks
<b>Answer any two</b>		
1. a)	Prove that Butterworth poles are situated on an $s$ -plane unit circle.	(10+15=25)
b)	The transfer function of an electrical filter circuit is given as follows: $H(s) = \frac{10}{s^2 + 4549s + 10349030}$ Realize the above transfer function using an active filter circuit. Find the pass-band gain and cut-off frequency.	
2. a)	What are <i>Rounding off</i> and <i>Truncation</i> type Analog to Digital converters (ADCs)?	6
b)	Explain the operation of successive approximation type ADC for 3 bits.	8
c)	Obtain a 4-bit binary representation of an analog signal value of 10.75 V using successive approximation type ADC. Reference voltage is 12 V. Find out the conversion time in seconds and quantization error in volts. The clock frequency is 1kHz.	7
d)	What are gain and offset errors of ADC?	4
3. a)	Explain the principle of operation of switched capacitor circuit. What are the main advantages of such circuits in IC technology?	6+4
b)	Derive the transfer function of a band pass filter using switched capacitor representation (Draw necessary circuit realization).	10
c)	Draw the Switched capacitor implementation of the following circuit. Assume switching frequency is 1kHz.	5
		
4.	Write notes on any <i>two</i>	(12½X2=25)
a)	Operation of a 3 bit unipolar R-2R ladder network based DAC	
b)	Linear model of phase locked loop (PLL)	
c)	State variable Filter	
d)	Storage Oscilloscope	