

**BACHELOR OF ELECTRONICS & TELE-COMMUNICATION ENGINEERING EXAMINATION, 2018**

( 1st Year, 2nd Semester )

**CIRCUIT THEORY**

Time : Three hours

Full Marks : 100


( 50 marks for each Group )

Use a separate Answer-Script for each group

*Answer all the parts of a question in the same place**All questions carry equal marks**Answer any three from Group-A and any two from Group-B***Group-A**

1. A voltage wave having the form shown in Fig. 1 is applied across a  $4\Omega$  resistance. Find the expression for the current  $i(t)$  using Fourier series. Also draw the amplitude and phase spectra.

(8+2)

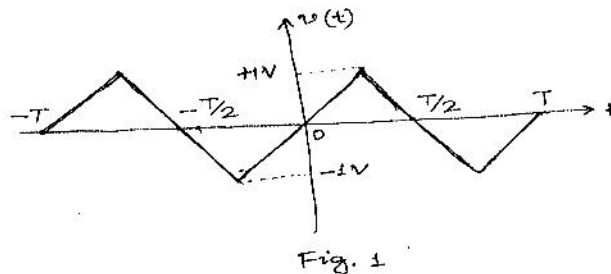

2. a) Calculate the Fourier transform of  $g(t) = \exp(-\alpha t)$ , where  $\alpha$  is a constant and it is either positive or negative.
- b) In the circuit of Fig. 2,  $i(t) = 10 \exp(-t) u(t)$  A, where  $u(t)$  is a unit step function. Calculate the voltage  $v(t)$  using Fourier transform method.

(3+7)

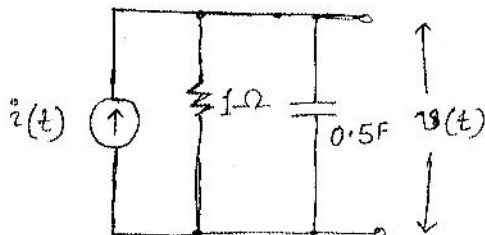


Fig.2

3. The waveform of input voltage,  $v_1(t)$  is shown in Fig. 3 and it is applied to the initially un-energised RC circuit shown in Fig. 4. Determine the output voltage  $v_2(t)$  for  $t \geq 0$  using Laplace transform method. Also sketch  $v_2(t)$  approximately.

(8+2)

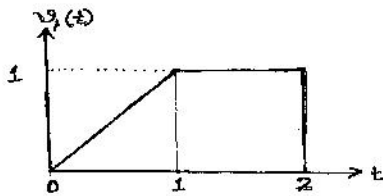


Fig. 3

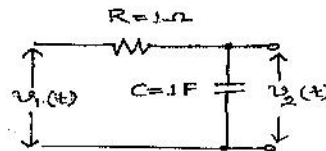


Fig. 4

4. The circuit shown in Fig. 5 is initially in the steady state with the switch S open. At  $t=0$ , the switch S is closed. Obtain the current through the inductor for  $t > 0$  using Laplace transform method.

(10)

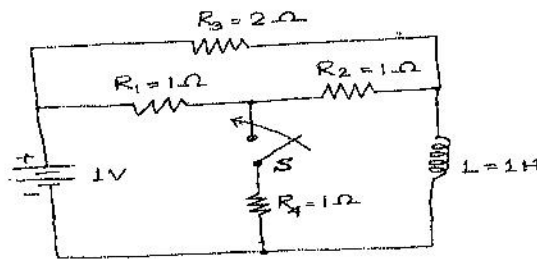


Fig. 5

**Group-B**

5. a) A sinusoidal voltage with variable frequency is applied to a series RLC circuit. Derive the expression for resonant frequency and frequency at which the voltage across the inductance  $L$  will be the maximum.

- b) Calculate the value of  $R$  in the circuit shown in Fig. 6 to yield resonance.


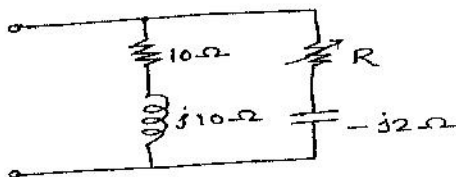


Fig. 6


(2+5+3)

6. a) For a circuit given in Fig. 7 with  $R_1 = 6.4 \Omega$ ,  $R_2 = 2.4 \Omega$ ,  $X_{L1} = 4.8 \Omega$  and  $X_{L2} = 8 \Omega$ , find
- Total conductance and susceptance of the circuit.
  - Total admittance

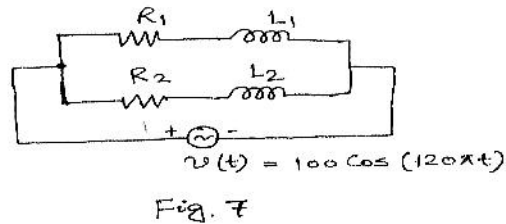- iii) Branch currents  
 iv) Power factor angle of the circuit.



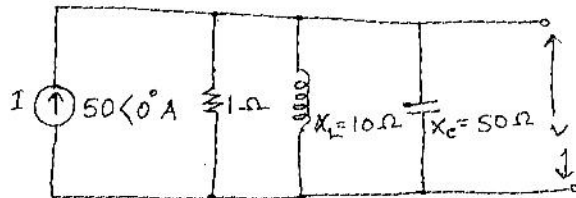
- b) Find voltage  $v$  in the circuit shown in Fig. 8.



(6+4)

7. a) What do you mean by fundamental cut-set of a graph?  
 b) For a resistive network shown in Fig. 9, draw the directed graph and tree of the network. Also develop the fundamental cut-set matrix and express the branch currents and branch voltages in terms of fundamental cut-set matrix.

(2+1+1+3+3)

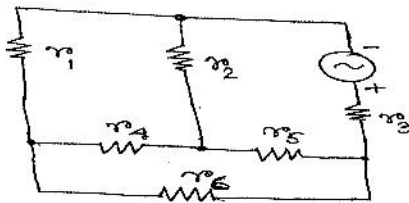

[ Turn over

## Group - B

Answer Question 1 and any FOUR questions from rest

1. What is mutual inductance? Describe the effect of mutual inductance in series and parallel combination of inductors. [Marks: 4+6=10]
2. Find the **h parameters** of the network shown in Figure 1. Comment on **reciprocal** and **symmetrical** property of the network. [Marks: 8+1+1]

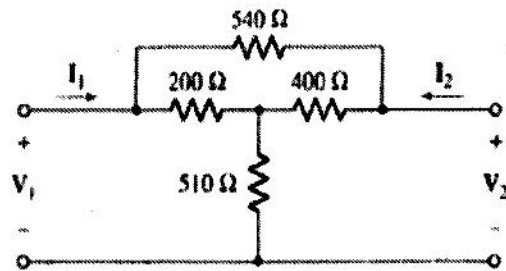


Figure 1

3. A) Determine the image impedance  $Z_{i1}$  &  $Z_{i2}$  of the T network shown below. [Marks: 5]

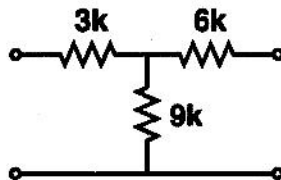


Figure 2

- B) Find the Norton equivalence of the circuit shown in Figure 3. [Marks: 5]

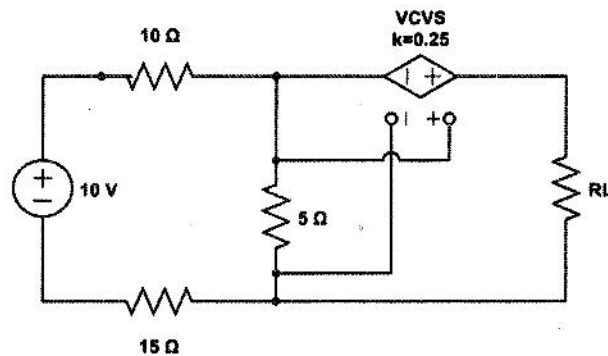


Figure 3

4. Find the **equivalent inductance** of the combination of inductors shown below. (Coupling Coefficient = 0.5) [Marks: 10]

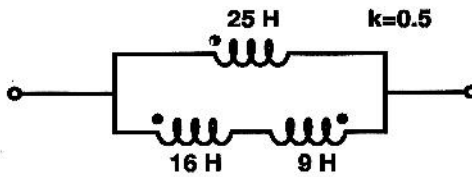


Figure 4

5. Determine the current  $I_L$  flowing through the 5k resistive branch. [Marks: 10]

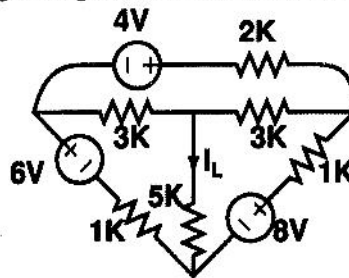


Figure 5

6. Determine the **ABCD matrix** of the network shown in Figure 6. Using those ABCD parameters find the **Y parameters** of the same network. [Marks: 5+5]

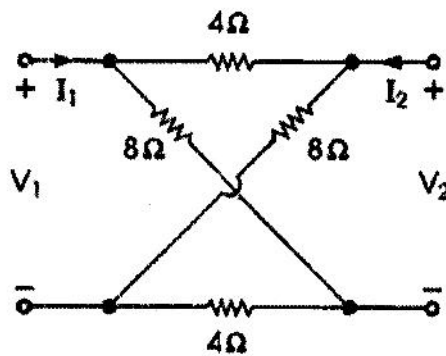


Figure 6

7. Obtain the loop current  $I_1$  and  $I_2$  of the network shown in Figure 7. (Mutual inductance  $M=2H$  and the RMS value of the applied voltage source is 100V) [Marks: 10]

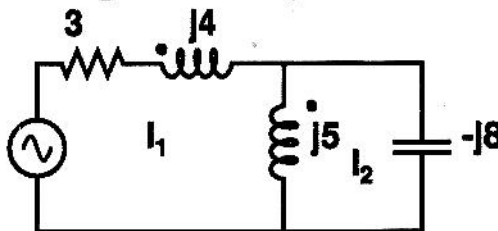


Figure 7